Wireless World

RADIO AND ELECTRONICS

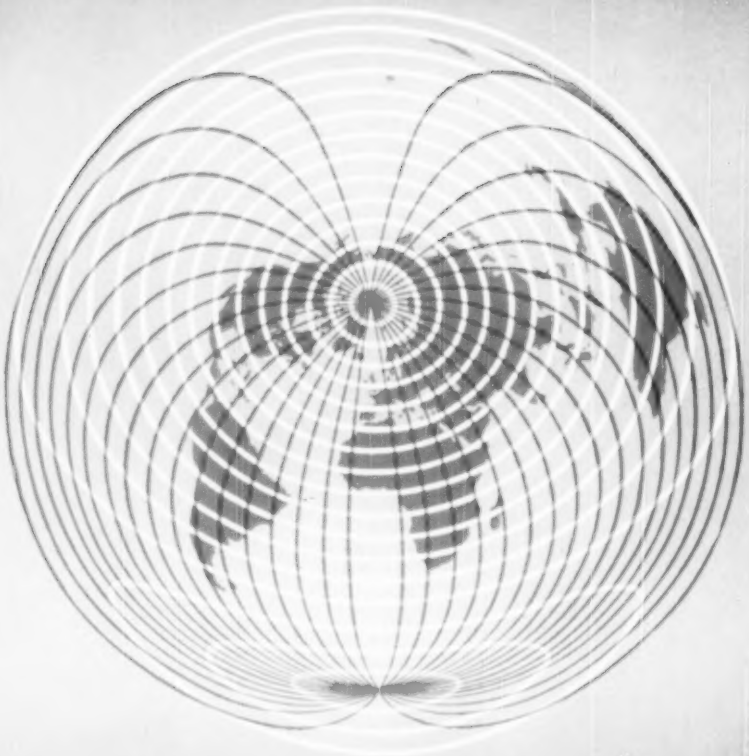

Vol LVI No 8 Two Shillings August 1950

Radio Engineers

SEND FOR

THIS NEW

FOLDER

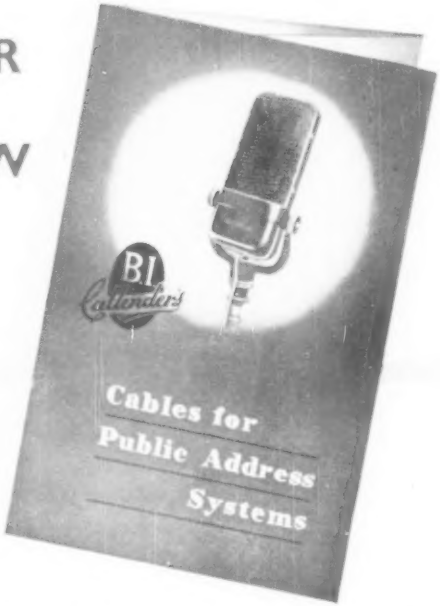

ON

BI Callender's

Cables for Public Address Systems

It contains specifications and illustrations of BICC microphone cables, loudspeaker cables, and associated wiring accessories suitable for all kinds of public address and paging systems. Write today for Publication No. 275 V

BRITISH INSULATED CALLENDER'S CABLES LIMITED
NORFOLK HOUSE, NORFOLK STREET, LONDON, W.C.2

AVO

Precision
ELECTRICAL TESTING INSTRUMENTS

The "AVO" ELECTRONIC TESTMETER

This instrument, which is an up-to-date example of current instrument practice, has been developed to meet the growing demand for an instrument of laboratory sensitivity built in a robust and portable form, for use in conjunction with electronic and other apparatus where it is imperative that the instrument should present a negligible loading factor upon the circuit under test.

The instrument consists basically of a balanced bridge voltmeter. It incorporates many unique features and a wide set of ranges so that in operation it is as simple to use as a normal multi-range testmeter.

The instrument gives 56 ranges of readings as follows :—

D.C. VOLTS : 2·5mV. to 250V. (Input Resistance 11·0 megohms.)
25mV. to 10,000V. (Input Resistance 110·0 megohms.)

D.C. CURRENT : 0·25μA. to 1 Amp (250mV. drop on all ranges).

A.C. VOLTS : 0·1V. to 2,500V. R.M.S. up to 2 Mc/s. With diode probe external 0·1V. to 250V. R.M.S. Useful measurements can be made up to 200 Mc/s. the applied voltage being limited to 100V. above 50 Mc/s.

A.C. OUTPUT POWER : 5mW. to 5 watts in 6 different load resistances from 5 to 5,000 ohms.

DECIBELS : —10db. to +20db. Zero level 50 mW.

CAPACITANCE : ·0001μF. to 50μF.

RESISTANCE : 0·2 ohms to 10 megohms.

INSULATION : 0·1 megohm to 1,000 megohms.

The thermionic circuit gives delicate galvanometer sensitivity to a robust moving coil movement, which it is almost impossible to damage by overload. The instrument is quickly set up for any of the various tests to be undertaken, a single range selector switch automatically removing from the circuit any voltages and controls which are not required for the test in question.

Size : 12½in. × 9in. × 5½in.
Weight : 12½lbs.

The instrument operates on A.C. mains, 100 - 130V. and 200 - 260V. 50 - 60 c.s.

PRICE
£35

Fully descriptive pamphlet available on application.

Sole Proprietors and Manufacturers

The AUTOMATIC COIL WINDER & ELECTRICAL EQUIPMENT CO. LTD.
WINDER HOUSE · DOUGLAS STREET · LONDON · S.W.1 *Telephone:* VICTORIA 3404/9

ETM.3

A

UNBREAKABLE RUBBER MOULDED PLUG

MOULDED PLASTIC SOCKET

BERYLLIUM COPPER CONTACTS

Control by **PAINTON**

& COMPANY LTD

KINGSTHORPE · NORTHAMPTON

"the pickup with three heads"....

The finest Pickup on the market at a competitive price

For Standard and Microgroove Recordings

Green Spot with .001" radius sapphire for microgroove recordings
Red Spot with .0025" radius sapphire for modern standard recordings
Yellow Spot with .003" radius sapphire for older standard recordings

These pickup heads are fitted with an easily replaceable armature system complete with a semi-permanent sapphire. Armature mass 20 milligrams.

Extremely low mass at needle point (4/5 m.g. only), allowing for reduction in downward pressure to 10/12 grams for standard recordings, and 5/7 grams for microgroove recordings.

Prices: With one Head £4 0 0 plus £1 14 8 Purchase Tax. Extra Heads each £2 10 0 plus £1 1 8 Purchase Tax. Spare Armature System with Sapphire 14/8 including Tax.

Telephone: Hipperholme 69169

A *Connoisseur* PRODUCT

Manufactured by A. R. SUGDEN & CO. (ENGINEERS) LTD. WELL GREEN LANE, BRIGHOUSE, YORKS.

Mullard

REVIEW OF NEW AND CURRENT VALVES

MULLARD MINIATURES. The Mullard range of miniature valves on the B7G (7-pin button) base includes both mains ("E") and battery ("D") types, and meets most requirements for miniature telecommunication receivers, industrial electronic equipment and light-weight miniature measuring instruments. The present range includes the following :—

EY91 Half-wave Rectifier
EC91 V.H.F. Grounded-grid Triode
EF91 High Slope, Sharp Cut-off R.F. Pentode (6AM6)
EF92 Vari-mu, R.F. or I.F. Pentode
EAC91 Diode Triode for frequency-changing up to 300 Mc/s
EB91 Screened Double Diode (6AL5) (separate cathodes)
EL91 Output Pentode (6AM5) (1.4W Output)
ECC91 V.H.F. Double Triode (6J6) (physical common cathode)
DK91 Vari-mu Heptode Frequency Changer (1R5)
DF91 Vari-mu R.F. or I.F. Pentode (1T4)
DF92 Sharp Cut-off R.F. Pentode
DAF91 Single Diode Pentode (1S5)
DL92 Output Pentode (3S4) (0.27W Output)
DL93 A.F. or R.F. Output Pentode (3A4)
DL94 Output Pentode (3V4) (0.27W Output)
DA90 R.F. Diode (1A3)
DCC90 R.F. Double Triode (3A5)
2D21 Gas-filled Tetrode (Vh = 6.3V)

A RANGE OF INDUSTRIAL PHOTOCELLS. The Mullard range of all-glass photocells finds a particularly wide range of applications in industry and research. The types with caesium/silver-oxide cathodes (type C), have a high sensitivity to incandescent light and near infra-red radiation and are particularly recommended for applications where a high output is required. For colour matching and photometric applications, photocells with caesium/antimony cathodes (type A) are available, with a particularly high sensitivity to daylight and radiation throughout the visible colour spectrum. The end-view photocell 58CV, is intended for use in compact photometric units where conservation of space is of utmost importance.

No.	Type	Cathode Surface	Base	Sensitivity (μA/l)
20CV	Vacuum	C	B8G	25
20CG	Gas-filled	C	B8G	150
90CV	Vacuum	C	B7G	20
90CG	Gas-filled	C	B7G	125
20AV	Vacuum	A	B8G	45
90AV	Vacuum	A	B7G	45
58CV	Vacuum	C	Wire-in	15
58CG	Gas-filled	C	Wire-in	85

MULLARD DISC-SEAL TRIODES FOR U.H.F.

For applications such as U.H.F. links, local oscillators, and wide band applications such as multi-channel communication systems, radar altimeters, etc., the use of frequencies up to 1500Mc/s or even 3000Mc/s is often required. The Mullard Disc-Seal Triodes have been designed specifically for such purposes.

In the ME1001, adequate cooling and low inductance are combined in the design of the anode and grid discs to give an anode dissipation of 10 watts and an upper frequency limit (as an oscillator) of 3750-3500Mc/s (8-8.5cm).

The ME1003 is basically similar in design to the ME1001, but the larger electrodes permit an anode dissipation of 25 watts. However, the larger clearances necessary to obtain this value, limit the upper frequency to 2500Mc/s.

PRINCIPAL CHARACTERISTICS	ME1001	ME1003
Heater Voltage (V)	6.3	6.3
Heater Current (A)	0.4	1.0
Max. Anode Voltage (V)	350	500
Max. Anode Dissipation (W)	10	25
Max. Anode Current (mA)	50	200
Max. Peak Anode Current (mA)	150	500
Power Output (W)	0.5 (at 3000 Mc/s)	6 (at 1500 Mc/s)
	3.5 (at 500 Mc/s)	30 (at 430 Mc/s)
Mutual Conductance (mA/V)	6	20
Amplification Factor	30	30

If you require full technical data on any of the valves described in this review, please check this form, pin to your letter heading and post to the address below.

Miniatures - - - - ☐
Industrial Photocells - - ☐
Disc-Seal Triodes for U.H.F. ☐

Signature .....

MULLARD ELECTRONIC PRODUCTS LTD., CENTURY HOUSE, SHAFTESBURY AVENUE, LONDON, W.C.2

MWT 36

Simon
SOUND SERVICE

It's so simple!

- Recording with a magnetic recorder is simplicity itself.
- The portable unit shown will record continuously for one hour and recordings may be played over on the machine as often as desired or erased and the wire used again and again for further recordings.

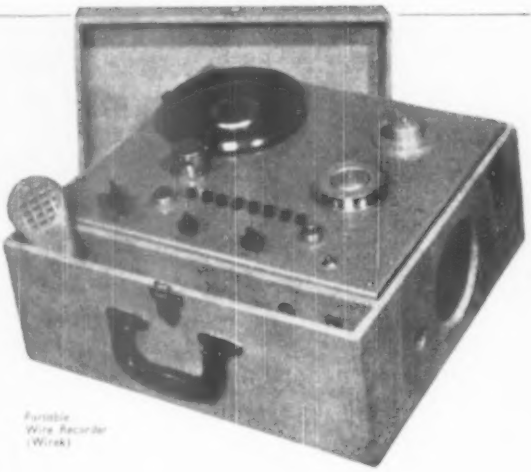

Portable Wire Recorder (Wirek)

IMPORTANT!
A new TAPE RECORDER will be available shortly

SIMON SOUND SERVICE

Recorder House, 48 50 George Street, Portman Square, London, W.1, England

Telephone: **Welbeck 2371 (4 lines)** Telegrams: **Simsale, Wesdo, London** Cables: **Simsale, London**

Sit back and enjoy the NEW—

'CONCERT MASTER'!

This latest high fidelity amplifier has all the features which you have asked for. Of impeccable performance, it is of compact size and includes a detachable control panel which is quite unique. It contains no valves, and has no H.T. or L.T. voltages. It is instantly removed by snap fasteners and makes the amplifier eminently suitable for fitting into a cabinet, the main amplifier being placed at the bottom and the control head on its six feet cable can be placed just where you want it. This last word in amplifier design will take high or low output pick-ups and has provision for radio and microphone inputs.

PRICE
£29.10.0
TWO YEARS' GUARANTEE

Write for your copy of our fully illustrated catalogue today!

(DEFERRED TERMS AVAILABLE ON ALL MODELS)

R.A. TUNING UNIT

A really fine design with lasting high performance. R.F. stage on all wave-bands. High fidelity superhet or T.R.F. performance. Suitable for any amplifier. Price **10 gns.** plus **£2.6.8** tax. (2 years' guarantee).

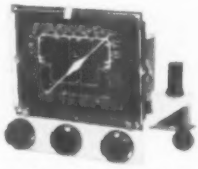

THE K.I. AMPLIFIER

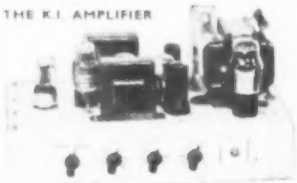

A seven-valve amplifier especially designed for the light-weight high-fidelity type pick-up. Independent bass and treble controls. Price complete, **17 gns.**, or in kit form, **13 gns.** Blueprint available separately 2/6.

THE TRICORNE SPEAKER CHAMBER

For optimum acoustic performance with any good 12-in. speaker. Labyrinth construction, walnut veneered and cross-braced.

Price **11 gns.** plus 20/- deposit (returnable) for crate.

Phone: WEStern 1350

Charles
AMPLIFIERS
(SALES) LTD.

Our equipment can also be seen at
Webb's Radio, Soho St., W.1.
University Recording Co., 16 Burleigh Place, Cambridge.
Ernest Buchan, 28 Belmont Street, Aberdeen.
Farmer & Co., 83 George St., Luton.
Signal Shop, 51 St. Mary Street, Bridgwater.

181 KENSINGTON HIGH STREET · LONDON · W.8

FOR THE UTMOST REALISM FROM RECORDS & RADIO

COSSOR

MODEL 1035

Double Beam

OSCILLOGRAPH

The unique Double Beam Tube enables the traces of two related phenomena to be examined simultaneously. Signals are normally fed through the Amplifiers. Calibrated Y1, Y2 and X Shifts give measurement of applied Signal Voltages and Time. The Time Base operates repetitively or by external trigger with positive or negative sync. selection. A Camera Model 1428 may be fitted for photographic recording.

Enquiries should be addressed to:

A. C. COSSOR LIMITED, INSTRUMENT DIVISION, HIGHBURY GROVE, LONDON, N.5.

Telephone: CANonbury 1234

AMBASSADOR
OF GREAT BRITAIN

FOR THE OVERSEAS BUYER

introduce a new receiver designed especially to provide superlative performance at minimum cost. In relation to performance this new receiver is the most competitive of any.

Its six valve superhet circuit covers six wavebands, four of which are electrically bandspread. Continuous bandspread coverage is provided between 9.4 and 51.8 metres. Two other bands cover respectively from 51.130 and 185.550 metres. All bands are coil ranges, thus ensuring high sensitivity.

This excellent receiver also features: Flywheel tuning; variable tone control; multi-coloured glass dial; Extension speaker and gramophone pickup sockets; a tuning indicator and an 8in. Rola fully dust protected loudspeaker.

Of special interest is the easy adaptability of the receiver to operate from a 6-volt battery.

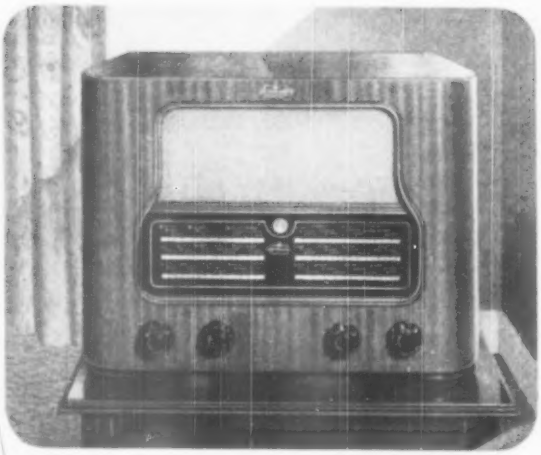

Full details and C.I.F. prices direct from

W. J. GROOM & CO. LTD.
22 FENCHURCH ST., LONDON, E.C.3

Advertisement of AMBASSADOR RADIO
BRIGHOUSE, YORKS, ENGLAND

The AIRMEC *Electronic method of*
FREQUENCY MEASUREMENT

An instrument suitable for frequency measurements up to 20,000 c/s or for high speed revolution counting up to 1,200,000 r.p.m. No load need be imposed on the equipment being tested and one advantage is that the meter will work with a great variety of pick-ups.

Accuracy is ±1% of full scale deflection and provision is made for quickly checking the calibration.

Pamphlet 20 gives further details.

Ranges	0-200, 0-2000, 0-20,000 c.p.s. or up to 1,200,000 r.p.m.
Accuracy	±1% of full scale deflection and unaffected by input wave form or supply within wide limits.
Calibration Check	A simple self checking calibration device is provided.
Input Signal	Input signal voltage may be any value from 0.1 volts to 20 volts peak.
Supplies	A.C. mains operated.

Type 726

AIRMEC LABORATORIES LTD.
HIGH WYCOMBE BUCKINGHAMSHIRE · ENGLAND
TEL HIGH WYCOMBE 2060 *CABLES: AIRMEC HIGH WYCOMBE*

DESIGNERS AND MANUFACTURERS OF SCIENTIFIC AND INDUSTRIAL ELECTRONIC EQUIPMENT

A.L.W.2

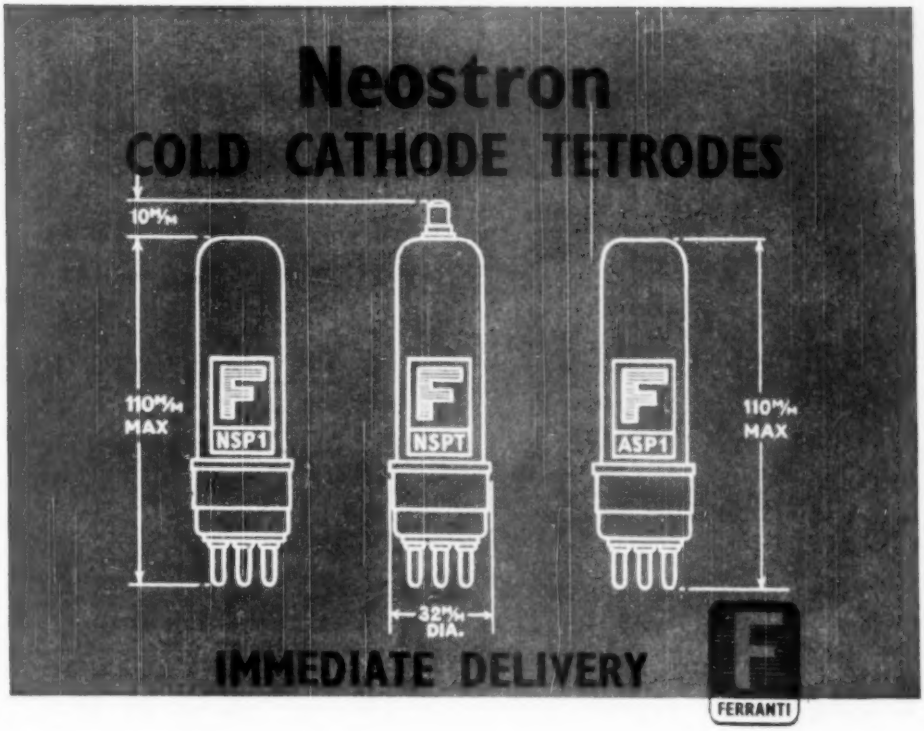

The Ferranti Neostron is a cold cathode tetrode filled with neon, designed for use as a stroboscopic light source, a flashing indicator, or an electronic relay.

The discharge in the anode is started by initiating a glow discharge between the screen and grid electrodes, the screen being at a fixed positive bias, a negative impulse being applied to the grid.

Operating Characteristics	NSP1	NSPT	ASP1
Max. Anode Voltage	400	650	400
Normal Anode Voltage	300	600	300
Mean Anode Current	40-100* mA	40-100* mA	40-100* mA
Peak Anode Current	250 Amps.	250 Amps.	250 Amps.
Max. Operating Frequency	250 c.p.s.	250 c.p.s.	300 c.p.s.
Anode Connection	in base	Top cap	in base
Gas Filling	Neon	Neon	Argon

**Dependent upon frequency of operation*

All types can be supplied with English 4 pin or American 4 pin bases.

FERRANTI LTD ELECTRONICS DEPT. MOSTON MANCHESTER 10

Recognised as the Most Reliable Valveholders

B11A—Sub Magnal

Ref. No. **S.P.11U** moulded in **Phenol-Formaldehyde with moulded-in metal mounting plate**
" " **A.P.11U** " " **Alkathene** " " " " " "
" " **A.A.11U** " " **Alkathene with integral Alkathene mounting flange**

THE McMURDO INSTRUMENT COMPANY LTD., VICTORIA WORKS, ASHTEAD, SURREY · ASHTEAD 3401

YOU CAN MAGNETICALLY RECORD
using your Gramophone Motor as a Drive

Necessary parts, also usable later for a more ambitious job, plans available, 1 Spool Diamond Magnetic Recording Tape and 1 take-up spool, 2 Corner Brackets, 1 Roller, 1 Record-playback Head Kit, 1 Friction Clutch, 1 Dual-purpose Supersonic Oscillator and Two-stage Preamplifier and your Radio Chassis. Set of parts £7 . 15 . 0, or items supplied separately.

Also Constructional Data for Wire and Tape Recorders 5s.

PARK RADIO OF MANOR PARK, 676/8, 783 Romford Road, London, E.12

Advance Signal GENERATOR B4

Here is a tried and proven general purpose sub-standard Signal Generator which is essentially simple to use. One special feature of the B4 is the accuracy of the R.F. output over the entire frequency range, achieved by the use of a crystal voltmeter and the subsequent elimination of all circuits having poor frequency characteristics. **£48**

Others of the many advantages of the B4 are described in Folder No. S/11/T, a copy of which will gladly be sent on request.

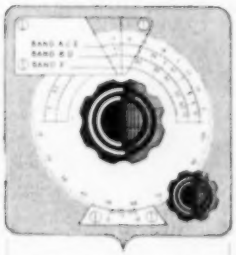

FREQUENCY RANGES

MODEL A

100 kc/s—70 Mc/s
in six bands

MODEL B

30 kc/s—30 Mc/s
in six bands

•

Output accuracy of both models is ± 1 db

ADVANCE COMPONENTS LTD

BACK RD, SHERNHALL ST, WALTHAMSTOW, LONDON, E.17. 'Phone: LARkswood 4366/7/8

B 1

WESTINGHOUSE BRAKE & SIGNAL CO., LTD., 82, YORK WAY, KING'S CROSS, LONDON, N.1

Here's the Master POCKET Set!

THE TRIMMER KIT

which no Amateur or Professional Radio or Television Engineer can afford to be without.

Contains

- ★ 1 End Trimmer
- ★ 1 Side Trimmer
- ★ 1 Yaxley Switch Contact Adjuster
- ★ 1 Low Capacity Trimmer
- ★ 1 Screwdriver
- ★ 1 Set of Feeler Gauges
- ★ 1 Set of six Box Spanners from 1 to 8 B.A.
- ★ 1 Set of four Spanners from 0 to 8 B.A.

In durable black crackle finish metal case

Order from:

J. & S. NEWMAN Ltd. 100 Hampstead Road, N.W.1. *Tel. Euston 5176*

Instruments for Research and Industry

Model 26 LABORATORY VALVE VOLTMETER

This instrument sets an entirely new standard of performance in mains operated valve voltmeters. It measures d.c. and a.c. voltages from 0.2 to 2000 volts and has an upper frequency limit of 200 Mc/s. Four resistance ranges extending up to 100 megohms and a decibel range are included.

The meter is a six inch movement with a mirror scale.

★ *Accuracy on all voltage ranges conforms to B.S. 89 : 1937 for First Grade moving coil meters—a performance which has not hitherto been claimed for any valve voltmeter.*

ELECTRONIC INSTRUMENTS LTD
17 PARADISE ROAD RICHMOND SURREY ENGLAND

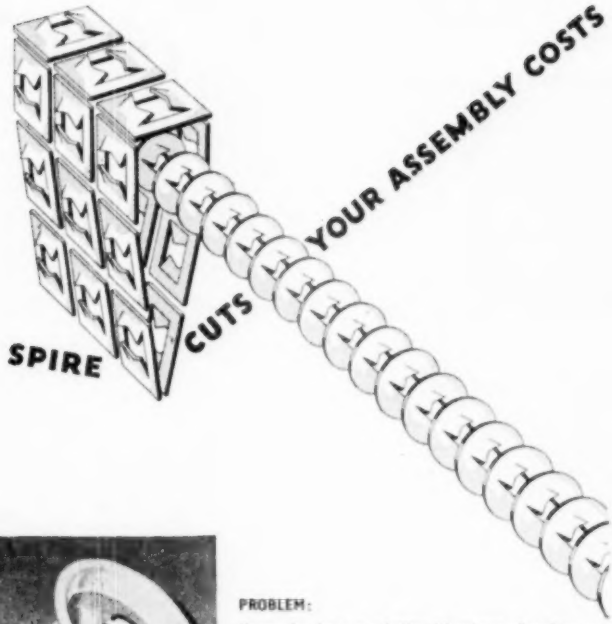

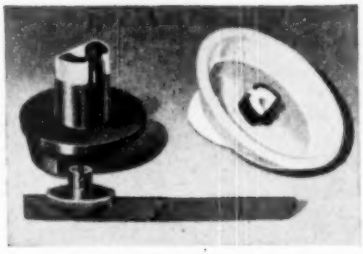

PROBLEM:
Secure knobs to a spindle without use of grub screws.

SOLUTION:
SCA and SCB Type 'Knob to Shaft' Clips hold moulded knobs securely under firm spring tension. No unsightly grub screws—expensive tapping operations and threaded inserts eliminated.

THAT'S FIXED THAT—FASTER, CHEAPER, BETTER

Here's another type of Spire fastener that is saving time and money. There is a Spire for almost any assembly job and it is amazing how much time and money they save. Why don't you see what Spire, fastest thing in fastenings, can do to help you? Write direct to us.

Spire Regd. **SPEED NUTS**

Enquiries to:
Simmonds Aerocessories Ltd., Byron House, 7-8-9, St. James's Street, London, S.W.1
HEAD OFFICE & WORKS: TREFOREST, GLAMORGAN. ALSO BIRMINGHAM, STOCKHOLM & MELBOURNE
198

LONDON CENTRAL RADIO STORES

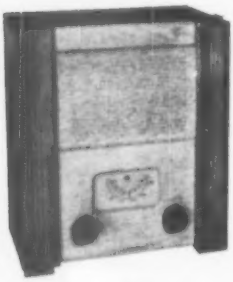

GOVERNMENT SURPLUS
—From stock

6-VALVE SUPERHET UTILITY RECEIVER

Not merely a "stand-by" but a really good set.

Every one guaranteed to be in working order.

Medium waveband only. Four valves, P.M. Speaker, complete in pine wood cabinet size 13½ × 12 × 6½in. In good condition. A.C. mains 200-250 volts. Price Carr. and pkg. 5/-

£3.19.6

BALL MICROPHONE

Manufactured by Standard Electric. All in perfect condition. Suitable for broadcasting and recording. Moving Coil (Dynamic). Unidirectional. No energising necessary. High Fidelity. Coil Impedance 15 ohm and will work very well in conjunction with an ordinary speaker transformer. Is of the type used by many leading bodies, such as the B.B.C. and G.P.O. for high fidelity reproduction, with sealed dust-proof cover. Guaranteed provided cover is not removed. (See illustration fully cover.)

£4.17.6

As we are still maintaining large stocks please refer to previous issues.

BRAND NEW ACCUMULATORS

Complete in strong case (as illustrated fully cover). British made. 6v 40a. Size 12 x 9 x 7in. Weight 45lb. **£3.10.-**. Carriage and pkg., 5/-

R1155 10-VALVE COMMUNICATIONS RECEIVERS.

These sets are as new. Freq. range 7.5 mc/s. 75 kc/s. In five wavebands. Complete with 10 valves, including magic eye. Enclosed in metal case. Every receiver is aerial tested. Complete with Power Pack and Loud Speaker, for A.C. mains 200-250 v. **£16.10.0**

(See fully cover for illustration.)

RECEIVER ONLY as new **£10.** (Carr. 5 pkg. 10/6).

FREE with each receiver! Complete circuit, description and modifications for civil use, reprinted from "W.W." July, 1946.

WALKIE-TALKIE Transmitter and Receiver CMA5818, Type 38 Mk. II

In perfect working order. Complete with four ARP12, one ATP4 valves, one pair throat mikes, one pair light weight headphones and aerial. In metal case. Free wiring diagram. Less batteries. Carr. and Pkg. 2/6. **£3.8.6**

PHILIPS 6-VALVE COMMUNICATIONS RECEIVER

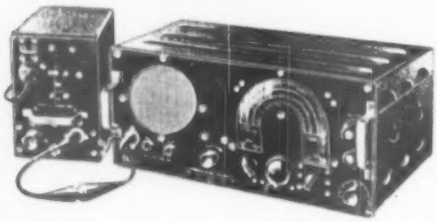

16-50, 200-550 and 800-2,500 metres. R/F. F.C. 2 I.F's D.D.T. Pentode Output. Spin wheel tuning. In black metal case with built in speaker. Complete with power pack A.C. 200-250 v. Can also be supplied with 12 v. D.C. power pack if required. BRAND NEW—EX GOVT. **£17.10.0**

PLEASE NOTE

We do not issue lists or catalogues.
Carriage charges relate to British Isles only.

23, LISLE ST. (GERrard 2969) **LONDON, W.C.2**

Closed Thurs. 1 p.m. Open all day Sat. and weekdays 9 a.m.—6 p.m.

Widney Telescopic Mountings

PRODUCED IN **3 SIZES**

Telescopic Mountings offer the most convenient means of obtaining complete accessibility of rack mounted equipment as each chassis can be withdrawn completely clear of its framework for easy examination.

WRITE FOR ILLUSTRATED CATALOGUE

Technical & Sales Agent
C. H. DAVIS
59, Brompton Road, LONDON, S. W. 3
Phone KENSINGTON 4201

Widney PRODUCT — ESTABLISHED 1898

MANUFACTURERS
HALLAM SLEIGH & CHESTON LTD
WIDNEY WORKS · BIRMINGHAM · 4

You are offering

***PEAK PERFORMANCE**

with the

GRAMPIAN D.P.I.

THE IDEAL MICROPHONE FOR P.A. WORK, BROADCASTING AND RECORDING

Here is a wide range high fidelity moving coil type Microphone which combines good sensitivity with a level response curve. Equally suitable for Auditorium or Outdoor Work, and its use can confidently be advised for Amateur as well as Professional use. Housed in modern streamlined die cast alloy case of great strength and finished in hammered metallic lacquer with chromium plated grille. Delivery from stock. List price £8.8.0

Dimensions 3" diam. 3¼" back to front. Net weight 2 lb. Frequency response 60-9,000 c.p.s. Output impedance 15 ohms. Fitting 5/16" B.S.F. Connection 2-pin plug.

GRAMPIAN P.A EQUIPMENT

Grampian Reproducers Ltd., Hampton Road, Hanworth, Middx.
'Phone: Feltham 2657.

NITROGOL *Capacitors*

QUALITY has always been the basis of Dubilier technical supremacy and in the television field too, this factor has confirmed Dubilier's lead in the international field.

Thus it is natural that only components of tested quality and worth will satisfy television engineers. Experience has proved that Dubilier Nitrogol Capacitors, acknowledged by technicians throughout the world for their reliability, are best suited to the manufacturer of television apparatus.

In such applications as radar, amplifiers, undersea cable repeaters and industrial electronic applications Nitrogol Capacitors are again a prime necessity.

Comprehensive catalogues giving detailed information of capacitors and technical service are available upon request.

DUBILIER
CONDENSER CO. (1925) LTD.

DUBILIER CONDENSER CO. (1925) LTD., DUCON WORKS, VICTORIA ROAD, N. ACTON, LONDON, W.3
'Phone: Acorn 2241 (5 lines). 'Grams: Hivoltcon, Wesphone, London. Cables: Hivoltcon, London. Marconi International Code

D38A

For the RECORD...

THIS is not an easy advertisement to write, so let us come to the point and be done with it.

R. & A. was started in 1930 by an engineer who already had over 20 years' practical experience behind him—16 of them in precision engineering, and 7 years in the design and quantity production of radio.

On that firm basis, the new company was established to manufacture reproducers and transformers for the radio equipment industry, AND NOTHING ELSE. Control and policy have since remained unaltered, and a number of the original employees are still with the company.

These facts suggest that over the years R. & A. must have accumulated a fair knowledge and understanding of equipment makers' problems—and a somewhat better than "fair" knowledge of loudspeaker manufacturing technique.

All this experience is at the disposal of radio and television manufacturers at home and abroad. As an introduction to it, will you please write for latest leaflets on the current range?

R&A

REPRODUCERS AND AMPLIFIERS LIMITED
WOLVERHAMPTON · ENGLAND
Telephone: Wolverhampton 22241 *Telegrams: Audio, Wolverhampton*

SPHERE INSTRUMENTS

TELEVISION ADAPTOR UNIT TYPE S.C. "88"

Adaptor Unit S.C. "88" eliminates costly troublesome conversions

IT ADAPTS THE "LONDON"-DESIGNED TELEVISION RECEIVER FOR SUTTON COLDFIELD RECEPTION — PERFECT SOUND AND VISION

Small and compact, the unit, embodying power-pack, and all the necessary "works," is simply fitted between aerial and set. Set itself is entirely untouched, and in its original state—thus retaining its full "design-efficiency." Of particular interest to "Fringe" viewers. Real saving of time, trouble and cost. Full details supplied.

Price 6 Gns. nett

Manufacturers:
SPHERE RADIO LIMITED
HEATH LANE, WEST BROMWICH, ENGLAND

"Cyldon"
VARIABLE *Capacitors*

TRANSMITTING

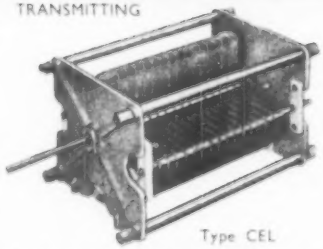

Type CEL

13½" long (excluding spindle). 8" wide. 7¼" high. Air gap, .218". Range of max. capacities, 100—1000pF.

MICA TRIMMERS *to* AIR DIELECTRIC HIGH-VOLTAGE *Transmitting Capacitors*

SYDNEY S. BIRD & SONS, LTD.
CAMBRIDGE ARTERIAL RD. ENFIELD, MIDDX.

POINTERS to SUPREMACY

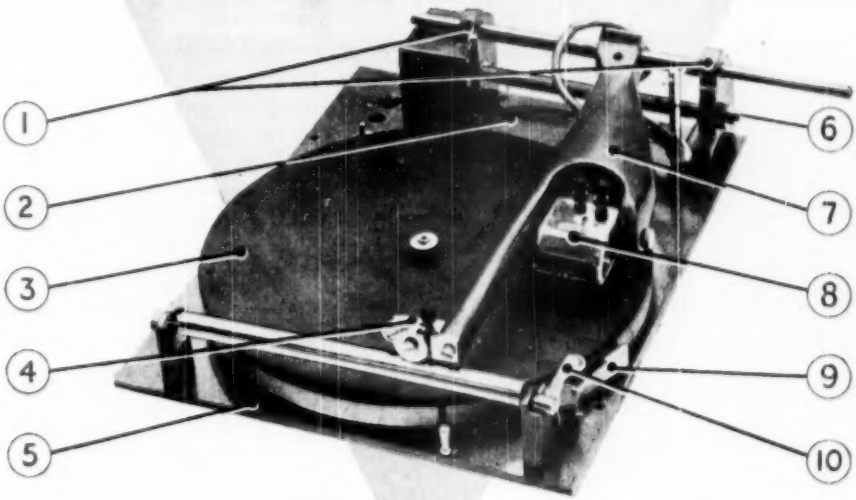

DIRECT RECORDING ON DISK

Below are just a few of the many outstanding features which have made the LED Recording Machine the considered choice of the discriminating professional sound recordist.

(1) **WIDELY SPACED PILLAR SUPPORTS** for cutterhead arm eliminate side play.

(2) **VIBRATION-FREE DRIVING MECHANISM** reduces background noise to the minimum.

(3) **CAST LIGHT ALLOY TURNTABLE WITH GUNMETAL RIM** assures maximum moment of inertia for minimum actual weight.

(4) **FINE ADJUSTMENT OF CUTTER ANGLE** compensates for smaller length variations of cutters.

(5) **ROBUST LIGHT ALLOY MOUNTING PLATE** with generous turntable bearing ensures stability.

(6) **PRECISION GROUND STAINLESS STEEL LEADSCREW** provides really accurate tracking.

(7) **RIGID CAST LIGHT ALLOY CUTTERHEAD ARM** supported at both ends to ensure consistent stability.

(8) **PATENTED ELECTRO - MAGNETIC CUTTERHEAD** with built-in equaliser, possessing exceptionally stable characteristics.

(9) **AUTOMATIC FRICTION BRAKE** ensures accurate turntable speed when reproducing.

(10) **SINGLE LEVER CONTROL** automatically engages tracking mechanism as cutter is lowered.

Full details and technical data on request.

M·S·S·RECORDING COMPANY LTD

POYLE CLOSE · COLNBROOK · BUCKINGHAMSHIRE · TELEPHONE · COLNBROOK 87 & 115

TELEVISION PRE-AMPLIFIER. This Ex-Govt. 1 valve pre-amplifier is extremely sensitive and stable. It makes an amazing improvement in both vision and sound reception in all fringe areas. Now available for both London (type A) and Birmingham (type B). Very small dimensions. Length 4in. Width 3½in. Chassis depth 1½in. Overall depth to top of valve 4½in.

Fitted with EF50 valve. Ready for use. Power requirements 6.3 v. LT 200 275 v. HT. Coax input and Output sockets. Ideal for "The Viewmaster," "The Inexpensive Television Set," Electronic Engineering Televisor and any commercial set with suitable power supply. Unique value. **15/-**. (Post 1/-). Tested and Guaranteed.

RADAR INDICATORS. Type VE. Grey Enamel case: L. 24in. D. 23in. W. 11in. Contains 16 valves, 6SN7 (7), 807 (3), VR150 (2), 2X2, 5U4G, 6AG7, 6SL7. Oil filled condensers 10 mfd. 600 v. (3), 6 mfd. (2), 1 5,000 v. (2). Potmeters (16). Small Electric Motors (2). Transformer Input 115 v. 60 c. Output 3,890 v. .0033 a. Another ditto. Output 6.3 v. 10 a., 6.3 v. 0.6 a., 5 v. CT. 3 a. 850 v. CT. 0.142 a. Filter chokes (2). 10 h. 2 a., 77 ohms also a very large quantity of precision resistors and condensers. 7in. CR tube mounting and focussing coils (no tube). Double deck chassis which slides in and out of outer case. Brand New and unused. Ideal for conversion to transmitter or TV. An outstanding bargain, **£12 10/-** carriage paid.

RADIO SET SCR 291 A COMPRISING: Federal U.S.A. 110 v. 50/60 cycles Communication Receiver, BC1147A. 13 valves, comprising 6SK7 (4), 6SH7, 6SA7, 6J5, 6H6, 6SJ7, 6SQ7, 6K6, or 6V6, 5U4G, VR150. 4 wavebands 1.5-3.1 mcs., 3.1-6.6 mcs., 6.6-14 mcs., 14-30 mcs. I.F. frequency 455 kcs. Front panel 19in. x 14in., rack mounted. CONTROLS.—Waveband switch, matching, tuning, A.F. gain, I.F. selectivity (band width), BFO, BFO On/Off, sensitivity, power on/off, AVC—manual. Built-in loudspeaker. Receiver section is entirely self-powered. A supersensitive receiver of the highest class. **Auxiliary Power Pack Control, Panel PN-31A.** 110 v. 50/60 cycles. 4 valves and stabiliser. 2X2, 5U4G, 6L6, 6AC7, VR150. 6 Potmeters, 6 toggle switches, 3 indicator lights. All circuits fully fused. 0-50 ma. meter. Unit self-contained. Rack mounted. Size 19in. x 10½in. Ideal for operating your transmitter. **Magneto Operated Telephone Circuit PN32A.** Handset and mag-handle on front panel. Size 19in. x 5½in. (The XYL can call you for meals with the phone). Whole equipment in magnificent cabinet type rack 32in. high, 20in. deep, 22in. wide. 71/8-page instruction book included. Brand new, unused. In original unopened packing. Securely packed in wooden container with fall-away front and rear, making set very quickly operative. Make your Ham Shack a real radio station with one of these magnificent equipments.

(ORIGINAL COST APPROX. £250. 17 only available. Our price, **£30** each, carr. paid.)

CANADIAN No. 58 MARK I TRANSRECEIVER. 35-50 metres. 16 section rod aerial. Operates from 180 v. dry battery which is included together with an extra one as spare. Range 5-10 miles. Greatly exceeded with wire aerial. 5 valves in receiver 3 in transmitter. Size 12in. x 7in. x 5in. Weight 18 lb. Supplied with 2 sets headphones and microphones. Brand new. Unused. Carriage paid. **10 gns.**

Q-MAX B4 40/60 w. TRANSMITTER. Shop soiled. Full guarantee. List price £75. 2 only to clear. **£50** each. Full details on application.

R.P. UNITS, TYPE 24. New condition. Complete with 3 valves. 20-30 mcs. Tunes to 5 spot frequencies. **14/-**. Carriage 1/4.

CONDENSERS. Brand new waxed tubular, 50 for **10/-**, (25 .1 mfd 1,000 v., 25 .25 500 v.) Post paid.

EP50 CERAMIC VALVE HOLDERS, 5/- dozen. Post 6d.

PAMPHONIC PA SPEAKERS. 10in. in handsome maroon metal cabinet. In original makers packing (not surplus). **55/-** each. Less than cost.

1155 RECEIVERS. Brand new in Transit Case. Aerial tested, **£7 19/6**. Carriage 10/-.

PROMPT DELIVERY AND SATISFACTION GUARANTEED AS ALWAYS.
2½d. stamped envelope must accompany all enquiries.

Lists Available

H.P. RADIO SERVICES LTD.

Britain's Leading Radio Mail Order House

Estd. 1935

55 COUNTY ROAD, WALTON, LIVERPOOL, 4

Tel. Aintree 1445 Staff Call Signs, G3DGL, G3DLV

QUALITY SUPERHET

By courtesy of the General Electric Co. Ltd. Kingsway, London, we have pleasure in introducing a new pre-tuned superhet, as described in their technical publication TP4. This receiver is the ideal unit for use with amplifiers such as the "Williamson" where reception conditions are unfavourable to a "straight" type of receiver.

Outstanding Features

- Four pre-selected wavelengths. 3 medium, 1 long.
- Two positions of selectivity. Bandwidth 6 kc/s. & 16 kc/s.
- Very efficient 9 kc. whistle rejector, giving approximately 40DB rejection.
- Variable switched bass and treble controls.
- Ample gain for lightweight pick-ups.
- Very low overall distortion.

Price: £16. 0. 0. **Purchase Tax: £3. 15. 0.**

DELIVERY 7 - 14 DAYS. TRADE ENQUIRIES INVITED.

ROGERS DEVELOPMENTS CO.,

"Rodevco House"

116 Blackheath Road, Greenwich, S.E.10

Telegrams: RODEVCO, GREEN, LONDON.

WITH THE OSMOR 'Q' COILPACKS

SUPERHET and T.R.F.

As specified for conversion of the Type 25 unit of the TR.1196, and for modernisation of war-time utility receivers and others.

The OSMOR "Q" Coilpack does not "whistle while it works" but gives you perfect performance in every way. And it saves time, money and hours of wasted effort puzzling over complicated wiring circuits. Just 5 connections, 5 minutes work and the job is done—and well done!

Send stamp for FREE new circuits, lists of Coils, Coilpacks, Dials and all Radio Components, etc.

★ **New wavelength scales** for Type A dials **8/-** each.

OSMOR RADIO PRODUCTS LTD., (Dept. W.9)

BRIDGE VIEW WORKS, BOROUGH HILL, CROYDON, SURREY.

Telephone: Croydon 1220.

VALVES **For SPECIAL PURPOSES**

× Meet us at THE RADIO SHOW CASTLE BROMWICH BIRMINGHAM Sept 6-16 ×

20A2

Indirectly Heated Gas Filled Tetrode for Use as a Grid Controlled Rectifier

RATING:

Heater Voltage (volts)	6.3
Heater Current (amps)	1.0
Approximate Arc Voltage Drop (volts)	9.0
Max. Peak Forward Anode Voltage (volts)	600
Max. Peak Inverse Anode Voltage (volts)	1300
Max. Shield Grid Voltage (volts)	–50
Max. Control Grid Voltage (volts)	–50
Max. Peak Cathode Current (mA)	1250
Max. Mean Cathode Current (mA)	250
Control Grid Series Resistance (M.ohms)	.01 to 1

BASE:—IO8

LIST PRICE:— £2.12.6 (Provisional)

DIMENSIONS:

Maximum Overall Length (mm)	110
Maximum Diameter (mm)	40
Maximum Seated Height (mm)	97

All maximum ratings are absolute values, not design centres.

IMPORTANT: Cathode and Heater should normally be tied externally. If left free the *Heater to Cathode Voltage* must *never exceed 25 volts peak*. The heater must be switched on for 15 seconds before anode voltage is applied.

EDISWAN

MAZDA

RADIO VALVES AND CATHODE RAY TUBES

THE EDISON SWAN ELECTRIC CO. LTD., 155 CHARING CROSS ROAD, LONDON, W.C.2

BA188

A CAPACITOR...

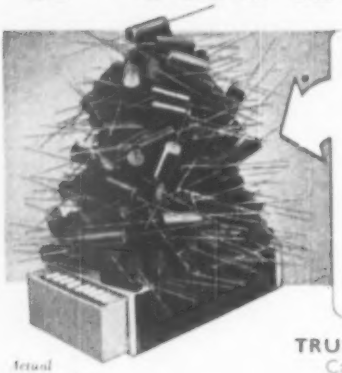

Actual photograph

for the tightest of TIGHT CORNERS

W99 MIDGET MOLDSEAL METALLISED PAPER

CAPACITANCE TOLERANCE: ± 20%
(Closer tolerances are available)

TEMPERATURE RANGE: −40° C. to +71° C.

INSULATION RESISTANCE: Not less than 20,000 megohms.

SELF HEALING

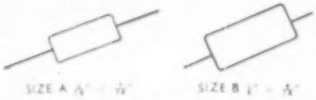

TRULY MINIATURE. There are more than two hundred Type W99 Capacitors piled on this standard match box! Another new development by Hunts to meet the increasing needs of designers and manufacturers for a quality capacitor for use in light weight, compact equipment employing miniature valves and for T.V. equipment.

Wkg. Voltage	Cap. µF	Size	Wkg. Voltage	Cap. µF	Size
150 D.C.	0.004 to 0.01	A	600 D.C.	2.5pF to 0.0005	A
	0.02 to 0.04	B		0.001 to 0.002	B
350 D.C.	0.001 to 0.003	A	300 A.C.	0.00005 to 0.001	A
	0.004 to 0.01	B		0.002	B

REGISTERED TRADE HUNTS CAPACITORS MARK

THE TRADE MARK OF RELIABILITY

Full details of all Hunt's types, samples and advice on any capacitor application, gladly supplied on request.

DRY ELECTROLYTICS · METALLISED PAPER · FOIL AND PAPER · STACKED AND SILVERED MICAS · ETC.

A. H. HUNT LTD., WANDSWORTH, LONDON, S.W.18 TELEPHONE: BATTERSEA 3131 ESTD. 1901

ICS

HOME STUDY backs radio experience with sound technical knowledge

MANY men who wished to link their radio experience with a sound technological background have received successful instruction by means of an ICS Course. Its value has been proved not only to amateurs but to men who already have a professional interest in radio and television engineering, including those taking qualifying examinations. It is invaluable, also, to students who wish to prepare themselves for a job in this field. Courses of instruction covering radio and, if necessary, television, include the following:

Complete Radio Engineering · Radio Service Engineers · Radio Service and Sales · Advanced Short-Wave Radio · Elementary Electronics, Radar and Radio · Television Technology

And the following Radio Examinations:

British Institution of Radio Engineers · P.M.G. Certificates for Wireless Operators · City and Guilds Telecommunications · Wireless Operators and Wireless Mechanics, R.A.F.

Write today for our FREE "**Radio**" booklet which fully describes the above ICS Courses and the facilities for the complete study of Radio and or Television technology. The ICS Advisory Department will also give free and impartial advice on the need of and the means of instruction.

International CORRESPONDENCE SCHOOLS

Dept. W.L.13, International Buildings, Kingsway, London, W.C.2

CELESTION

The Foremost Name in Sound Reproduction

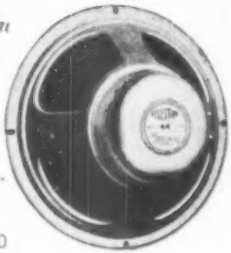

MODEL P44.

- Overall Diameter 12 3/16"
- Voice Coil Impedance ohms 3.0
- Magnet Pole Diameter 1½"
- Flux Density (Gauss) 10,000
- Total Gap Flux (Maxwells) 60,000
- Peak Power Capacity 10W

The General Public should please order through their Local Dealers.

Manufacturers are invited to write for details of the full range of Celestion speakers.

CELESTION, SUMMER ROAD THAMES DITTON, SURREY

Telephone: EMBERBROOK 3402-5

Where excellent quality reproduction is essential . .

. . the Metrovick

AUDIO AMPLIFIER

is the instrument to use

This instrument is designed to give excellent quality reproduction with the added advantages of being a self-contained unit, portable and attractive in appearance. Thus it will prove ideal for Public Address work, educational authorities and similar organisations.

SPECIFICATION

Supply :	200/250V 50 c/s single-phase ; consumption approximately 170 VA for full output.
Input :	Gramophone 0·2V for full output. Microphone 0·02V for full output. The two circuits can be mixed as required.
Impedance :	7 ohms, 15 ohms and 45 ohms.
Output :	20 watts with negligible distortion.
Tone Control :	Continuously variable.
Response :	± 1 db from 30 to 15000 c/s at zero position of tone control.
Controls :	These are recessed to avoid damage and are illuminated when in operation.
Dimensions :	18½" × 8½" × 10¼".
Finish :	The instrument is housed in an attractive steel case, stove enamelled in cream or blue as desired. A leather carrying handle is fitted.

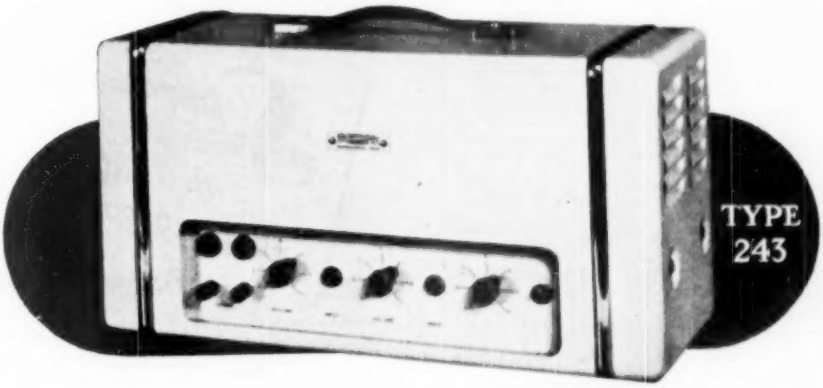

METROPOLITAN-VICKERS ELECTRICAL CO. LTD.

TRAFFORD PARK, MANCHESTER 17

R/E903

D. COHEN

Radio and Television Components

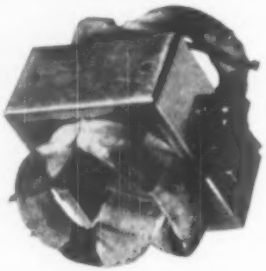

LINE AND FRAME COIL ASSEMBLY. Frame coils wound but not fitted (full instructions supplied). High impedance frame, matching 5:1. Low impedance line (as illustrated). **7/6**.

PERMANENT MAGNET FOCUS ASSEMBLY, with variable adjustment. **8/-**.

12in. WHITE RUBBER MASK, with TRIPLEX glass, **15/-**.

CONSTRUCTOR'S PARCEL comprising 5-valve Superhet chassis with transformer cut-out, size 13½in. x 6in. x 2in. with L.M. & S. scale 7in. x 5in. Backplate, two supporting brackets, drive drum, pointer, two-speed spindle, .0005 twin gang condenser, set of 6 iron cored long, medium and short wave coils. Mains trans., input 205-245 v., H.T. 280 v., 6 v. 3 amp., 4 v. 3 amp. Auto-wound, **22/6**.

WAVE CHANGE SWITCHES. 3 pole 2-way and 4 pole 5-way, **1/2**; 4 pole 4-way, **1/9**; 1 pole 12-way, **2/6**; 2 pole 12-way, **3/6**.

MAINS TRANSFORMERS. All these set out below are manufacturers' surplus, and not made down to a price.
Primaries 200-250 v., 50 cycle. Post and packing in each case 1/- extra.
Semi-shrouded, drop-through 280-0-280 80 mA., 5 v. 2 amp., 6 v. 3 amp., **15/-**.
Semi-shrouded, drop-through 280-0-280 80 mA., 4 v. 6 amp., 4 v. 2 amp. This trans. has 110-250 volt input, and could be used as an Auto-Trans. approx. 80 watts, **12/6**.
Drop-through type 350-0-350, 70 mA., 6 v. 2.5 amp., 5 v. 2 amp., **13/6**.
Drop-through or upright mounting, Auto-wound H.T. 280 v. at 360 mA., 4 v. 3 amp. (separate winding), 6 v. 3 amp., **10/6**.
Auto-transformer—very small dimensions—110-250 v. input, 70 v. 2 amp., and tapping for dial lamp, **5/-**.

HEATER TRANSFORMERS. Primaries 230-250 v., 6 v. 1½ amp., **6/-**, 2, 4 or 6 v. 2 amp., **7/6**. Post and packing on each 9d.

VOLUME CONTROLS. 1.5, with switch, ¼, ½, 1 and 2 meg., **3/3**, 20, 25 and 50k, **3/-**. Post and packing 3d. each extra.

LINE CORD, 3-way, 3 amp., 180 ohm per yard, **10d**.

METAL BRAIDED WIRE, with P.V.C. outer insulation, per yard **6d**.

CO-AXIAL FEEDER, 80 ohm, per yard **8d**.

POST ORDERS ONLY

67, RALEIGH AVENUE, HAYES, MIDDX.

TELE-RADIO (1943) LTD.

TO BUYERS, DESIGNERS and PROTOTYPE CONSTRUCTORS

Since our inception we have specialised in saving you the headaches of obtaining those components which have been rather scarce and in short supply.

We are maintaining that "Service" in offering you the largest range of Welwyn high stability resistors, Oak switches—made up to your requirements—precision resistors accurate to ±1%. Matched valves. Close tolerance condensers and a general range of fine quality components which we believe will enable you to cut down the paper work and obtain most of your needs under the one roof.

Our prompt postal service is always at your disposal. Cash with order or C.O.D.

SHOP HOURS
Monday 9 a.m.—6 p.m. Thursday 9 a.m.—1 p.m.

OUR ONLY ADDRESS:-

177, EDGWARE ROAD, LONDON, W.2.

TELEPHONE: PADdington 6116/5606.

Why you should use...

Superspeed SPECIAL *Activated* ROSIN CORED SOLDER

1. Maximum "Wetting" Capacity.
2. Accelerated Fluidity.
3. Moderate soldering bit temperatures.
4. Mechanical bonding and perfect Electrical conductivity ensured.
5. Minimum amount of solder used per joint.
6. Residue sets hard, is non-corrosive, and of high dielectric strength.
7. No harmful fume deposits.
8. Continuous, unvarying core.
9. Even distribution of activator in core.
10. Approved by Air Ministry and General Post Office.

Supplied in a wide range of Gauges and Alloys on 1 lb and 7 lb reels, works coils, or as required. Prices on application.

Sole Manufacturers:

H. J. Enthoven & Sons, Ltd.

89, UPPER THAMES STREET, LONDON, E.C.4.

Phone: Mansion House 4533. Works: Rotherhithe, Croydon, Derbyshire

The closest approach to the original sound in speech and music reproduction

THE ACOUSTICAL Q.U.A.D. AMPLIFIER will provide a standard of reproduction notably in advance of any equipment ever offered to the public. Besides being capable of amplifying a PERFECT programme input with the highest degree of accuracy yet achieved, it is also capable of providing the nearest approach to the original sound which it is possible to obtain from ANY practical programme source. Two developments are described on this page. Full details of the complete equipment will be sent on request.

1. ***The provision of low audio distortion together with a high margin of handling capacity for component frequencies beyond the operating range.***

In audio amplifiers, feedback is normally used to reduce harmonic distortion in the operating range. Similarly, intermodulation products within the operating range are reduced in like proportion. In all feedback circuits however, frequency components well beyond the operating range are not attenuated by the feedback and are therefore presented to the input at a level greatly in excess of their original value. These frequency components are significant in practical applications of music reproduction.

In the Q.U.A.D. amplifier a very low distortion content for audio frequencies is obtained, yet without incurring modulation distortion by possible conversion of very low beats produced by choral singing, strong unison playing, etc.

2. ***The inherent quality of the programme.***

In *all* programmes from radio, records, etc., there is to a greater or lesser extent a distortion component which rises with frequency — tracing distortion, phase effects at the microphone, discontinuity, etc. Since this distortion increase is continuous, a point is reached where the extreme frequencies (if any) are adding little to the musical content of the programme yet the distortion products are becoming distressingly audible.

In most demonstrations of high quality equipment this is more or less covered by the fact that nearly all high quality loudspeakers tail off at high frequencies in some random manner more or less suitable to the recording or programme picked for demonstration. The introduction of very wide range loudspeakers and the progress towards a closer approach to the original sound makes it essential to control the harmonic range in a more scientific manner.

It is obvious that for the highest possible quality, the rate or slope of harmonic attenuation is related to the rate at which the inherent programme distortion increases with frequency range.

The Q.U.A.D. Quality Control Unit incorporates the development of a low pass filter the slope of which can be continually varied from 10db per octave up to 100db per octave. Its point of insertion in the harmonic frequency range is switchable and covers all practical requirements.

This development in turn enables the bass and treble controls to be designed more accurately to fulfil their true function of correction rather than compromise, since they are no longer required to contend with harmonic and similar programme distortions.

Acoustical Q.U.A.D. amplifier and quality control unit complete . . . **£33**

(The Quality control unit is available as a separate unit for use only ***with existing QA12/P amplifiers.)***

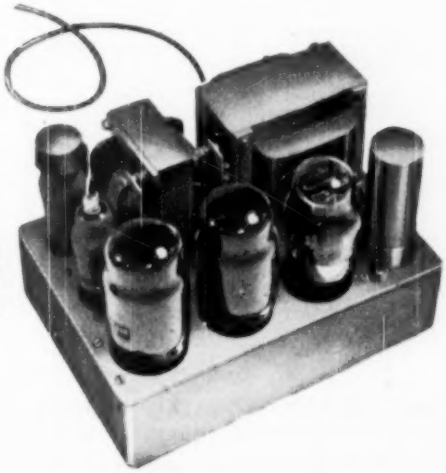

ACOUSTICAL
MANUFACTURING CO LTD
HUNTINGDON · HUNTS · TEL: 361

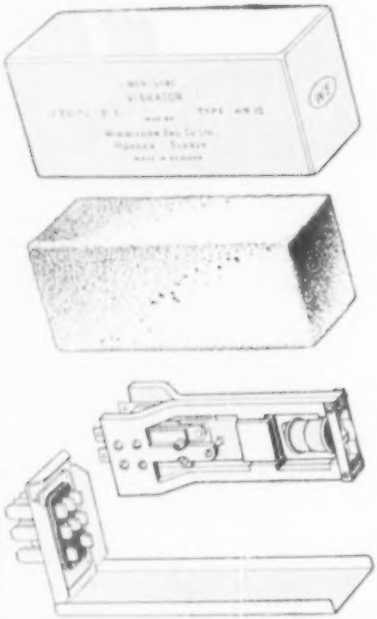

NEW!
Heavy Duty VIBRATOR

Introducing, after a lengthy period of research, a "big brother" to the popular standard WIMBLEDON Vibrators. It has all their desirable qualities, but is produced specially for heavy work. Note these advantages.—

1. Carefully designed and tested.
2. Made throughout from selected high grade materials.
3. Will give satisfactory service over a long period.
4. Reliable in operation under rated conditions of use.

Available in both SYNCHRONOUS and NON-SYNCHRONOUS Types; POWER UNITS to suit.

Write for illustrated leaflet to

WIMBLEDON
ENGINEERING COMPANY LIMITED
GARTH ROAD · LOWER MORDEN · SURREY · TEL.: DERWENT 4814-5010

ORC 4

New Wharfedale Microgroove Equaliser and L.S. tone control unit

Inserted in a Loud-speaker circuit this new tone control unit gives a falling characteristic of about 3 D.B. per octave at 500 C.P.S. upwards. The unit, a tapped inductance with a six-position switch, is ideal for matching Microgroove recording characteristics or for use as a scratch filter on worn records. It is recommended for speakers of 2/16 ohm impedance up to 30 watts.

Microgroove Equaliser and L.S. Tone Control Unit. Dimensions: 7in. x 4¼in. x 4¼in. *Weight:* 2lb. 6oz.

Price **50/-**

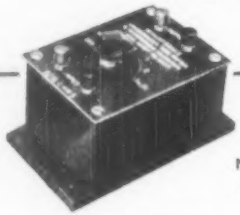

MODEL MG1.

WHARFEDALE WIRELESS WORKS
BRADFORD ROAD, IDLE, BRADFORD, YORKS

CONSTANT VOLTAGE POWER SUPPLY UNITS

MODEL 101-C

Output: 250/400v. 0.250mA max.
Stability: Better than 0.1%.
Output Impedance: Less than 1 ohm.
Output Ripple: Less than 2mV. R.M.S.
Mains Supply: 200/250v. 45-60c/s.
Regulation down to zero load.

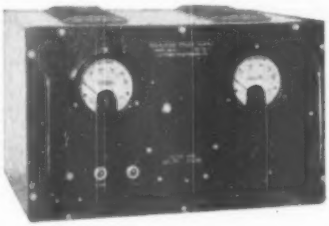

DETAILS ON REQUEST.

ALL-POWER TRANSFORMERS LTD.
CHERTSEY ROAD, BYFLEET, SURREY
Tel: Byfleet 3224/5.

An achievement of some magnitude in diminutives

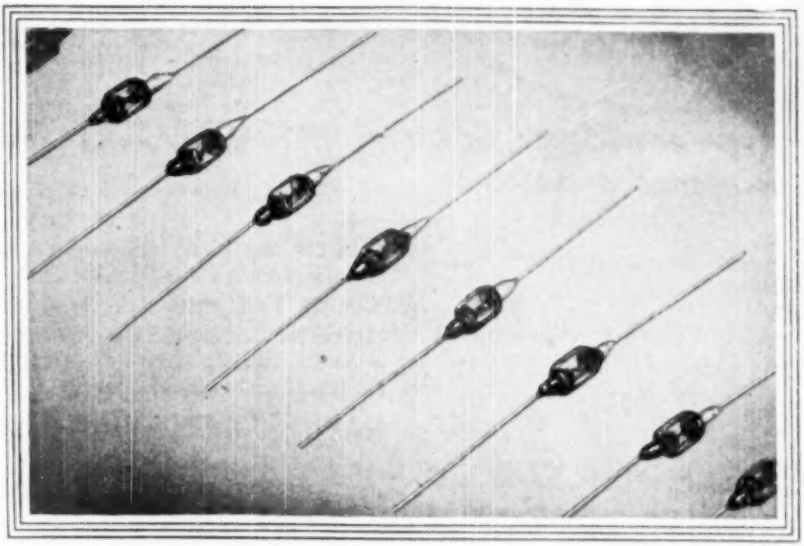

The new G.E.C. Germanium Crystal Rectifiers

Designed for soldering into circuits

1. Provides a high frequency Diode requiring no heating power.
2. Very small in physical size.
3. Of low forward and high reverse impedance.
4. Extremely low shunt capacitance — only 1PF.
5. So constructed as to give a unit of high stability and consistency.
6. Outstanding in its property to resist severe mechanical shock or vibration.
7. Indefinitely long life.

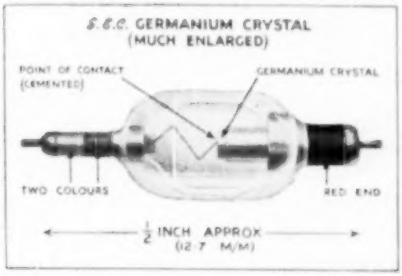

The General Electric Company Ltd. welcomes, and will give sympathetic consideration to enquiries to meet specialised requirements and specific circuit applications. Write and ask for particulars of types available to Osram Valve and Electronics Dept., Magnet House, Kingsway, London, W.C.2.

THE GENERAL ELECTRIC CO. LTD., MAGNET HOUSE, KINGSWAY, W.C.2.

TELCON'S LATEST MAGNETIC DEVELOPMENT

H.C.R. ALLOY

is now available in commercial quantities

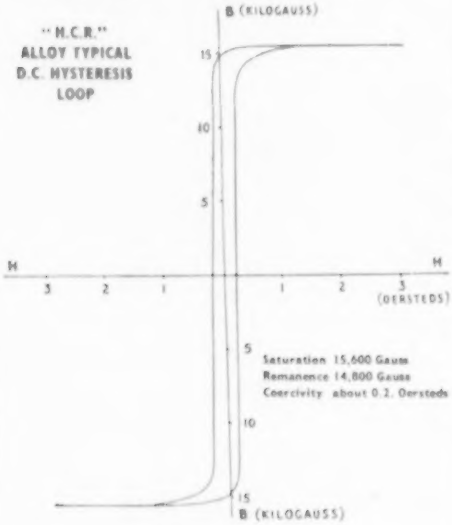

The magnetic properties of this alloy make it suitable for mechanical rectifiers, magnetic amplifiers and special forms of reactors.

TELCON Founded 1864

Full technical details on request from

THE TELEGRAPH CONSTRUCTION & MAINTENANCE CO. LTD.
Founded 1864
Head Office: 22 OLD BROAD ST. LONDON E.C.2 Tel: LONdon Wall 7104
Engineering to: TELCON WORKS GREENWICH S.E.10. Tel: Greenwich 3291

Quality HR *Television*

Sets, Chassis and Components

NEW

PM FOCUSSING UNIT

Rear operated shift controls.

Remote focussing control, worked through gears by key extending beyond cap of CR tube.

Alcomax III magnet.

Tube supporting plate for solid fixing concentric with neck of tube.

Type PM1SA for tetrodes and PM20A for triodes. **Price 36/-**

For further details ask for Technical Publication No. 44

SCANNING UNITS *for aluminised CR tubes, for circuit see Technical Publication No. 38A*

10KV. RF. E.H.T. UNITS:

TELEVISION RECEIVERS and COMPLETE SETS in SINGLE CHASSIS FORM, all with ALUMINISED CR TUBES. Circuit booklet 1/6 post free.

HAYNES RADIO LTD. Queensway, Enfield, Middx.

THE

PYROBIT

NEON MAINS TESTER WITH SCREWDRIVER

For all voltages from 60 to 440

Incorporating the most sensitive neon tube possible.

Indicating — Polarity, Potential, High Frequency, Aerial Radiation, etc., etc.

Send now for full details, prices and terms.

Sole Makers:

THE ACRU ELECTRIC TOOL MFG. CO. LTD.

123, Hyde Road, Manchester, 12

Tel. Ardwick 4284

5181

We thought of everything

. . . when we designed and built the B50 and B51

Microphones we thought of everything. Asymmetrical physical design for easy use in

either hand . . . press-to-speak switch which can be locked in the

"ON" position by rotating with thumb or forefinger . . . die-cast aluminium case finished in hard-

wearing plastic enamel . . . comprehensive range of switching arrangements to suit most possible demands

colour-coded by disc indicator on each instrument . . . two types—B50 with dynamic insert

which can safely be used under tropical and marine conditions, and where utmost reliability is essential, and

B51 with crystal insert where high output is essential. Both types

can confidently be specified for use with mobile

equipment and transmitters for speech

frequencies. And, of course VITAVOX

inherent quality is incorporated in both.

VITAVOX

MICROPHONES
LOUDSPEAKERS

Vitavox Limited, Westmoreland Road, London, N.W.9, England.
Telephone: COLindale 8671-2-3. *Telegrams*: Vitavox, Hyde, London
Cablegrams: Vitavox, London, England.

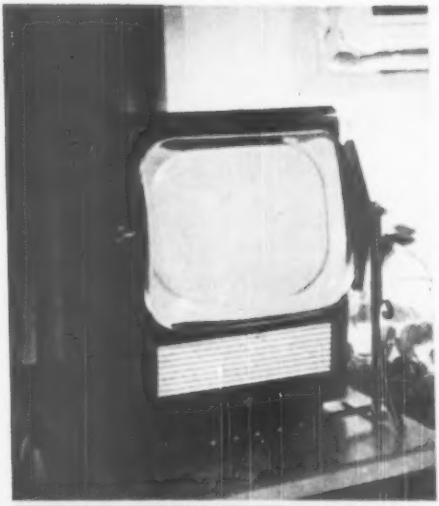

You've asked for it! .. and here it is!

From the moment that we released the Magnavista Console Lens with bronzed, wrought-iron stand, we have been asked for a companion table model. Here it is! This elegant stand carries the incomparable Magnavista Lens, which can be tilted and elevated to fit perfectly any type of receiver.

Available for 9", 10" or 12" receivers.

Type A.3, 9" Lens £6 6 0
Type C.2, 10" or 12" Lens ... £6 16 6

The MAGNAVISTA TELEVISION LENS

The only Television Lens computed by optical experts

METRO PEX LTD., 38, Gt. Portland Street, London, W.1, and King's Heath Station, Birmingham

DURALUMIN

FOR T-V AERIALS

DURALUMIN, the aluminium alloy which combines great strength with lightness, is ideally suitable for television aerials. It is of good appearance, withstands wind and weather, will not rust and is non-magnetic. Moreover, DURALUMIN is easily workable without the aid of special tools.

Our range of non-ferrous metals covers every requirement in the wireless field, whether it be aluminium alloys, brass or copper, and is available in a variety of forms including extruded rods and sections, tubes, sheet, strip and wire.

BOOTH

JAMES BOOTH & COMPANY LIMITED
ARGYLE STREET WORKS · BIRMINGHAM 7

High Fidelity Reproduction.

TYPE "K"

The S. G. Brown Type "K" Moving Coil headphones, with the following outstanding characteristics, supply that High Fidelity Reproduction demanded for DX work, monitoring and laboratory purposes, etc.

CHARACTERISTICS.

D.C. RESISTANCE, 47 Ohms.

IMPEDANCE 52 Ohms. at 1,000 c.p.s.

SENSITIVITY, 1.2 x 10⁻¹⁰ Watts at 1kc. = .0002 Dyne cm²

Descriptive Literature on request

PRICE £5.5.0 PER PAIR

Your Local Dealer can supply

For details of other S. G. Brown Headphones (prices from 30/- to 77/6) write for illustrated Brochure "W.W."

HEADPHONES WHICH UPHOLD BRITISH PRESTIGE

Telephone Watford 7241

S.G.Brown, Ltd.

SHAKESPEARE STREET, WATFORD, HERTS.

INSIDE INFORMATION

about the switch that is superior

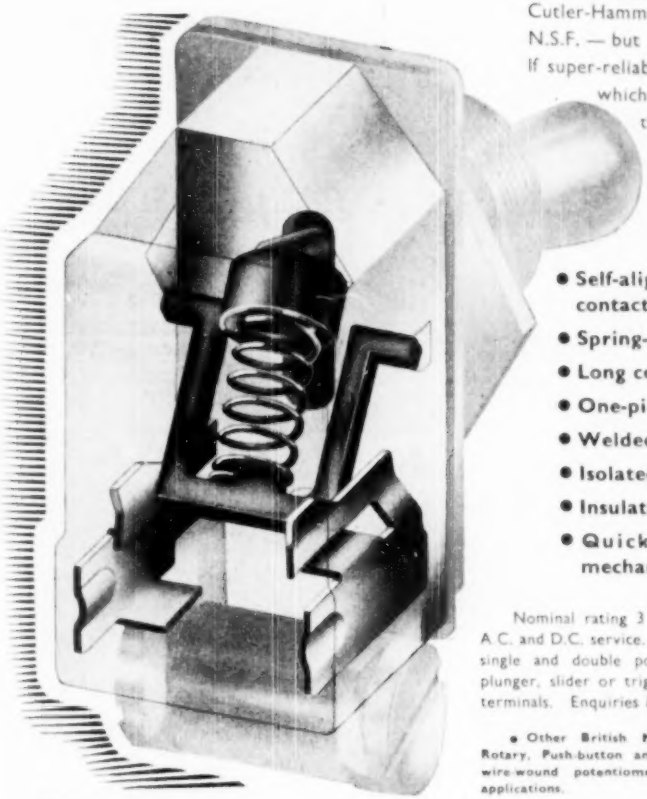

We agree that there are cheaper 3 amp. toggle switches than the Cutler-Hammer types made by British N.S.F. — but there are none better. If super-reliability is the yardstick by which you choose a switch then this is the switch for you.

NOTE THESE C-H FEATURES

- **Self-aligning "wiping" moving contact.**
- **Spring-leaf fixed contacts.**
- **Long coil spr .**
- **One-piece moulded case.**
- **Welded terminal plates.**
- **Isolated toggle lever.**
- **Insulated terminal bridge.**
- **Quick make and break mechanism.**

Nominal rating 3 amps. 250 volts—suitable for A.C. and D.C. service. Available in a wide range of single and double pole types operated by lever, plunger, slider or trigger, with screw or solder-lug terminals. Enquiries invited.

• Other British N.S.F. products include 'Oak' Rotary, Push-button and Slider switches; Carbon and wire-wound potentiometers for Television and Radio applications.

NSF

CUTLER-HAMMER
APPLIANCE SWITCHES
C-H

BRITISH N·S·F CO. LTD
KEIGHLEY · YORKS

Phone: Keighley 4221/5. Grams: ENESEF, Keighley.

LONDON OFFICE: 9 Stratford Place, W.1. Phone: Mayfair 4234.

Licensees of Igranic Electric Co. Ltd. for the above products of Cutler-Hammer Inc. Milwaukee, U.S.A.

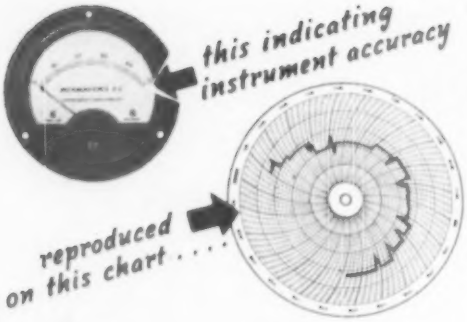

by the

Fielden

Servograph

SERVOGRAPH OPERATES DIRECTLY FROM VERY LIGHT CURRENT SOURCES, consuming but a few Micro-watts for full scale deflection. Its working principle is unique and sets up a new high standard of accuracy and robustness for graphical recording meters. SERVOGRAPH's accuracy is to *BSS.89 for Grade 1 Indicating Instruments*—because its servo-driven pen arm removes all load from the instrument movement, admits a robust and trouble-free pen, and maintains this accuracy with full or empty ink reservoir. Needing no levelling, it operates correctly in any position and can be connected directly to tachometers, thermo-couples, resistance thermometers, CO_2 indicators, pH meters and so on, repeating their accuracy on the chart. Equally useful, too, as an ammeter, voltmeter, etc., it may embody a moving iron, moving coil, dynamometer or electrostatic movement.

Please write for technical leaflets 100 M.

Movements available from 50 micro-amps. or 15 millivolts upwards

FIELDEN (ELECTRONICS) LTD.

PASTON ROAD · WYTHENSHAWE · MANCHESTER
FIELDEN ELECTRONICS (AUSTRALIA) PTY. LTD.
409 COLLINS STREET · MELBOURNE · AUSTRALIA
Specialists in Industrial Electronic Equipment

ACCELERATION of production-line speed means economy . . . .

Wherever heat applications are specified in production lines, consult Radiant Heating Ltd. Our special gas equipment can give optimum speed together with precision and economy . . .

Write to :

RADIANT HEATING LTD

for advice on heating problems

9 BARNSBURY PARK, N.1. Phone : NORth 1677/8.

W.W.

+SECOND EDITION NOW OUT! 248 PAGES!

SOUND REPRODUCTION

By G. A. Briggs

REVISED & ENLARGED, WITH 10 NEW CHAPTERS AND 193 ILLUSTRATIONS INCLUDING 75 ENTIRELY NEW DIAGRAMS.

Greatly enlarged, this fascinating work contains all the principal features from the first edition, additional pages on Cabinet Design, Disc Recording, Needles and Grooves, Pick-ups and Micro-grooves and new chapters on the following :—

EXPONENTIAL HORNS & MULTIPLE SPEAKERS. CABINET LINING. QUESTIONS AND ANSWERS. AIR LOADING. CROSSOVER NETWORKS. DIRECTIONAL EFFECTS. MAGNETIC RECORDING. RIBBON SPEAKERS. NEEDLE INSPECTION. SAPPHIRE, TUNGSTEN AND DIAMOND.

OBTAINABLE FROM RADIO DEALERS, BOOKSELLERS OR DIRECT FROM THE PUBLISHERS:

SOUND FULL MEANING 10/6 (11/- POST FREE)

LOUDSPEAKERS

By G. A. Briggs

3rd Edn. (4th Impression)

NOW READY!

The Why and How of Good Production

88 PAGES
36 ILLUSTRATIONS

5/- (5/3 Post Free)

Enjoyment of these books is enhanced by the occasional flashes of humour now expected from Mr. Briggs.

Wharfedale WIRELESS WORKS

BRADFORD ROAD, IDLE, BRADFORD, YORKS.

Telephone : Idle 461. Telegrams : "Wharfdel, Idle, Bradford."

PREMIER RADIO COMPANY

MORRIS & CO. (RADIO) LTD.

PREMIER TELEVISOR KITS

FOR THE LONDON OR BIRMINGHAM FREQUENCIES

USING 9" OR 12" MAGNETIC CR TUBES

£19. 19. 0. (Carriage & Packing 15.-) *including all parts, valves and loud speaker, but excluding CR TUBE*

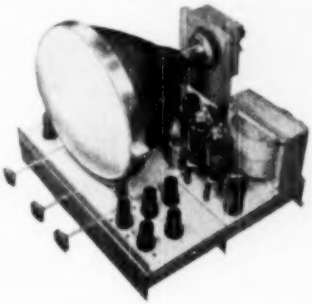

CIRCUIT DETAILS

The Vision Receiver consists of 4 R.F. stages (EF54's) which are followed by a Diode Detector and Noise Limiter (6H6) which is directly coupled to the Video valve (EF54).

Complete Kit with valves, **£3 16 0.**

Carriage and packing 2/6.

The Sound Receiver comprises 3 R.F. stages (6SH7's) followed by a Double Diode Triode (6Q7), which acts as Detector and L.F. Amplifier. A Noise Limiter (EA50) is also incorporated. The output valve (6V6) drives a 10in. P.M. Moving Coil Speaker with closed field magnet, which is included in the Time Base Kit.

Complete Kit with valves, **£3 1 0.**

Carriage and packing 2/6.

The Time Bases employ blocking oscillators on both line (6SH7 and 807), and Frame (VR137 and 6V6). E.H.T. (non-lethal) is taken from the Line Output Transformer through a voltage doubler employing two valves (VU111). The Sync separators are 6H6 and 6V6. Permanent Magnet Focusing.

Complete Kit with valves, **£8 5 6.**

Carriage and packing 5/-

The Power Supply is from a double wound mains transformer completely isolating the receiver from the mains. The H.T. Rectifier is a SU4G.

Complete Kit with valves, **£4 16 6.**

Carriage and packing 5/-

"MAGNETIC" CONSTRUCTION BOOK 3/-

EACH KIT OR INDIVIDUAL PART AVAILABLE SEPARATELY

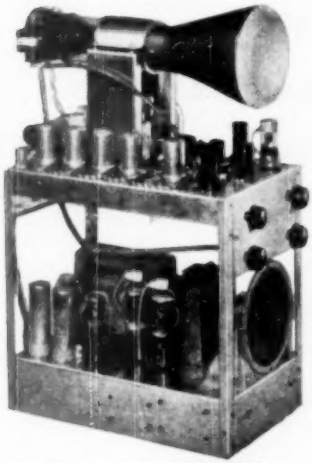

A well-made walnut finish **PEDESTAL CABINET** is available from stock at **£5 10 0**, plus 7/6 carriage and packing.

Working models can be seen during transmitting hours at our Fleet Street and Edgware Road branches.

FOR THE LONDON OR BIRMINGHAM FREQUENCIES

USING VCR97 TUBE

£17. 17. 0.

(including Tube)

As is usual in all Premier Kits, every single item down to the last Bolt and Nut is supplied. All chassis are punched and layout diagrams and theoretical circuits are included.

Five Easy to Assemble Kits are supplied :

VISION RECEIVER with valves, carriage 2/6	£3 13 6
SOUND RECEIVER with valves, carriage 2/6	£2 14 6
TIME BASE with valves, carriage 2/6	£2 7 6
POWER SUPPLY UNIT with valves, carriage 5/-	£6 3 0
TUBE ASSEMBLY, carriage and packing 2/6	£2 18 6

This unit includes the VCR97 Tube, Tube Fittings and Socket and a 6in. P.M. Moving Coil Speaker with closed field for Television. The instruction book costs **2/6**, but is credited if a Kit for the complete Televisor is purchased.

Any of these Kits may be purchased separately ; in fact, any single part can be supplied. A complete priced list of all parts will be found in the instruction book.

20 Valves are used, the coils are all wound and every part is tested. All you need to build a complete Television Receiver is a screwdriver, a pair of pliers, a soldering iron and the ability to read a theoretical diagram.

The following sensitivity figures prove that the Premier Televisor Kits are capable of reception at greater distances than any other standard commercial kit or receiver whether T.R.F. or Superhet.

VISION RECEIVER

Sensitivity	25μv for 15 v. peak to peak measured at the Anode of the Video Valve.
Sound Rejection	Better than 40 db.
Adjacent Sound Rejection	Midland Model. Better than 50 db.

SOUND RECEIVER

Sensitivity	20μv. Vision Rejection better than 50 db.

When ordering Televisor Kits

PLEASE STATE IF THE LONDON OR BIRMINGHAM MODEL IS REQUIRED

Our NEW SUMMER CATALOGUE—Now ready—Price 6d.

BRANCHES AT

207, EDGWARE RD., W.2 Phone : AMBassador 4033

AND AT **152-153, FLEET STREET, E.C.4** Phone: CENtral 2833

All **POST ORDERS** to 167, LOWER CLAPTON ROAD, LONDON, E.5 'Phone AMHurst 4723

Terms of Business: Cash with order or C.O.D. over £1. Send 2d. Stamp for list.

EDGWARE ROAD IS OPEN UNTIL 6 p.m. ON SATURDAYS

THE RADIO TELEPHONE YOU CAN TUCK UNDER THE DASH

B.C.C. V.H.F.

RADIO TELEPHONE EQUIPMENT

The B.C.C. Mobile Radio-Telephone illustrated here will give two-way communication with the Fixed Station up to a distance of 25 miles or with the portable Pack-set up to 5 miles.

This B.C.C. equipment sets a new standard in V.H.F. Communications Technique and has been approved by the G.P.O. The complete range consists of:

Fixed Stations ...Models L111 & H111
Mobiles ... ...Models L67 & H67
Pack Sets ... ...Models L45V & H45V
Hand Portables ...Models L45AV & H45AV

This equipment can be supplied to cover any spot frequency in the 75-100 Mc/s or 150-185 Mc/s bands.

All enquiries to:—

MARCONI'S WIRELESS TELEGRAPH Co. Ltd., Chelmsford, Essex.

NOTE THESE FEATURES

Size T.R. 11½in. × 8in. × 4in. (30 cm. × 21 cm. × 10 cm.)
Power Pack 8in. × 5½in. × 3½in. (21 cm. × 14cm. × 8cm.)
Weight T.R. 15½ lbs. (7kg.), Power Pack 9½ lbs. (4.2kg.)

The Transceiver is easily installed below the instrument panel with the small power pack in any convenient place. The remarkably low battery drain permits connection of the set to the car batteries, obviating the cost and weight of auxiliary accumulators or larger dynamo.

BRITISH COMMUNICATIONS CORPORATION LTD. Gordon Avenue, Stanmore, Middlesex. Tel. GRImsdyke 1455

PLAN YOUR CAREER

RADIO - TELEVISION and other INDUSTRIAL ELECTRONIC subjects

ELEMENTARY & ADVANCED COURSES

DAYTIME

- Principles and Practice of Radio—1 year.
- Telecommunication Engineering—2 years.
- Electronic Engineering—3 years (*including one year's practical training in E.M.I. Factories*)—leading to C & G full Technological Certificate.
- Marine and Air Radio Officers' Course (*for P.M.G. Licence*).

also HOME STUDY

- Radio
- Television
- Industrial Electronics
- Maths.
- Physics.

Write for FREE BOOKLET to Dept: 16

E.M.I. INSTITUTES

10 PEMBRIDGE SQUARE, NOTTING HILL GATE, LONDON, W.2
Telephone: BAYswater 5131/2.

Associated with H.M.V. MARCONIPHONE COLUMBIA ETC

E.1668

M.R. SUPPLIES Ltd

This month we are able to offer some exclusive and remarkable bargains. Notwithstanding the sensational nature of some of these offers the material is new, perfect and entirely satisfactory, as is to be expected with our merchandise. All prices net.

KLEENAIR AIR CONDITIONING UNITS. For elimination of dust, smoke, odour and all traces of Carbon dust from the atmosphere. Fitted Delco silent running induction motor (no radio interference) and mounted in handsome powder coated 14in. diameter with grille in front and louvres at the side. Operation 200/250 v. A.C. For wall or ceiling mounting, no hole required. Consumption 40 watts. Colours—Ivory, Bronze, Blue or Green (give second choice). These units bear a list price of £9/15. We now offer a limited number brand new, at only **35/-** each (dea. 2/6).

(We also have some of these Kleenairs for 110 v. A.C.).

EXTRACTOR FANS (Air Conditioning & Engineering, Ltd.). Operation 200/250 v. A.C. with excellent induction motor. Efficient 8in. impeller in 12in. square mounting frame with rubber cushions. Colour Ivory and Blue. Air Displacement 36,000 cub. ft. per hour, silent running. These units bear a list price of £8/16. We now offer a limited number, brand new, at only **52/6** (dea. 2/6). Early application for above two items is advised.

DELCO INDUCTION MOTORS (Shaded Pole). A few of these, very slightly soiled at a fraction of list price. Dia. 12in., length 9in. External end operator is provided with detachable lever of shaft. For 110 v. A.C. or two in series for 200/240 v. A.C. Price **11/6** each, **two for 20/-**, post paid. Also Hoover Shaded Pole Motors, 200/250 v. A.C. with double ended shaft, frame 3½in. x 3½in., 1,200 r.p.m., **29/6** (dea. 1/-).

AUTOMATIC VOLTAGE REGULATORS (Carbon Pile). Automatically holds supply at any voltage between 190 and 250 v. A.C. Loading up to 500 watts. Contained in enclosed steel case 6½in. x 7½in. x 10½in. high, with terminal panel and pre-set adjustment on 17in. Easy to install—diagram supplied. Ideal for television and lighting. Brand new, **57/6** (dea. 4/6).

LONDEX A.C. RELAYS. 200/250 v. A.C. coil. Type L.F. (unmounted). With 3 changeover and one make 4 amp. switches, **19/6**. Also Londex low-capacity Aerial Change over Type, operation 110 and 200 v. A.C. Equip. is all 4 amps. mounted on baseboard 6in. x 4in., **15/6** (dea. either 1/-). We have a large number of miniature Londex and other relays—details on request.

SYNCHRONOUS ELECTRIC CLOCK MOVEMENTS. 200/250 v. 50 c/s. Fitted spindles, 4in. hands, reversible and seconds hands, single-hole mount, silent running, supplied, with plastic dust cover and fixs. ready for use, **27/6**. Set of three bands for 5/7in. dial, 2 in. deep, 9d.

SELENIUM RECTIFIERS. (All full-wave unless otherwise stated. D.C. delivery up to 24 v., 1.5 amp.) **12/6**. 24 v., 4 a., **25/-**. 24 v., 6 a., **27/6**. 42 v., 4 a., **37/6**. 16 v., 8 a., **29/6**. 110 v., 500 m.a. (half-wave) **18/6**. (Four of these will provide mains voltage rectification and inductor full-wave rectified D.C. approx. 220 v. 1 amp.). Price effour, **£3/8/6** (dea. 3/-). Very special offer of Fuseel Cooled Industrial type High Duty Selenium full-wave Rectifiers. D.C. delivery 20 v. 20 amps., or 40 v. 10 amps., either **72/6**. (These are listed at £6 each). A pair in bridge will supply 20 v. 50 amps., **£7** the pair (dea. 2/6). Also same type, pair in bridge to supply 40 v. 20 amps., **£7** pair. Or to supply 120 v. 10 amps., **£7** pair. Four in bridge to supply 240 v. 10 amps., **£13** the four (dea. 5/-).

SOLENOIDS. Powerful unidirectional pull approx. 40 lb. pull. Pot 3½in. x 3½in. with rocking arm mounted on the bracket, 12/24 v. D.C., **10/6** (dea. 1/-).

PUBLIC ADDRESS SPEAKERS. Brand new G.E.C. 10 watts Pressure Unit (15 ohms and—low impedance—speaker rated) with 30in. all metal Projector Horn, **£5/17/6** (carriage paid England). Or with 40in. all metal Exponential Horn, **£8/15/-** (carriage paid).

STEEL TRIPODS for all P.A. speakers, ext. to 11ft., very strong and rigid, **55/-** (dea. England).

M. R. SUPPLIES Ltd., 68, New Oxford Street, London W.C.1

Telephone: MUSeum 2958

ELPREQ NEWS

SOMETHING TO MAKE

THIS month why not make an electronic timer, a device which can be put to dozens of uses, i.e., if you are interested in photography it can be used to control time exposures or enlargings, etc. The instrument can be set to any length of time from parts of seconds up to 3 minutes; after the pre-set period the timer will switch other apparatus on or off. Circuit diagrams and instructions, **2/3d.** Complete Kit of Parts including valves, mains transformers, power pack, large and small condensers, sensitive relay, pot meters, metal chassis, etc., **59/6d.**, post free.

MOVING COIL UNITS.

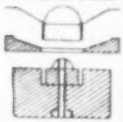

THESE are perfect speakers in miniature. The illustration of the 3 main parts shows speech coil, dust cover and permanent magnet. The front is fitted with protective grill and the diameter of the front is 1⅝in. and the depth is 1¼in. Price **4/9d.** each.

Note—these can also be used as microphones. We can also supply a suitable matching transformer at **3/6d.**

SALFORD SIGNAL GENERATOR.

THIS is a precision laboratory instrument with a particularly fine attenuator and R.F. meter, internally modulated and with built-in power pack for working direct from A.C. mains. Frequency range is 5.5 to 55 mc/s. Limited quantity only, price **£12/10/-** each plus partly returnable packing case and carriage charge of 10/-.

THIS MONTH'S SNIP.

THIS is the communications receiver type No. R.1155 which is one of the finest communication sets ever made. Designed by leading engineers and made by one of our famous Companies, this receiver will undoubtedly give you years of good listening. Most readers will know it fairly well. The receiver covers the broadcast bands, long waves and medium waves, and short waves up to 20 mc/s. It contains 10 valves and really brings the stations in. August prices: **£6/10s.** for a good complete receiver; **£7/10/-** for same grade receiver tested and re-aligned; **£8/15/-** for unused receiver; or **£9/15/-** for unused receiver tested and re-aligned. All plus partly returnable packing case deposit and carriage charge of 10/-.

BELLOWS COUPLING.

THIS is a coupling unit for ¼in. spindles which opens and closes rather like a bellows or concertina. It is very useful where two spindles are out of alignment, and where the device to be controlled screws in and out such as in slug tuning. Price **1/11.**

CRYSTAL DIODES.

THE simple crystal set which will operate without batteries is definitely coming back into popularity again. The new germanium crystal diodes are ideal for these receivers and are probably the cause of this new interest. Price **3/6** each.

SERVICE DATA.

OUR folder No. 2 consists of 100 data sheets covering most of the popular American T.R.F. and superhet receivers "all dry" etc., which have been imported into this Country. Names include Sparton, Emmerson, Admiral, Crossley, R.C.A. Victor, etc. Each sheet gives circuit diagrams and component values, alignment procedure, etc., etc. Price for the folder of 100 sheets is **£1.** Post free.

TRANSMITTING VALVES

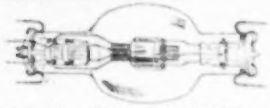

THE valve illustrated is the VT31 a transmitting tetrode with an R.F. output of 250 watts. The overall size of this valve is 14¼in. long by 6¼in. across the bulb. We are able to offer this American made valve at **18/6** which is only a fraction of original cost. So this is your chance to do some experimenting or to make that special piece of equipment. Its heater is rated at 12 v. 8 a. We have many other transmitting valves in stock at equally interesting prices, see list a few below and invite your enquiries for any not listed —

803 Tetrode 125 watts, htr. 10v. 5a., **10/-**
805 Triode 125 watts, htr. 10v. 3½a., **10/-**
813 Tetrode 100 watts. htr. 10v. 5a., **35/-**
DET4 Triode 25 watts, htr. 4v. 2a., **12/6**
RK28A. See 803 above.
TZ40 Triode 40 watts, htr. 7.5v. 2.5a., **27/6**
DET25 Triode 36 watts, htr. 5v. 1.25a., **15/-**
TZ05 20 Triode 40 watts, htr. 6v. 1.1a., **15/-**
807 Tetrode, 30 watts htr. 6.3v. 1a., **5/6**
6L6 Tetrode 12.5 watts, htr. 6.3v. .9a., **8/9**
6J6 Dbl Triode 3.5 watts, htr. 6.3v. .45a., **10/6**
35T Triode 50 watts, htr. 5v. 4a., **25/-**.
PLEASE INQUIRE ABOUT OTHER TYPES.

RECTIFYING VALVES (MERCURY).

VU2 9600 m.A. @ 4,000v. htr. 4v. 1a., **7/6.**
866A 250 m.A. @ 10,000v. htr. 2.5v. 5a., **10/6**
872 1250 m.A. @ 10,000v. htr. 5 v. 7.5a., **17/6**
RZ1 150 750 m.A. @ 1,000v. htr. 4v. 1a., **15/-**
VU508 1,000 m.A. @ 8,000v. htr. 4v. 1a., **15/-**
GU21 3,500 m.A. @ 11,000v. htr. 4v. 11a., **45/-**
OTHER TYPES WITH OUTPUTS UP TO 5 AMPS.

RECEIVING VALVES.

WE carry a full range of all types ancient and modern, send for special list, or if in a hurry ask us to send your valves C.O.D. We also stock Tungar Rectifiers, Voltage Regulators, Photo Cells, Magnetrons, Clystrons, Thyratrons, etc., etc. Send us your enquiries.

EQUIP YOUR LABORATORY.

IN the service room or the laboratory, you have often needed current at various odd voltages. We can supply a transformer which unmodified will give, 2, 4, 6, 8, 10 or 12v or by adding one additional winding of 5 turns which can be done without dismantling (there is plenty of room between the winding and the laminations) any voltage between 1 and 13 may be obtained. Over 10 amps may be drawn from this transformer at these voltages. Price **12/6** each.

PLUG & SOCKET.

THIS brass cased plug and socket is extremely robust and ideal for P.A. or outside work. Ideal also for taking power to units as it insulates the ends of the wires. Contacts are quite suitable for carrying up to 10 amps so this can be used for lighting or power. Price **2/6** per pair.

RELAYS.

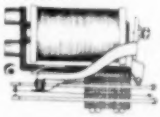

AMERICAN made with heavy duty contacts. Sensitive type which closes at approximately 4 m.A., **12/6.** Non-sensitive type for closing on 12-24v., **4/6.**

EXTRA light weight, extra sensitive for high speed or radio control work, weight only 1½ oz., closes on 2 m.A., solid, platinum change-over contacts, adjustable pressure. Price **13/6.**

CONTACTOR for breaking 25 amps, coil voltage is 24v. D.C., but with a re-wind or a small rectifier these will close off A.C. mains. Very heavy duty solid silver contacts. Price **1/6**, **15/-** doz.

POST Office types. Upright mounting, prices as follows: sensitive types with coil resistances of 2,000 ohms and over with 1 pr. of contacts **7/6**, with 2 pr. of contacts, **8/-**, then **6d.** extra per pair of contacts.

Medium sensitivity type 1,000 ohms and over with 1 pr. of contacts, **4/6** extra contact as above.

Low voltage types coil resistances of 100 ohms and over with 1 pr. of contacts, **3/6** extra contacts as above.

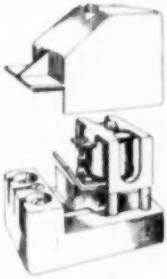

TOTALLY enclosed, in bakelite, this relay has a 24v. coil but can of course be re-wound for mains operation. Its contacts are suitable for breaking 20 amps. Price, **4/6**, **48/-** doz.

IMPULSE OPERATED RELAYS.

THIS is sometimes known as Selector Switch 10B. It consists of a solenoid, the armature of which is connected to a ratchet wheel so that each time the solenoid is energised the ratchet wheel moves round one notch. Secondary switches are built-in which permit continuous running, inching, following a four position switch and undoubtedly a host of other operations. Articles have appeared in journals showing how these may be operated by radio impulses and thus control models. Price **3/9** each, **38/-** per dozen.

OUR BARGAIN CORNER.

IT will pay you to find time to call upon us at our Ruislip Show-rooms. Our "Bargain Corner" is particularly popular as there are truly bargains to be picked up. For instance last month we had H.R.O. receivers at only 30/- each, not complete, of course, but undoubtedly real bargains. Our premises are very close to Ruislip Manor Underground Station. We close Wednesday afternoon, but are open until 5.30 p.m. on Saturday.

Orders under £2 add 1/6, under £1 add 1/-. Portable items can be sent C.O.D. additional charge approx. 1/-. Good stock of all items at time of going to press. List 6d.

Telephone: Ruislip 5780

ELECTRONIC

PRECISION EQUIPMENT (2) ELECTRON HOUSE, Windmill Hill, RUISLIP MANOR, MIDDX.

THE PROVEN LONG-DISTANCE AERIAL

TYPE FA22

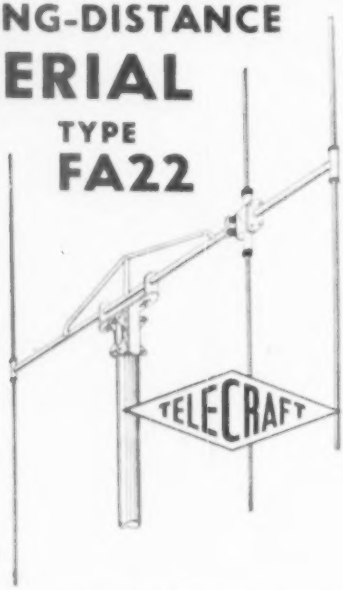

Specially designed for long-distance reception. In actual tests greater signal strength has been received than from any standard aerial, due to the fact that the FA22 is an engineered array which can be safely erected in the most exposed positions and has many other unique features. The special TELECRAFT pole-mounting device gives perfect balance, together with easy rigid fixing at almost any point. All connections guaranteed waterproof. Mast clamp is adjustable to fit any mast 1½"-3" diameter. No extra struts are necessary as the unit provides its own "Cantilever" supports.

AERIAL COMPLETE
less Mast & Lashings - - - £5.12.6

LONDON AND MIDLAND FREQUENCY
LB Adjustable lashing, 22/6. 2in. or 4in. Mast, 30/- per pr.

Dealers Report GOOD RECEPTION from these areas with this Aerial

LEEDS	SWINDON	HASTINGS
BURNLEY	IPSWICH	WORTHING
LIVERPOOL	MONMOUTH	CHICHESTER
COLWYN BAY	DOVER	PORTSMOUTH
LLANDUDNO	MARGATE	PETERBOROUGH
SWANSEA	ROSS-ON-WYE	SOUTHWOLD
BRISTOL	WELSHPOOL	DONCASTER
BRIGHTON	DEAL	ETC., ETC.
BATH	FOLKESTONE	

DEFINITE PROOF THAT THE FA22 IS A TV AERIAL OF OUTSTANDING MERIT

ASK YOUR DEALER ABOUT IT or in case of difficulty write to :—
HEAD OFFICE & FACTORY

TELECRAFT

LIMITED
Specialists in the Manufacture and Design of TV Aerials since 1937

QUADRANT RD., THORNTON HEATH, SURREY
THOrnton Heath 2985
Depots : BRISTOL, BIRMINGHAM, WORTHING

SRC on the move

Our friends will be pleased to learn that we have moved to a newly built factory. Increased production space will mean better service

STABILITY RADIO COMPONENTS LTD.

COMMERCE ESTATE, WOODFORD AVENUE, LONDON, E.18.
BUCKHURST 6501/2

WILLIAMSON AMPLIFIERS

built to specification—W.W., *August 1949*

The fidelity of reproduction given by the Williamson Amplifier is now an accepted standard throughout the world. This high standard is made possible by the following important features.

- Specially designed output transformer.
- Low phase shift.
- Heavy feedback, which includes the output transformer and all the valves.

These features make possible :

- Low linear distortion, with less than 0.1 per cent. harmonic content.
- Low intermodulation distortion.

PRICES :

Amplifiers	from **£19 19 0**	No tax
Pre-Amplifiers. . .	from **£8 0 0**	
Tuners	from **£10 10 0**	Plus tax

Full details from the manufacturers :

GOODSELL LTD.,
40, GARDNER STREET, BRIGHTON, SUSSEX
Telephone : 26735

Demonstrations at :—
HOLLEY'S RADIO STORES, CAMBERWELL
H.P. Terms Available

GOODMANS

AUDIOM Loudspeakers

The unrivalled series of medium and heavy duty P.M. reproducers.

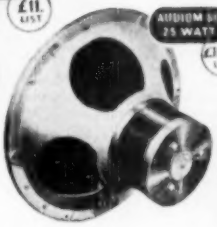

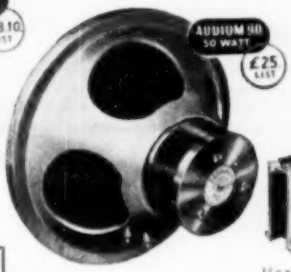

AL-6 CABINET LOUDSPEAKER
incorporating
Goodmans 12" Audiom 60
Finish: natural polished seasoned mahogany
Size: 17" x 17" x 8½".
List Price: £11 5s.

Connection: two-way moulded plug and socket.
Available with transformer, £2. 10s. extra.

Meet us at the
RADIO SHOW
Sept. 6-16. Stand 85.

Heavy duty multi-ratio transformer Model MR/T4

GOODMANS INDUSTRIES LIMITED

Lancelot Road, Wembley, Middlesex. *Telephone:* Wembley 1200 (8 lines). *Telegrams:* Goodaxiom, Wembley

Simple *and* Reliable

IN areas where the cost of installation and maintenance of line communications is prohibitive, the Redifon GR. 49D comes into its own. Many hundreds have already been supplied for small communities, oilfields, forestry workings and similar assignments. Equally suitable for static or mobile installations, the set is a complete transmitting and receiving station and can be used for point-to-point or ground-to-air services with both C.W. and R.T. facilities. Radio Telephony operation is as simple as using an ordinary dial telephone, and the fully tropicalised design ensures low operating costs and complete reliability under the most adverse climatic conditions. Contact Redifon for full details.

COMMUNICATIONS
Redifon
Radio

Radio Communications Division

REDIFON LIMITED, BROOMHILL ROAD, WANDSWORTH, S.W.18

DESIGNERS & MANUFACTURERS OF RADIO COMMUNICATIONS & INDUSTRIAL ELECTRONIC EQUIPMENT. Phone: VANdyke 5691

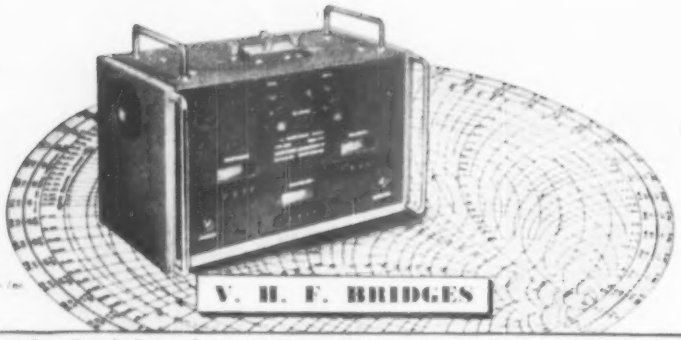

V. H. F. BRIDGES

for balanced and unbalanced measurement at frequencies between 1 Mc/s and 100 Mc/s.

Wayne Kerr

THE WAYNE KERR LABORATORIES LIMITED, NEW MALDEN, SURREY PHONE: MALDEN 2202

The Revolutionary

GOLDRING

Headmaster

HYPERFIDELITY

PICK-UP

With an interchangeable Pick-Up Head for every type of record.

Supplied in attractive Display Carton complete with Goldring Tonaliser and Transformer

★

Goldring Products include:-

PICK-UPS, PICK-UP HEADS, SAPPHIRE JEWEL POINT NEEDLES, AND RADIOGRAM ACCESSORIES.

Write for full Descriptive Lists and Technical Information

ERWIN SCHARF

49-51a DE BEAUVOIR ROAD, LONDON, N.1

Telephone: CLISSOLD 3434

OKERIN

- ***WAXES***
- ***DI-JELLS***
- ***COMPOUNDS***

Electrical Engineers know the variety of uses for which Okerin waxes are produced.

We are constantly meeting the special need for industrial purposes and this service is at your disposal. Just let us know your requirements.

Telephone: Temple Bar 5927

ASTOR, BOISSELIER & LAWRENCE LTD.

Sales Dept.: Norfolk House, Norfolk St., Strand, W.C.2

Works & Laboratories: West Drayton, Middlesex

THE 'Antex' TELEVISION AERIAL

goes further afield!

NOW A POLE MOUNTED MODEL!

By the introduction of this pole mounted type the manifold advantages of the famous 'Antex'—stronger signals, reduction in interference and its highly directional properties—are brought to the outlying areas. Simple in design, simple to instal, the 'Antex' is essentially a trouble-free aerial.

The impedance is 70-80 ohms; forward gain 5.0 db (approx. 2 db greater than a normal 'H' array); front/back ratio 22.0 db; weight 1½lb.

MODEL XP 'ANTEX' for London Area.
MODEL XP B 'ANTEX' for Birmingham Area.
Complete with pole mounting fitting

Retail Price £2. 3. 0.

The Electrical and Mechanical Design is fully protected. Pat. No. 630795 & Prov. Pat. 12178/49 & Reg. Des. 859630.

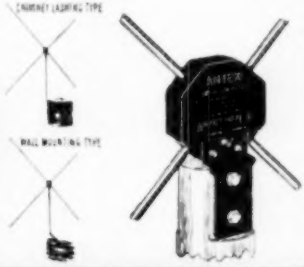

ANTIFERENCE LIMITED
67 BRYANSTON STREET · LONDON · W·1

Webb's RADIO

FOR

"LONG-PLAYING"

GRAMOPHONE EQUIPMENT

Call and hear 33⅓ r.p.m. apparatus at Webb's, giving high-fidelity reproduction with almost non-existent surface noise—a revelation in general realism.

CONNOISSEUR DUAL-SPEED MOTOR.

A precision-made mechanism, giving either 78 or 33⅓ r.p.m. at the turn of a switch. A.C. operated 200/250 volts, **£13 15 0**. Plus P.T. **£5 19 2**

CONNOISSEUR "SUPER LIGHTWEIGHT" PICK-UP.

Has three interchangeable heads for Standard, Microgroove and older standard recordings. Low downward pressure of 10/12 grams for standard recordings, and 5/7 grams for microgroove.
Price of Pick-up with One Head **£4 0 0**. Plus Purchase Tax **£1 14 8**
Extra heads cost each **£2 10 0**. Plus Purchase Tax **£1 1 8**.
Transformer **15/-**.

"COSMOCORD GP.20" PICK-UP.

A high fidelity crystal pick-up taking interchangeable heads for standard and microgroove work. Output 0.5 volts at 1,000 c.p.s. Permanent sapphire. Has automatic bass boost allowing direct fitment to domestic radio.
Price with one head, **£2 10 0**. Plus Purchase Tax **£1 1 8**.
Alternative head, standard or microgroove, costs **£1 10 0**, plus **12/4** Purchase Tax. Pressure automatically adjusted by changing the head, being 12/14 grams for standard, and 6/10 grams for microgroove.

DECCA "337B" DUAL-SPEED HIGH FIDELITY PLAYING DESK.

Built in strong wood case, covered leather cloth with carrying handle. Size 15½ x 13½ x 6½in. high. Robust constant speed induction motor giving both 33⅓ and 78 r.p.m. Two interchangeable 3-pin plug-in pick-up heads with sapphire styli for 33⅓ and 78 r.p.m. records. Difference in weight of heads provides automatic weight compensation. Spring balanced arm.
Price **£11 14 6**. Plus Purchase Tax **£5 1 7**.

DECCA "33A" OPEN TYPE PLAYING DESK.

Robust, constant speed 33⅓ r.p.m. motor, rubber covered turntable. Lightweight pick-up with spring balanced plastic arm, replaceable crystal capsule with sapphire stylus.
Price **£8 4 2**. Plus Purchase Tax **£2 13 10**.

DECCA "33B" PLAYING DESK WITH LID.

Same specification as "33A" for motor and pick-up. Fitted in leather cloth covered wood case with lid.
Price **£9 8 6**. Plus Purchase Tax **£3 13 0**.

DECCA "33C" PLAYING DESK WITH LID.

As model "33B" but fitted with "Decca ffr" lightweight pick-up, either type "C" 850 ohms impedance, or type "D" 4,200 ohms impedance.
Price **£8 8 6**. Plus Purchase Tax **£3 13 0**.

DECCA "LONG-PLAYING" HEADS.

For fitment to existing standard type "Decca ffr" pick-ups. Supplied with a compensating counter-weight. Type "C" 850 ohms, and type "D" 4,200 ohms.
Both types, price **£2 8 0**. Plus Purchase Tax **£1 0 11**.

Webb's Radio, 14, Soho St., Oxford St., London, W.1.

Phone: GERrard 2089. Shop hours 9 a.m.—5.30 p.m. Sats 9 a.m.—1 p.m.

CLYDESDALE

Bargains in Ex-Service Radio and Electronic Equipment

THAT "SHARP CHANNEL" Q5'er

BC-453 (and equivalent ARC-5 series) Command Receiver is quite effective and justifiably popular as a sharp channel I.F. system to follow any conventional communication receiver having an I.F. of 190 to 550 kc/s. The receiver operates with an I.F. of 115 kc/s. Except for rewiring the heater circuit (24 volt as is) to conform with the supply available, no further major modifications need to be done.

The BC-453 makes an excellent car radio for M.W. reception, and can be readily modified by installing the CARLTON COIL UNIT, price 10/6d. from us, correcting the valve heater circuit to conform with supply available, and installing a speaker and HT Vibro-pack.

CLYDESDALE'S PRICE ONLY **63/-** CARRIAGE PAID

Circuit diagram supplied with each unit.

150 WATT RIG COMPONENTS OR V.F.O.

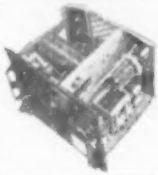

Ex-U.S. Tuning Range "B" constitutes a basis for a 7 Mc/s ECO stage with a PA assembly capable of handling 150 watts.

Numerous components include a double spaced 125 Pf. PA variable with S.M. drive plus a 150 Pf. variable condensers with micro-drive. Tapped tank coils and low loss switches.

Enclosed in a black crackled case 12 x 9½ x 8½in. with handles.

CLYDESDALE'S PRICE ONLY **19/6** CARRIAGE PAID

A.C. Mains Power Unit with Built-in Modulator. For W.S 16 Transmitter.

A complete 110 to 250 volt cycle A.C. Mains Power Unit, consisting of one L.T. supply transformer — 3/4v. 4a. for the rectifier, etc., at 3.25-0-3.25v. 8a. winding supplying the 6.3v. circuit of a built-in modulator, suitable for swinging a transmitter carrier of 100w. input, plus an outlet for the supply of an external transmitter. A 200-0-200v. 50 m.a. fully smoothed supply for bias needs a second transformer (H.T.) 500-0-500v. 200 m.a. (twice) rectified and smoothed, one supply for the internal modulator, the second supply is carried to an outlet for external use. Valves include: 3/6C5, 2/807 and 2/AV1

CLYDESDALE'S PRICE ONLY **£12/10/0** CARRIAGE PAID

Brand New.
Hybrid Unit MI-7182 by RCA.

This unit is electrically similar to an A.C. Bridge consisting of four arms (3 600 ohm. and 1 variable).

When the bridge is in balance, no signals are inter-transferred. Frequency range 300-3,000 cycles. 11 x 10½ x 6½in.

Finished Dove grey complete with instruction book and circuit.

CLYDESDALE'S PRICE ONLY **45/-**

5 Valve Superhet Feeder.

Type 78 Superhet "feeder" receiver unit with a frequency range of 2.4 to 5 and 5.8 to 13 Mc/s in two switched bands. This receiver can be easily modified for use with a Mains power unit.

FEATURES: Built in 100 kc/s crystal substandard. 53:1 ratio frequency calibrated drive. Dessynn trimmer control provides a 15 Kc/s remote variable tuning control. Illuminated dial etc.

Originally intended for a 26v. heater supply, but can be very simply altered for standard input.

CLYDESDALE'S PRICE ONLY **47/6** CARRIAGE PAID

Circuits supplied with each unit.

19in. Rack Mounting A.C. Mains Power Unit type 3.

A complete A.C. Mains power supply with variable input voltage tappings, switched 0-200/210/220/240/250 and fitted with 0-300 VDC and 0-150 m/a. Meters in H.T. output circuits.

Double choke smoothing with paper condensers and 5Z4 rectifier. Output 200VDC 40 m/a. and 6.3v. 3a. An extremely versatile power pack.

CLYDESDALE'S PRICE ONLY **£3/19/6** CARRIAGE PAID

Order direct from:—

CLYDESDALE SUPPLY CO. LTD. 2 BRIDGE STREET GLASGOW - C.5

Phone: South 2706/7 Visit our Branches in Scotland, England and Northern Ireland

---

Only with CO-AX R.F. CABLES

AIR-SPACED ARTICULATED

THE LOWEST EVER CAPACITANCE OR ATTENUATION

IMMEDIATE DELIVERIES

SPECIALISTS IN AIR-SPACED ARTICULATED CABLES SINCE 1934

TRANSRADIO LTD
CONTRACTORS TO H.M. GOVERNMENT
138A CROMWELL ROAD LONDON SW7
ENGLAND

LOW ATTEN TYPES	IMPED OHMS	ATTEN DB/100 FT AT 100 Mc/s	LOADING PF PER FT	OD"
A1	74	1.7	0.11	0.36
A2	74	1.3	0.24	0.44
A34	73	0.6	1.5	0.88
LOW CAPAC TYPES	**CAPAC PF PER FT**	**IMPED OHMS**	**ATTEN DB/100 FT AT 100 Mc/s**	**OD"**
C1	7.3	150	2.5	0.36
PC1	10.2	132	3.1	0.36
C11	6.3	173	3.2	0.36
C2	6.3	171	2.15	0.44
C22	5.5	184	2.8	0.44
C3	5.4	197	1.9	0.64
C33	4.8	220	2.4	0.64
C44	4.1	252	2.1	1.03

HIGH POWER FLEXIBLE

PHOTOCELL CABLE

VERY LOW CAPACITANCE

BAFFLETTE

Extension Loudspeakers

- Superior Quality.
- Superior Appearance.
- Greater Reliability.
- Better Value.
- Advance Design.

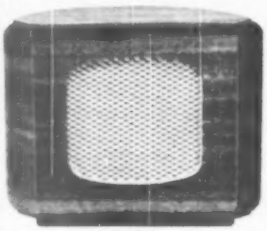

BABY

- **MINOR 52/6**
- **BABY 39/6**
- **MAJOR 65/-**

With Transformers a few shillings extra. All fitted with "Out-of-sight" volume controls.

OTHER MODELS

BONNIE	49 6	JUNIOR	59 6
STANDARD	£4 4 0	DE LUXE	£4 15 0
CONSOLE	£6 15 0	PRESTIGE	£12 19 6

Richard Allan

RADIO LTD., BAFFLETTE HOUSE, BATLEY, YORKS.

Dealers who experience difficulty in obtaining supplies should order direct stating usual wholesalers

INTRICATE PARTS

but not too intricate for

Bullers

Made in Three Principal Materials

FREQUELEX
An insulating material of Low Di-electric Loss, for Coil Formers, Aerial Insulators, Valve Holders, etc.

PERMALEX
A High Permittivity Material. For the construction of Condensers of the smallest possible dimensions.

TEMPLEX
A Condenser material of medium permittivity. For the construction of Condensers having a constant capacity at all temperatures.

BULLERS LOW LOSS CERAMICS

BULLERS LTD., 6, Laurence Pountney Hill, London, E.C.4
Telegrams: "Bullers, Cannon, London"

Phone: Mansion House 9971 (3 lines)
Manchester Office: 196, Deansgate, Manchester

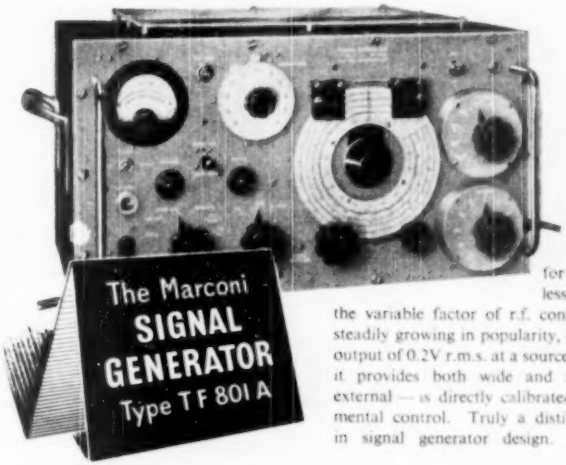

Equipment without Equivalent

MARCONI TEST EQUIPMENT is without equivalent. Signal Generator TF 801A, for instance, has the unique feature of contactless waveband selection thereby eliminating the variable factor of r.f. contact resistance. The instrument, which is steadily growing in popularity, has a range of 10-300 Mc/s and a maximum output of 0.2V r.m.s. at a source impedance of 75Ω. A.C. mains operated, it provides both wide and narrow band modulation — internal and external — is directly calibrated in frequency and is fitted with an incremental control. Truly a distinguished example of Marconi ascendancy in signal generator design. Full specification available on request.

Please ask for folder
"SUMMARY OF COMMUNICATIONS TEST GEAR"

MARCONI INSTRUMENTS LIMITED

ST. ALBANS, HERTFORDSHIRE · Telephone: St. Albans 6161/5

Northern Office: 30 Albion Street, Hull · **Western Office:** 76 Portview Road, Avonmouth · **Midland Office:** 19 The Parade, Leamington Spa · **Southern Office & Showrooms:** 109 Eaton Square, London, S.W.1

LASKY'S RADIO

The World Renowned for Service & Reliability

RECEIVER UNITS TYPE 25. The Receiver section of the TR1196 equipment. Easily converted to an all-wave receiver. 6 valve superhet. Supplied with the 6 brand new valves: 2 EF36; 2 EF39; 1 EK32; 1 EBC33. Full details and circuits supplied free with each unit. These units are slightly store soiled. **LASKY'S PRICE, 22/6.** Carriage 2/6 extra.

The Receiver Type 26. Less valves. **LASKY'S PRICE, 8/6.** Carriage 2/6 extra.

RADAR INDICATOR UNITS. BRAND NEW IN ORIGINAL WOOD TRANSIT CASE. Contains 2 cathode ray tubes, 1 soft.—VCR517, and 1 3in.—VCR139A. Also the following valves: 3 SP61; 1 6J5; 3 EA50; 1 D1. Dozens of components, including 7 potimeters, resistances, condensers, etc. Enclosed in metal cabinet, size: 12in. x 9in. x 19in. Weight 40lbs.

LASKY'S PRICE, 79/6d. Carriage 7/6d. extra.

EX A.M. COMMUNICATION RECEIVER TYPE R1155. Brand new in wood transit case. Aerial tested before despatch. Supplied complete with 10 valves. Circuit: B.F.O., A.V.C., R.F., A.M.P., 2 I.F. stages, magic eye, etc. 5 Frequency ranges: 18.5-7.5 Mc/s; 7.5-3.0 Mc/s; 1500-600 Kc/s; 500-200 Kc/s; 200-75 Kc/s. Full modification data and circuit details supplied free with each receiver.

LASKY'S PRICE, £12/10/-. Carriage in wood case, 7/6 extra. Complete kit of parts, including output valves and rectifier for building power pack and output stage for the R1155 Receiver, as described in the modification instructions. **PRICE 56/- complete.** Carriage Free.

The above power pack and output stage, fully assembled in black crackle steel case ready for use. **PRICE, 79/6 complete.** Carriage 5/- extra. **The R1155**, as above. Only slightly store soiled. **PRICE, £10/10/-.** Carriage 7/6.

THE VIEWMASTER. The television set you can build at home, from standard parts. London or Midland versions. Send today for 32-page illustrated instruction book and 8 full size working diagrams. Price 9/-. POST FREE. All components for building the Viewmaster available from stock for immediate delivery.

PRE-AMPLIFIER for the Viewmaster, full data and circuit price 1/-, post free. Kit comprises the following: 1 chassis with screened valve holder, 5 condensers, 5 resistances, 2 coils and valve, price 44/10. The pre-amplifier kit less valve, 23/6. Please state London or Midland when ordering.

LASKY'S ARE FIRST AGAIN! Special Buy. TYPE 6501 CATHODE RAY TUBES.

9" magnetic deflection, 6.3 volt heater. Working E.H.T. 5,000 volts. Brilliant black and white picture, flat face. Full data and connections supplied with each tube.

LASKY'S SPECIAL PRICE 99/6 Insurance and carriage per passenger train 10/- extra. Supplied complete with suitable square white mask and safety glass as illustrated. These cathode ray tubes are supplied in their original cardboard cartons. **Make no mistake, they are genuine black and white television cathode ray tubes, and are not Government surplus.**

SPECIAL OFFER. 2 VU111 E.H.T. Rectifiers. Two for 7/-. Post and packing, 1/6.

INEXPENSIVE TELEVISION. Using Ex-Government surplus equipment. Data book No. 4. Revised and enlarged edition. **PRICE 2/6 PER COPY.** Post Free.

SPECIAL OFFER VCR.97 Ex-GOVT. CATHODE RAY TUBES. Brand new, fully guaranteed. **LASKY'S PRICE 22/6.** Carriage and insurance 7/6 extra.

ANTENNA ROD SECTIONS. Each rod is steel heavily copper plated, 12in. long. Any number of rods can be fitted together.
LASKY'S PRICE 2/6 PER DOZEN. POST FREE.
SPECIAL OFFER 3 DOZEN FOR 6/-. POST FREE.

Send 2½d. stamp for a copy of our current stock list of Ex-Government and new radio and radar equipment, The Lasky's Radio Bulletin.

370, HARROW ROAD, PADDINGTON, LONDON, W.9
(Opposite Paddington Hospital) **Telephone: CUNningham 1979**
Hours: Monday to Saturday, 9.30 a.m. to 6 p.m. Thursday, Half day.

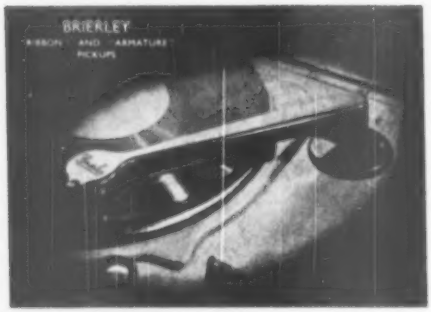

THE USE OF BRIERLEY PICKUPS AND 2-SPEED TURNTABLE WITH L.P. DISCS

The characteristics of BRIERLEY PICKUPS due to the uncompromising pursuit of extremely low mass of the moving parts with the associated greatly extended frequency response, are particularly essential on L.P. discs where the top resonances of all pickups is unavoidably about an octave lower than on normal shellac pressings.

"REPRODUCTION OF RECORDS—I" deals with the correct use of low output wide range pickups giving precise constructional and assembly details of essential associated equipment.

Obtainable from your local bookseller, radio shop or direct.
Price 3/6. By post, 3/11.

We apologise to those who earlier in the year had to wait for their copy of this booklet; delivery is now by return.

J. H. BRIERLEY (GRAMOPHONES & RECORDINGS) LTD.
56, TITHEBARN STREET, LIVERPOOL, 2.

TELEVISION
INTERFERENCE Suppressors!

No adverse effect. In stocks. P444 (plug-in). P445 (screw-in).

Fit in a second!

A.F. BULGIN & CO. LTD
BYE PASS ROAD, BARKING, ESSEX Phone: RIPPLEWAY 5474-5

1/6

Varley
Products of Quality & Reliability

MAINS TRANSFORMERS
A. F. TRANSFORMERS
THERMAL DELAY SWITCHES
SMOOTHING CHOKES
POWER RESISTANCES

Made by
OLIVER PELL CONTROL LTD
Telephone: WOOLWICH 1422-426
CAMBRIDGE ROW · WOOLWICH · S.E.18

ULTRA
eccentricities
NUMBER ONE

One of our eccentricities is that we are concerned to give Ultra TV Dealers as much help as possible in installing and servicing Ultra TV receivers. We take the view that accidents can happen. Components can fail. No TV that has ever been made has been immune from trouble of some kind or another. But 90 per cent of the difficulty in coping with breakdowns is diagnosing what has gone wrong. That is why we have always taken so much trouble in the preparation of servicing information for the benefit of Ultra TV dealers. This information not only takes the form of Service Sheets that are available immediately sets are in production, but also includes, for example, the issue, monthly, of a publication we call "TV GEN," which gives up-to-the-minute "gen" which will help Ultra television Dealers' servicemen.

A feature of recent issues of "TV GEN" has been extracts from the log books of the fellows in our Service Department who deal with telephone enquiries. For example, one of our Dealers recently 'phoned us on a matter that was troubling him. A particular Ultra TV set had been perfectly satisfactory for about three months when "sound on vision" appeared, due to one particular valve becoming microphonic, which when replaced, overcame the trouble. After about three months, however, the same trouble appeared again. The reply we gave on the 'phone, and printed in "TV GEN", was that the set was in use where signal strength was exceptionally strong, and we thought, therefore, that the variable sensitivity control probably was set at, or near, the high attenuation end of its travel, making the cathode and the suppressor grid of the valve in question some 80 volts above earth, which tends to produce microphony. Hence, in areas of very high signal strength a suitable aerial attenuator should be used; so that the variable sensitivity control can be used for normal adjustment and set at a position which does not "encourage" microphony.

Such "eccentricities" as this help to give Ultra TV Dealers confidence in our products, and in turn, they can give the very best advice and service to both potential and actual owners of Ultra radio and television products.

ULTRA ELECTRIC LIMITED
WESTERN AVENUE · ACTON · W.3.

Sintered Permanent Magnets

ALNICO · ALCOMAX · HYCOMAX

This Photo Electric Exposure Meter made by The Pullin Optical Co. Ltd. incorporates a Sintered Alcomax II Magnet.

ACTUAL SIZE OF MAGNET

MUREX LTD. RAINHAM · ESSEX · ENGLAND
LONDON SALES OFFICE
CENTRAL HOUSE · UPPER WOBURN PLACE · W.C.1

Where small complex shapes with high magnetic efficiency and stability are required sintered permanent magnets are essential.

FOR THE DISCRIMINATING PA MAN

PORTABLE BATTERY MAINS AMPLIFIER BM40

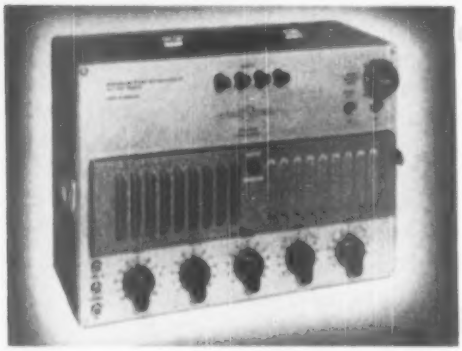

An attractive appearance and unique construction combined with first-rate performance give this instrument a hallmark of distinction. Peak power 40 watts, 30 watts undistorted. Designed for both A.C. Mains and 12-volt battery operation. Provision for independent electronic mixing of two microphones and one gramophone channel. Built-in vibrator. Special tone control circuit, with independent bass boost and cut, and treble boost and cut.
These and many other features make the BM40 the most up-to-date amplifier available.
List price **£45.**

MOBILE CAMPAIGN OUTFIT MAIS

An ideal equipment for mobile applications, giving crisp, clear messages. The outfit comprises: 15 watt amplifier for either 6 volts or 12 volts operation; hand microphone type M.C.B., and co-axial weatherproof loudspeaker. A gramophone input and battery-saver switch are incorporated.
List price **£42.**

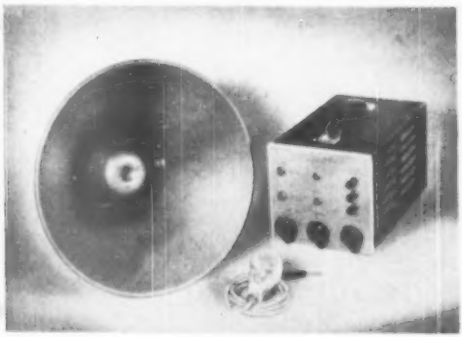

30 WATT PORTABLE AMPLIFIER PA30 B

A 30 watt amplifier for public address men. Inputs for moving coil or ribbon microphones and gramophone. Tone control. Illuminated panel and output signal level indicator. Outputs: 7.5, 15 ohms and 100 volt line. Operates from 200/250 volts A.C. mains, or 12-volt battery when used with battery adaptor unit type LT30. An ideal equipment for P.A. vans, general installations and outdoor requirements. Supplied in a handsome portable case.
List price: PA30 B Amplifier, **£35.**
LT30 Battery Adaptor, **£12 10s.**

BIRMINGHAM SOUND REPRODUCERS LIMITED
CLAREMONT WORKS, OLD HILL, STAFFS TEL. CRADLEY HEATH 62122

Wireless World

RADIO AND ELECTRONICS

40th YEAR OF PUBLICATION

Managing Editor: HUGH S. POCOCK, M.I.E.E.
Editor: H. F. SMITH

In This Issue

EDITORIAL COMMENT 273

HEARING AID DESIGN. By *A. Poliakoff* 274

LIVERPOOL HARBOUR COMMUNICATIONS 277

FLYBACK E.H.T. By *W. T. Cocking* 279

STANDING WAVES ON R.F. CABLES. By "*Cathode Ray*" 283

NEW SCANNING CIRCUIT. By *P. R. J. Court* 287

WORLD OF WIRELESS 291

ELECTRONIC CIRCUITRY. By *J. McG Sowerby* 293

SHORT-WAVE CONDITIONS. By *T. W. Bennington* .. 295

FROM TELEVISION AERIAL TO RECEIVER By *F. R. W. Strafford* 296

BLACK-SCREEN TELEVISION 298

M.K.S. SYSTEM OF UNITS 299

UNBIASED. By "*Free Grid*" 300

LETTERS TO THE EDITOR 301

AUGUST 1950 RANDOM RADIATIONS. By "*Diallist*" 304

PUBLISHED MONTHLY: Price 2/- (on last Thursday of preceding month) by ILIFFE & SONS LTD., Dorset House, Stamford Street, London, S.E.1. *Telephone:* Waterloo 3333 (60 lines). *Telegrams:* "Ethaworld, sedist, London." *Annual Subscription:* Home and Overseas, £1 6s. 0d.; U.S.A. and Canada $4.50. BRANCH OFFICES: *Birmingham:* King Edward House, New Street, 2. *Coventry:* 8-10, Corporation Street. *Glasgow:* 26a, Renfield Street, C.2. *Manchester:* 260, Deansgate, 3

Mullard

Important trends in valve design

MULLARD ELECTRONIC PRODUCTS LIMITED have pleasure in introducing a new series of advertisements which will describe important trends in the design of receiving valves. Special emphasis will be laid upon television, and forthcoming announcements will deal with basic developments from the Mullard laboratories. In this connection it is undoubtedly correct to say that the successful penetration of world markets by British Television Manufacturers is largely dependent upon valve and tube technique.

Mullard have borne this vital factor in mind in their development programmes, and are already able to offer setmakers valves specifically designed for efficient television reception under all conditions and by any system. This, coupled with the established Mullard network of overseas distribution, will enable exporters to attack new markets with considerable advantage.

Once again, Mullard invite readers of the "Wireless World" to apply for reprints of this important series of advertisements, the first of which will appear in the September issue. Requests should be made to the address below.

Mullard VALVES AND TUBES FOR RADIO AND TELEVISION

MULLARD ELECTRONIC PRODUCTS LIMITED, Century House, Shaftesbury Avenue, London, W.C.2

MVM 136

Wireless World

VOL. LVI. No. 8. AUGUST, 1950

Long-playing Records

THE release in this country last month of long-playing (microgroove) records, was an event of very considerable importance and one which is likely to have as significant an influence on the trend of sound reproduction as the advent of electrical recording.

Long playing time is naturally the chief attraction to the public, but to the technically minded the introduction of a new moulding material with lower surface noise and better wearing qualities than shellac will be recognized as the basic development. The reduction of surface noise is so considerable that even after reducing maximum amplitudes to the limitations imposed by 240 or more grooves per inch, there is still room to accommodate an increased dynamic range, compared with shellac pressings, before noise level is reached. There is little doubt, too, that with equal care in the choice of pickups and reproducing styli, and in keeping the grooves free from dust, the increase of surface noise with successive playings is much less in the new materials.

To the unaccustomed eye the turntable speed of 33⅓ r.p.m. seems unconscionably slow and has given rise to predictions of high-note loss at the low linear speeds near the centre of the record. Such misgivings are quite unfounded. Normal tracing distortion is, in fact, less than with standard 78 r.p.m. records, because both lateral velocity and stylus tip radius have been reduced to a greater extent than the linear speed.

The new records have a different recording characteristic and will require separate treatment in the matter of frequency compensation; the weight on the stylus must be reduced to 8 gm or less, and there is also the question of adequate turntable performance at 33⅓ r.p.m. None of these matters should present any insuperable difficulty.

British long-playing records have been exported to America now for some time and have already established a high reputation for quality. It is unlikely that in this country they will immediately supersede the 78 r.p.m. shellac record, for it will be many years before a comparable library of subjects can be built up in microgroove. Not all subjects call for the long playing time and other qualities of the new system, and can be produced more cheaply on shellac.

Television Isolationism

WE remember a story, current on the continent of Europe many years ago, that was supposed to epitomize the alleged British traits of insularity and self-satisfied complacency. During a season of heavy winter gales, so the story ran, a leading London newspaper came out with the headline "GREAT STORM RAGING IN CHANNEL: CONTINENT CUT OFF."

Unless wiser counsels prevail, there seems some risk that, in the sphere of television, the continent may, as the story put it, be cut off from Great Britain. To avoid charges of being insular ourselves, perhaps we had better hasten to reverse that last sentence, but we admit to being complacent enough to think that the continent as well as Great Britain will lose something unless the easy interchange of programmes is facilitated by the adoption of common standards.

Two or three continental readers have accused *Wireless World* of being "isolationist" in continuing to advocate the general adoption of the British 405-line standard. "Now that the continent has expressed its preference for 625 lines," they say, "why not urge your home authorities to change over at once to that definition."

To give way thus to a majority vote is no doubt in keeping with the principles of international democracy, but, before Britain is asked seriously to do so, we feel a valid explanation of why the 625-line standard is preferred is due to us.

Hearing Aid Design

Some Essential Qualities of a Good Instrument and Their Practical Realization

A. POLIAKOFF (Multitone Electric Company)

MANY technical people regard hearing aids and everything and everyone connected with them with considerable suspicion. They think that a three-valve amplifier with a crystal microphone, no matter how much miniaturized, remains a three-valve amplifier by whatever name you call it, and irrespective of what you charge for it. And what about all the theories and systems of response curve compensation for various types of deafness which have been put forward and then declared untenable by official reports? This I believe to be a very general state of mind among men who are extremely well informed in most other branches of electro-acoustics.

That there is room for more than one point of view may be judged from the fact that when we entered the hearing-aid field in 1933 we firmly believed in drastic tone control (many readers will remember our tone control transformer), and in low prices for all kinds of hearing aids. Now, after seventeen years' work we make an instrument, our latest, with no tone control other than a choice of three earpieces, and charge for it more than any other British manufacturer, 39 gns.

A medium-sized manufacturer cannot, as a rule, engaged in large-scale basic research; he can, however, draw conclusions from his continuous practical work, which, if carefully conducted, becomes almost equivalent to pure research.

A hearing-aid manufacturer who is also a direct supplier on a large scale has the great advantage of being able to submit thousands of cases that pass through his hands every year to any reasonable test and to experiment with them to his heart's content.

Most hard-of-hearing people are anxious to co-operate and will undergo many tedious tests. The tests themselves may be tedious, but the subject is fascinating and of very great complexity. This may appear puzzling in view of the fact that the Medical Research Council in their report* laid down a response curve which they proved to be the best for most deaf people. Where, then, are the complications? Why the continuous need for experimentation? Surely everything has been settled now? The answer is that the response curve is just one variable among many; an important one, but probably not the most important.

In addition there is a large number of other things to consider. Most people have two ears with sufficient hearing to work on. Receivers in parallel and with the same characteristics can be used on both ears or one at a time. Alternatively, receivers with different characteristics can be used. Binaural listening, that is, by using two distinct amplifiers and microphones, is another alternative. Bone-conduction can be used singly, or mixed with air-conduction. Another variable is that one can work for maximum intelligibility in quiet surroundings, "dead" rooms, noisy surroundings or in resonant rooms, and so on.

Even when all technical requirements are satisfied we are left with the partly psychological problem of size, appearance and weight. No user wants to look like a military radio-set operator, and, whatever is visible he prefers shall have the appearance of a personal article such as a cigarette case, rather than a severely technical-looking object.

I would list the attributes of a good aid in the following order of importance:—

1. Giving the patient his optimum volume in all reasonable conditions of use. In most cases this cannot be achieved without automatic volume control.
2. Avoidance of pronounced peaks.
3. Low case noise.
4. (and last). A nice-looking response curve.

This order of priority must not be taken as a reflection on the conclusions of the Medical Research Council's Report, which states in any case "Startling changes of the overall articulation efficiency do not result from minor departures from the optimum response curve."

I shall now endeavour to demonstrate the importance of the other attributes.

Optimum Volume

Everyone, whether of normal or sub-normal hearing, has a preferred volume of listening which generally, but not always, corresponds to the highest score in a speech intelligibility test. If the level of speech falls far below this optimum, the percentage intelligibility rapidly declines, and it also goes down if the optimum is much exceeded. With many deaf people the effect is very marked. For them a small increase of stimulus produces a large increase in sensation. The phenomenon is known by the term "recruitment," and is not detectable by the normal audiogram taken at threshold. Thus, if the patient has a mean loss of 40db at threshold and it is desired to make him hear speech of normal strength (60db) at its right level, it would be wrong to conclude that in the majority of cases the level from the hearing aid should be set at 40 + 60db. On the contrary, one is more likely to find that the patient

* No. 261, "Hearing Aids and Accessories," published by H.M. Stationery Office.

prefers to listen at some very low level such as 75 db. To determine the patient's volume requirements there are three quantities to measure: the *optimum* volume, the *maximum* tolerable, and the *minimum* giving sufficient intelligibility.

For some time now we have been using a very simple device which we have called an "Optimeter" for ascertaining these volume levels. This is simply a valve voltmeter with the meter scale calibrated directly in decibels above threshold. The "Optimeter" is connected in parallel with the earpiece of the hearing aid being demonstrated to the patient, and normal conversational voice is used for testing. The results recorded are then the true volume in his ear, subject only to the small correction of variation between earpieces. The minimum, optimum and maximum readings are then noted. The results thus obtained, although less accurate than with an elaborate speech audiometer, have the great advantage of being a measurement under actual working conditions. The speech audiometer, if properly designed, has an entirely flat response, whereas the hearing aid is certainly bound to be more "peaky" and to have a far less low-note response. What is required are the limits *with the hearing aid to be used* and not purely theoretical limits.

We have been measuring, systematically, a very large number of cases that have passed through our various offices in the last twelve months. The curve (Fig. 1) represents the result of these measurements on a sample of 500 cases. Considering the optimum volume only, the following percentages may be given to save unnecessary integration:—

Percentage of cases tested	Optimum volume
13.0	75 db or under
49.5	85 db ,, ,,
84.5	95 db ,, ,,
92.0	98 db ,, ,,

This appears to us to be a very interesting result. Nearly half of all the cases tested have an optimum volume not exceeding 85 db, that is to say, needing an amplification for normal speech of only 25 db.

These measurements also disclose a large number of cases with exceedingly narrow ranges between the minimum and the maximum (Fig. 2). There are other cases, the easy ones, which have an enormous range between minimum and maximum or whose maximum is outside the range of normal instruments.

It has been clear to us for some time, long before we made systematic measurements of the volume requirements of all cases, that automatic volume control was an absolute essential for some cases and was very useful for most. Our first instrument incorporating automatic volume control was of the box type, called the "Reactor," and was made in 1936. Further development of automatic volume control suffered a setback by the need to make subsequent models of hearing aids wearable, with the consequent restriction of space available for additional components. It was not until 1948 that we incorporated it in our "Monostat" instrument (described in the *Wireless World*, October, 1948).

Our work with the "Optimeter" showed us the need for extremely wide control over volume compression to fulfil all the conditions. By varying separately the degree of compression, the amplification of the instrument for weak signals and the efficiency of the earpiece, we believe that we are now able to meet any requirements, even extremely freak ones. Since automatic volume control no longer properly described what we were doing, and, anyway, is apt to give the idea of complete levelling up, we have now introduced the expression "Contrast Control." In our new instrument, the "Selector," we are able to obtain as much compression as a range of from 20 db input to 6 db output and to decrease this compression by successive stages to completely linear amplification.

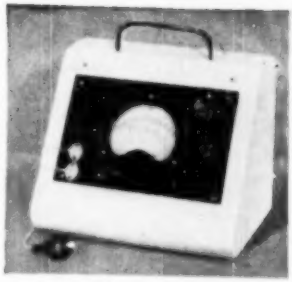

Multitone "Optimeter" for measuring volume levels in association with the patient's own hearing aid.

For the majority of cases of deafness, absence of pronounced peaks is quite important. In manufacturing on a large scale this is one of the most difficult things to achieve, especially as response curves of

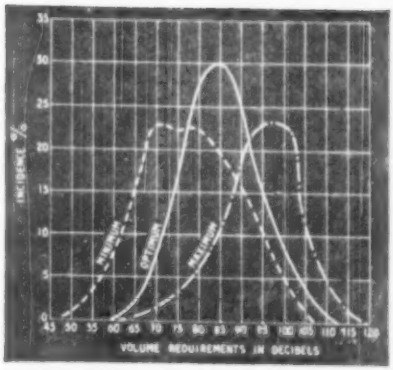

Fig. 1. Curves showing volume requirements, plotted from observations of 500 cases.

Fig. 2. Tolerance range (difference between minimum and maximum) in 500 cases.

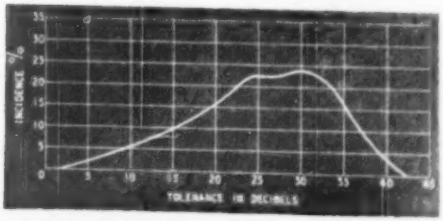

both microphones and earpieces vary considerably with temperature. Case resonance often varies even from case to case, and, lastly and most important of all, the ear cavity and the seal vary from patient to patient to a very large degree. It is very disheartening for a manufacturer, after exerting himself to the utmost to level out peaks, to find some users who will not give up their original quite "peaky" instruments. There are many people who seem to need, or who have become accustomed to a hearing aid giving them a "kick," without which they feel it is not functioning. We believe, however, that these exceptions are not sufficiently numerous to justify any diminution of effort in this direction.

There has been no change in the position with regard to the withdrawal of overtime working by a section of the printing industry. A slight reduction in the number of pages in "Wireless World" is still unavoidable. All journals printed in London are similarly affected, to a greater or lesser extent, but journals printed in the provinces are not affected. It is greatly regretted that publication of our last issue was delayed.

Case Noise

Practically everyone nowadays wears the hearing aid somewhere on the person. The effect of the smoothest response curve and of the best automatic volume control can be completely ruined by the noises and crackings which the user hears as he moves or breathes if the instrument has bad case noise. Insulation of the microphone by rubber mounting is not in itself sufficient to avoid the case noise. The case has to be acoustically "dead" and its surface exceedingly smooth. On the "Selector," access to the battery compartment is given without the use of hinges by means of a special slide action which has enabled the case to be constructed in a manner combining great rigidity with comparatively low weight. This has been found to give acoustically superior results to the more conventional types of construction. There are no surface decorations; the grille is recessed and the whole is covered with lacquer which is fired on to give the smoothest possible surface.

Response Curve

Our practice now is to modify the response curve in suitable cases by means of earpieces and not by anything done to the amplifier. In addition to the normal earpiece, there is a choice of an earpiece with reduced high-note response and a less efficient earpiece with a continuously rising response curve. The first is required for people who dislike an appreciable output in the high notes, while the second, coupled with the control set to maximum compression, enables us to deal with cases of deafness which have usually been considered to be outside instrumental help.

In the latest Multitone "Selector" hearing aid, special attention has been given to the mechanical design and surface finish to minimize "case noise."

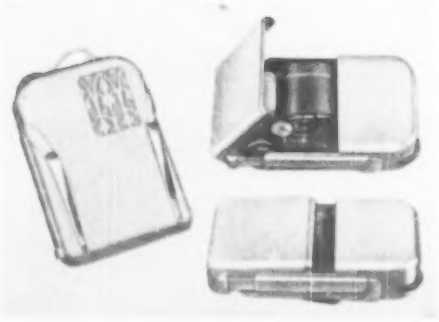

I have now described the methods which have evolved gradually as a result of continuous practical work. All this is applied, however, to monaural aids, and there is no doubt in our minds that every effort should be made to produce sufficient simple binaural aids for similar cases. The advantage of a binaural aid in a resonant building is tremendous. It is really a question of simplifying the apparatus sufficiently and educating the public to the great advantages of the binaural instrument. We have so far done only experimental work, but hope that in the not-too-distant future to make something available to the general public. Meanwhile, the hearing problem in theatres, cinemas and other auditoria remains very difficult. With a monaural aid the best solution is undoubtedly an inductive pick-up from a loop under the carpet, which we introduced in 1937 under the name "Telesonic." The user is provided with a coil to plug- or switch-in instead of the microphone, or the theatre, cinema or hall lends him a special receiver for use while he is there.

It is a curious fact that every two years or so a controversy breaks out in the Press around the prices of commercial hearing aids. Comparisons are invariably made with wireless sets, and suggestions made with a varying amount of delicacy that hearing-aid manufacturers must be in a very good occupation indeed. I have already mentioned that we entered this field believing in very low prices and that our latest instrument, the "Selector," costs 39 guineas. Can such prices be justified? If hearing aids were sold on the same basis as radio sets they could, of course, not bear scrutiny. Most hearing-aid manufacturers and suppliers, however, give service and facilities to their clients which have no parallel in commerce. Further, the quantities are small and changes of design frequent. The continuous miniaturization of the hearing aid will undoubtedly continue at the present, or even a greater, rate and is an exceedingly expensive business. Most manufacturers and suppliers have quite cheap models as well as their more refined ones, and before the advent of the Government aid were used to providing instruments through hospitals at prices as low as 6 guineas, complete, before the war and 9 guineas after the war.

For a long time the fitting of hearing aids has been more of an art than a science. Knowledge and understanding of the subject are accumulating every day, but a great deal of fundamental research remains to be done before the fitting of instruments can become completely systematized.

Liverpool Harbour Communications

New Ship-to-Shore V.H.F. System for Pilotage and Docking Operations

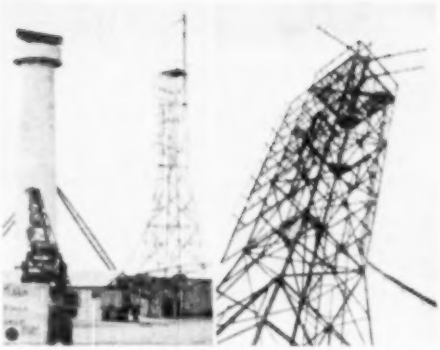

Aerial arrays at Port Radar (Gladstone Dock). Above the 32-element beam aerial for Channel 1 are seen the Channel 2 Yagi aerial for distances up to the Bar Lightship and two Yagi aerials pointing to dock stations up river.

NOW that the marine radio system at Liverpool has completed initial trials and has been handed over to the Mersey Dock and Harbour Board, we are able to supplement the preliminary information given in our August, 1949, issue.

It will be recalled, that to keep pilots in touch with the latest radar information regarding shipping in the approach channel, and to enable shipmasters to get advance information of berthing arrangements, the harbour authorities gave a contract to British Tele-

Fig. 1. Plan of area covered by Liverpool harbour communications.

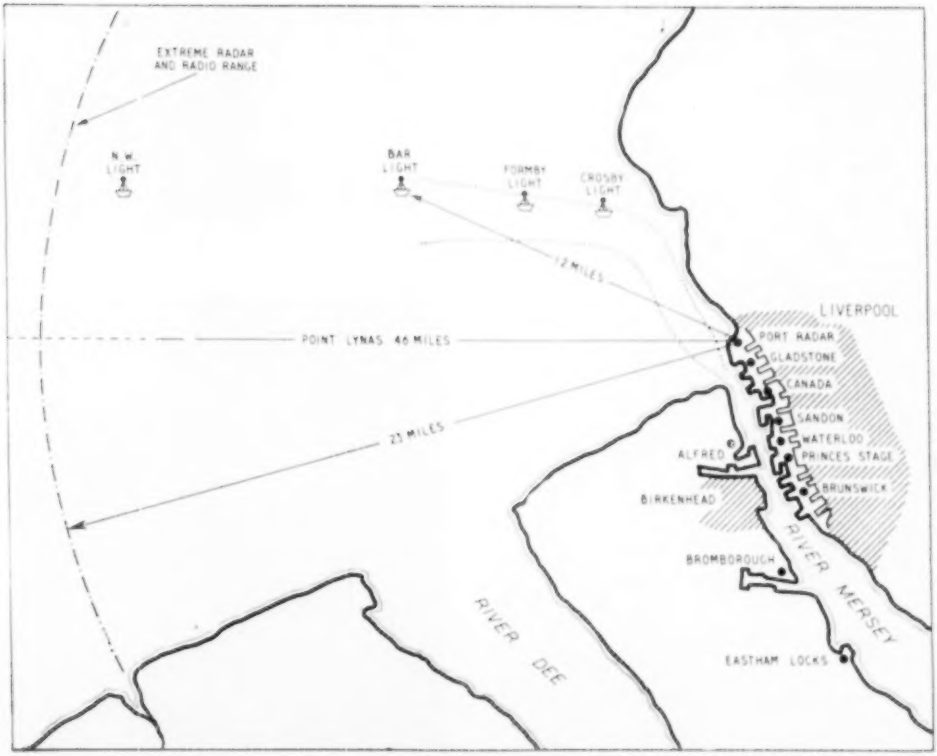

communications Research for an installation comprising 10 shore stations and 150 portable radio-telephone transmitter-receivers. Research into the problem involved in giving reliable service over the large area covered by the docks and approaches (Fig. 1) was carried out by B.T.R., and the manufacture of the equipment was undertaken by the Radio Gramophone Development Company, who also contributed to the design of the portable transmitter-receivers.

These portables, which weigh 20lb are powered by a 4-volt accumulator and use a vibrator h.t. supply. They are hermetically sealed against total immersion, and now form an essential part of the harbour pilots' kit. The performance of the portable is the keystone of the whole communication system; the receiver sensitivity of 15μV determines the power required at the shore transmitters, and the portable transmitter power of 250mW the height and gain of the aerials and fixed receiver sensitivity necessary for reliable service at the stipulated maximum range of 24 miles.

Figures derived from a paper by T. L. Eckersley (*J.I.E.E.* Vol. 80, March, 1937, p. 286) produced the curves of Fig. 2, from which it was calculated that for an aerial power of 250mW, the signal strength at the land station receiver terminals from a simple dipole would be of the order of 0.4μV.

This level of signal is well down into the noise region, and below a manageable signal strength at the shore station. To this, aerial feeder losses must be added, and to facilitate calculations, these losses were fixed at 3db.

This indicated that a high-gain beam aerial should be employed. It had been ascertained that a signal of 3μV was required at the shore receiver terminals, and this called for an aerial gain of some 20db, not including feeder losses.

Consideration was then given to the transmitter power required at the shore station, utilizing an aerial with a gain of 20db, to produce the required field strength at the portable equipment.

As a 15μV signal at the input terminals of the portable was considered reasonable for a good signal/noise ratio, it was found that the transmitter power required would be approximately 35 watts.

In practice, somewhat higher aerial powers (45 watts) at the land station were obtainable than were originally thought to be possible, and the portable set's sensitivity was also improved (i.e., 10μV for 10db signal-to-noise). This produced a slight unbalance in signal levels biased in favour of shore-to-ship, but this was considered to be an advantage when operating in bad weather and high winds.

It was decided that the aerial to be employed should be a 32-element centre-fed beam with a meshed metal reflector, which came as near as was practicable to giving the required gain (i.e., 18db) with a theoretical beam width of 2.15°. The overall size of this aerial is approximately 30ft long and 12ft wide. It is mounted on an 80 ft tower situated approximately 50ft from Port Radar control room.

Channel 2 at Port Radar, which requires an operational range of 14 sea miles, employs a Yagi type aerial with one driven element and four directors, giving a forward gain of 5 or 6db. This aerial is mounted on a metal pole extending 20ft above the beam aerial on the same tower. At this height (i.e., 100ft ± sea wall) it is visual distance to the Bar Lightship, thus eliminating the requirement for a high-gain aerial array.

There are six channels in all, two for navigational

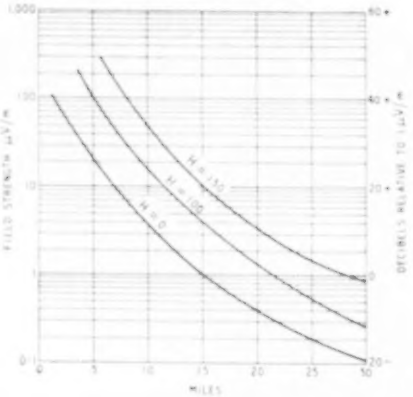

Fig. 2. Field strength over water at 150 Mc/s with 250 mW in a single dipole aerial at heights (H) of 0, 100 and 150ft above sea level.

Six-channel crystal-controlled portable transmitter-receiver, Type HPS1, for use by harbour pilots.

Operations room at Port Radar showing Channel 1 and Channel 2 shore station equipment.

aid and harbour supervision, and four for docking communications. The land transmission frequencies are from 163.1 to 163.6Mc/s and the mobile transmission frequencies from 158.6 to 159.1Mc/s. The channels are separated, 100kc/s apart and the "go" and "return" frequencies are spaced 4.5Mc/s apart (at the receiver intermediate frequency). The two frequencies used for navigational and harbour supervision are Channel 1 and Channel 2 and the shore station equipment for these channels is located at Port Radar. The other four frequencies (Channels 3-6) are shared between nine dock stations, each of which has individual shore station equipment. The division is so arranged that docks the farthest distance apart share channels, and a code calling system is used, employing a 1000-c/s note, which permits the portable sets to call the required shore station.

At four-hourly intervals, day and night, the radar equipment is switched on and the positions of all vessels in the seaward direction, both under way and at anchor, are transmitted over Channel 1 for the benefit of any shipmaster who may wish to plot the information. This is then followed by similar information given over Channel 2 to vessels which may be needing it in the river area. After the shipping, a statement of local weather conditions is transmitted over both channels, together with any local navigation warnings.

At all times between these regular transmissions, communications may be established over both Channels 1 and 2 with vessels entering or departing from the Port. The portable sets are taken aboard ships by the pilots at their boarding stations which, inward bound, are off Point Lynas, or at the Bar Lightship. As soon as inward-bound ships arrive within the Port communications area they call up the operation room at Port Radar over Channel 1 and give their name, draught and expected time of arrival at, say, the mouth of the river, or at the Princes Landing Stage, whichever may be appropriate. This information is passed by landline to the departments concerned. When the vessels come within range of the Dock Station equipment the pilot can then communicate direct with the Dock Master for information as to the particular berth the ship is to occupy. This will enable the shipmaster to prepare to rig derricks and remove appropriate hatch covers in advance and so save valuable time in unloading.

Under adverse weather conditions the combined radio and radar equipment operates to enable vessels to enter and traverse the Crosby Channel and proceed to anchorages in the river or directly into dock, as may be required. Likewise, vessels leaving port may seek and obtain information which will give them safe passage to the Irish Sea. In circumstances of particularly heavy traffic on Channel 1, vessels within the shorter range of Channel 2 may be requested to use this channel to free the longer range channel for communications with vessels farther away from the Shore Station.

At the official hand-over ceremony, which took place on 1st June on board S.S. *Galatea* near the Crosby Light Float, all aspects of the service were convincingly demonstrated on the return passage to the Gladstone Dock under shore radar and radio control. As an example of what can be achieved in the economical planning of an installation to serve local geographical and organizational requirements, the Liverpool communication system is a happy augury for the successful extension of v.h.f. radiotelephone service to other large ports in this country and overseas.

Flyback E.H.T.

1. Characteristics of Pulse Systems

By W. T. COCKING, M.I.E.E.

It is now the standard practice in television receivers to derive the e.h.t. supply for the cathode-ray tube from the voltage pulse developed in the line-scanning circuits during flyback. The system works exceedingly well; it is inexpensive and, because of the small reservoir capacitance needed, it is a safe one. Its only major disadvantage lies in its rather poor voltage regulation.

The regulation is important because it affects both picture size and focus. If V_T is the final anode voltage of the c.r. tube, the picture width and height for constant deflecting current are inversely proportional to $\sqrt{V_T}$. Also the current in the focus coil, or the field strength needed for optimum focus, is proportional to $\sqrt{V_T}$. For small changes of voltage the percentage change of picture size is very nearly one-half the percentage change of voltage; thus, a fall of 10% in voltage means an increase of 5% in the linear dimensions of the picture.

On a picture 10in wide this is an increase of 0.5in and is quite a lot. Changes of this order do frequently occur between a near-black raster and a near-white one. Their effect is very obvious when the brightness control is operated. Fortunately, such large changes of picture brightness do not often occur in a normal programme. The mean brightness level is remarkably constant and it is rare for it to change sufficiently for noticeable alterations of picture size to occur, even when the regulation of the e.h.t. supply is far from good, except after a break in the programme when the announcer is faded-in following a near-black interval.

The effect of e.h.t. regulation on focus is much more difficult to assess and it obviously depends to a large degree on the depth of focus of the scanning beam. The modern tendency in tube design is to shorten the tube, which not only increases the deflection angle but increases the angle of beam convergence and so shortens the depth of focus. The effect of e.h.t. regulation on focus is, therefore, likely to increase in the future.

Since it is not easy to measure degrees of focus, it is hard to give any figures for the effect of e.h.t. regulation. It has been observed experimentally in

a particular case that if the raster is focused with a current of 120 μA at 4.35 kV there is noticeable defocusing when the voltage rises to 4.8 kV, which, in this case, occurred at a current of 45 μA.

Most c.r. tubes are rated for a peak current of about 150 μA but, because of the line and frame fly-back intervals, the maximum mean current on a peak-white raster does not exceed 120 μA. On a black raster the current is zero so that in theory it is necessary to consider current *changes* of 120 μA. However, if the raster is black one cannot see it and it does not much matter what happens to it. In general, it seems reasonable to consider a mean current of 60 μA for an average picture and to assume that normal mean-current changes are restricted to ± 40 μA about this figure. Changes of ± 60 μA are likely to occur so infrequently that some distortion of the picture when they do occur may well be tolerable.

It should be understood that the currents referred to are all mean currents corresponding to the mean picture brightness. The instantaneous currents corresponding to the picture detail are supplied by the reservoir capacitance and do not enter into the present discussion.

One cannot lay down any definite figures for an acceptable standard of e.h.t. regulation, but it is suggested that for current changes of ± 40 μA a change of picture size of ± 2.5% would not be objectionable. With constant deflector-coil current this is 10% regulation for 80 μA change of current. This corresponds to a source impedance at 5 kV of 500/80 = 6.25 MΩ and is of the order obtained with the *Wireless World* Television Receiver. Experience with this set indicates that neither the change of picture size nor the change of focus is sufficient to be objectionable. Indeed, neither is noticeable on normal programmes. The change of picture size usually becomes evident only on a change from one programme to another, for which the mean level of brightness may be appreciably different. It only becomes obvious when a programme is faded-in from a near-black raster.

In this article, therefore, we shall take the foregoing figures as representing an acceptable standard of performance but it is, of course, plain that a higher standard is desirable if it can be obtained with reasonable economy.

Line-Scan Circuit

The voltage regulation of a fly-back e.h.t. system depends upon the scanning circuit itself on the one hand and upon the rectifier system on the other. A joint analysis of the two together is impracticably complex. In general, the regulation of the rectifier system alone is, or can be, much better than that of the scanning system. For the present, therefore, only the latter will be considered and it will be assumed to work into an ideal rectifier. That is to say, all rectifier diodes will be assumed to be "ideal" with zero forward and infinite back resistance, and the reservoir capacitance will be assumed large enough to absorb or supply current without the voltage across it changing by any appreciable amount. The voltage across it will be assumed to be capable of changing only over intervals of time which are lengthy compared with the duration of a scanning line.

In order to determine the effect of the scanning system upon the regulation of the e.h.t. supply it is necessary to analyse such a system in conjunction with an ideal rectifier. So far as the writer is aware no such analysis has previously been published. It is carried out fully in the Appendix* and a design procedure is derived from the results.

The analysis is straightforward but its interpretation is difficult because certain equations cannot be brought into suitable form to permit substitution in others. This has made it necessary to present the results in graphical form and involved some rather laborious computation.

Practical line-scanning circuits vary greatly in detail but most arrangements are substantially alike in their fly-back conditions. The deflector coil with the shunt and leakage inductances of the transformer is equivalent to a simple inductance, and the various circuit capacitances to a capacitance in shunt with it. The only variations from this are brought about by some stray capacitances and leakage inductances which cannot always be exactly represented by this simple arrangement. They are often of negligible importance, however.

Power lost to the circuit in various ways is best allowed for by a resistance in shunt with the LC circuit. This is not exact when the damping circuit comprises a series resistor and capacitor across the deflector coil; it is still less exact when a resistor, a capacitor and an inductor, all in series, are used for damping. It is very near reality, however, when damping is provided mainly by iron losses plus, possibly, a shunt resistor. This includes the case of a damping diode, for such a diode is inoperative throughout fly-back.

It is important to realize that the valves associated with the circuit are all cut-off during the entire fly-back period, except, of course, the e.h.t. rectifier. The type of output valve used and the presence or absence of a damping diode thus make no difference to the present discussion.

The basic circuit, shorn of damping arrangements, is given in Fig. 1. In practice, the transformer primary

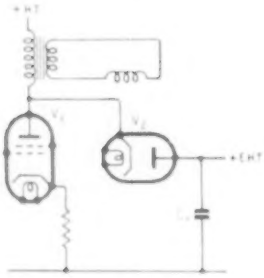

Fig. 1. Basic circuit of typical line-scan stage with e.h.t. rectifier.

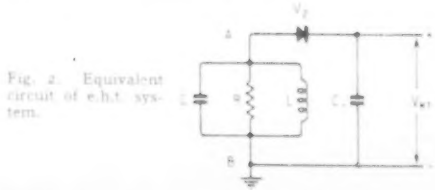

Fig. 2. Equivalent circuit of e.h.t. system.

* This will be included with the second half of the article.

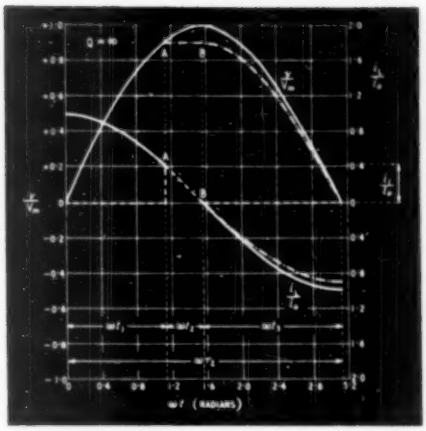

Fig. 3. Variations of voltage and current in an undamped circuit, (solid line) with the e.h.t. rectifier disconnected, (dotted line) with the rectifier connected. The dash-line curve shows the current through the rectifier.

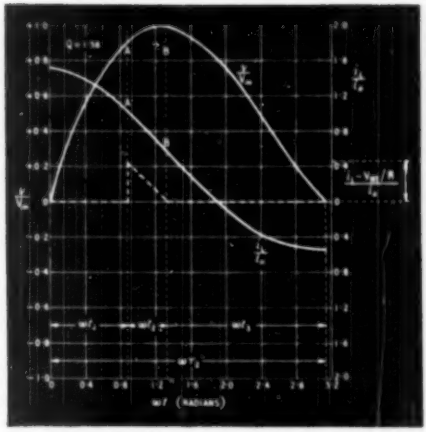

Fig. 4. Variations of voltage and current in a circuit of Q = 1.58 (solid line) with e.h.t. rectifier disconnected. The dash-line curve shows the current through the rectifier and the dotted line the current in L when the rectifier is connected. The curve beyond B is not shown.

is often used as a step-up auto-transformer between V_1 and V_2, but this is immaterial at present. The equivalent circuit has the form shown in Fig. 2. When the valves are cut off at the end of the scan to initiate fly-back there is a current in L which is the peak value of current reached during the scan; this is designated i_0. The energy in the magnetic field of the coil is then $Li_0^2/2$.

Because the scan current varies with time there is a back e.m.f. across L during the scan and so a charge on C. At the instant of fly-back the voltage across C is LI/τ_1 where I is the peak-to-peak scanning current in L and τ_1 is the scan period. The energy stored in C is $CV^2/2 = CL^2I^2/2\tau_1^2$.

The relation between i_0 and I depends on the circuit damping, as will be shown later; but I can never be less than i_0 nor greater than $2i_0$. For a given value of I the inductive energy is a minimum when $i_0 = I/2$ and taking this value it becomes $LI^2/8$. The ratio of magnetic to electric energy is thus $\tau_1^2/4LC$. It will be seen later that under this condition $LC = \tau_2^2/\pi^2$ where τ_2 is the fly-back period; and so the energy ratio becomes $(\pi\tau_1/2\tau_2)^2$ and for the B.B.C. transmissions this has the value 76.5.

The energy stored in C at the end of the scan is thus very small compared with that stored in L and we are justified in neglecting it in comparison. It is to be noted, too, that we have computed the ratio for the worst case of $I = 2i_0$; had we taken the other limit of $I = i_0$ the ratio would have been 306 : 1.

The effect of neglecting the initial charge on C is considerably to simplify the analysis but to make the calculated value of the peak voltage on fly-back in error by the initial voltage on C—a matter of 150—250 V in 3—6 kV.

Taking for simplicity, therefore, an initial condition of a current i_0 in L, C being uncharged, the current in L continues to flow in its initial direction and it flows into C. The voltage across C therefore rises and as it does R draws current. This continues until the energy in L has disappeared, being partly dissipated in R and partly stored in C.

If R were infinite, so that there were no dissipation of energy, all the initial energy from L would have been transfered to C. The voltage across C would then have its maximum value V_m and we could write $Li_0^2/2 = CV_m^2/2$, whence $V_m = i_0\sqrt{L/C}$. This is the maximum possible value of V_m. In practice it is always less because there is always some dissipation of energy.

After the maximum voltage on C has been reached C starts to discharge and supplies current to R and L. The current in L is zero but is changing at its maximum rate when the voltage on C is a maximum. When C discharges, therefore, the current in L reverses, passing through zero to increase in the negative direction. As the voltage falls R takes less and less current, the current in L increases negatively, and its rate of change falls off. Eventually C is fully discharged, R draws no current, there is a maximum negative current in L and zero rate of change of current. The energy stored in C at the time of maximum voltage has, less that dissipated in R, then been transferred back to the magnetic field of L.

If the circuit were left to itself the whole process would repeat until all the energy had been dissipated in R. If R were infinite it would go on for ever and the current and voltage would oscillate continuously. With finite damping the oscillations become negligible after a number of cycles which depends on the degree of damping.

In the television application the end of fly-back and the start of the following scan are taken as occurring at, or very shortly after, the first half-cycle of oscillation when the current is at, or just beyond, its first negative maximum. When a damping diode is not used this negative current maximum can only be very small—at most 10-15% of the initial current. When diode damping is employed the nega-

tive current maximum can advantageously be made as large as possible, for subsequent oscillation is inhibited by the diode.

In all cases we are interested only in this first half-cycle and its duration must coincide with, or be less than, the time allotted in the transmissions for fly-back. The solid line curves of Fig. 3 show the way in which voltage and current vary during this half-cycle for the ideal case of zero damping and Fig. 4 shows their variations for a degree of damping such that the overshoot is 33⅓%. By overshoot is meant the ratio of the magnitude of the first negative current maximum to the initial current. In Fig. 3 the voltage wave is sinusoidal and the current co-sinusoidal; in Fig. 4 they are damped sine and cosine waves.

The E.H.T. Rectifier

Now let us consider the action of the e.h.t. rectifier V_2 in Figs 1 and 2. We assume that the reservoir capacitor C_r is charged to a voltage V_{R1}. Let the voltage across the resonant circuit be v and its maximum value be V_m. Then as long as v is less than V_{R1}, the diode V_2 is non-conductive and v varies in accordance with the normal laws of the tuned circuit alone. It follows the voltage curve of Fig. 3 or 4. This happens until the point A is reached, at which v and V_{R1} are equal. The diode then conducts.

As the diode is assumed to be ideal and as V_{R1} is assumed to be constant, so far as short-term variations are concerned, the voltage across the circuit is now clamped at V_{R1} and cannot rise further. The top of the free voltage curve is thus cut-off. If the voltage is constant the capacitance C can draw no more current and R draws a constant current V_{R1}/R. The current in L, less that drawn by R, thus flows through V_2 into C_r.

In reality, if current flows into C_r the voltage across it must rise, and therefore C must take some current. However, we are assuming that C_r is so large that the voltage rise across it is negligible.

If the voltage is constant the rate of change of current in L must be constant, and so the current must fall linearly with time. This is shown by the portion AB in the curves of Figs 3 and 4. This process goes on until the current in L has fallen to the value needed by R at the voltage V_{R1}. This is zero in Fig. 3 and a finite value in Fig. 4. There is then no surplus current to flow through V_2.

After this C starts to discharge and supplies current to L and R and so the voltage falls, cutting off the diode. The reservoir capacitance cannot, of course, discharge to supply them for V_2 cannot pass reverse current. After the point B, therefore, we are left with a free resonant circuit and the response can be calculated as one having C charged to V_{R1} and a current in L equal to V_{R1}/R as initial conditions.

Because energy has been abstracted from the circuit during the conductive period of the diode there is this much less energy left in the circuit to be transferred to the magnetic field in the negative quarter cycle. The result is that the overshoot is less than it would be if the e.h.t. circuit were absent. This is plainly shown by the dotted curves of Fig. 3. The effect of the e.h.t. circuit is thus to damp the resonant circuit.

The current through V_2 has the triangular waveform shown in Figs 3 and 4. It has an amplitude $i_1 = V_{R1}/R$ and flows for a period t_2. The mean current during t_2 is one-half the amplitude and the quantity of electricity passed to C_r is the product of this mean current and its duration t_2. In the equilibrium condition this must equal the quantity of electricity withdrawn from C by the demands of the cathode-ray tube during one complete scanning cycle of duration τ. This is the interval between the start of successive fly-backs and is 68.77 μsec for the present transmissions. This mean current is designated i_{R1}. Except when a voltage-multiplying rectifier is used the load current i_{R1} is the same as the tube current i_T and the circuit voltage V_{R1} is equal to the tube voltage V_T.

It is now easy to see how a variation of tube current affects the e.h.t. voltage. If i_{R1} increases a greater quantity of electricity must be passed through V_2 to C_r. Therefore the peak current $i_1 = V_{R1}/R$ or the conduction time t_2 or both must be greater. In practice both increase, for diode conduction must start earlier to permit an increased current to flow. It can start earlier, however, only if V_{R1} falls. With the lower voltage R draws less current and so the time of diode cut-off is a little later.

Increasing the tube current thus inevitably means a fall of V_{R1}. Conversely, decreasing the current causes the voltage to rise to a maximum of V_m at zero current. If it is necessary for the tube current to vary from zero to some maximum value the e.h.t. voltage will vary from V_m to some minimum value. What this is depends only on the conduction time t_2 corresponding to the minimum permissable voltage.

If the regulation is to be good it is necessary to choose this minimum voltage very close to V_m. Unfortunately this means that there is relatively little current in L at this time. If the peak current through V_2 is to be sufficient, therefore, it is necessary to start with a large value i_0 of initial current. All this means, in effect, is that for good regulation it is necessary for the volt-amperes of the deflection circuit to be large compared with the power drawn from the e.h.t. circuit, which is not a very surprising conclusion.

(To be continued)

CLUB NEWS

Birmingham.—Members of the Slade Radio Society are visiting Elmdon Airport on August 18th, and a d.f. test will be held by the club on August 30th. At the meeting on September 1st two members will give their experiences in constructing and operating the "View Master" television receiver. Sec.: A. N. Smart, 116, Westmore Road, Erdington, Birmingham, 23.

Brighton.—At the meeting of the Brighton and District Radio Club (G3FAE) on August 8th in the Eagle Inn, Gloucester Road, at 7.30, F. Hiss, G3DGU, will describe and demonstrate an amateur communications receiver for amateur operation. Sec.: L. F. Holden, 17, Harrington Road, Brighton.

Coventry.—A lecture on a.c. theory—one of series in preparation for the radio amateurs' examination—will be given to the Coventry Amateur Radio Society (G2ASF) on August 14th. Meetings are held on alternate Mondays at the B.T.H. Social Club, Holyhead Road, at 7.45. Sec.: R. G. Lines, (G2FOH), 142 Shumcliffe Road, Coventry.

Warrington.—Provisional arrangements for the inter-club "top band" telephony contest to be held in the area on September 24th provide for operating periods from 3 to 5 and from 7 to 10 p.m.

Watford.—Meetings of the Watford and District Radio and Television Society are held on the first and third Tuesdays in each month at the "Cookery Nook," The Parade, Watford. There will not be a meeting on August 15th. Sec.: R. W. Bailey (G3QH), 32, Cassiobury Drive, Watford.

These Valves make News!

TYPE 8D5

Bulb diameter, ⅞in. max.
Sealed height, 1⅞in. max.

FIRST Noval Based Low Microphony Pentode Amplifier

Type 8D5 fulfils the long outstanding requirement for a low microphony single ended valve of small overall dimensions. The outcome of 18 months' intensive development and experimental work, this valve exhibits the lowest hum and microphony factor commercially attainable in a miniature type at the present time.

Type 8D5 is primarily designed for use in the early stages of high gain A.F. amplifiers. By virtue of its thorough screening and the careful choice of base connections employed, it is also suitable for R.F. amplification up to 30 Mc/s.

CHARACTERISTICS

Heater Voltage	6.3 volts
Heater Current	0.15 amp.
Anode Voltage	300 volts max.
Screen Voltage	125 volts max.
Mutual Conductance	1.25 mA/V
Anode Impedance	2.3 meg.

INTER ELECTRODE CAPACITANCES

Input	4.0 pF.
Output	4.0 pF.
Control Grid to Anode	0.01 pF. max.

Application Notes

Although the valve may be used successfully when mounted in any position, it will retain its characteristics better when the axis is vertical. Residual hum is caused by capacitances between pins and between contacts in the socket; it is of the order of 20 μV when the grid input impedance is 2 megohms and a P.T.F.E. socket is employed. If no "hum-dinger" is used, the heater lead connected to pin No. 4 should be earthed, together with connections to pins 1, 6 and 9.

BRIMAR

WRITE NOW TO DEPT. 4530
for data sheet on the above valve

TECHNICAL ADVICE SERVICE

STANDARD TELEPHONES AND CABLES LIMITED, FOOTSCRAY, SIDCUP, KENT.

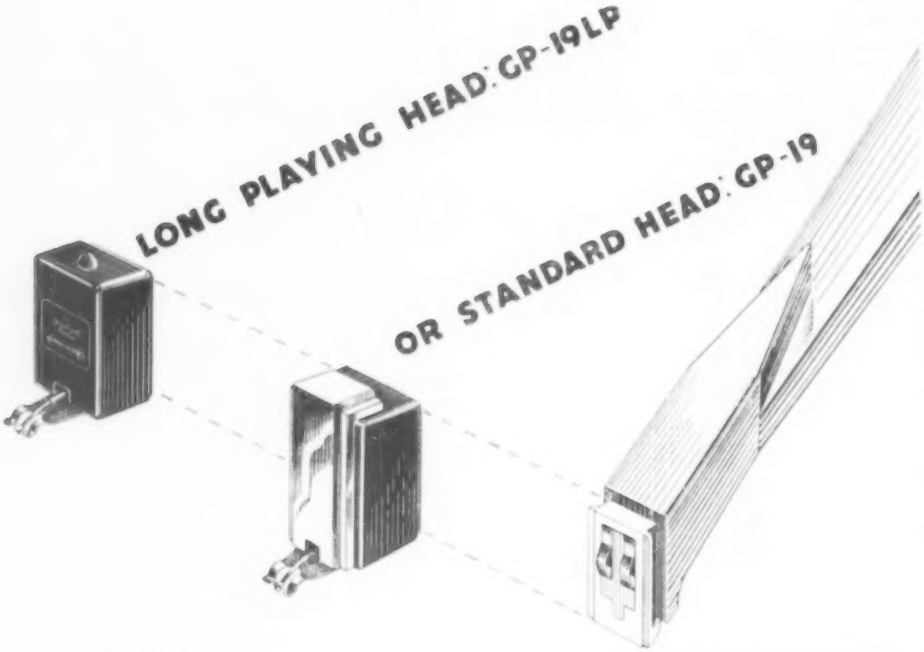

INTERCHANGEABLE ON THE GP20 NEW TRUE FIDELITY PICK-UP

Long-playing micro-groove records are here. And so is the GP.19LP Head, specially made for them. It is interchangeable with the Standard GP.19 Head on the famous GP.20 Pick-Up. The man with a GP.20 and these two heads is equipped for the finest possible reproduction from *any* record—standard or micro-groove, 78 or 33⅓ r.p.m.

GP-20	*Complete pick-up with Standard Head*	£2 10 0 (*plus 21/5 P.T.*)
GP-20LP	*Complete pick-up with Long Playing Head*	£2 10 0 (*plus 21/5 P.T.*)
GP-19	*Standard Head as fitted to GP-20*	£1 10 0 (*plus 13/4 P.T.*)
GP-19LP	*Long Playing Head as fitted to GP-20LP*	£1 10 0 (*plus 13/4 P.T.*)

SOME CHARACTERISTICS

GP-19 HEAD

Output ½v. at 1,000 c.p.s.—5 to 20 times greater than comparable magnetic types.
Range 30-10,000 c.p.s.
Low needle pressure—14 grms.—virtually eliminates record wear.

GP-19LP HEAD

Output ½v. at 1,000 c.p.s.
Response is flat from 30 c.p.s. to 3,000 c.p.s. with a rising characteristic above this frequency.
Needle pressure 7 grams.

BOTH HEADS

Automatic bass-boost without additional equalisers.
Can be fitted to domestic radios.
Needle talk and motor rumble negligible.
Unbreakable and non-hygroscopic crystal element.
Permanent sapphire stylus eliminates needle change.

COSMOCORD LIMITED · ENFIELD · MIDDLESEX

Standing Waves on R.F. Cables

When Travelling Waves Interfere With Each Other

By "CATHODE RAY"

THE introduction to this story appeared last month, so I had better begin by recapitulating. We saw how a f. cable, such as that used to connect television aerials to receivers or transmitters, is (neglecting loss resistance) electrically equivalent to a chain of series inductances and parallel capacitances, in which these components are infinitesimally small and infinitely numerous; and that on this basis it is quite easy to discover the main facts about such cables. One of these facts is the existence of a continuously growing phase lag along it; which means that if a.c. is put in at one end by a generator (such as a receiving aerial or a transmitter) it takes time to reach the other. Another important fact is that at first, while the current is on its way, the cable appears to the generator to be a resistance having the value $\sqrt{L/C}$, where L and C are respectively the inductance and capacitance of any length. This is the so-called characteristic resistance, denoted by R_0. Since R_0 is a resistance, the current everywhere along the line is in phase with the voltage. If the far end of the cable is closed by a load resistance R equal to R_0, the ratio of voltage (V) to current (I) arriving there satisfies Ohm's Law, and the power is completely absorbed. But if R is greater than R_0, the voltage rises, and in so doing drives part of the current back towards the generator. The ratio of the surplus voltage (v) to the reflected current (i) must of necessity equal R_0; and from this we calculated that

$$\frac{i}{I} = \frac{v}{V} = \frac{R - R_0}{R + R_0}$$

(Although we didn't actually consider what would happen if R was less than R_0, this eventuality is covered if we assume that i and v can be negative. A negative current going backwards is the same as an increase in the forward current.)

As an example of all this we assumed the values shown here in Fig. 1. The 400-V generator with 100-Ω internal resistance, connected to a 100-Ω cable, sends 2 A down it at 200 V. Arriving at the other end, this power finds a 300-Ω load, which does not agree with 200 V, 2 A. By the time the current through it has reached 1 A the voltage across it has risen to 300 V, giving a 100-V surplus back pressure to return the surplus 1 A along the line. So 100 watts is returned to the generator, and is totally accepted by it because the generator resistance is the right value for 1 A at 100 V. The net outgoing power is therefore 400 − 100 = 300 W, the same as is being absorbed by the load.

That is as far as we got, with a sinister hint that there were complications in store when we came to consider the current and voltage, owing to the phase lag introduced by the cable.

Let S stand for the speed of the waves along the cable, in metres per second. In one second, they would travel S metres (if the cable were long enough). In the period of one cycle, which is $1/f$ of a second, obviously they travel S/f metres, which is one wavelength, denoted as usual by λ. So points on the cable S/f metres (or one wavelength) apart have a phase difference between them of one whole cycle or 360°. Along cables with air-spaced conductors, S is very nearly equal to 300 million—the speed of free electromagnetic waves—but the higher permittivity of solid spacing reduces S, so that λ along such a cable is shorter than in space. If, for example, S is 200 million, and f is 50 Mc/s, λ is 200/50 = 4 metres, compared with 6 metres in space.

Stationary Wave Pattern

The one place where we already know the relative phases of the original and reflected voltage and current waves is at the point of reflection—the load end of the cable. When, as in Fig. 1, R is greater than R_0, the reversal in direction of the reflected current is equivalent to its being exactly opposite in phase to the original (arriving) current; that is to say, the amount going on into the load is less than the original. The reflected voltage is also opposite in phase to the original, but as it adds to the back voltage due to the resistance it increases the voltage across the load.

Now let us move towards the generator end, examining conditions as we go along. We start with 1 A, 300 V at the load end. At a distance of quarter of a wavelength (λ/4) the original and reflected waves are spaced apart by half a wavelength

Fig. 1. Numerical example of a cable or feeder line joining a generator (shown inside the dotted line) to a resistive load. I, V and P are the original current, voltage and power travelling towards the load, and i, v and p the current, voltage and power reflected by it.

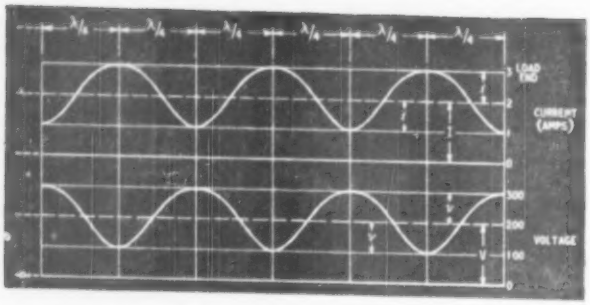

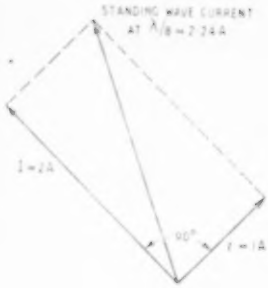

Left: Fig. 2. Stationary distribution of r.m.s. current and voltage near the load end, under the conditions specified in Fig. 1. Right: Fig. 3. Vector diagram for calculating current at odd multiples of λ/8 from the load end in Fig. 2.

($\lambda/2$)—that being the total return journey to and from the load—and by 180° in phase. So at that point the two currents are in phase, giving a total of 3 A, and the voltage is 200 − 100 = 100 V. Moving along another $\lambda/4$, we are $\lambda/2$ from the load, and the phase difference is 360°. So at that point we get back to the same conditions as at the load—1 A, 300 V. Another $\lambda/4$ brings us to a 3-A, 100-V point. And so on, all the way. The reflected current and voltage alternately add to and subtract from the 2 A, 200 V travelling from generator to load. At intermediate points there are phase differences other than 180° or 360°, so the net current and voltage vary in the wavelike manner shown in Fig. 2. These are not travelling waves, like those causing them; they are a stationary pattern of steady r.m.s. values, such as would be indicated by meters connected at points along the line. So, not unnaturally, they are called *standing waves*. Incidentally they are not sine waves. If they were, the values at $\lambda/8$ intervals would be the same as if there were no reflected wave; but at those points the phase differences are 90° or 270° and, as Fig. 3 shows, the reflected wave raises the value from 2 A to 2.24 A and the voltage in the same ratio.

Matching and Efficiency

The ratio of maximum to minimum current or voltage is called the standing wave ratio. In this example it is 3/1. It is a thing that can be measured, by running a suitable voltmeter along the line. Obviously, it is a good way of finding out how nearly the load matches the line. If there is a perfect match ($R = R_0$) the standing wave ratio is 1. At the other extreme, if the end of the line is left open ($R = \infty$) or short-circuited ($R = 0$), the whole of the power is reflected, so that at certain points, $\lambda/2$ apart, the current or voltage is completely cancelled out, and the s.w.r. is ∞.

From our previous calculations of the amount reflected it can easily be deduced that the s.w.r. in general is equal to R/R_0.

And so we come at last to the generator again. Clearly the state of things there will depend on the length of the cable, in λ units. Fig. 2 shows that if it happens to be an exact number of half-wavelengths the current and voltage will be the same as at the generator—1 A, 400 V. Since the generator e.m.f. is 400 V, that means a drop of 100 V in the internal resistance (100 Ω), which is right for a current of 1 A. So far as the generator is concerned it is now feeding a load of 300 Ω, just as if it were connected direct to R. So the original input resistance of the line—100 Ω—is raised to 300 Ω directly the reflected wave reaches the generator. The original "error" in the amount of power issued is exactly corrected. Even this "error" is right, really; because a temporary over-issue was necessary to fill up the line with waves of energy. I don't know what you think, but this always strikes me as a very pretty example of how natural laws always win, even when we think we have caught them out.

But what if the cable length is not an exact multiple of $\lambda/2$? Suppose we knock off $\lambda/4$, so that the generator connects at a 3-A, 110-V point? The cable will then look to the generator like a 100/3 = 33.3-Ω resistance. If such a load resistance were connected directly to the generator, the total resistance in circuit would be 133.3 Ω, the current would be 400/133.3 = 3 A, the terminal voltage would be 400 × 33.3/133.3 = 100, and the power into the load would be 3 × 100 = 300 W. Which all agrees perfectly with the cable figures. So again everything is completely legal; there isn't a loose end anywhere.

At intermediate cable lengths the current at the generator is not in phase with the voltage, so the input impedance includes reactance as well as resistance; but the outgoing power is still the same, and everything sorts itself out.

This does not mean that the exact cable length is unimportant. At a $\lambda/2$ point the power lost in the generator is $1^2 \times 100 = 100$ W. But at an odd $\lambda/4$ point it is $3^2 \times 100 = 900$ W. Rather a difference in the efficiency! At the $\lambda/2$ point it is 300/400 = 75%; at the $\lambda/4$ point it is 300/1200 = 25%. If the load resistance were a perfect match to the line—100 Ω—the power supplied would be a maximum—400 W—but the efficiency would be only 50%. So it might well be considered better to arrange for a deliberate mismatch and get 300 W for a loss of 100 W rather than 400 W for a loss of 400 W. But the great advantage of working under matched conditions is that the exact length of cable doesn't matter, and the frequency can be varied without upsetting things. For instance, suppose the cable is 25 wavelengths long, and operated under 300-W, 75% efficiency conditions. If the frequency increased by 1%, the cable would then be 25¼ wavelengths long and the efficiency would fall to 25%, if

indeed the generator managed to survive its load falling from 300 Ω to 33.3 Ω and its dissipation going up from 100 W to 900 W. So in such a case it would be better to use 300-Ω cable, so as to have no standing waves.

Reverting to Fig. 2, suppose we knock off the 300-Ω load and the λ/4 length of cable nearest it, and substitute a 33.3-Ω load. This fits the 3-A, 100-V conditions at the point where it is connected, and the generator will not know what we have done. The input end of the line still looks like a 300-Ω resistance. What we have done, therefore, is to take advantage of the peculiarities of standing waves for the purpose of feeding a 33.3-Ω load under 300-Ω conditions. The cable is acting as a 3 : 1 transformer as well as a transmission line. But there is no need to have standing waves along the whole of it. Fig. 2 shows that a single λ/4 section is enough. A 1% change of frequency will not cause an appreciable difference in the working conditions over such a short length. For the rest of the distance 300-Ω cable should be used.

From our study of Fig. 2 the principle of the quarter-wave transformer just described should be clear. A load resistance of 3 R_0 at one end is transformed to $R_0/3$ at the other. If we multiply these end values together we get R_0^2. The same result would be obtained no matter what load resistance was used. Call it R, and the resistance to which it is transformed at the other end R'. Then $R' R = R_0^2$, so the required R_0 is $\sqrt{R' R}$. To make a 2,000-Ω load look like 80 Ω, then, what we want is a quarter-wave length of line having a characteristic resistance equal to $\sqrt{80 \times 2{,}000} = 400$ Ω.

Reactances Made Here

But what if the load includes some reactance? This can be brought within the foregoing scheme, because a mixed impedance can always be represented as a pure resistance in parallel with a pure reactance. And the reactance can always be cancelled out by connecting in parallel an equal reactance of the opposite kind.

This is where we can be very cunning, taking advantage of the fact that lengths of line other than multiples of λ/4 are reactive. I have already pointed out that if they are either open- or short-circuited they are bound to be pure reactances, because there is nowhere for power to be dissipated. Suppose we short-circuit the end of our 100-Ω cable with 2 A at 200 V coming along it. No voltage can be established across a short-circuit to oppose the arriving 200 V, so the whole of it occupies itself by driving −2 A in the opposite direction. Now 2 A arriving and −2 A going is equivalent to 4 A arriving, so that is the current flowing through the short circuit. The reflected wave is equal to the original wave, and at the shorted end the voltages cancel out and the currents double. At a distance of λ/4 the opposite takes place; the voltage is 400 and the current is 0, so the input impedance of a quarter-wave "hairpin" is infinitely great (or, in practice, very large). In fact, it can be used as an insulator for that particular frequency, notwithstanding that its d.c. resistance is negligible.

These facts can be shown with vector diagrams, as in Fig. 4. The condition at the end is at (a), with the reflected voltage v cancelling V, and the reflected current i doubling I. At a λ/4 distance, V is quarter of a cycle earlier and v is quarter of a cycle later, so they add up to double, as at (b), where the situation is reversed. The diagram for half-way between, at λ/8, is like (c), where the resultants or net voltage and current are shown dotted. The thing to note is that they are exactly at right angles to one another, which is what happens with a pure reactance. And the current is lagging the voltage, which means the reactance is inductive. If you draw the vector diagram for other intermediate points you will find that they all indicate pure inductive reactances, but that the value varies from 0 to ∞ as you move from the shorted end. Similarly an open-circuited piece of cable not exceeding λ/4 in length gives every possible value of capacitive reactance. These "stubs" are very much used in feeder systems for cancelling unwanted reactances.

Loss Resistance

One could go on *ad lib* about the various practical devices and dodges based on standing-wave phenomena, but let us give some attention to one aspect of the matter we have conveniently ignored hitherto—the loss resistance. Part of it is contributed by the actual resistance of the wires or tubes, but of course the usual sources of r.f. loss such as dielectric loss

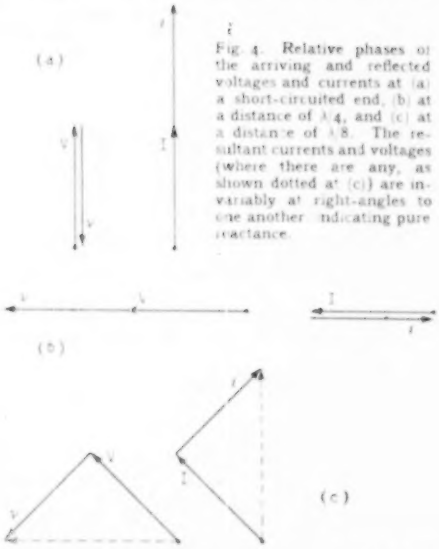

Fig. 4. Relative phases of the arriving and reflected voltages and currents at (a) a short-circuited end, (b) at a distance of λ/4, and (c) at a distance of λ/8. The resultant currents and voltages (where there are any, as shown dotted at (c)) are invariably at right-angles to one another, indicating pure reactance.

Fig. 5. The full line represents the constant signal level along a loss-free perfectly matched cable, and the dotted curve shows the exponential fall-off due to uniformly distributed loss.

and radiation can be represented in an inclusive resistance figure. Fortunately, the cable has to be very bad before loss resistance makes much difference to R_0, except perhaps to throw in a little reactance. But although the loss resistance of reasonably good cables can usually be ignored in connection with R_0, it does not follow that it can be ignored altogether. Its most important effect is to take a rake-off from the power flowing along it. This is usually expressed in db per 100 feet. If, say, 20% of the power (approx. 1 db) is absorbed in the first 100 feet, the second 100 feet absorbs 20% of that, or 16% of the original, and so on, giving an exponential die-away curve, like the dotted line in Fig. 5, compared with the straight and level line representing a theoretical perfect cable. The reflected waves, if any, also decline in this way, so that if the cable is long their effect by the time they reach the generator may be a good deal less than in the foregoing theoretical calculations.

Another simplifying assumption we have been making is that the resistance of the generator is equal to R_0, so that reflected waves are completely accepted by it. The generator resistance affects the reflected wave just as the load resistance affected the original wave; so if it is not equal to R_0 part of the reflected wave will be reflected again; part of that will be reflected at the load, and so on. If there is a big mismatch ratio at both ends, and the line is low-loss, and of such a length as to bring all the travelling waves more or less into phase with one another, very large voltages and currents can build up at $\lambda/2$ intervals. If a transmitting aerial becomes disconnected in a gale, the first symptom may be sparking across the line due to this build-up. The phenomenon is analogous to the signal magnification obtained with a low-loss tuned circuit.

It is very easy to get the idea that mismatching at the generator end would alter the standing wave ratio. But this is quite wrong. The waves reflected at the generator travel down the line towards the load at the same speed as the original waves; and, depending on their phase, have the effect of increasing or reducing the total voltage and current going in that direction. But the same thing could be done by altering the generator voltage, and nobody who has studied the thing at all would imagine that doing so would alter the proportion reflected by the load. So the standing wave ratio still depends only on R/R_0, except of course in so far as it is reduced towards the generator end by line loss, which causes the reflected wave to become weaker in proportion to the original wave.

Lastly, for the benefit of readers who disapprove of the "it can be shown" style of these two articles, I have provided an appendix (left) setting out the calculations in full.

APPENDIX

E = e.m.f. of generator
r = internal resistance of generator
V = voltage across } line, in the original wave
I = current in }
v = rise in voltage due to mismatch at load end
i = current returned to line by v
R_0 = characteristic resistance of line
R = load resistance
ρ = standing-wave ratio
R_1 = input resistance of quarter-wavelength line terminated by R.

Line losses are neglected, and the authority for statements (1)—(4) below is Ohm's Law. It may be helpful to take another look at Fig. 1.

$$V = \frac{ER_0}{R_0 + r} \quad \ldots \quad (1)$$

$$I = \frac{V}{R_0} \text{ and } \frac{V}{I} = R_0 \quad \ldots \quad (2)$$

$$\frac{v}{i} = R_0 \quad \ldots \quad (3)$$

$$\frac{V + v}{I - i} = R \quad \ldots \quad (4)$$

Substituting $\frac{V}{R_0}$ for I (2) and $\frac{v}{R_0}$ for i (3) in (4) —

$$\frac{V + v}{V - v} = R$$

$$\frac{V}{R_0} - \frac{v}{R_0}$$

$\therefore \frac{V + v}{V - v}$ (which, by definition, $= \rho$, and, since the currents are proportional to the voltages, $= \frac{I + i}{I - i}$)

$$= \frac{R}{R_0} \quad \ldots \quad (5)$$

Standing-wave Ratio

$\therefore (V + v) R_0 = (V - v) R$
$\therefore v(R + R_0) = V(R - R_0)$

$\therefore \frac{v}{V}$ (which, from (2) and (3) $= \frac{R_0 i}{R_0 I} = \frac{i}{I}$)

$$= \frac{R - R_0}{R + R_0} \quad \ldots \quad (6)$$

Reflection Coefficient

Repeating (4) $R = \frac{V + v}{I - i}$

Owing to 180° phase displacement along the $\lambda/4$ line

$$R' = \frac{V - v}{I + i}$$

From (3) $V - v = \frac{R_0}{R}(V + v)$ and $I + i = \frac{R}{R_0}(I - i)$

$$\therefore R' = \frac{V - v}{I + i} \cdot \frac{R_0}{R} \cdot \frac{R_0}{R}$$

$$= \frac{R_0^2}{R}, \text{ and } R_0 = \sqrt{R'R} \quad \ldots \quad (7)$$

Quarter-wave Transformer

NEW TEST RECORDS

A SERIES of special recordings, pressed in material with low intrinsic background noise, has been issued by the British Sound Recording Association for test and demonstration purposes. The subjects are as follows:

PR100. History of the gramophone, a concise summary by Leo Watts.

PR101. Unaccompanied violin, without distracting rhythmical pattern or melody, for judging quality of reproduction at high frequencies.

PR102. Unaccompanied bass viol (bowed and plucked strings) for low-frequency tests.

PR103. Test frequency record with bands at 1 kc/s intervals from 10 kc/s to 1 kc/s, 500 c/s, 200 c/s, 100 c/s and 50 c/s, each of 12 seconds' duration, preceded and followed by 20-second 1000 c/s reference bands.

Enquiries should be addressed to the Hon. Librarian, B.S.R.A., 9, Stanton Road, West Wimbledon, London, S.W.20.

New Scanning Circuit

Line-Scan Current Generator

By P. R. J. COURT, Grad.I.E.E. (Pye, Ltd.)

ONE of the major advances in the design of domestic television receivers in recent years has been the introduction of a.c./d.c. technique, thus permitting the elimination of the bulky and expensive mains transformer. This is now almost universal practice, together with the technique of deriving e.h.t. for the c.r. tube from the line-scanning circuit.

For the line time base to function satisfactorily with the limited h.t. voltage imposed by a.c./d.c. operation, and at the same time to supply e.h.t., it is generally necessary to use an energy-recovery stage employing an "efficiency diode" (or triode). The diode converts some of the energy stored in the inductance of the deflection system after the trace period, into useful deflection power. It contributes approximately the first 20 per cent to 40 per cent of the trace current, the actual proportion being a function of the losses of the system. The theoretical limit for an ideal system with no losses, is 50 per cent.

In order to realize maximum efficiency and optimum linearity, the output valve should be "cut off" for the period during which the efficiency diode is operating. When the diode portion of the trace is complete, the output valve is arranged to start conducting, and supply the remainder of the trace current.

Although such circuits have already been treated very fully by other writers,[1,2] it is of advantage at this point to describe briefly the operation of a simple sawtooth-driven line-scanning circuit, employing an efficiency diode, as in Fig. 1.

A positive-going sawtooth voltage, generated by some external oscillator, is applied to the grid of the output pentode V_1 which works into a load consisting mainly of the deflector-coil inductance, reflected back via the output transformer T. V_1 is biased so that the first part of the sawtooth waveform, which corresponds to the diode portion of the trace current, is beyond "cut-off." This is illustrated in Fig. 2 (a).

The anode current, and hence the current in the deflector coils L_1, L_2, increases linearly at a rate governed by the linear rise of grid voltage. Under these conditions, the pentode is working as a "constant-current" generator, the current rise being substantially independent of the load impedance. The current increases until the grid is rapidly returned beyond cut-off by the sawtooth flyback. The stored magnetic energy causes a free oscillation to ensue, at the natural resonant frequency of the system, the first half-cycle of which provides the current retrace. The deflector-coil current reverses, reaching a maximum value in the opposite direction, determined by the Q factor of the resonant circuit.

At this point, the free oscillation is halted by the action of the efficiency diode V_2, the anode of which is driven positively as the second half-cycle commences. The diode then presents a low impedance in parallel with the deflection system, through which the current decays exponentially. It is this decay of current, the greater part of which approximates to a linear change, which provides the first part of the trace. As it approaches the minimum value, the output valve takes control once more, supplying the balance of the trace current. Fig. 2 (b) shows the approximate current relationships in the deflection system.

Corresponding to the linear rise of deflection current, a steady positive voltage is developed across the major inductive component of the deflector-coil impedance, plus a small sawtooth voltage due to the minor resistive component. During the current retrace, a large amplitude negative pulse of approximately semi-sinusoidal form occurs. The deflector-coil voltage waveform is shown in Fig. 2 (c).

The diode conducts during the trace period, developing a steady automatic bias across its bypassed cathode-load resistance R, the voltage being approximately equal to the anode potential during the mean trace period. It is, of course, cut off during the retrace period.

The average diode conduction is controlled by the value of the cathode-load resistance. Ideally it is

Fig. 1. Simple sawtooth-driven line-scanning circuit employing an efficiency diode to start the deflection.

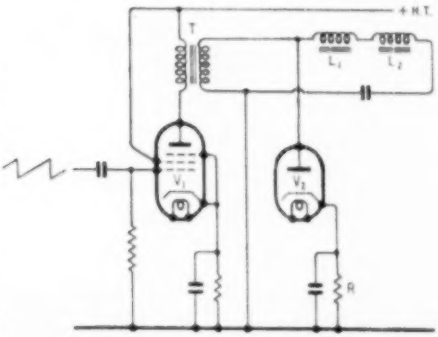

[1] A. W. Friend, "Television Deflection Circuits" (Parts I and II) *R.C.A. Review*, Vol. VIII, No. 1, March, 1947.

[2] O. H. Schade, "Magnetic Deflection Circuits for Cathode-ray Tubes." *R.C.A. Review*, Vol. VIII, No. 3, September, 1947.

O. H. Schade, "Characteristics of High-Efficiency Deflection and High-voltage Supply Systems for Kinescopes." *R.C.A. Review*, Vol. XI, No. 1, March, 1950.

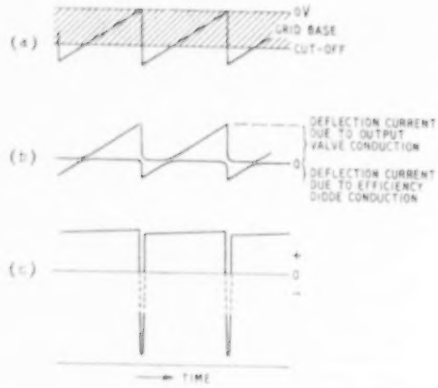

Fig. 2. (a) Sawtooth driving voltage in relation to grid base. (b) Current relationships in the deflection system of Fig. 1. (c) Voltage waveform appearing across the deflection system.

Right: Fig. 3. Basic circuit of a self-driven line-output stage.

necessary to control the instantaneous conduction during the trace period, otherwise the diode will tend to maintain a constant voltage across the deflection system; i.e., to eliminate the sawtooth component which must be present if the current waveform is to be acceptably linear. Better results are obtainable with a triode rectifier (for example the 6AS7G, which was specially developed for this purpose), the conduction of which is readily controlled by the application of a suitable waveform to its grid. If, for reasons of economy, it is necessary to employ a diode, a compromise may be made by inserting a controlling voltage in series with it. The voltage may be developed by the output valve and transferred by a suitable impedance network to the cathode of the diode. By suitably adjusting the magnitude and phase of the controlling voltage, the linearity of the trace may be adjusted to the optimum. The circuit of Fig. 7 employs a diode controlled in this manner.

For economic reasons, it is clearly advantageous to dispense with the separate sawtooth generator needed for the arrangement of Fig. 1 and to employ a self-driven circuit. The omission of a separate oscillator valve and its associated components contributes materially towards reducing the overall cost of the television receiver, and if this can be achieved without sacrifice of performance, the economy is entirely justified.

The design of a self-driven line-scanning circuit is attended with three additional problems which must be overcome if its performance is to be not inferior to that of a conventional separately-driven circuit.

With the latter, it is a relatively simple matter to achieve the desired balance between diode and output valve conduction. For example, it is apparent from Figs. 1 and 2 (a) that the instant at which V_2 starts to conduct may be readily controlled by a simple adjustment of its bias and/or the amplitude of the applied sawtooth waveform. In the case of a self-driven circuit, however, this constitutes an important design problem.

Self-driving Operation

In general, the self-oscillating type of line-output stage is arranged as a switching device, as in Fig. 3. L represents the inductance of the deflector coils reflected back via the output transformer. R represents the total circuit resistance including the internal resistance of the valve, while S represents the valve acting as a switch. When S is closed the current through L rises exponentially in accordance with the expression:—

$$i = I\,(1 - e^{-(R/L)t})$$

For the current rise to be substantially linear, the time constant of the circuit, L/R, must be long compared with t, the time duration of one scanning cycle. The limiting factor is R, which consists mainly of valve resistance, and which should clearly be as low as possible. This imposes rather severe limitations upon the choice of valves which may be satisfactorily used in such a circuit, unless considerable non-linearity is tolerable.

The tendency for the controls to be interdependent (i.e., amplitude control affecting frequency, etc.) is a difficulty common to all self-driven circuits. It is very desirable that this disadvantage should not be present in a commercial receiver, for in the hands of a non-technical viewer, the setting up of such controls can be very exasperating.

The circuit described below is a self-driven line-scanning output stage, for use in conjunction with an efficiency diode, which overcomes all of the problems outlined above, and which has a performance at least equal to that of an equivalent, separately driven circuit.*

The basic circuit of the time base is shown in Fig. 4. The oscillatory circuit is between the screen and control grids of the output pentode V_1. The turns ratio of the oscillator transformer T_2 is approximately 1:1. This transformer has a low Q at its

Fig. 4. Basic diagram of the new scanning circuit.

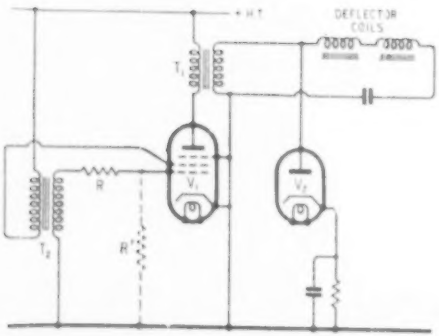

* Patent Application No. 11409/49.

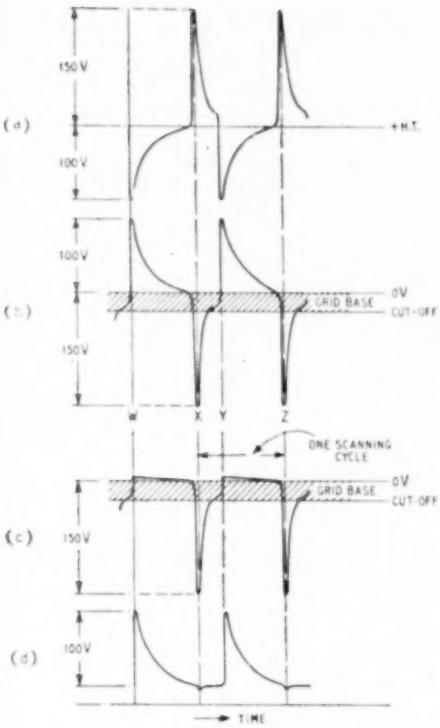

Fig. 5. Voltage waveforms encountered in the oscillatory circuit of Fig. 4. At (a) is shown the voltage at the screen-grid (that is, across the primary of T_2), at (b) the secondary voltage of T_2, at (c) the grid voltage and at (d) the voltage across R. This last is the difference between the voltages of (b) and (c).

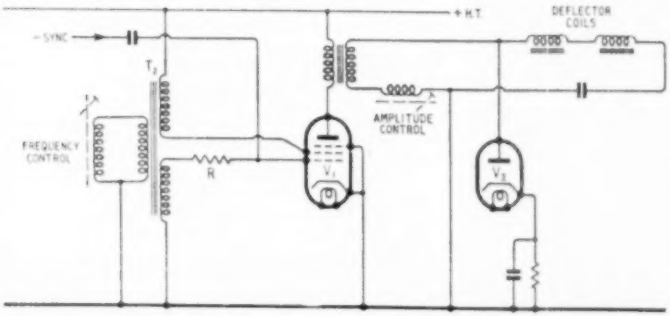

Fig. 6. Method of controlling amplitude and frequency by inductances, and of applying sync pulses.

natural resonant frequency, which is in the region of 40 to 50 kc/s. V_1 is the efficiency diode.

The operation of the circuit may best be understood from a study of Fig. 5, which shows the voltage waveforms encountered in the oscillatory circuit, commencing at the point where the grid approaches the potential at which the valve starts to conduct (point W along the time axis). The screen-grid current will cause that electrode to go more negative, while the voltage across the transformer secondary will consequently become more positive and so on. The valve will thus rapidly reach an unstable limiting condition, with the screen grid at a low potential, and the voltage across the transformer secondary highly positive.

The control grid will endeavour to follow the positive excursion of the secondary of T_2, but due to grid current flow, will have a low impedance represented by R'. R and R' form a potential divider, where R≫R', so that the grid potential will remain almost constant at slightly above zero volts during the positive excursion of the transformer secondary. With the grid slightly positive, the primary circuit appears as an inductance, L_p (the primary inductance of T_2), in series with a resistance, R_i (the internal screen-cathode resistance of the valve), and the voltages developed across the windings of T_2 will decay at a rate controlled by the primary "time-constant," L_p/R_i. (R_i will actually vary during this period, so the term time-*constant* is perhaps a misnomer.) The screen-grid potential will rise, and the secondary potential will fall. The control grid potential will also fall, only very much more slowly due to the effect of R – R'.

A condition is reached when the grid potential falls below zero volts, and the grid impedance R' becomes very high. The screen-grid current then rapidly falls to zero, and a large positive potential appears across the primary of T_2, the rate of rise being controlled by the resonant frequency of the transformer. Correspondingly, a large negative potential is developed across the secondary. The grid is able to follow the negative excursion of the secondary, because it now has a high impedance, and the valve is thus cut off.

These voltages actually represent the first half-cycle of a heavily damped oscillation which follows from the instant of cut-off. The return function is rather complex, being partly sinusoidal, modified by the heavy damping across the windings due to the low circuit Q. As the grid voltage enters the conducting region, the waveform flattens off as the additional damping of the output valve comes into play.

A condition is finally reached when the output valve takes control once more, and the operation repeats itself (point Y).

The complete cycle, so far as the actual scan is concerned, is from X to Z, with the valve cut off from X to Y, and conducting from Y to Z.

The relative durations of the periods of conduction and cut-off are governed by a number of factors, including the negative bias due to the

d.c. component of the grid current flowing through R, and the turns ratio of the oscillator transformer T_1.

By a suitable adjustment of these factors, the valve conduction time may be made exactly correct to suit the losses of a particular deflection system, and a satisfactory balance made between the portion of the trace supplied by the output valve and that furnished by the diode.

It will be seen from Fig. 5 (a) that during the conduction time of V_1 the screen-grid potential is rising. This has a very desirable effect upon the anode current, compensating to a large extent for the non-linear rise of current which would otherwise occur. This linearizing effect of the screen grid waveform considerably eases the impedance requirements for the output valve and permits the use of almost any type of line output pentode or tetrode.

Any other irregularities in the scanning waveform are reduced by the action of the efficiency diode, and the sawtooth current delivered to the deflector coils is linear within 3 per cent. A fair impression of the degree of linearity can be obtained from Fig. 8, which is a photograph of a familiar test pattern displayed on the screen of a receiver incorporating the circuit.

More Efficient

The repetition frequency is governed mainly by the "time constant" of the circuit during the conduction period, and control of frequency is effected by varying the inductance of the windings of this transformer. This may be achieved either by varying an air gap in the magnetic circuit or, preferably, by varying an inductance in parallel with one of the windings. The variable inductance may be made of smaller and more practicable proportions, if it is connected across a separate small winding arranged on the oscillator transformer, as in Fig. 6. The variable inductance may be a simple wave-wound coil with adjustable dust-iron core.

The scan amplitude is preferably controlled by means of a variable inductance in series with the deflector coils as in Fig. 6. The two inductances may be made of identical construction. As the oscillatory circuit is apart from the anode, variation of amplitude in the anode circuit has no appreciable effect upon the frequency.

Synchronizing is effected by feeding negative-going pulses into the grid circuit as shown in Fig. 6. These initiate the negative grid excursions at points X and Z in Fig. 5.

It is found that this type of scanning circuit is about 25 per cent more efficient than an ordinary sawtooth-driven output stage, using identical power valves and energy recovery circuits, due to the fact that the grid is slightly positive during the entire conduction time of the valve; the circuit is therefore particularly suitable for use in an a.c./d.c. television receiver, where the h.t. voltage is limited.

The bias voltage developed by the efficiency diode may be used to boost the h.t. supply to the output valve by any of the usual methods, and e.h.t. may be derived from the flyback voltage developed across the scanning output transformer in the conventional manner.

Fig. 7 shows the complete circuit, including refinements such as h.t. boost for the output valve, flyback e.h.t. supply, and a linearity control as used in the Pye LV30 series of television receivers.

Acknowledgment: The author would like to thank L. Lax, D. Ing. A.M.I.E.E., (Pye, Ltd.) for his valuable technical advice during the development of the circuit.

Fig. 7. Complete circuit, with refinements, as used in Pye LV30 series of television receivers.

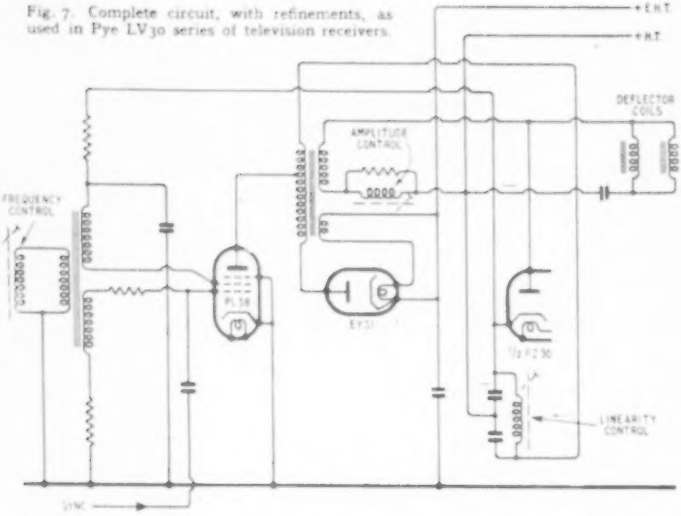

Fig. 8. Photograph of a test pattern on the screen of a television receiver incorporating the new scanning circuit, indicating the degree of linearity obtained.

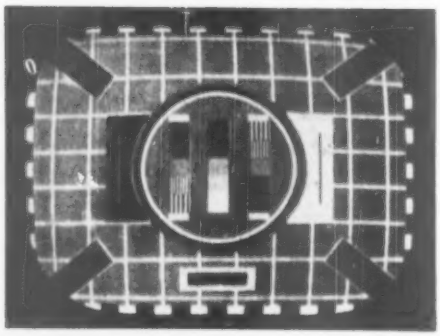

WORLD OF WIRELESS

Another Frequency Conference • Radar Volunteers Radio or Cable? • Wrotham Television Station?

Frequency Allocations

A GIGANTIC task faces the delegates attending the Extraordinary Administrative Radio Conference which, opening at the Hague on 1st September, will be attended by representatives of the 64 member countries of the International Telecommunication Union. They have to complete and approve frequency allocation plans for the majority of services—aeronautical, maritime, broadcasting, etc.—in the various bands throughout the spectrum.

The Atlantic City Conference of 1947 divided the spectrum between the various services and made provisions for the setting up of planning bodies to prepare schemes for the allocation of frequencies within these bands to individual countries or users. It was originally intended that the task of the Hague Conference would, in general, be limited to approving these plans, but it now appears that in some cases completely new schemes will have to be drawn up at the Conference.

With some services it is possible for allocations to be made on a regional basis, but with h.f. broadcasting (extending from 5.95 to 26.1 Mc/s), for instance, it has to be global. A plan has, however, been drawn up on a frequency-sharing and time-sharing basis as a result of conferences held in Mexico, Florence and Rapallo. One of the main difficulties, however, with this and other such plans, and especially that for the fixed services, is that they are based not on present needs but on anticipated requirements for some years to come.

It should be pointed out that the Conference will not be considering the European medium- and long-wave broadcasting bands, which were, of course, covered by the Copenhagen Conference.

Radar Reporting

THE formation of a Radar Reporting Unit, with its headquarters in London, is announced by the Air Ministry. This Unit, which will be known as No. 3700 (County of London) R.R.U., is being raised as part of the R.A.F. Control and Reporting System, and will be concerned with the operation and maintenance of "Chain Home" radar stations.

Men and women living in London and the Home Counties with some technical knowledge of radar, and especially members of the Radar Association, who are prepared to devote a few hours a week to training, are invited to call at, or write to, the Unit's headquarters at 77, Hallam Street, London, W.1. The commanding officer is Group Capt. E. Fennessy, O.B.E., director of the Decca Navigator Co., whose wartime service was largely devoted to the development and operational problems of radar navigational aids. He will hold the R.Aux.A.F. rank of Wing Commander.

Extending Television

THE site has now been chosen for the last of the chain of five high-power television stations. The transmitter to serve the Bristol Channel area will be erected at St. Nicholas, near Cardiff, Glam, and will be linked to the London studios by cable.

The laying of a co-axial cable between Birmingham and Manchester, where it is to be extended to Holme Moss, has led to the rumour that future stations will not be linked by radio. The fact is that a co-axial cable linking Birmingham and Manchester was planned by the Post Office for telecommunications, and it was therefore decided to add the necessary circuits to provide the television link. It is understood that the link between Holme Moss and the Scottish transmitter will be by radio.

New London Station?

WHEN originally announcing the plan for extending the television service, London was included in the chain of high-power stations. By comparison with the Sutton Coldfield station, and those planned for Holme Moss, Kirk o'Shotts and Cardiff, the Alexandra Palace transmitter is of low power. This fact has prompted the South Coast Televiewers' Association to start a campaign for a new high-power transmitter for London. The proposal is that the station erected at Wrotham, Kent, for experimental e.h.f. transmissions on both a.m. and f.m., should be equipped for television. The 470-foot mast, which is similar to that in use at Sutton Coldfield, is over 1,200 feet above sea level.

It is also stressed by the campaigners that the B.B.C.'s lease of the Alexandra Palace expires in 1956, by which time part of the new White City studio centre will be in use, but that will not solve the transmitter problem for which no provision is made in the White City plans.

The fact that Wrotham was recently used to provide the radio link between Southend and London for a television programme adds weight to the argument that the proposed station could readily be linked by e.h.f. radio with the studio centre.

Training Servicemen

WITH the object of assessing the need for service technicians in the television areas a census of servicemen on the staffs of dealers is being undertaken by the British Radio Equipment Manufacturers' Association. Having assessed the need, suitable action can then be taken by the association to stimulate the provision of training facilities.

Meanwhile the R.I.C., in co-operation with the Ministry of Education, is organizing a short course at the Regent Street Polytechnic for full-time and part-time teachers of radio and television servicing in technical colleges—64 of which run courses at present. The lectures, which have been arranged with a view to increasing teachers' background knowledge of the industry, will be given mostly by well-known members of the industry. The course will also include visits to factories and manufacturers' training centres.

PERSONALITIES

Frederick E. Terman, Dean of Engineering at the Stanford University, U.S.A., and author of a number of books including "Radio Engineering," has been awarded the Medal of Honour of the American I.R.E. "for his many contributions to the radio and electronics industry as teacher, author, scientist and administrator."

J. H. D. Ridley has been appointed head of the B.B.C.'s Engineering Secretariat, the section dealing mainly with the control of expenditure in the Engineering Division, in succession to F. Williams, now Superintendent Engineer (Studios).

F. Butler, B.Sc.(Hons.), M.Brit.I.R.E., has been appointed in succession to J. W. Whitehead, M.Brit.I.R.E., as examiner in radio transmission by the British Institution of Radio Engineers. They are both known to readers of *Wireless World*.

E. T. A. Rapson, M.Sc., M.Brit.I.R.E., has been appointed by the Brit.I.R.E. as examiner in mathematics which is to be a compulsory subject for graduateship from May, 1951. Since 1933 he has been on the staff of the Southall Technical College, first as head of the radio engineering department and for the past five years as head of the combined radio and electrical engineering departments.

OBITUARY

Alfred Clark, who was one of the founders of the group of companies controlled by Electric and Musical Industries, died on June 16th at the age

of 78. He was an American by birth and commenced his career in the organization set up by Edison to start the American gramophone industry in 1896. From 1931 until his retirement in 1946 he held responsible positions in the Gramophone Co. (H.M.V.), being chairman or managing director for 9 years. He became a British subject in 1926.

IN BRIEF

Broadcast Receiving Licences current in Great Britain and Northern Ireland at the end of May totalled 13,410,136, including 336,730 television licences.

Australian Television.—Approval has been given by the Australian Government for the provision of an experimental 625-line television station in Sydney preparatory to establishing a television service in the Commonwealth. It is understood that the Government has approved in principle the participation of private enterprise in the development of television.

Increased Power.—The maximum power (150 kW) permitted under the Copenhagen Plan for the medium-wave (1,268 kc/s) B.B.C. Home Service transmitter at Droitwich is now being used instead of 60 kW as heretofore. The power of the Norwich transmitter radiating the same service has also been increased, from 7.5 to 15 kW. The permitted power for Norwich is 20 kW. The transmitter now being used at Droitwich is that which, prior to the introduction of the Copenhagen Plan, radiated the Light Programme on 1,500 metres.

Scientific Instruments.—During the annual exhibition organized by the Scientific Instrument Manufacturers' Association, which is being held from September 4th to 8th at the Examination Hall, Queen Square, London, W.C.1, a series of technical papers covering the development and use of a variety of scientific instruments will be read. Details of the lectures and tickets for admission are obtainable from the Scientific Instrument Manufacturers' Association, 17, Princes Gate, London, S.W.7.

I.E.E. Council.—As a result of the ballot for the vacancies occurring on the Council of the I.E.E. on the 9th September, the following members of the Radio Section have been elected to serve:—Sir Archibald J. Gill (Engineer-in-Chief, G.P.O.), President; Harold Bishop (Chief Engineer, B.B.C.), Vice-President; C. E. Strong (Standard Telecommunication Laboratories) and Dr. R. A. Smith (Telecommunications Research Establishment), ordinary members.

Committee of the I.E.E. Radio Section for the coming session, which begins in October, is announced by the Institution. The new Chairman is C. F. Booth (Staff Engineer in Charge of G.P.O. Radio Development Branch); Vice-Chairman, Dr. F. C. S. Megaw (Engineer-in-Charge of Radar Research at the Admiralty Signal and Radar Establishment); ordinary members, F. C. Cheery (City & Guilds of London Institute), C. W. Oatley (Engineering Laboratory, Cambridge University) who for the past few months has filled the vacancy caused by Dr. Bowker's resignation, M. J. L. Pulling (B.B.C. Senior Supt. Engineer, Television) and P. H. Spagnoletti (Bolster-Brandes Ltd.).

Fellowship of the American Institute of Radio Engineers has been awarded to Prof. Willis Jackson, head of the Electrical Engineering Dept. of the Imperial College of Science and Technology "for his service as an educator and his many contributions to the literature in both the radio and electrical fields." It has also been awarded to Rudolph Kompfner "for his research in electron tube theory and particularly for his original contributions to the concepts of the travelling-wave amplifier." It was on this subject that he contributed to Wireless World in 1947.

Evening Classes.—Five courses of evening study for amateurs are to be held during the coming autumn and winter at the Literary Institute, Cranbrook Road, Ilford, Essex, by an arrangement between the R.S.G.B. and the Essex County Council education authority. The syllabus includes a six-months' course in preparation for the Radio Amateur's Examination (Wednesdays); refresher courses for newly licensed amateurs (Mondays and Tuesdays); a course covering television receiving technique (Mondays), and a class for morse and operating procedure. The fee for each of the courses is 5s for students living in the administrative area of the Essex County Council and 7s 6d for others. Applications must be made in the first instance to C. H. L. Edwards (G8TL), 10, Chepstow Crescent, Ilford, who is a member of the R.S.G.B. Council.

Development of a multiple aerial system for television and e.h.f. broadcasting for erection at the top of the Empire State Building in New York is being undertaken by R.C.A. The plan provides for the erection of five television aerials and three f.m. aerials on a 199ft column, bringing the overall height to 1,450ft above street level. Tests will be undertaken to ascertain the effects of simultaneous transmissions from all the aerials. The television aerials will transmit in the 50, 70, 80, 180 and 200 Mc/s bands.

Raw Materials.—We hope readers will forgive us for referring to our basic raw material—paper—but the annual report of the Waste Paper Recovery Association stresses that the recovery of waste paper—a prime contributor to the supply of paper-making raw materials—is a "permanent national need." During the war the paper salvaged rose to 61 per cent of the total paper consumed, whereas last year it dropped to 29 per cent.

Interference Suppression.—The British Automobile Association has asked its 900,000 members to "help in eliminating interference with television by fitting suppressors as soon as possible." The Association adds that the effect on the engine is almost negligible.

Plastics Exhibition.—The date and further details of the British Plastics Exhibition and Convention to be held at Olympia, London, next year, are announced by our associate journal *British Plastics*, which is organizing the show. The date is 6th to 9th June. The exhibitors will be British and Commonwealth firms who produce, mould or make plastics materials or supply raw materials or equipment to the plastics industry. The Convention will include lectures for technicians and the chemical and consumer industries, as well as lectures on such subjects as the use of plastics in the home.

BUSINESS NOTES

Decca Marine Radar, Type 159A, has been granted the Ministry of Transport's Certificate of Type Approval. Among the 200 ships fitted with this equipment since its introduction last September is the South-Eastern Gas Board's new collier *Mitcham*, on which the scanner had to be fitted to a special mast permitting it to be lowered when the vessel passed under the Thames bridges.

Ediswan exhibited for the first time their new Mark II 8-channel electrocardiograph at the technical exhibition held in connection with the Sixth International Congress of Radiology held in London in July. A feature of the model is the new design of moving-coil pen recorder.

Tannoy.—The assets, undertaking and goodwill of Tannoy Products have been acquired by Sound Rentals, Ltd., who have previously installed and rented Tannoy equipment. Guy R. Fountain, the founder of Tannoy, is chairman and governing director of the organization which will operate under the title Tannoy Products (Sound Rentals, Ltd.). The address is Canterbury Grove, West Norwood, London, S.E.27 (Tel.: Gipsy Hill 1131).

Midlands television service depot has been opened by A. C. Cossor, Ltd., in Baker Street, Handsworth, Birmingham, 21. The manager is R. G. Colby. It is planned to inaugurate a training school for television servicemen in the near future. The depot will not handle repairs to broadcast receivers, which will continue to be dealt with at the company's main service depot at 31, Corsica Street, London, N.5.

Philco-Thorn Agreement.—Under an arrangement recently made between Thorn Electrical Industries and the Philco Corporation of Philadelphia, radio and television sets will be manufactured in this country by Thorn to designs provided by Philco (Overseas), Ltd., who will distribute them.

Aerialite, Ltd., have brought into service vehicles equipped for undertaking field-strength tests, specially in television "fringe" areas, and for demonstrating television aerials.

G.E.C.—Three changes in the staff of the Radio Department, of which M. M. Macqueen is manager, are announced by the G.E.C. W. A. C. Maskell, who has been assistant manager for four years, is now deputy manager. R. G. E. Mayo is now assistant manager (broadcasting) and A. E. Potton, assistant manager (batteries).

Marconi's W.T. Co. announce that R. P. Raikes has been appointed Publicity Manager in succession to the late W. G. Richards.

Ediswan announce the appointment of R. K. Cox as manager of its Sheffield district office.

Belling & Lee have acquired a factory on the Netherton Trading Estate, Liverpool, for the manufacture of television aerials.

Aerial Installation Company, of which V. E. Hands, late of the B.B.C. Engineering Division, is director, has been formed to provide an aerial erection service in East Anglia. The address is Harvey's Yard, Rawstorn Road, Colchester, Essex (Tel.: Colchester 3288).

THE "BELLING-LEE" PAGE

Providing technical information, service and advice in relation to our products and the suppression of electrical interference

THE BANDWIDTH OF TELEVISION AERIALS

Dealers and Service Engineers often ask us for data concerning the bandwidths of our range of television aerials.

This question falls into the "How long is a piece of string?" category.

It is very natural for this question to be asked, however, because satisfactory television picture resolution is intimately bound up with it.

During the last war bandwidth was an all important parameter in radar technique, particularly for accurate target ranging, where the shape of the leading edge of the received pulse had to be maintained within close limits.

Furthermore, aerials, feeders and input circuits were lavishly designed with little regard for expense. In these circumstances controlled and repeatable bandwidths were achieved.

When one asks the question "What is the bandwidth of your L.700 aerial?" they should say "I have your model L.700 aerial. It is connected by 57ft. 4½in. of L.600 feeder to such and such a make of receiver; what is its bandwidth?"

In other words the bandwidth of an aerial depends upon the following parameters:—

1. The intrinsic bandwidth of the aerial, with its active dipole short circuited at the centre. (To some extent dependent upon height above ground.)
2. The length and characteristics of the feeder to which it is connected.
3. The magnitude and phase of the input impedance of the receiver.

We can take a complete installation and measure the impedance across the input circuit of the receiver by at least three methods. There is the slotted line method devised originally (we believe) by Bruckmann; there is the Impedometer, which is a short section of low loss line using two directional couplers and an electrostatic probe, and thirdly an admittance bridge of special design.

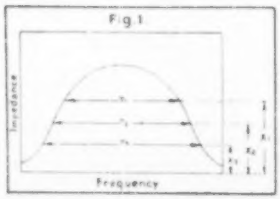

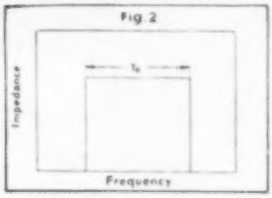

Having measured the impedance variation with frequency we proceed to plot it on graph paper and obtain a somewhat flat sort of resonance curve something like that shown in Figure (1).

We must now decide what the bandwidth should be.

Since the curve is a smooth one it could be Y_1, Y_2, Y_3, or any other Y. Of course if it were possible to obtain an impedance response as in Figure (2) (and it is not), then the bandwidth would be simply Y_0.

Bandwidth must be tied up with amplitude therefore, and it is customary to define bandwidths as that which obtains when the response of the resonant curve falls to $\frac{1}{\sqrt{2}}$ (3 db.) of its maximum value.

So far so good, but an inspection of the impedance curve for the value of Y for a 3 db. drop in amplitude is just not the frequency response of the aerial, and this is where so many make a fundamental error.

It would be true if the voltage developed in the aerial was independent of frequency, but this is not true of the dipole.

The voltage developed in it, for a constant field strength, falls off as the frequency is varied about the resonant value, so that the true response is sharper (i.e., the bandwidth is less) than the impedance curve would indicate.

The problem of determining, to any degree of reliable accuracy, the overall response bristles with technical difficulties.

It is true to say that each installation would have to be separately assessed.

Having given the bandwidth for 3 db. loss for a particular installation what does this mean in terms of picture resolution?

If the receiver is really capable of resolving in *perfect black and white*, the 3 Mc/s bars on the test card, one might be somewhat fussy about maintaining the input bandwidth, including aerial and feeder, at say 3 Mc/s for a 1 db. drop.

But supposing the signal is weak, and there is a lot of interference present; in the circumstances the eye will tell the brain that the picture is poor.

Reducing bandwidths throughout the receiver *and aerial* will lose the 3 Mc/s bars, but the improvement in signal-to-noise ratio will delight the eye as many can well testify.

Let us therefore not worry too much about bandwidth at the present moment.

When legislation puts a stop to interference; when high definition receivers are a reality; when manufacturers standardise input circuit and impedances—then we can say we have a technical foundation upon which accurate bandwidths of aerial systems can be established.

In the meantime we can say with confidence that any television receiver capable of resolving 3 Mc/s will do so when connected to any "Belling-Lee" television aerial correctly installed.

It is not every maker who claims that his receiver is capable of resolving 3 Mc/s even under ideal conditions.

The above illustration is of the "Belling-Lee" "Multitod" long distance television aerial.

The list price of the elements, crossarm and support is **£9 . 3 . 6**, but this is sold only complete with 14-foot metal mast and cap.

List number:

L698 (London)

L699 (Midland) **£13 . 18 . 0.**

Chimney lashings extra.

L680/R. Double lashings and brackets **£2 . 11 . 6.**

BELLING & LEE LTD

CAMBRIDGE ARTERIAL RD., ENFIELD, MIDDX., ENGLAND

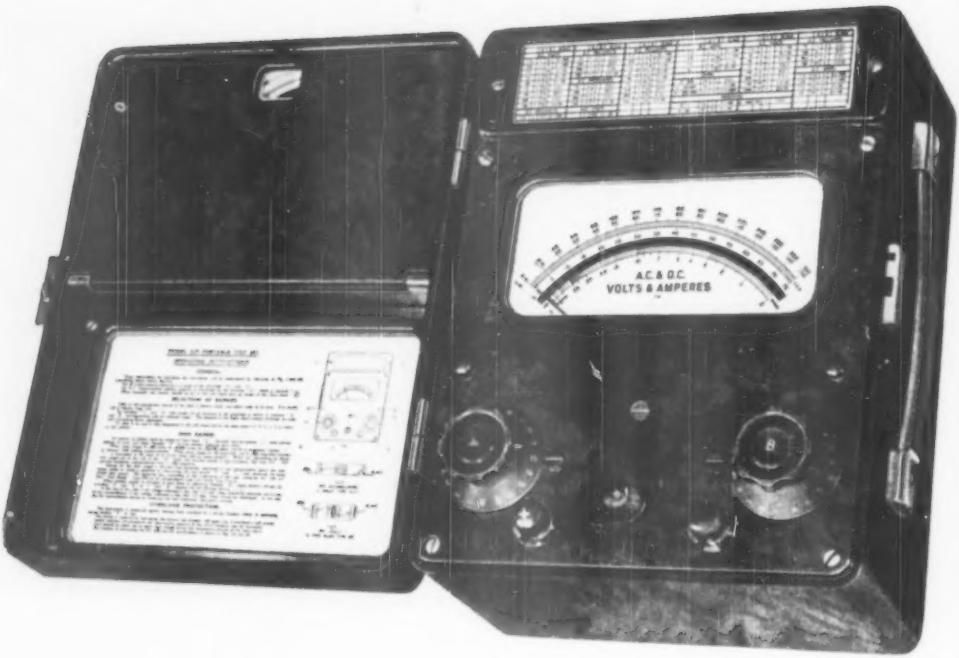

The WESTON S.75 Multi-Range Test Set

53 Ranges with Rotary Switch Selection

This uniquely comprehensive Test Set has 53 ranges for measuring AC and DC current and voltage, resistance and insulation. It is completely self-contained, with internal batteries to provide power for the ohms ranges and self-contained power pack for insulation measurement at 500 v. Selection is carried out by two 20-position switches. A fully protective safety device is fitted and is operative for forward or reverse overload. The 150 division 6" scale is uniformly divided and is fitted with an anti-parallax mirror. The set is enclosed in a handsome bakelite case and fully complies with B.S.S. No. 89 covering first grade instruments. Full details of this, and other Weston electrical measuring instruments will gladly be supplied on request.

SANGAMO WESTON LIMITED

ENFIELD, MIDDLESEX

TELEPHONE: ENFIELD 3434 (10 LINES) AND 1242 (4 LINES)
TELEGRAMS: SANWEST, ENFIELD

AREA DEPOTS:

201 St. Vincent Street, Glasgow.	Central 6208
Milburn House, Newcastle-on-Tyne.	Newcastle 26867
22 Booth Street, Manchester.	Central 7904
33 Princess Street, Wolverhampton.	Wolverhampton 21912

ELECTRONIC CIRCUITRY

SELECTIONS FROM A DESIGNER'S NOTEBOOK

By J. McG. SOWERBY

(Cinema-Television, Ltd.)

Reducing Drift in D.C. Amplifiers—1

THE interpretation of the letters "D.C." in the heading does not yet seem to be universally agreed. By some it is taken to mean "direct current," and by others "direct coupled," while others use both interpretations indiscriminately. However, all such amplifiers are intended to accept signal inputs down to zero frequency, and thus differ from the ordinary audio amplifier in which the amplification begins to fall off below some low frequency—generally in the region of 50 c/s.

The need to amplify signals well below 50 c/s arises in all sorts of applications as, for example, when it is required to record the variation of daylight falling on a photocell, or when studying the vibrations of a large mechanical structure such as a bridge or road. In such applications the signals may be so low in frequency as to be stated in cycles per hour or cycles per minute, rather than cycles per second. At the same time the same amplifier may also be called upon to amplify signals up to or exceeding 10 kc/s in some applications. In such cases it is only safe to assume the worst and build an amplifier capable of accepting zero frequency if necessary.

It is an unfortunate fact that all straightforward d.c. amplifiers suffer from "drift," or a more or less slow change in output even when no input is applied. The magnitude of this drift varies with different circuits, and a few of the well established anti-drift arrangements will be discussed here. As the subject is a large one and space is limited, it will only be possible to touch on a few major points, and there can be no pretence of completeness.

The way in which drift arises can be seen by considering the triode amplifier stage of Fig. 1. The valve is supplied with grid bias by a suitable battery and with h.t. by another (both assumed of perfectly constant voltage). An anode load R_a is provided and the voltage drop across it, due to the anode current I_a, is $I_a R_a$. The resistors R_1, R_2 are chosen so that the p.d. across R_1 is the same as that across R_a when no input is applied. It follows that initially there is zero p.d. across the output terminals 1, 2. When an input signal is applied, an amplified version of the instantaneous input p.d. appears across 1, 2, to which a c.r.t., a further amplifier stage, a microammeter, etc., may be connected. Provided the resistors remain perfectly constant in value there is perhaps no very obvious reason why the p.d across 1, 2 should not remain zero in the absence of any input. Unfortunately it does not, and more or less slow fluctuations of p.d. are found at the output, and these are termed drift. This difficulty does not arise if the stage is used as an audio amplifier because the output is then taken from the terminals 3, 4 coupled through the time constant CR. This time constant rarely exceeds one second, so that any slow changes at the anode are not transmitted to terminals 3, 4. It is the requirement to extend the frequency response to zero frequency, and the consequent need to dispense with C, that leads to drift being observed in d.c. amplifiers.

The drift may arise from a number of causes such as changes in the resistors with temperature and/or time, and changes in potential of the sources of supply. With sufficient care, drift from these causes can be almost eliminated, as constantan or manganin resistors can be used, and modern voltage stabilizers can be very stable indeed. Probably the most prolific source of drift is changes of temperature and/or emission of the cathode. The filament or heater could, of course, be supplied from a stabilized source, but high-current low-voltage stabilizers tend to be rather uneconomical unless a number of similar d.c. amplifiers are to be used simultaneously—as in multi-channel vibration recording, for example. For this reason a good deal of work has been done at various times and places, aimed at reducing the drift experienced with fluctuating cathode temperature or emission by the use of special circuits. In the best apparatus, or when the gain of the d.c. amplifier is very great, these circuits are often used together with a stabilized heater supply.

It was pointed out[1] some years ago that the cathode fluctuations of a practical valve can be represented by assuming it perfect—as far as its cathode is concerned—and inserting a fictitious generator (v in Fig. 1) in series with its cathode lead. Over a reasonable range about the rated heater supply voltage, the value of v is nearly proportional to the applied heater voltage. In Fig. 1 the heater is operated directly from the a.c. mains via a transformer, so that mains fluctuations will produce proportional fluctuations in the heater supply potential. The

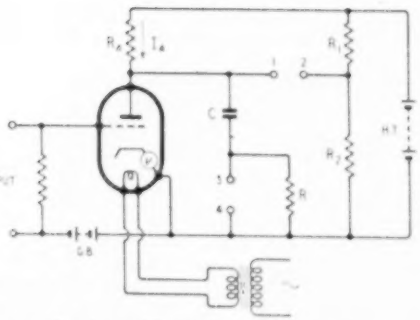

Fig. 1. Simple amplifier arranged for d.c. output.

[1] Miller, S. E. *Electronics*, Nov. 1941, p. 27.

magnitude of the effect is considerable, and in Fig. 1 it might well be found that $v = 0.1$ volt for a 10-percent change in mains supply potential—this being a typical figure which varies somewhat from valve to valve. In Fig. 1, v appears directly between grid and cathode, and so a mains supply change of 10 percent is equivalent to a change of input of 0.1 volt. As this is subject to the full amplification of the valve (say 30) the drift at the output reaches the not inconsiderable figure of 3 volts. If a second stage with the same amplification were added the drift at the output would be 90 volts, in an amplifier with an overall amplification of only 900. Such drift is rarely tolerable, but by the use of special circuits the effect can be markedly reduced.

Bridge Circuits

Probably the simplest—and historically the first[2]—method of attacking this difficulty is by the use of a second valve to form the bridge circuit of Fig. 2. In this arrangement V_1 corresponds to the valve of Fig. 1, and V_2 is a similar dummy valve. If the anode currents in the two valves are equal, and if the anode loads are equal, there will be zero p.d. across 1,2 in the absence of any input. If now the heater potential changes slightly, a small voltage v will be introduced into the cathode lead of V_1, and a small voltage v' into that of V_2; in consequence

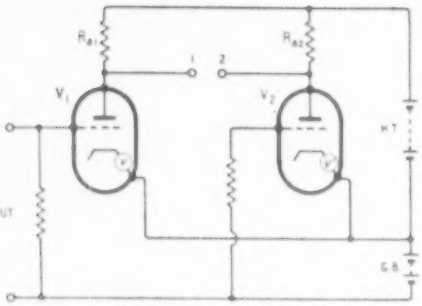

Fig. 2. Using a dummy valve (V_2) to form a bridge.

Fig. 3. Cathode-coupled double valve as a bridge.

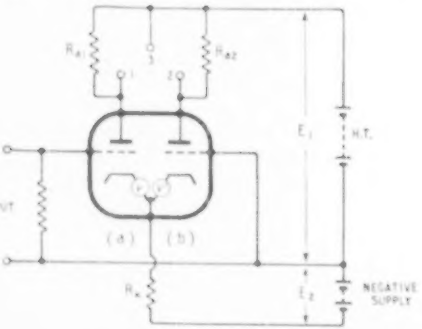

the anode currents of the two valves will change. If $v = v'$ the changes in the anode currents will be the same in the two valves and the p.d. across 1,2 will remain unchanged. If, however, v and v' are unequal, the potential arising across 1,2 will be that corresponding to an input signal of $(v - v')$. As v and v' are unlikely to differ by more than 20 percent, the circuit reduces the effect of cathode fluctuations by a factor of at least five.

By adjusting the operating conditions of the two valves this result could be improved, but another difficulty arises owing to the use of two separate valves having separate heater-cathode assemblies. With two such assemblies, there is no guarantee that the thermal time constants will be equal, so that a sudden small change in heater potential can lead to a transient drift lasting seconds or minutes. This may ultimately dwindle to zero as v and v' become equal after a period, but the transient drift that takes place during this equalizing process is nearly as troublesome as a steady change. The difficulty can be partially eliminated by the use of a double triode where two separate triodes are placed in the same envelope. Much better still is the use of a double valve arranged round a genuinely common cathode. There are few such valves available, but good results have been obtained with the American types 6SC7 and 12SC7. Not only does the common cathode ensure equal thermal time constants in the two valves, but also increases the likelihood of equality between v and v'. With such valves the effect of heater fluctuations can usually be reduced by a factor of 20 (or more, although this may necessitate selection of valves).

Single-ended Output

A similar anti-drift circuit is the cathode-coupled phase splitter shown in Fig. 3. In this circuit a stabilized negative supply, E_2, is provided to which the common cathode is connected through a large resistance R_k. When an input is applied, a nearly balanced push-pull output is obtained at the terminals 1,2. Like the previous circuit, that of Fig. 3 is a form of bridge, and if $v = v'$, the p.d. between 1,2 is not affected by heater fluctuations. If v and v' are unequal, the p.d. produced at 1,2 is that which would be obtained if $(v - v')$ volts were applied at the input. In a common-cathode valve, v and v' are not likely to differ by more than 5 percent in practice, and the amplification between input and output is:

$$A_{1,2} = \frac{\mu R_a}{r_a + R_a}$$

Where μ = amplification factor } of one
r_a = anode resistance } section.
$R_a = R_{a1} = R_{a2}$

So far the performance of the circuit in Fig. 3 is the same as that in Fig. 2.

It has been pointed out,[1] however, that the circuit in Fig. 3 also discriminates against heater fluctuations even when a single-ended output is taken between terminals 1,3 or 2,3, provided $v = v'$. The reason for this can be seen in the following way. The total cathode current of the valve is approximately E_2/R_k if E_2 is large compared with the grid base of the valve. If the heater supply voltage is changed it gives rise to an equivalent voltage v in the cathode lead, and this merely adds to E_2, so that the cathode

[2] Bowden, J. C., and Fogelson, P., *J. Sci. Inst.*, Vol. 16, p. 81 (1939) and earlier references in a-c/d.c. by J.C.B. given therein.

current increases to $(E_g + v)/R_g$. If $E_g = 100V$, and $v = 0.1V$ (likely values) the cathode current changes by only 0.1 percent. Analysis shows that the factor by which the effect of heater fluctuations is reduced, as compared with the circuit of Fig. 1, lies between $g_m R_k$ and $(1 + g_m R_k)$, where g_m is the mutual conductance of one triode. If—as is usually the case—v is not quite equal to v' then, as before, it is as if $(v - v')$ were applied to the input. The amplification when used single-ended is about half that for the push-pull case, so that the expression above now becomes:

$$A_{1,2} \simeq A_{2,1} \simeq \frac{\mu R_a}{2(r_a + R_a)}$$

This circuit is particularly useful, as it can be used as a single-ended or push-pull stage; and in addition to the signal input grid, a second grid is available for zero setting or the injection of negative feedback.

(To be concluded)

SHORT-WAVE CONDITIONS

June in Retrospect: Forecast for August

By T. W. BENNINGTON

(Engineering Division, B.B.C.)

DURING June the average maximum usable frequencies for these latitudes decreased considerably during the day-time, and increased slightly by night. This is in accordance with the normal seasonal trend, which should, now that the summer solstice has been passed, undergo a reversal.

Day-time working frequencies for long-distance communication continued relatively low, though not perhaps so low as might have been expected. The higher short-wave frequencies, whilst they were seldom or never usable in east-west directions, continued to be well received over north-south paths. For example amateurs on the 28-Mc/s band, whilst not receivable from North America, came in well from South America and Africa, and the 29-Mc/s broadcasting band continued to give good service in many distant localities to the south, south-east and south-west of this country. Medium high frequencies were usable over a large part of the day and the lowest frequency necessary for night-time working was of the order of 12 Mc/s.

Medium-distance communication by way of Sporadic E continued to be very prevalent, and the 28-Mc/s amateurs made almost daily use of this phenomenon for "short skip" contacts with practically every country in Europe. Sporadic E was also responsible for the London television on 41.5 Mc/s being heard in Czechoslovakia and other of the more distant countries of Europe and for Swedish and Russian v.h.f. stations being frequently receivable in this country.

Sunspot activity was, on the average, much lower than during the previous month. The sunspot number for June was about 70, as compared with 122 for the same month of last year.

June was an exceptionally "quiet" month, the only severe ionospheric storm occurring on 24th-25th. Minor storms took place on 2nd, 6th, 9th-10th and 29-30th.

Forecast.—During August day-time m.u.fs should increase a little and those for night-time decrease somewhat, as compared with those for July.

Working frequencies for long-distance communication should, however, still be relatively low by day and high by night, and long-distance propagation on the higher short-wave frequencies is likely to be rare, except over north-south paths. Medium high frequencies should remain usable for a large proportion of the total time, and frequencies below 11 Mc/s should seldom be really necessary at night.

Medium-distance communication will be by way of the regular E and F₁ layers for a considerable part of the day, and relatively high frequencies, having regard to the distance, should be usable both by day and night. Sporadic E should continue to be prevalent—though somewhat less so than during the past two months—and medium-distance communication by way of it should frequently be possible on the higher frequencies. Ionospheric storms are not usually prevalent in August.

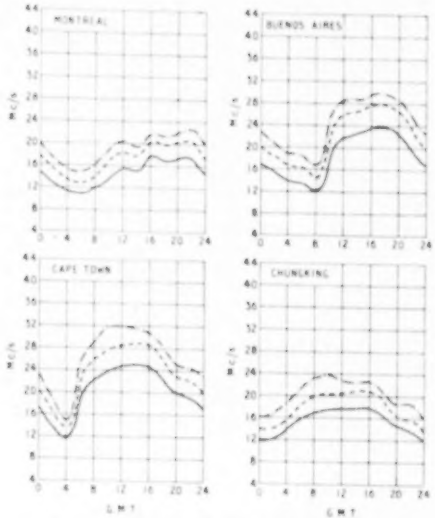

The curves indicate the highest frequencies likely to be usable over four long-distance circuits during the month.

MECHANO-ELECTRONIC TRANSDUCER

AUTHORITY has been given for the importation of a limited stock of R.C.A. Type 5734 triode transducer valves. This valve, in which the anode is formed by a shaft projecting through a flexible metal window in the end of the tube, is a device for translating small mechanical displacements into current or voltage variations. With an anode load of 75,000Ω the sensitivity is 40 volts per degree of deflection; the mechanical resonance of the free cantilever structure inside the valve is 12 kc/s.

It is intended that the valves should be used by research organizations and colleges, and many applications are being found for them in surgery, as well as in optics and vibration studies. Enquiries should be addressed to R.C.A. Photophone, 36, Woodstock Grove, London, W.12.

From Television Aerial to Receiver

Relation Between Field Strength and Receiver Sensitivity

By F. R. W. STRAFFORD, A.M.I.E.E. (Belling & Lee, Ltd.)

THE B.B.C. has published a contour map[1] of television field strengths covering the area served by the Alexandra Palace transmitter. In fact, field strengths have been recorded beyond the normal service, but good care has been taken to indicate that reception in such districts may be variable and/or uncertain.

The published field strengths for a given locality are average; that is to say, a continuous record of field strength in a particular location has been taken and a mean is drawn through the chart. Also, the field strength is corrected to that which will obtain at a height of 30 feet from the ground to the centre of a dipole. The meaning of field-strength figures in terms of receiver sensitivity depends on the type of aerial and the length and kind of feeder used for connecting to it and it is not always clear how the one can be interpreted in terms of the other. A simple formula connecting the two can be derived and in what follows it will be assumed that the field strength given in the final empirical formula is that obtaining at a height of 30 feet. Generally, outdoor television aerials are installed at a greater height, but as the variation of field strength with height is by no means linear in built up areas it is hopeless to introduce an appropriate correction factor.

The Simple Dipole

Experience has shown that, generally, the formula provides a somewhat lower figure than that obtained by measurement; this is all to the good, however.

The simple conventional dipole consists of a cylindrical conductor nearly one half-wave in length at the operating frequency. Its length is great compared with its diameter and it is split at the centre, the e.m.f. generated between the tips being transferred, by means of a low impedance feeder, to the receiver.

Although we visualize tuned circuits as combinations of coils and capacitors in the strictly physical sense in which we know them, the dipole is a sort of tuned circuit in which the inductance, capacitance and resistance is distributed as indicated in Fig. 1; this immediately suggests transmission line theory to the reader and, indeed, the dipole is a special form of transmission line possessing high characteristic impedance and radiation loss.

Providing the electromagnetic field is uniform and its electric vector lies parallel to the axis of the dipole, the magnitude of the e.m.f. generated between the inner tips of the aerial can easily be calculated to a close degree of approximation. That this is so is confirmed by various experiments details of which need not be given here.

[1] B.B.C. Engineering Division and Mr. R.H. Logan.

It will be noted from Fig. 2, that the current and voltage induced in the dipole are distributed in amplitude somewhat as shown by the dotted curves. One would expect this, because it would be surprising to find current at the outer tips. On the other hand one would expect these tips to be "hot" in the voltage sense.

If, by some miracle, the current distribution could be maintained constant throughout the length of the dipole then a field of E volts per metre would obviously generate an e.m.f. equal to the field strength multiplied by the length of the dipole. For the half-wave dipole the generated e.m.f. would be given by:

$$e = \frac{E\lambda}{2} \qquad (1)$$

wavelength λ (of course) being given in metres.

Now, if the diameter of a half-wave dipole is quite small compared with its length, the classical theory shows that the current and voltage distribution are almost exactly sinusoidal in amplitude over its length. Therefore, the e.m.f. generated must be the mean value of this sine curve which is given by:

$$e = \frac{1}{\pi}\int_0^{\pi} \sin\theta \, d\theta = \frac{2}{\pi} \qquad (2)$$

Hence, the e.m.f. generated in the dipole, in terms of the incident field strength, is obtained by multiplying equations (1) and (2) which gives:

$$e_D = \frac{E\lambda}{\pi} \qquad (3)$$

Now this is the open-circuit e.m.f. which would exist between the adjacent points at the centre of the dipole if it could be cut and the parts separated without altering the current. The dipole, however, must be terminated by a resistance equal to the resistance (at the centre) of the dipole and, as is well known from elementary theory, the voltage will then fall to half the value when matched for maximum power transfer.

The matched output from the dipole is that which will obtain when a resistive load of about 73 ohms is connected across the inner tips (Fig. 3).

This provides the basic formula:

$$e_M = \frac{E\lambda}{2\pi} \qquad (4)$$

Now, the aerial physicist must not be too unkind to the writer at this stage. This article is directed to the practical engineer who uses formulae without always possessing the ability to derive them from first principles. The writer has thought over several ways of "putting it over," and the foregoing treatment, while lacking rigour and the inclusion of all the variables—and there are many—gives a close first approximation, and a derivation which should make fairly simple reading.

A more rigorous analysis leading to Equ. (3) is

TABLE 1

Type of Aerial	K_A
V	0.5
Dipole	1.0
H	1.8
3-element Yagi	2.5
4-element Yagi	3.0

TABLE 2

db Loss	K_F	db Loss	K_F	db Loss	K_F
0.5	0.95	3.0	0.71	6.0	0.50
1.0	0.90	3.5	0.67	7.0	0.45
1.5	0.85	4.0	0.63	8.0	0.40
2.0	0.80	4.5	0.60	9.0	0.35
2.5	0.75	5.0	0.56	10.0	0.32

given in the Appendix. This, as before, assumes sinusoidal current distribution through the aerial, and a uniform field.

Equation (4) provides the first approximation to the correctly terminated output from a half-wave dipole. Two factors K_A and K_F must be included to allow for the type of aerial employed and the losses introduced by the length of feeder inserted between the dipole and the receiver. It must be assumed that the characteristic impedance of the feeder is chosen to match the radiation resistance of the dipole and the input resistance of the receiver. A figure of 75 to 80 ohms is usually taken. When an "H" type aerial with $\lambda/4$ spacing is employed, the radiation resistance is lower, and is of the order of 50 ohms. If the spacing is reduced to $\lambda/10$ the radiation resistance may be as low as 10 ohms. Providing the matching precautions are taken the formula is still valid—indeed moderate mismatching does not have a great effect.

The value of K_A is given in Table 1 for certain popular outdoor television aerials of half-wave dimensions.

The feeder attenuation factor K_F is obtained by taking the manufacturers' attenuation loss in db per 100 ft at the television frequency and adjusting it, *pro rata*, for the length employed. K_F is given in Table 2 in terms of the db loss for the type and length of feeder employed.

The final formula for estimating the e.m.f. at the input of a receiver matched throughout to the aerial via a feeder is:

$$e_R = \frac{E\lambda K_A K_F}{2\pi} \qquad (5)$$

Example: Given a field strength of 200 μV/m, and "H" aerial, and 75 ft of feeder whose loss is 4 db per 100 ft, we work as follows:

K_A (Table 1) = 1.8

K_F (Table 2) = 0.71

λ = 6.67 metres (London vision).

$$\text{then } e_R = \frac{200 \times 6.67 \times 1.8 \times 0.71}{2\pi}$$

= 270 microvolts (slide rule).

A field strength of 100 μV/m would provide an input e.m.f. of 135 microvolts and so on.

The reader may be assured that if he uses this formula and, in addition, knows the sensitivity of his receiver for peak white picture, he will be able to decide the type of aerial and permissible feeder loss having regard to the local field strength.

Naturally, the results will be more accurate when the site is free from surrounding buildings, trees, etc. The B.B.C. field strength contours cannot include every contingency, and there will be badly sited cases where the formula fails because the field strength differs very considerably from that given on the map.

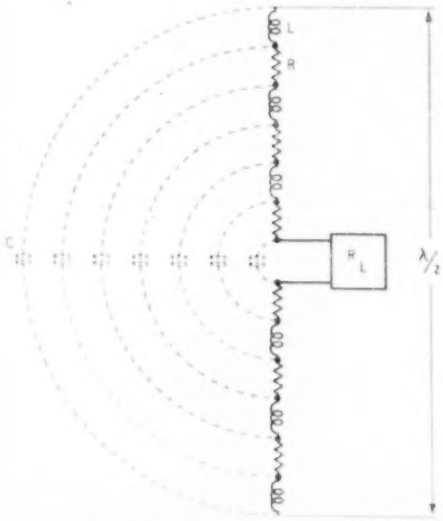

Fig. 1. The dipole is an incompact tuned circuit in which L, C and R are distributed.

Fig. 2. Voltage and current distribution along a simple half-wave dipole.

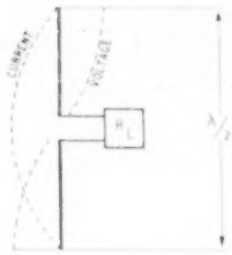

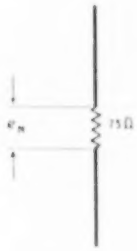

Fig. 3. "Matched" dipole.

APPENDIX**

The total effective e.m.f. induced in an earthed vertical wire of height h on the assumption of a uniform vertically-polarized electromagnetic field is given by:

$$E_e = \frac{E}{\sinh Ph}\int_0^h \sinh P(h-x)\,dx$$

$$= \frac{E}{P}\tanh\frac{Ph}{2} \qquad (10)$$

In the above formula E is the field strength and P is the

** "An Experimental and Analytical Investigation of Earthed Receiving Aerials," by F. M. Colebrook, *J. Instn elect. Engrs*, July 1932, Vol. 71, No. 427.

propagation constant of the wire in terms of ordinary transmission-line theory.

Now P is of the form $\alpha + j\beta$ and may be written as

$$P = \alpha + j\frac{2\pi}{\lambda}$$

In the special case where $h = \frac{\lambda}{4}$ (quarter-wave element only) we obtain from Equ. (1.0)

$$e_s = \frac{E}{\alpha + j\frac{2\pi}{\lambda}} \tanh \frac{\lambda}{8}\left(\alpha + j\frac{2\pi}{\lambda}\right) \quad \ldots \quad (1.1)$$

In these circumstances α is negligibly small compared with $\frac{2\pi}{\lambda}$ so that by simplification we arrive at

$$e_s \approx \frac{E\lambda}{j2\pi} \tanh j\frac{\pi}{4}$$

$$= \frac{E\lambda}{2\pi} \quad \ldots \quad (1.2)$$

This is the effective e.m.f. generated in a quarter-wavelength wire with respect to earth. A half-wave dipole is obviously two of these elements in series, since the mid-point is at earth potential.

Hence, the open circuit effective e.m.f. at the centre of a half-wave dipole is double that given by equation (1.2), which is $E\lambda/\pi$ and agrees with Equation (3) in the text.

Black Screen Television

New Pye Receivers

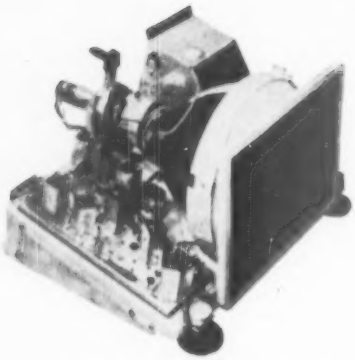

Chassis of Pye LV30 receiver showing the "dark screen" attached to the mask of the C.R. tube.

IN order to improve the contrast of television pictures under conditions of high ambient lighting, the new Pye receivers are provided with a grey-coloured screen in front of the cathode-ray tube. This screen is of tinted plastic material and has a 50 per cent light transmission. Because of the loss of light in it the picture produced by the tube must be twice as bright as usual for the same final brightness.

The improved contrast comes about because room lighting must pass through the screen twice. It must pass through it to reach the c.r. tube and be reflected from its face, and it then passes through it, again with the picture. Therefore, only 25 per cent of the externally incident light appears and there is a 2:1 improvement in the ratio of the picture brightness to external light.

Normally, the "blackest" black is the white face of the c.r. tube and a true black is obtainable only when viewing in darkness. With ambient lighting the "black" is the tube face and it only appears black in contrast to the brightness of the whiter parts of the picture. When the dark screen is used the tube face is effectually darkened and the blacks in the picture are improved.

The receivers incorporating this screen have a 9-in tube operating at about 6.8 kV. For the line time base a single-valve generator is used* and it is completely screened to reduce radiation. The frame time base is more conventional, but its two valves are combined as a triode-pentode. A permanent magnet is used for focusing and has a simple adjustment. For picture-centring two other magnets fitted between the focus magnet and the deflector coils, are employed. This is an unusual arrangement which permits very simple adjustment.

The receiver proper is a straight set and separate r.f. chassis are available for the London and Birmingham areas. Four-circuit filter-type couplings are used and are claimed to give unusually high selectivity. There are only two panel controls, Brightness and Sound Volume. As a table model (LV30) the set costs 39 gns, and as a console (LV30C) 45 gns, including purchase tax; in both cases the cabinets are of wood.

* See page 287.

NEW BOOK

A Home Built F.M. Receiver. By K. R. Sturley, Ph.D., M.I.E.E. Pp. 85+ix; figs. 57. *Electronic Engineering*, 28, Essex Street, Strand, London, W.C.2. Price 4s 6d.

EXPERIMENTERS and music lovers with a flair for building electrical reproducing equipment will find this book a valuable guide if they should contemplate assembling an f.m. receiver for the forthcoming 90-Mc/s transmissions from Wrotham. It is essentially practical, but as frequency modulation is new to broadcasting in this country, some space is devoted in the early chapters to explaining how f.m. differs from a.m. and the new problems it creates in the design of a receiver.

The set described is built in unit form, an ideal arrangement since individual units can so easily be modified, or changed, to a new design should the need arise. A separate chapter is devoted to each unit.

Basically, the set consists of an r.f. stage, frequency changer with separate oscillator, automatic frequency control, four i.f. stages (including two limiters), Foster-Seeley discriminator and a high-quality audio amplifier. It is a.c. operated.

As an aid to aligning the i.f. amplifier and discriminator a small oscillator covering 8 to 9Mc/s is described. The procedure is quite adequately explained.

The book is well illustrated with photographs, circuits and practical wiring diagrams.

H. B. D.

HIGH QUALITY REPRODUCTION

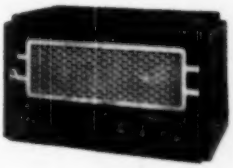

'FIFTY and THIRTY WATT" CINEMA AMPLIFIERS as illustrated for single or double P.E.C. input with separate adjustable bias. Full range of tone controls to suit all needs with built-in Exciter Supply if required.
PRICES range from **34½ gns.** to **42½ gns.**

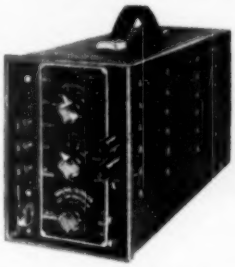

TYPE C.P. 20A AMPLIFIER
For AC Mains and 12 volt working giving 15 watts output, has switch change-over from AC to DC and "Stand-by" positions. Consumes only 5½ amperes from 12 volt battery. Fitted with mu-metal shielded microphone transformer for 15 ohm microphone, provision for crystal or moving iron pick-up with tone control for bass and top. Outputs for 7.5 and 15 ohms. Complete in steel case with valves.
PRICE **£28 . 0 . 0.**

FOUR-WAY ELECTRONIC MIXER
This unit has 4 built-in balanced and screened microphone transformers, normally of 50-30 ohms impedance. It has 5 valves and selenium rectifier supplied by its own built-in screened power pack consumption 20 watts. Suitable for recording and dubbing, or large P.A. Installations since it will drive up to six of our 50 watts amplifiers whose base dimensions it matches. The standard model has an output impedance of 20,000 ohms or less, and any impedance can be supplied to order. PRICE **£24 0 0.**

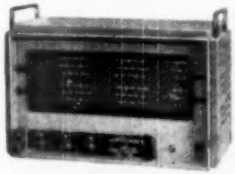

OTHER MODELS IN OUR RANGE OF AMPLIFIERS
"SUPER-FIFTY WATT" - - - - - PRICE **36½ gns.**
"THIRTY WATT" - - - - - - - - " **30½ gns.**
"10-15 WATT RECORD REPRODUCER" " **25½ gns.**

These are fitted in well ventilated steel cases with recessed controls, as illustrated.

Full details upon request.
EXPORT ENQUIRIES INVITED.

VORTEXION LIMITED, 257-261 THE BROADWAY, WIMBLEDON, LONDON, S.W.19
Telephones: LIB 2814 and 6242-3 Telegrams: "Vortexion, Wimble, London."

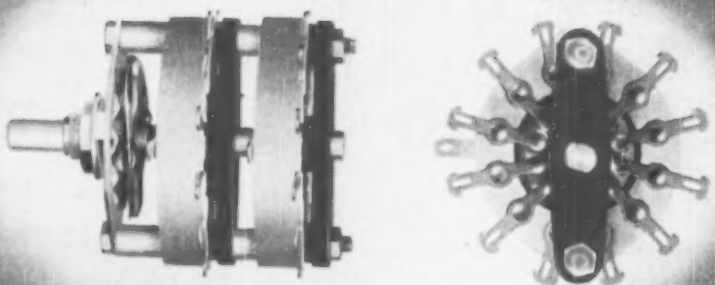

CERAMIC SWITCHES

For applications where only the best is good enough. Stators and rotors of Frequentite "R" ceramic. All contact members of silver alloy.

Wright and Weaire Limited

138, SLOANE ST. · LONDON · S.W.1. *TEL. SLOANE 2245* · FACTORY · SOUTH SHIELDS, CO. DURHAM.

THEY SANG THE PRAISES OF THE 10 INCH ★

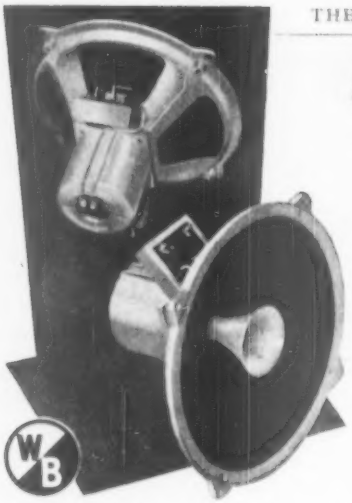

NOW we present a 12" Stentorian

Concentric Duplex

HIGH FIDELITY REPRODUCER

Similar in construction to our highly successful 10" Concentric Duplex, it combines the same high quality with large power handling capacity, achieved by a very high flux density magnet, and special cone material (made from newly-developed long fibre pulp) which enables a resonant point of below 50 c.p.s. to be obtained. The all-metal high frequency diaphragm and speech coil gives rigidity of construction and maximum driving efficiency. This rear assembly is totally protected by a bakelite and perspex housing.

Full details of both 10" and 12" models on request.

SPECIFICATION OF 12" Series Gap magnet of Alcomax 3.
Flux in LF gap 14,000 gauss on 1½" pole
" " HF " 17,000 gauss " " "
Power handling capacity, 15 watts. Frequency range 30-17,000 c.p.s. Fundamental bass resonance, 45 c.p.s.

PRICE Complete with cross-over network and transformer, **£15 - 15 - 0**
" Without transformer, **£14 - 14 - 0**

★ The "WIRELESS WORLD" said: "The makers' claim of a frequency range of 50 to 14,000 c.s can be substantiated . . . gives a clean and full-bodied bass response of surprisingly good quality for a 10 in. diaphragm."

WHITELEY ELECTRICAL RADIO CO. LIMITED · MANSFIELD · NOTTS

M.K.S. System of Units

Discussion at the I.E.E.

ALTHOUGH the m.k.s. system of units was adopted internationally no less than 15 years ago, many of the people who are (or ought to be) concerned seem to have only a very hazy idea of what it is all about. Very briefly, it is a system designed to put an end to the confusing mixture of three systems of electrical and magnetic units: the c.g.s. electrostatic and electromagnetic systems, and the practical system that includes the familiar volts, watts, farads, etc. By substituting the metre for the centimetre and the kilogramme for the gramme in the c.g.s. systems, and making an appropriate choice of a fourth quantity, a single absolute system of units is established which has the great advantage of including all the existing practical units and of rendering the two c.g.s. systems redundant.

Notwithstanding international adoption of the m.k.s. system, there is still room for local discussion of such matters as how it should be brought into use, or indeed whether it should be brought into use at all. And apart from that, one important question was left open—the question of whether the m.k.s. system should be employed in its rationalized or its unrationalized forms.

Rationalization

The object of rationalization is to make the appearances of 4π in fundamental formulæ correspond more closely to their geometry. It is a question that has to be settled before one can seriously go ahead with the m.k.s. system at all, because it affects the size of the units of magnetic field strength and magnetomotive force and a few others, as well as the so-called permeability and permittivity of free space. So it was not before time that the whole subject was laid open for discussion by the Institution of Electrical Engineers, on the basis of four short papers read on 30th March.

The first paper was devoted to the system itself, with the pros and cons of rationalization confined to a more or less objective appendix. The other three papers frankly advocated rationalization.

In spite of this lead it was rather surprising—considering the reluctance of even such people as engineers to alter the habits of a lifetime—that not one of the many who took part in the discussion offered any real resistance to the new system, or even to the more debatable rationalization. Some accepted it without enthusiasm, but they accepted it. Since the m.k.s. system has hardly made any headway yet in British text-books, another surprise was to hear so many professors and lecturers claiming to have taught it for a considerable time. American text-books, on the other hand, have gone over almost entirely to m.k.s., with a majority in favour of rationalization. The contrast here may be due not so much to British conservatism as to difficulties and delays in the British publishing trade.

Almost the only objections that can be raised against the m.k.s. system are that certain c.g.s. units, notably gauss and oersteds, are so well established that they will be difficult to displace; and that in some situations the m.k.s. units are of awkward sizes. Thus, designers of small radio equipment may find it inconvenient to think of flux densities per square *metre*; and in the fundamental Coulomb formula for the force between charged bodies, the force set up by unit charges (each 1 coulomb) unit distance apart (1 metre) amounts to about a million tons. It was generally conceded, however, that such criticisms are nothing to the inconveniences of the mixed systems, and though physicists will probably cling to the c.g.s. system, so that engineers (especially in electronics) will not be able to be entirely ignorant of it, the basing of electrical engineering courses from the outset on the m.k.s. system is both practicable and desirable. The last of the four papers dealt particularly with this aspect, and proposed a teaching sequence.

With regard to rationalization, its more logical relationship to the geometry of electromagnetic relationships was brought out in the papers and discussion. Tables of fundamental formulæ were shown in rationalized and unrationalized forms. The two crucial ones appeared to be the inverse-square law (referred to above), into which rationalization introduces a 4π, and the m.m.f. formula, from which it removes a 4π so that the official unit of m.m.f. becomes what engineers have long unofficially used—the ampere-turn. Whereas the former is of theoretical interest, the latter is in everyday practical use in both light and heavy electrical engineering; so that apart from considerations of logic there is little doubt as to which system renders 4π the less inconvenient. Dr. Booker's 1946 I.E.E. paper emphasizing the value and appropriateness of the rationalized m.k.s system in electromagnetic wave theory was referred to by several authors and speakers.

The Fourth Quantity

There was some difference of opinion as to whether μ_0 or the coulomb was the fourth quantity defining the m.k.s. system, though μ_0 has official recognition. It was pointed out that the name "permeability of free space" for μ_0 is misleading and ought to be displaced by some such name as "magnetic space constant"; and similarly for κ—the permittivity or "dielectric constant."

If this discussion was at all representative, it showed electrical engineers to be overwhelmingly in favour of the rationalized m.k.s. system. The moral would seem to be that all concerned (and especially those in the magnet industry) should familiarize themselves with it as rapidly as possible, so as to reduce to a minimum the duration of the changing-over period.

UNBIASED | By FREE GRID

The Radiokelemeter

NEXT spring we shall be celebrating two momentous events, namely this journal's fortieth birthday and the opening of the Festival of Britain. The Government has asked everybody to do something out of the ordinary in honour of the Festival and I think that *Wireless World* ought to comply with the wishes of Whitehall. I suggest that this journal should use its influence to rescue the racing world from the thorough mess into which it has been plunged by the introduction of the photo-finish camera.

Before the introduction of this highly controversial device nobody thought of disputing the judge's word, but such uncertainty exists nowadays that many a welsher has given the crowd a totally unnecessary run for its non-existent money. I am not, of course, trying to suggest that these cameras are inaccurate, for the opposite is the case. It is, however, common knowledge that in many cases the photo is difficult to interpret and has led to a lot of genuine ill-feeling culminating in the unprecedented act of the judge, at the Sandown Park meeting in June, of calling upon the stewards to help him to "read" the photograph.

Now I feel sure that by the adoption of radio principles this vital problem of "Wots won?" could be solved, and the camera relegated to the Science Museum; but it is not an easy problem to tackle. It would be simple enough if the Jockey Club would permit us to fit each horse with I.F.F. which would be automatically touched-off as the leading horse thrust its nose through an e.h.f. beam positioned horizontally across the track in line with the winning post.

But the Jockey Club is not likely to permit any horse-borne apparatus. We have until next April to get the problem solved, but at present I can only suggest the erection of a bridge across the track, level with the winning post. On this could be mounted a series of radar transmitters, one for each horse, radiating vertically downwards. Obviously the nose of each horse as it passed would cause a split-micro-second shortening of the "there-and-back" beam between its respective transmitter and the ground. Unfortunately, however, horses don't run with neat spacing between them and often finish with a klystron-like bunching. Horse-borne I.F.F., therefore, seems the only solution, and I have already sounded a well-known jockey as to the attitude of his club in the matter but he treated me with such unseemly levity that I was left wondering if there was not some vital point which I had overlooked.

Unseemly levity.

Your help is earnestly requested, as the radiokelemeter must be ready by April for the first Newmarket meeting of 1951.

Radiotelearchics

A READER writing from wildest Westmorland, says I have shown myself to be a complete back number in demanding that manufacturers supply us with a simple radiotelearchic unit for the fireside operation of our receivers.

From the documentary evidence which my correspondent—who has helped me on a former occasion—has sent me, it appears that an apology is due from me to at least one well-known radio manufacturer who marketed such a device before the war. Unfortunately the Editor is as adamant as the B.B.C. about advertizing. Perhaps it will be sufficient if I say that the set which featured this magic unit was one to which, so its makers used to allege, people were always going home to. No doubt the war was responsible for causing the unit to go into temporary oblivion, but surely it is about time for it to reappear.

Information Please

BEING a married man words have always had a snake-like fascination for me and it is hard to get away from them, in fact I don't think I want to do so, my sentiments being much the same as those of the sailor when an eminent medical dipsopractor offered to cure him permanently of his desire for a pint.

"Words, words, words."

But to return to words; some time ago I set out to find the origin of the termination "tron" which we and the nuclear physicists use such a lot in words like magnetron and cyclotron. I felt sure that it was not merely the hindquarters of "electron," lopped off and put to other uses, and I sought your aid. By the kindly help of one of you I found that I was quite right in my surmise.

The word I'm now tracking is "radio." Its origin is, of course, fairly obvious even to those of you who played noughts and crosses when you ought to have been reading about the radii or rods of light which used to emanate from the heads of the ancient classical deities. What I seek to know is when the word radio was first used as a synonym for wireless. It was firmly established at the time of the Berlin conference in 1903 but it was, of course, shamelessly stolen from the X-ray people who used it before Marconi filed his first patent. Can any of you tell me who stole it and when?

This brings me to the word "radiogram," which we older wireless men often self-righteously allege was deliberately filched by the makers of radio-gramophones, from the radio-telegraphic world where it had long been established as the recognized abbreviation for radio-telegram. Maybe this was so, but it does not alter the fact that we in our turn stole it from the X-ray people who coined it to describe the first crude X-ray pictures they made. Nowadays, I believe, they use the totally incorrect word radiograph, being led astray by the evil example set by the photographic world which, with the exception of the well-known publication "Photograms of the Year," employs the misbegotten noun (?) "photograph."

LETTERS TO THE EDITOR

The Editor does not necessarily endorse the opinions expressed by his correspondents.

Preferred Valves

AS a remedy for the confused valve situation in this country, I would like to commend to all radio trade organizations the excellent example set by the Scientific Instrument Manufacturers' Association in preparing a short list of preferred types for use in all new designs of instruments. This body, at least, has seen the advantage of restricting the variety of valves in circulation when it comes to capturing the world's markets, and the list contains no more than 230 types with only two main bases, international octal for normal-sized valves and B7G for miniatures.

If more lists of this type were in force, the commercial competition between manufacturers (which is responsible for the present position) would perhaps turn towards producing only the limited number of preferred types, but at keener and keener prices. Classification would become a dream and there would be no further need of those vast encyclopædias that announce with evident satisfaction that they contain sixty thousand valve characteristics and have more to follow. But perhaps this is all heresy and bad for business?

JAMES FRANKLIN.
London, S.W.4.

Pickups and Hum

AS a mere amateur I hesitate to cross swords with the professionals on the question of liability of ribbon and moving-coil pick-ups to hum pick-up, but the explanation is, I think, so simple that it may have been overlooked by the experts. More than anything else, hum pick-up depends on the alternating magnetic field in which the coil is situated. In the moving-coil, unlike either the moving-iron or the ribbon, the coil is virtually completely screened by the magnet and polepieces. Proof that this is, in fact, the reason for the coil's superiority in this respect is obtained by removing the polepieces from the magnet with the coil left in position; the hum then becomes comparable with—or even worse than—that of the ribbon.

N. M. REDDINGTON.
Barnstaple, Devon.

Tungsten Carbide

CONCERNING B. E. Berry's letter in the June *Wireless World* on the suitability of tungsten carbide for gramophone record reproduction, I should like to add to this controversy by stating my own experiences on the matter.

I agree with Mr. Berry's statement that pitting due to faulty sintering should be observed during the polishing operation on the needle, and rejected at that stage, but I have found that no matter how carefully this operation is carried out it is impossible to obtain a finish equal to that of corundum. It would appear logical that if hard metal-like substances were equal in finish to corundum, instrument and watchmaking concerns would have switched to bearings of this material long ago. It can be pressed to the required shape say, of a cup or "V" jewel, leaving only the final grinding and polishing operation to be done. With sapphire, on the other hand, we have to begin by slitting plates from irregular pear-shaped boules; between this first operation and the last much waste of material occurs, but it is still used for the simple reason that next to diamond there is nothing better.

E. R. WALLWORK.
Colton and Company
(Lapidaries), Ltd.,
London, S.W.18.

Low-Power Broadcasting

DESPITE the introduction of new frequencies, there are still a number of areas in the U.K. where reception of either the B.B.C. Home or Light Programme is unsatisfactory. Typical examples of such areas are East Anglia, and parts of the South Coast.

Concurrently with the expansion of the Television Service, surely the B.B.C. can undertake the straightforward task of providing an adequate sound coverage for the whole country. I say straightforward, as the development of low-power, synchronized, and remotely controlled transmitters removes any question of technical or manpower difficulties being put forward as reasons for inactivity.

Mention of these low-power transmitters leads me to question whether the present policy of endeavouring to cover relatively large areas by single, high-power, medium-wave sets is the most advantageous from the Home listener's point of view. Black spots, or should I say, "black areas" are bound to occur, and large sections of the community may be without a service in the event of local power failures or faults on the transmitter.

Portable Model B.65 (open)

Can you provide a public address system at a moment's notice? With a B65 it is simple—just place the equipment in a suitable position and switch on. Incorporated within an easily portable case are the amplifier complete with loudspeaker, rotary transformer, 6-volt unspillable accumulator and microphone with cable. Power output is approximately 5 watts. The equipment is a most useful outfit for political meetings, religious gatherings, auctioneers, etc., and numerous other applications where no electric supply mains are available.

Price complete **£29 10 0**

An external speaker can be attached if desired.

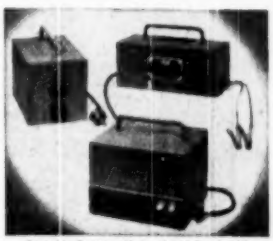

Portable Battery Mains Amplifier B.619

Operates on 12-volt battery or, by means of separate plug-in adaptor unit, on A.C. mains. Power output approximately 15 watts.

Full details of these models and others in the large Trix range of equipment available on request.

Send for latest catalogues and price list.

THE TRIX ELECTRICAL CO. LTD.
1-5 Maple Place, Tottenham Court Road, London, W.1. 'Phone: Museum 5817
Grams & Cables: "Trixodio, Wesdo, London."

AMPLIFIERS · MICROPHONES · LOUDSPEAKERS

In addition, there is also the point that transmitters on high-power probably cause just as much interference to Continental programmes, as similar Continental transmissions cause to us here in the British Isles.

Would it be asking too much to suggest that the Government and the B.B.C. examine the possibilities of future replacement and development programmes being based on the lower-powered transmitter; i.e., of not more than 20-kW output, not only in this country, but also in all the countries of Western Union? The implementation of such a plan would cost money, but it is better to have really good interference-free broadcasting services, covering the whole country, and pay extra for them, than allow the present unsatisfactory trend to continue unchecked.

P. A. WORSNOP.

Thorpe-le-Soken, Essex.

Bridge Modifications

WHEN constructing the Wide Range R-C Bridge described by H. E. Styles in your March number, I found that I did not possess a single-pole, 6-way, rotary switch but had several 2-pole, 6-way switches. In order to make the fullest use of the switch I made the small modification to the original circuit shown in the accompanying drawing and I think this may be of some interest to your readers.

The advantage of this modification is that it enables resistors and capacitors to be measured on the same scale without reversing any external switch.

In my own instrument I use a single scale calibrated in "factors" by which the value of the standard resistor or capacitor is multiplied or divided, according to which position switch W is in, to obtain the value of the unknown component. Positions of switch W are simply marked × and ÷ on the panel.

This modification necessitates two switch positions for matching an external "standard" but I find internal standards as shown in the circuit diagram quite adequate to cover all ordinary requirements.

The instrument, either modified or unmodified, works extremely well and, given good ears and a quiet room, is capable of giving very accurate results.

J. A. L. GORRINGE.

Chesham Bois, Bucks.

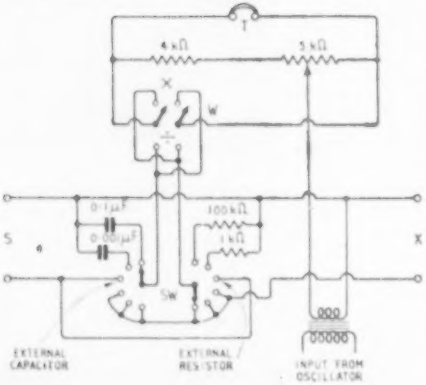

Curious Effect

I HAVE noticed a similar effect to the one mentioned by A. F. Davidson (*W.W.*, May, 1950). My television receiver is built around the *Wireless World* time base and I use a 12-in tetrode tube.

Recently, about fifteen minutes after switching off, I noticed a steady flash of light on the screen at the bottom left-hand corner. I checked e.h.t. and power supplies to confirm that no voltages were applied to the tube. To make doubly sure I disconnected the set from the mains, also aerial and earth, but the streak persisted.

Suddenly the streak moved and I found it was caused by my hand moving near the tube face. This gave me a clue to the cause. The "Perspex" screen which I use in front of the tube had attained a high electrostatic charge—in fact, sparks could be drawn from the screen. Rubbing the "Perspex" with a cloth caused the streak to jump violently and lengthen to more than two inches. Eventually quite a bright flash covering a large area of the screen occurred and the effect could be produced no longer.

Apparently the charged "Perspex" induced an opposite charge on the tube front face and the electron movement in one particular part of the screen was sufficiently violent or intense to excite the screen to luminosity. I have never noticed the effect during a programme—the beam current and screen brilliance would probably mask any flashes due to electrostatic charge.

It would be interesting to know if Mr. Davidson is using a similar type of protective screen. Probably the surface of glass is sufficiently hygroscopic to prevent the accumulation of a high charge under normal circumstances; thus the effect may rarely be produced by a glass screen.

D. W. E. WHEELE.

Grantham, Lincs.

Slow Starters

IN his article in the June *Wireless World*, Free Grid refers to a radio-operated remote control unit for armchair adjustment of radio sets.

While I should not like to discourage the manufacture of such an original accessory, I believe that the listener of to-day is oppressed by a greater evil than the lack of remote control.

I refer to the infuriating half minute that we have to endure while an a.c. set "warms up." Many is the time that I have missed the time signal or the announcement of the title of a piece of music due to this defect.

The mind of the listening public has to be half a minute in advance of true time.

Could not the efforts of manufacturers be diverted a little to research into methods of improving upon this half-minute?

PHILIP A. C. MORRIS.

Manchester, 13.

Superhet Radiation

IT seems that radio listeners in the North of England are fated to a particular form of radio interference: superheterodyne local oscillator radiation.

This now makes itself apparent when a neighbouring receiver with i.f. of, say, 460kc/s, is tuned to the 692-kc/s transmission. The local oscillator operates on 1,152kc/s which, when radiated, effectively heterodynes the 1,151-kc/s North transmission.

One remedy is obvious: completely re-align the offending receiver with the i.f. about 470 kc/s, making the heterodyne whistle 11 kc/s, not usually troublesome. But further troubles rear their heads when the neighbour, with carefully re-aligned receiver, listens to the 692-kc/s transmission and decides that he likes the reproduction best with the radio a little off tune!

Suggestion to radio designers: screened oscillator circuits and r.f. stages.

H. R. McDERMOTT.

Branch Secretary, Radio and Television Retailers' Association.

Darlington, Yorks.

Williamson Amplifier

THERE seems to be a greater risk of h.f. instability in the output stage of a Williamson amplifier

when using 6L6's, and I would suggest to builders who suspect this fault, to try neutralizing the stage. In my own case, a pair of 4-mmF ceramics cross-connected directly between pins 5 on one holder and 3 on the other transformed an uncertain 4 watts into a rock-steady 15. But test your condensers on a megger before fitting, or the cure will be much worse than the disease.

H. C. MANNING.

Lisburn,
Northern Ireland.

MANUFACTURERS' LITERATURE

Portable Wire Recorder, the "Wiramphone," is marketed by Geo. C. F. Kauderer, Maiden, Holland, and described in an illustrated leaflet in English.

Yachtsman's Receiver; descriptive leaflets of the Edelystone "720," made by Stratton & Co.

"Pioneering in Space," a review of research and development since 1922, by the Radio Division, Standard Telephones and Cables, New Southgate, London, N.11.

Television Test Gear; descriptive catalogue from Marconi Instruments, Ltd., St. Albans, Herts.

Iron Dust Cores in "Caslite," a brochure containing design information from the Plessey Co., Ltd., Ilford, Essex.

R.F. High-Voltage Units catalogued in a set of technical leaflets from Hazlehurst Designs, 186 Brompton Road, Knightsbridge, London, S.W.3.

Switches for mains voltages catalogued in a booklet from Arcolectric Switches, Ltd., Central Avenue, West Molesey, Surrey.

Electronic Instruments, test gear and laboratory apparatus described in leaflets from Labgear, Ltd., Willow Place, Cambridge.

"Asbestos Textiles and the Electrical Industry," a well-illustrated booklet on the various forms and uses of asbestos, from Turner Brothers Asbestos Co. Ltd., Rochdale.

Industrial Battery Chargers described in an illustrated catalogue from G.E.C., Magnet House, Kingsway, London, W.C.2.

Television Pre-amplifier; a technical specification from Rainbow Radio Manufacturing Co. Ltd., Mincing Lane and Mill Lane, Blackburn, Lancs.

Communication Receiver Type CC150 described in a technical specification from Hamtime Communication Receivers, 10 Elm Street, Wellingborough, Northants.

"The Home Constructors' Handbook," containing eleven circuit diagrams, price lists and a catalogue, can be obtained from Roding Laboratories (Electronics), 70 Lord Avenue, Ilford, Essex, price 1s 6d.

Williamson Amplifier and other products described in a brochure from Radio Trades Manufacturing Co. (Ealing) Ltd., 141 Little Ealing Lane, London, W.5.

Capacitor Price List, issued in May, 1950, by Claude Lyons Ltd., 180-182 Tottenham Court Road, W.1, cancels all previous lists.

ONLY BULGIN IS GOOD ENOUGH

FOR OVER 25 YEARS
THE CHOICE OF CRITICS

LIST NO. P.215 standard Jack plugs, to B.S.666, for use with all jacks to same B.S. With highly polished moulded bakelite type Cap-head, internal terminals (6 B.A. binder-head) and ample space for cord-strain anchorage. Polished nickel-plated electrodes.

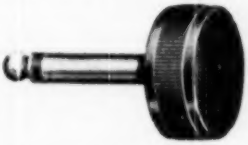

LIST NO. D.54 etc., Signal Lamp fittings for: '0.5W. Indicator-neons, 200–250V.' by Osram, Philips, Siemens, Ediswan, etc. Specify voltage, and S.E.S. or S.B.C. (double-contact) Cap and holder. Fixes by 1 1/32in. ø hole to panels > 5/16in. thick. For neons: Red, Orange or Clear transparent lenses are recommended. (Full colour range available).

LIST NO. K.334 etc. Engraved legended knobs for T.V. and like uses. Highly polished, normally in dark chocolate brown; BRIGHTNESS or CONTRAST or FOCUS or VOLUME or SWITCH. Fix to standard "¼in. ø" shafts (0.247in.–0.249in. ø), fitted with hardened-steel 4 B.A. grub-screw. Legend fitted gold-matt. Also moulded in black.

LIST NO. D.9 Signal Lamp Fitting for 10-12 mm. ø M.E.S.-cap bulbs, and fitting to > ¼in. panels by ¼in. ø hole, NOW IMPROVED in design and fitted two rear 6 B.A. binder-head screw terminals. Case now 'dead.' Full range of translucent or transparent lenses, in all usual colours. Bezel normally black, moulded; also supplied ("D.9 M") in polished metal, nickel-plated, or chromium to order.

LIST NO. P.194 new miniature 6-pole plug and socket for mains connections, etc. Plug (normally 'dead') fixes to apparatus. Socket (normally 'live,' fully insulant-shrouded) connects to cable and supply. Normally Black-moulded, highly polished. With Ag.-plated pins and sockets; for soldered cable- and wiring-connections. Plug fixes by ⅜in. ø hole, to panels up to ¼in. thick.

★ SEND FOR ILLUSTRATED CATALOGUE (W.W. 180) ★
PRICE 1/- POST FREE

A. F. BULGIN & CO. LTD., BYE-PASS RD., BARKING, ESSEX
Telephone: RIPpleway 3474 (5 lines)

BULGIN *Components*

RANDOM RADIATIONS

By "DIALLIST"

Scra-a-tch

THE B.B.C. justly prides itself both on the technical excellence of its recording department and on the vastness of its library of gramophone records. Having spent many interesting hours in the company of members of its recording staff and having read not a few of the excellent papers they have written on their own pet subject, I know what a high standard they strive to maintain and how critical they are of shortcomings. That's why I don't understand how it is that there is not far stricter vetting of the records used to fill in the gaps that occur when programme items pan out at something less than their scheduled time. To say that the reproduction from some of these is appalling is to speak over-kindly; one's candid opinion of it can hardly be expressed on the chaste pages of *Wireless World*.

Missing Link?

One can't help feeling that there must be a lack of liaison between the engineers of the recording (and reproducing) department and those who are entrusted with the choice of records. It is of little use to design the best possible reproducing gear if it is to be fed with worn-out disks. To overhaul the whole library of records might be a task too big to be considered; but couldn't each day's quota of stand-by records be critically tested before being passed to the people responsible for using them? If something of the kind is already done, then, either, the tests are not sufficiently thorough, or the standards by which records are judged are not very exacting. If worn or otherwise faulty records were ruthlessly scrapped and replaced by new ones all would soon be well.

Some Time to Wait

IN THE TRAIN the other day I heard the question: "When are you going to get a television set?" put by one man to another. The answer was: "When the programmes go on all day, when it's in colour and when sets cost half what they do now." Somehow, I can't regard any of these conditions as likely to be realized in the immediate future. I sincerely hope that television never will "go on all day," for nobody would ever get any work done! I'm sure that receivers costing under £20 won't come along, unless some entirely new technique is developed. Colour television certainly will arrive and it may do so fairly soon. In America the F.C.C. turned down both the 4-channel system and that using a revolving disk with coloured "windows" in the receiver. It also laid down that to be acceptable a colour system should (1) give a good monochrome image on an existing receiver, (2) enable a full-colour image to be received with reasonably inexpensive gear and (3) occupy a channel no wider than that needed by a monochrome system. It is reported that a method based on a form of pulse modulation has been perfected; but the F.C.C.'s judgment upon it will not be published for a month or two.

International Television

THE OFFER of the Radio Industry Council to install at its own expense temporary apparatus suitable for providing a television link between this country and France is a noble one and it is to be hoped that the P.M.G. will see his way to accepting it. It was announced some time ago that the authorities of both countries had agreed to the exchange of television programmes; the snag which has so far hindered progress seems to have been the cost of the cross-channel link, which would have fallen on our G.P.O. and the French P.T.T. Now that the R.I.C. has offered to foot the bill for a temporary link one trusts that all may be plain sailing. Not the least of the advantages of putting up a temporary link is that it would enable a thorough try-out of the exchange system to be made, only if it were found completely satisfactory would ways and means of erecting a permanent link need to be considered.

Mutual Benefit

Both we and the French have, I believe, much to gain from television programme exchanges. On our part, we could expect an increase in the number of those "actual event" items which are the life-blood of television. France stands to benefit even more than Britain. Getting French television going has proved a very sticky business so far; on the one hand the present rather scrappy programmes can't be improved or extended until there are more viewers to justify the expense; on the other, there won't be any rapid increase in the number of viewers unless the fare provided is more satisfactory. Programme exchanges with us would enable this

ASSOCIATED ILIFFE TECHNICAL BOOKS

"WIRELESS WORLD" PUBLICATIONS

	Net Price	By post
SHORT WAVE RADIO AND THE IONOSPHERE. T. W. Bennington	10/6	10/10
RADIO VALVE DATA. Characteristics of 1,600 Receiving Valves	3/6	3/9
RADIO DATA CHARTS, by R. T. Beatty, M.A., B.E., D.Sc., Fifth Edition—revised by J. McG. Sowerby, B.A., M.I.E.E.	7/6	7/11
WIRELESS DIRECTION FINDING. By R. Keen, M.B.E., B.Eng.(Hons.). Fourth Edition	45/-	45/9
GUIDE TO BROADCASTING STATIONS. Fifth Edition	1/6	1/7
BASIC MATHEMATICS FOR RADIO STUDENTS, by F. M. Colebrook, B.Sc., D.I.C., A.C.G.I. Second Edition.	10/6	10/10
WILLIAMSON AMPLIFIER: Articles on design of a high-quality Amplifier	3/6	3/9
SUPERHETERODYNE TELEVISION UNIT. An alternative (long-range) unit for use with the equipment described in Television Receiver Construction	2/6	2/9

A complete list of books is available on application

Obtainable from all leading booksellers or from

ILIFFE & SONS LTD., Dorset House, Stamford Street, London, S.E.1.

CRAFTSMANSHIP

"I can most certainly say at this stage that the workmanship and finish are of a quality which I have never before encountered in the radio industry, despite the fact that my association with the industry in one capacity or another extends back over 27 years. I think you are to be congratulated all the more on this achievement in view of the increasing tendency nowadays towards inferior workmanship and design."

Part of a letter from a purchaser who is a very well-known engineer and whose identity is known to the Editor of "Wireless World."

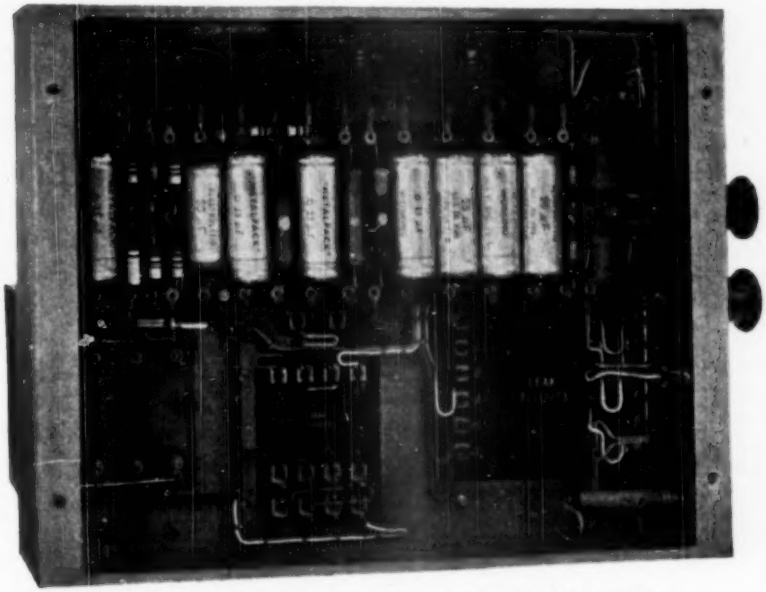

UNDER CHASSIS VIEW OF THE TL 12 POWER AMPLIFIER

LEAK equipment is built to laboratory standards in materials and workmanship by experienced men.

TL/12 TRIPLE LOOP FEEDBACK AMPLIFIER *Price* **£25.15.0** RC/PA REMOTE CONTROL PRE-AMPLIFIER *Price* **£6.15.0**

The high standard of workmanship of the TL/12 amplifier is apparent on inspection. Our claimed performance figures are substantiated by a NATIONAL PHYSICAL LABORATORY REPORT on tests they have made of the TL/12. We were the first manufacturers to publish such a report (August 1949), just as we were the first manufacturers to market amplifiers with a distortion content as low as 0.1% (see "Brit. I.R.E. Journal" advertisement, Sept. 1945).

These amplifiers are the choice of many distinguished audio engineers for high quality reproduction in their own homes.

APPLY TO YOUR LOCAL DEALER FOR FREE 16-PAGE ILLUSTRATED BOOKLET W/TL/12 OR WRITE TO US.

H. J. LEAK & CO. LTD. (Est. 1934)

BRUNEL ROAD, WESTWAY FACTORY ESTATE, ACTON, W.3.

Phone: SHEpherds Bush 1173/4. Telegrams: Sinusoidal, Ealux, London. Foreign: Sinusoidal, London.

NOT JUST A FEW BARS BUT A COMPLETE INTERLACED PATTERN!

THERE are cheaper Pattern Generators than the **Murphy T.P.G. 11** but their performance is limited. You pay more for the Murphy because it gives you the first essential—**THE COMPLETE SYNCHRONISING WAVEFORM AS USED IN THE B.B.C. TRANSMISSION**—*necessary* for the correct alignment of Television receivers.

Far better to pay the extra cost and have a Murphy T.P.G. 11 with a pattern which checks EVERYTHING rather than a cheaper unit which gives an oversimplified pattern with many deficiencies. The Murphy is cheaper in the end—and a lot more satisfactory!

★ *In one large firm of Television Service Engineers, the introduction of the Murphy T.P.G. 11 enabled the time taken on diagnosis, repair and re-alignment to be cut by half!*

THERE IS NO SUBSTITUTE FOR THE

MURPHY TV PATTERN GENERATOR (TPG 11)

F. LIVINGSTON HOGG

SPECIALIST IN HIGH GRADE INSTRUMENTS FOR THE COMMUNICATIONS INDUSTRY

65, BARNSBURY STREET, LONDON, N.1.

For further details and appointments for demonstrations Telephone TUDor 5277.

LAWRENCES

PHOTO-MULTIPLIER CELLS TYPE 931A. High vacuum type, with high response in visible region. Great sensitivity, low noise level, freedom from distortion, low dark current and small size. Ideal for Film Scanning, Colorimetric measurement, Spectrography, Astronomical measurements, Alpha Particle Counting and Facsimile Transmission, etc. Equivalent to Type 27M. Complete with special 14 pin holder and circuit, new, **27/6.**

EDDYSTONE RECEIVER TYPE 640. This renowned communication set tunes 1.7-30 mcs., embodies latest features, crystal gate B.F.O., etc. Electrical Bandspread, Flywheel Tuning, Illuminated Dial. For A.C. Mains. Used only a few hours, and as quite new. A bargain **£20.**

MARCONI STANDARD SIGNAL GENERATOR TYPE TF1440. For A.C. 230v. Turret Grid Range Switching. 85kc/s-30 mcs. Internal or External Modulation, with depth control. Precision Output Attenuator and Multiplier, 1 microvolt 1 volt. Also Output Meter. A laboratory instrument, suitable for the most exacting requirements. Size 20in. × 10in. × 12in. As new, guaranteed perfect. **£70.**

NEW TRANSFORMERS. Type 901145. Primary: 0-190-210-230-250v. 50-60 c.s. Sec. 2.5-0-2v. 5a., 5.0-5v. 3 a. Potted, 4in. tube terminal panel. In maker's cartons **13/6.** Also Power Transformers. Primary as above. Sec.: 400-350-0-350-400v. 150 ma., 6.3v. 6a. C.T., 5v. 3 a. Screened, fully shrouded drop-thru. type. No better transformer is made. In maker's cartons, **35/-.**

NEW CENTIMETRIC COMPONENTS for 1, 3 and 10 cm. bands. Magnetrons, Klystrons, Gas Gaps, Launching Sections, Waveguide sections. Full details on request.

NEW RADAR UNITS TYPE AM-SA/APS4, with Cathode Ray Indicator ID11/APS4. Superbly constructed American equip. containing: three 6J6, two 6V6, one 3FP7, etc. In maker's cartons, **56/-.**

MARCONI WAVEMETERS TYPE 094. A V.H.F. instrument of the highest quality. Tuning range 170-450 mcs., silver plated R.F. components. H.R.O. type bonus kit. Complete with Calibration Charts, Plugs, in fitted transit cases. New and perfect. **£7.**

INTERFERENCE SUPPRESSORS. Fitted in Aerial Lead-in to set. Small unit in screening can, 1in. × 1in. × 2½in., **3/9.** Aerial lightning Arrestors, highly efficient. Model is evacuated glass tube resembling a valve. With insulated holder **3/6.**

MISCELLANEOUS CLEARANCE BARGAINS. Whip Aerials, 9ft., **3/-**; ditto Auto Type, with base insulator, **6/6.** Antenna Tuning Units, with relay and meter, **8/6.** Air Blowers 24v. **4/9.** Thyratrons, Type 2050, gas filled, octal, **7/6.** G.E. Chokes, potted 8H 100 m.a., **7/6.** Condensers .02 mfd. 6 kV., can, **2/6**; 1 mfd. 2 kV., can, **3/6**; 4 mfd. 2 kV., can, **3/6**; 10 mfd. 450 v. miniature, can, **3/-**; 1,000 mfd. 20v. can, **1/9.** Condensers No. 19 set, **2/6**; ditto 8KB7AN, **7/6**; ditto L.F.F. 1KD6G, AHK1, **3/6.** Dynamotors Type 35, 6-12-200v., **4/9.** Headsets 1151R, **5/-.** Headsets moving coil, with M.C. Mike, **8/6.** U.S.A. Inertia Switches **5/-.** Dummy Load Lamps for T.X. **3/6.** Motors A.C. Sync., U.S.A. type KC22, 115v. 0.2 a., with gearbox final r.p.m., torque 100 in/lbs., very small, **12/6.** Plugs, Aerial, 7/8 set, **1/9.** Jones Plugs and Sockets, various, **1/6** pair. Receivers R1155 **7/6.** Receivers BC933A **£7.** Command Receivers R28/ARC5 and R27/ARC5 **42/6.** I.F.F. sets Type AHK1 **25/-.** Rheostats 1,100 ohm 4 a., panel mounting, **12/6.**

Experienced export shippers. All prices include U.K. carriage. Terms C.W.O. satisfaction guaranteed, or money immediately refunded.

LAWRENCES

61, BYROM STREET, LIVERPOOL, 3.

Telephone: CENtral 4430.

VALVES!! VALVES!!

RECEIVING, TRANSMITTING, MAGNETRONS, KLYSTRONS, CATHODE-RAY TUBES, PHOTOCELLS, ETC.

LARGE QUANTITIES & GREAT VARIETIES

IMMEDIATE DELIVERIES FROM STOCK

WRITE OR 'PHONE:—

S. Szymanski

(pronounced SHE-MAN-SKEE)

ELECTRONIC ENGINEER & STOCKIST

95 STRODES CRESCENT

STAINES - MIDDLESEX

TELEPHONE: STAINES 3971

PROBABLY THE LARGEST ACTUAL STOCKIST IN ENGLAND

WHOLESALE & EXPORT ONLY

GARLAND RADIO

AMPLIFIER KIT AC111: This popular amplifier kit has now been supplied to many of the leading schools and colleges, as well as a host of private users. For operation from A.C. mains 200/250 v. 7 valves incl. rectifier. Push-pull output up to 10 watts (2 × 6V6G) to 3Ω or 15Ω speaker (state which). Supply available for tuner unit etc. 280 v. 30 mA. approx. High and Low Gain inputs. Separate Bass and Treble controls. Partridge output transformer. Negative feedback. Complete kit, with circuits and instructions, **£7.**

"VIEWMASTER" TELEVISOR: Instructions, **5/-.** Components supplied separately (any individual component supplied) or in kits as follows: Whiteley, **125/-**; TCC London, **135/-**; TCC Midland, **140/-**; Westinghouse, **62/6**; Morganite (incl. V.C's), London, **35/9**; Midland **35/-**; Plessey, **112/6**; Colvern, **19/3**; Wearite Coils, London, **22/-**, Midland **38/-.**

"ELECTRONIC" TELEVISOR: London Handbook, **2/6**; Wiring Diagram **2/6**; Midland Handbook and wiring diagram, **4/6**; Chassis with valveholders, coilformers, etc., mounted, vision **22/6**; sound **18/9** (please specify London or Midland); T/Base **17/6**; P/Unit, **25/-**; Gantries, etc. **9/-**; Coils and Chokes, London **15/-**; Midland **17/6**; Focus Coil **30/-**; Scanning Coils **25/6**; Line Output Transformer **25/6**; Mains Transformer, **90/-**; 4 Kv. Transformer, **67/6**; 5 Kv. Transformer **72/6**; SH Choke **18/6**; 10H Choke **13/-.** All the above are designer-approved components.

SPECIAL OFFER OF AC DC TRF PACK, all brand new goods. Drilled chassis, 3 octal valveholders; twin-gang .0005 mfd. ceramic insulation; two trimmers; 5kΩ volume control with switch; valves KTW61, 6SH7, 25A6G; metal rectifier; 5in. P.M. loudspeaker; output transformer; L.F. choke; 8-16 mfd. electrolytic; and 3 yds. 1-way 3 amp. flexcord. The lot, with free circuit of TRF receiver, for **55/-.** This offer is for one month only.

19in. RACK MOUNTING AMPLIFIER A1104, with power pack and local control panels. As an amplifier or modulator, 15 watts (MHL4 into two PX25's push-pull) with 1000 cps. local oscillator for C.W. Power pack has 500-0-500 v. 120 mA. 3 x 4 v. Ct; 1 x 10 v., transformer; double choke, each section 2CH 150 mA. input choke, 200 mA. 2½in. meter, etc. Local control panel has 12 v. 1A. bridge rectifier, transformers, etc. Push-pull input and output transformers on amplifier. Supplied less valves. Callers only, **£3 10/-.**

RACKS, for above or other equipment, 19in. x 5ft. 6in. Collect or carriage forward, **£1.**

SELENIUM RECTIFIERS: Output up to 24 v. 1 A. **15/-.**

ALADDIN COIL FORMERS, Type F804. Complete with Iron-dust cores, 5d. each, **4/6** per doz., **48/-** per gross, **£12** per 1,000.

PLEASE ADD POST OR CARRIAGE TO ALL ITEMS.

GARLAND BROS.

Chesham House, Deptford Broadway, London, S.E.8.

Telephone: TIDeway 4412/3.

FIGHTING THE CRIME WAVE...
with G.E.C.
QUARTZ CRYSTAL UNITS

The Police "999" emergency call system depends for its successful operation on instantaneous radio communication between Police headquarters and the fleet of patrol cars. Radio equipment in the patrol cars is used under the most arduous conditions but it must be available for instant use 24 hours in the day.

No wonder then that more and more Police authorities throughout the country are using G.E.C. quartz crystals in their radio equipment.

Pioneering research and experience in making over a million units, ensure a product of the highest quality. For all your quartz crystal requirements be sure to specify G.E.C.

Quick delivery service for urgent requirements for experimental or replacement purposes.

Write for our leaflet QC.4904

SALFORD ELECTRICAL INSTRUMENTS LTD
PEEL WORKS, SILK STREET, SALFORD 3, LANCS.
A Subsidiary of
THE GENERAL ELECTRIC CO. LTD., OF ENGLAND

Cold Cathode Diode

NT2

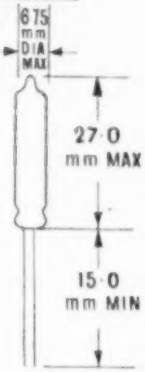

The NT2 is a very small cold cathode diode of wide application: e.g. in counters, storage circuits, low current stabilisers and so on.

It is moreover an ideal indicator tube giving a clear bright indication with currents as low as 0.3mA.

RATINGS

Nominal strike voltage	**80 V.**
Nominal maintaining voltage at 0·5 mA.	**60 V.**
Maximum power dissipation ..	**0·06 W.**
Maximum current for continuous operation	**1 mA.**

HIVAC
THE SCIENTIFIC VALVE
BRITISH MADE

GREENHILL CRESCENT
HARROW-ON-THE-HILL, MIDDX.
Telephone : HARrow 2655

ALEC Davis SUPPLIES Ltd.

Department W.W
18, TOTTENHAM COURT ROAD, LONDON, W.1.
Phone: MUSeum 2453, 4539

SHOP HOURS: Mondays to Fridays 9—5.30. Saturdays 9—1

FULL MAIL ORDER FACILITIES

RELAYS

(ex Ministry)

P.O. 600 and 3,000 types

AS FOLLOWS

D.C. COIL RESISTANCE: 10 ohms to 42,000 ohms, also double-wound coils. Special coils wound to spec. in quantities.

CONTACTS: Make (M) Break (B) Change-over (C) in twin silver, heavy duty, and twin platinum in any combination to 8 sets.

MAINS TRANSFORMERS. FULLY INTERLEAVED. SCREENED AND IMPREGNATED. ALL PRIMARIES ARE 200/250 v. Half Shrouded.

HSM63 (Midget). Output 250/0/250v. 60 m/a. 6.3v. at 3 amps. 5v. at 2 amps. 15/-
HS63. Output 250/0/250v. 60 m/a. 6.3v. at 3 amps. 5v. at 2 amps. 15/6
HS40. Windings as above. 4v. at 4 amps. 4v. at 2 amps. 15/6

Output

HS2. 150/0/250v. 80 m/a. 17/6
HS30. 300/0/300v. 80 m/a. 17/6
HS3. 350/0/350v. 80 m/a. 17/6
HS2X. 250/0/250v. 100 m/a. 19/6
HS75. 275/0/275v. 100 m/a. 19/6
HS30X. 300/0/300v. 100 m/a. 19/6
HS3X. 350/0/350v. 100 m/a. 19/6

Fully Shrouded

Output

FSM63 (Midget). Output 250/0/250v. 60 m/a. 6.3 v. at 3 amps. 5v. at 2 amps. 15/6
FS2. 250/0/250v. 80 m/a. 19/6
FS30. 300/0/300v. 80 m/a. 19/6
FS3. 350/0/350v. 80 m/a. 19/6
FS2X. 250/0/250v. 100 m/a. 21/6
FS75. 275/0/275v. 100 m/a. 21/6
FS30X. 300/0/300v. 100 m/a. 21/6
FS3X. 350/0/350v. 100 m/a. 21/6

All the above have 6.3-4-0v. at 4 amps., 5-4-0v. at 2 amps.

FS43. Output. 425/0/425v. 200 m/a. 6.3v. 4 amps. C.T. 6.3v. 4 amps. C.T. 5v. 3 amps. Fully shrouded. 42/6
FS50. Output. 450/0/450v. 250 m/a. 6.3v. 2 amps. C.T. 6.3v. 4 amps. C.T. 5v. 3 amps. Fully shrouded 62/6
F30X. Output. 300/0/300v. 80 m/a. 6.3v. 7 amps. 5v. 2 amps. Framed. Flying leads 26/6
F35X. Output. 350/0/350v. 250 m/a. 6.3v. 6 amps. 4v. 8 amps., 4v. 3 amps., 0-2-6.3v. 2 amps. Fully shrouded 59/6
FS160X. Output 350/0/350v. 160 m/a., 6.3v. 6 amps., 6.3v. 3 amps., 5v. 3 amps. Fully shrouded 37/6
FS43X. Output. 425/0/425v. 250 m/a. 6.3v. 6 amps. 6.3v. 6 amps. 5v. 3 amps. Fully shrouded 57/6
HS6. Output. 250/0/250v. 100 m/a. 6.3v. 6 amps. C.T. 5v. 3 amps. For receiver R1355. Half shrouded 24/6
HS150. Output. 350/0/350v. 150 m/a. 6.3v. 3 amps. C.T. 5v. 3 amps. Half shrouded 25/9

The above have inputs of 200/250v.

C.W.O. (add 1/- in £ for carriage), all orders over £2 carriage paid. Trade enquiries invited.

H. ASHWORTH (Dept. W.W.)
676 GT. HORTON RD., BRADFORD, YORKS.

G2AK ***This Month's Bargains*** **G2AK**

Vibrator Packs, 12 v. input. Output 300 v. at 100 mA, fully smoothed. **19/6,** plus 1/6 post.

Vibrator Packs, 6 v. input. Output 180 v. at 40 mA, complete with all smoothing (metal rectifiers). **19/6** each, plus 1/6 post.

Tub. Condensers, 01/5 kv. **1/6**; 02/8 kv. **2/-,** plus post 6d.

Special for AR-88 Users. Matching speakers, 2/5 ohms, black crackle case, **£3 15s.,** carr. paid.

AR88 Spare Crystals for D model only. 455 kc/s., **15/-** each.

Power Transformers. 320-320-130 mA, 6.3 v. 5 a. C.T., 5 v. 3 a. Primary 200/250 v. 50 c. Drop through type, **22/6,** post 1/6.

Special Offer. Four 807 valves for **£1.**

H.T. Dry Batteries. These are heavy duty 157 v. plus 5/2 v. in hermetic sealed metal cases. 10½in. x 4½in. x 4in. Weight 11 lb. These are special mercury type batteries and are first-class value at **8/6,** plus 1/6 postage.

Moving Coil Hand Microphones, with switch, **3/11** each.

Transformer, for above, **2/-** each.

500 Micro-amp Meters, scaled 0-600, **5/-** each.

70 Ohm ¼in. Dia. Co-Ax. Cable, 8d. per yard. Postage 1/6 any length.

70 Ohm Twin Feeder Cable (not screened), **5d.** per yard. **300 Ohm Twin Ribbon Feeder, 5d.** per yard. Postage 1/6 any length.

H.R. Headphones, brand new, **8/6** per pair, plus 1/- postage.

Moving Coil Headphones, with Moving Coil Hand Microphone, **6/-,** postage 1/-.

Coils, etc.—Denco T.R.F., L. & M.W., **6/6** pair. All other Denco products in stock. Douglas DS dual-range coil with circuits, **5/-** Osmor coil packs from **33/-.** Wearite "P" coils, **3/-.** Midget I.F.s **16/6** pair (465 kc/s.).

Speakers,—2½in., **12/11**; 3½in., **13/11**; 8in., **15/-**; 10in., **£1.**

PLEASE PRINT YOUR NAME AND ADDRESS.

CHAS. H. YOUNG, G2AK

All Callers to ***110 DALE END, BIRMINGHAM***
Phone: CENTRAL 1635

Mail Orders to ***102 HOLLOWAY HEAD, BIRMINGHAM***
Phone: MIDLAND 3254

"You're CERTAIN to get it at ARTHURS!"

★ **VALVES:** We have probably the largest stock of valves in the country. Send your enquiries.

AVO METERS IN STOCK

Avo Model 7	£19 10 0
Avo Model 7, high resistance	£19 10 0
Avo Model 40	£17 10 0
Valve Tester	£16 10 0
Test Bridge	£11 0 0
Avo Minor, AC/DC model	£8 10 0
Electronic Test Meter	£35 0 0
Signal Generator	£25 0 0
Valve Characteristic Meter	£40 0 0

TAYLORS METERS. List on request.

DECCA PICK-UPS	£3 15 5
DECCA HEAD	£2 19 2
ADAPTOR for Garrard	3 8
COSSOR DOUBLE BEAM OSCILLOSCOPE	£85 10 0

"Viewmaster" Television Kits in stock for Birmingham and London areas. Please state which required.

LATEST VALVE MANUALS
Mullard - 5/- ea.
Mazda - 1/- ea.
Brimar Teletube & Radio - 4/-
Post 4d. each extra

LONDON'S OLDEST LEADING RADIO DEALERS

Arthurs EST. 1919

PROPS: ARTHUR GRAY, LTD. Terms C.O.D. or cash with order

Our Only Address: **Gray House, 150/152 Charing Cross Rd., London, W.C.2** TEMple Bar 5833/4 and 4765

ELECTRICAL, TELEVISION & RADIO ENGINEERS.

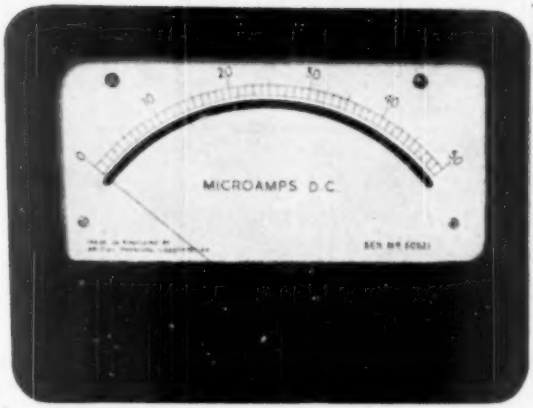

SIZE	2½"	3½"	5"
RANGE	25μA to 50A	10μA to 50A	10μA to 50A
PRICE			
50μA	55 -	61 -	93 -
200μA	45 -	51 -	83 -
1mA	35 -	41 -	73 -

All sizes available with MIRROR SCALE

1st Grade Accuracy

SENSITIVE PANEL MOUNTING METERS

For particulars of these and our full range of measuring instruments write to :—

BRITISH PHYSICAL LABORATORIES

HOUSEBOAT WORKS · RADLETT · HERTS · Telephone: RADlett 5674-5-6

UNIVERSITY RADIO

Offer Guaranteed Used Equipment at Attractive Prices

G.E.C. 30/60-watt Amplifier, mic. and gram. inputs. Output imp. 2.5/600 ohms, 200/250 v. AC. Perfect £17 10 0

Hallicrafter S.38 Communication Receivers, AC/DC 110/230 v. New condition £21 0 0

Taylor Valve Tester, Type 45, complete and as new £10 0 0

Taylor Valve Tester, Type 45A, complete and as new £11 10 0

Radiovision Commander Communication Receiver, complete and as new £32 10 0

Peto Scott Trophy 8 Communication Receivers. Perfect ... £9 0 0

Howard Communication Receiver, model 460, complete and perfect £21 0 0

Q Max Transmitter, model B4.40, mains operated, complete with valves and perfect ... £28 10 0

University 10-watt quality Amplifiers, two inputs, high gain, neg. feedback, separate bass and treble controls, output imp. 2.5 and 15 ohms. Valves, 6Q7, 6SN7, two 6V6's P.P., 5Z4 rect., AC 200/250volts. Built on heavy gauge aluminium chassis. A real quality job ideally suited for use with radio feeder unit. New and guaranteed £8 15 0

Portable Disc Recording Units by B.S.R., type DR33C, fitted Connoisseur playback pick-up and 8in. speaker, less amplifier. In absolutely new condition £70 0 0

Eddystone 640 Communication Receivers. Complete and as new £20 0 0

R1155's. Brand new in transit cases ..... each £9 0 0

T1154 Transmitters. As new, complete with valves £7 10 0

Portable Wire Recorder by UTAH, U.S.A. In perfect condition complete with microphone and wire £65 0 0

WE NEED GOOD USED EQUIPMENT URGENTLY. PLEASE SEND, BRING OR PHONE FOR OFFER

Marconi U.H.F. Signal Generator, type TF517E. Perfect ... £22 10 0

G.E.C. Miniscope. Complete and as new £13 0 0

Advance Signal Generator, model I type E 150 kc.60 megs. As new £14 10 0

Wavemeters 1191, complete and perfect £7 10 0

One only. Deccalian Record Player. As new £18 10 0

Spring Drive Disc Recording Unit, complete with tracking gear and cutting head. Perfect £12 10 0

Hunt's Capacity and Resistance Bridge, model CRB. As new £10 10 0

Hunt's Capacity and Resistance Bridge, CRB. Perfect ... £8 10 0

Taylor Signal Generator, model 658. As new £10 10 0

Taylor Capacitance and Resistance Bridge, Model 110A. As new £10 10 0

Collaro AC/DC Gram. Motor with Pickup. New condition ... £7 10 0

Universal Avo Minor. As new £5 10 0

Taylor Junior Universal Test Meter, 120A £5 10 0

Cossor Double Beam Oscilloscope. As new £35 0 0

Cossor Double Beam Oscilloscope. In good condition £27 10 0

Garrard Two-speed Gram. Motor, 33 and 78 r.p.m. Perfect £10 10 0

Weston Meter, model E772, 1,000 o.p.m., complete with valve analysing adaptors. As new £16 10 0

Weston Meter, model E772, as above, less adaptors. As new ... £11 10 0

Evershed's 500 v. Bridge Megger, with built-in resistance box. As new £12 10 0

Evershed's 500 v. Megger, in aluminium case. New condition £10 0 0

Evershed's Wee Megger, in leather case. Perfect £8 10 0

WE HAVE OTHER EQUIPMENT ARRIVING DAILY: **ALL S.A.E. INQUIRIES WELCOMED.**

CASH OR CHEQUE WITH ORDERS. ALL ITEMS LISTED ARE CARRIAGE PAID UP TO 50 MILES.

22 LISLE STREET, LEICESTER SQUARE, LONDON, W.C.2

'Phone GERrard 4447 and 8582. Hours 9 to 6. Thursdays 9 to 1.

APOLOGIES

We apologise for an error which occurred in the details given for our Output transformer type 2836 in the Williamson Amplifier booklet. There is a choice of seven output impedances by series parallel connection. These are :— 1.25, 2.8, 5, 7.8, 11.3, 15.3 and 20 ohms.

This incidentally is the component that has aroused so much interest in the U.S.A.

By the way, there is now an improved version type 2836B leakage reactance under 15m/hys. Primary inductance is still 100 hys minimum, price 90/-.

SAVAGE DEVIZES

SAVAGE TRANSFORMERS LTD. · NURSTEED ROAD, DEVIZES, WILTS.
TELEPHONE DEVIZES 596.

THE FIDELIA

Features: triode variable selectivity, infinite impedance detector, electronic bass and treble controls, triode output stage; 7 wave-bands 13-50, 190-550 and 1,000-2,000 metres. Audio amplifier response 30-15,000 cycles; bass, treble and volume controls operate on gramo, suitable for light weight p.u. Price £17 2 6. Also available heavy model, £21 5/-. "Precision" 5 valve chassis, £12/17 6. A 7-8 watt amplifier £16 16/-.

7 VALVE RADIO-GRAM CHASSIS

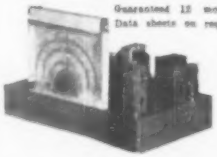

Guaranteed 12 months
Data sheets on request

ELECTRO Acoustic DEVELOPMENTS
18 Broad Rd., Willingdon, Eastbourne, Sussex

Stars for Sale!

★ 3 SPEEDS — 33⅓ - 45 - 78 rpm.

★ INTERCHANGEABLE HEADS *for Microgroove or Standard Records*

★ AUTOCHANGE UNITS *for 10" or 12" Mixed Records*

★ Interested in the NEW Long-Playing, Unbreakable MICROGROOVE RECORDS ?

Send for details of the new motors —record players & auto changers now becoming available.

Smith RADIOCRAFT Ltd
PHONE 54971
64-71 CHURCH GATE LEICESTER
Shops 53971 G2RI

PRATTS RADIO

1070 Harrow Road, London, N.W.10

Nr SCRUBBS LANE Tel. LADbroke 1734

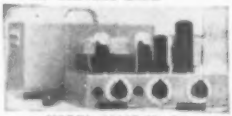

MODEL AC10E £8 18 6

AMPLIFIERS. College general purpose units. **Model AC10E** 10 watt 4 valve unit. Neg. feedback. Separate mike stage, separate inputs for mike and gram with twin faders. Tone control. Complete in case with chrome handle, **£8 18/6.** (Carriage 5/- extra.)

Model AC18E, 6 valve unit with output of 18½ watts. Push-pull output with feedback over 3 stages. Separate mike stage. Inputs as AC10E. Complete with case and chrome handles, **£13 19/6** (carr. pd.). **Model U10E,** 6 valve unit for DC/AC mains. Spec. as AC18E. 10 watts output with feedback over 3 stages. Separate mike stage, **£11 11/0** (carr. 5/- ex.). All above have outputs to match 3, 8 or 15 ohms Speaker, and are ready for immediate use. Finish blue stove enamel. Input volts average, mike .003 v., gram. .3 v. No pre-amplifier required. **Model AC4C** record/radio amplifier. Chassis model. 5 valves P.P. output with feedback over 3 stages. Output 8-10 watts. Supplies H.T. and L.T. for tuning unit. Output to 3, 8 and 15 ohm speaker, **£9/18/6** (carr. pd.). **Model AC4C,** AC or **U4C** AC/DC. 3 valve chassis units. 4 watts output to 3 ohms, **£4 19 6** (carr. 2/6). 3 waveband superhet tuning unit available. Price **£9 13 10** tax paid. Stamp for amplifier list. Above are as supplied to clubs, schools, hospitals, etc.

MODEL AC4C 99 6

SPEAKERS. Truvox 2½in., **17/6**; 12in., **37/6**; Scentorian, 2½in., **15/6**; 5in., **17/6**; Plessey, 5in., **9/6**; 8in., **11/9**; 10in., **17/6**; Rola mains en., 6½in., 700 ohm field, **10/-**; Goodmans 8in., **16/6**; 12in., **130/-** (all less o/transfr.).

TRANSFORMERS. E.H.T. 2.5 Kv. 4 v., 4 v. C.T. Input 200/20/40 v. (for VCR97), **27/6** (tested 15 Kv.). 2 x 350 v. 80 mA., 0, 4, 5 v.; 0-4, 6.3 v., **21/6.** Filament, input 230 v., output 6.3 v. 1½ A., **5/6.** Output 6V6 to 3 ohms, **3/11**; Ultra midget 154/354, **3/11**; 6V6 P/P. to 3, 8, 15 ohms, **18/-.**

VARIABLE CONDENSERS. 2 gang .0005, **4/3**; 3 gang, **6/9**, with fit. and shaft 2½in. Presets. Ceramic 50 pf., **4d.**; 100 - 500 pf., **1/3.** **CONDENSERS.** B.I. 500/550 v. C/b'd. Blocks, 8 mfd., **3/3**; 8 - 8, **4/9**; 8 - 16, **6/-.** Hunts 8 mfd., **2/3**; 16 mfd., **3/6**; 16 + 8, **3/9** (all 450 v.). T.C.C. 25 mfd. 25 v., **1/-**; 25 mfd. 12 v., **8d.**

Open 10-6. Callers welcome. Nearest Tube Kensal Green. All Goods New and Unused. C.O.D. or C.W.O. Post free over £1.

RADIOMENDERS LIMITED

FOR SPECIAL TRANSFORMERS AND REWINDS

We specialise in

AMATEURS' WINDINGS, TRANSFORMERS ALL TYPES, CHOKES, PICK-UP COILS, INSTRUMENT COILS, Etc.

Highest workmanship Good Delivery

☆

RADIOMENDERS, LTD.

Television & Radio Apparatus, Transformer & Coilwinders.

123-5-7 Parchmore Road,
THORNTON HEATH, SURREY

LIV 2261. Trade enquiries invited. Established 16 years.

SUPACOILS OFFER

- A complete range of High Q variable iron dust cored coils in wavelengths 10-30, 16-50, 30-75, 75-200, 190-550 and 800-2,000 metres; Aerial, H.F. or Oscillator ..... 3/- ea.
- **MODEL 30** famous 3 waveband superhet Coil Packs, aligned 29 9 ea.
- **MODEL 40** Coil Packs—similar with R.F. stage aligned ... 57.6 ea.
- **MODEL 30 TUNING UNIT** consisting of 30 Coil Pack, pair of "M.M." I.F. Transformers, matched 2-gang and attractive dial. Components aligned together as a unit and sealed ... 54 9 inc.
- **RECORD CHANGERS.** Collaro, £10 15/-; Plessey, £18 6 8; Richard Allan (in de luxe cabinet) £27 19 0
- **COMPONENTS.** Speakers, pickups, chassis, dials, resistances, condensers, etc., in stock, or special components obtained to order.
- **FREE.** A copy of the enormously successful Home Constructor's Handbook, which contains eleven tested circuit diagrams, useful data, hints on construction and servicing and a complete resistance colour code, will be forwarded FREE with orders of 20/- or more, or a copy can be obtained for 1/6 only from

SUPACOILS (Mail Order Office)
98, Greenway Avenue, London, E.17

PREMIER RADIO COMPANY

MORRIS & CO. (RADIO) LTD.

PREMIER MIDGET RADIO KIT

Redesigned and easier than ever to build. Includes an attractive walnut or cream plastic cabinet 9½ in. × 6½ in. × 6in.
The valve line-up is 6K7, 6SH7 and beam power output 6V6G(G) in the A.C. model and 6K7, 6SH7 and 12A6 in the A.C./D.C. model. Both use metal rectifiers and one for use on 200-250 volt mains. The dial is illuminated and the receiver presents an attractive appearance. Medium and long waveband coverage. Complete kit of parts with valves, speaker, cabinet and point-to-point diagrams. Please state if A.C. or A.C./D.C. is required. **£4.19.6** Inc. P.T.

NEW 3-BAND MIDGET SUPERHET KIT

Redesigned to cover the short, medium and long wavebands (16-50, 190-545, 1,000-2,000 metres). A.C. valve line-up, 6K8, 6K7, 6Q7, 6V6G. Beam power output. A.C./D.C. valve line-up is the same excepting output valve is 12A6. Both use metal rectifiers and are for use on 200-250v. mains.
In cream or walnut cabinet as illustrated. Illuminated dial. An attractive and powerful receiver.
Complete kit of parts with Valves, Speaker, Cabinet and point-to-point diagrams.
Please state if A.C. or A.C./D.C. is required. **£6.19.6** Inc. P.T.

CATHODE RAY TUBES. ALL NEW AND PERFECT.

CV. No.	Civil's No.	Dia. in inches	Focus	Defln.	E.H.T.	G.E. for TV	Price	Roll. pkg and Insro
254	—	9	E.S.	Mag	5kv	Expensl.	40/-	10/-
279	—	3.75	E.S.	E.S.	1kv	Expensl.	10/-	3/6
600	3CP1	3	E.S.	E.S.	2kv	Yes	25/-	5/6
601	3BP1	3	E.S.	E.S.	2kv	Yes	27/6	7/6
602	3JP1	3	E.S.	E.S.	1.5kv	Yes	15/-	5/6
718	5FP7	5	E.S.	Mag	2kv	Expensl.	20/-	7/6
741	5LP1	5	E.S.	E.S.	2kv	Yes	27/6	7/6
796	5AP1	5	E.S.	E.S.	1kv	Yes	15/-	5/6
817	5EP1	5	E.S.	E.S.	2kv	Yes	15/-	5/6
1132	VCR139	3.56	E.S.	E.S.	3kv	Yes	15/-	5/6
1131	VCR517	12	E.S.	E.S.	4kv	Yes	80/-	15/6
1138	VCR138	3.5	E.S.	E.S.	2500v	Yes	10/-	5/6
1140	VCR140	12	Mag	Mag	4kv	Yes	90/-	15/6
1379	4GR3	4	E.S.	E.S.	3kv	Yes	15/-	5/6
1381	4GR4	5.75	E.S.	E.S.	3kv	Yes	15/-	5/6
1384	—	11.5	E.S.	E.S.	4kv	Expensl.	40/-	10/-
1385	—	6.25	E.S.	E.S.	3kv	No	17/6	5/6
1511	VCR511	11.75	E.S.	E.S.	4kv	Expensl.	60/-	10/-
1516	VCR516A	9	Mag	Mag	3kv	No	40/-	10/-
1521	VCR521	3.5	E.S.	E.S.	4kv	No	5/-	1/6
1529	VCR529	1.75	E.S.	E.S.	800v	Yes	15/-	5/6
1593	VCR517	6	E.S.	E.S.	2kv	Yes	20/-	5/6
1791	5JP1	5	E.S.	E.S.	2kv	Yes	27/6	7/6
2080	EM14-1	3	E.S.	E.S.	800v	Yes	17/6	5/6
2726	—	5.25	E.S.	E.S. Mag	4kv	Expensl.	20/-	7/6

TRANSMITTING AND SPECIAL PURPOSE VALVES

805A	10/-	813	5/-	2B34	7/6	E1148(CV12)	20/-	MU300/E(CV1068)	15/-
807	10/-	1625	5/-	VS69	7/6	EBT1(CV138)	20/-	U180(CV187)	6/6
810	5/-	715A	6/6	QDT/6C	6/6	V866(CV1066)	6/6	N309(CV1199)	5/-
872A	10/-	2K41	6/6	DET24	10/-	V1006(CV1006)	6/6	CV6(Klystron)	5/-
866B	10/-	867	6/6	2E26	10/-	V1100(CV1020)	7/6	GU50(CV1072)	7/6
878	10/-	100TH	20/-	EK32	12/6	U11(CV1113)	5/-	1626(CV1750)	3/6
861	20/-	4C27	10/-	307A		PT15B(CV1046)	5/-	RL6(CV1102)	6/6
829	10/-	6X2	2/6	297A	15/-	VU133A(CV924)	6/6	GU18(CV1080)	6/6
832	10/-	7C6	3/6	304A	2/6	AD1(CV1114)	6/6	VU960(CV29)	6/6
803	10/-	8005	3/6	836	3/6	DQ7(CV1141)	6/6	E1148(CV76)	40/-
203A	10/-	9004	3/6	QV1/10	6/6	U7A(CV1204)	6/6	931A	30/-
1616	5/-	7193A	10/-	1ST	6/6	RL18(CV1107)	5/-	Base	2/6
8012	10/-	2D21	7/6			HY114B(CV1005)	6/6		

152-153, FLEET STREET, E.C.4. *Phone: CENtral 2833*—**and at—207 EDGWARE RD., W.2.** *Phone: AMBassador 4033*

207, Edgware Road is open until 6 p.m. on Saturdays. All post orders to **167 Lower Clapton Road, London, E.5.** Phone: AMHerst 4721.

Terms of Business: Cash with order or C.O.D. over £1. Send 2d. stamp for list.

M·O·S STOCKTAKING SALE

All items FREE carriage paid home.

EKCO TA94 LOFT TV AERIALS. List price 25/-. Our price **21/6**

AERIAL RODS. 48 sections 12in. copperplated tubing for aerial erection—push fit sections. **8/9**

3-WAY PATCH CORDS. Fitted jack plug each end. Length 3ft. 6in. *Each* **2/6**

ALTERNATORS. Type U2, 80 v. 1,200-2,400 r/s. 1,200 w. 24 v. D.C. excitation. *BRAND NEW* **£5**

ALTERNATORS, MOTOR. 24 v. D.C. input 200-250 v. 50 ~, output 80 watts. Completely enclosed, with starter switch, and metered output. **£4**

AMPLIFIERS A1134A. Complete with valves (or less valves 5/- each). **10/-**

POWER UNITS 280. Complete with 6 valves—2 VU133, 2 CV34, 1 5U60, 1 VR53, 7 relays, 4 metal rectifiers, etc. *Brand new in transit cases.* **27/6**

R1355 RECEIVERS. *Brand new* (or as new 35/-). **70/-**

R3515 RECEIVERS. *Brand new in transit cases.* **£3-10-0**

MODULATOR TYPE 53. With 1 VT120, 2 VR53, 1 6V6, 1 807, 3 CV37, 1 VU806, 24 v. Blower Motor suitable for conversion for A.C. mains. In case 16in. × 12in. × 9in. *Brand New in cartons* (Callers only.) **17/11**

CRYSTAL DIODES (CV 226). First class permanent crystal detector. *BRAND NEW* in lead cartons. **3/-**

"F" VOLTAGE REGULATORS for voltage and current control of 24 v. D.C. generators with protection against overload. Capacity 25 watts each unit (with carbon pile). *Brand new ONLY* **10/-**

WIRELESS SET No. 18. 4-valve receiver covering range 6-9 mcs. Battery operated. IF 465 k.c. Complete with valves. *Condition new.* **17/6**

DUAL-GANGED VOLUME CONTROLS. Morgan, 50,000 ohms per section. Same type, but 4 gang. **2/-**

POTENTIOMETER KIT. 50 assorted wire-wound and carbon controls. Values from 1 ohm upwards. The lot **10/-**

50 OHM 25 WATT WIRE WOUND RESISTORS with slider. Complete with 2 clips. **2/6**

100 OHM 100 WATT VITREOUS ENAMEL RESISTORS. Clip on type. **2/6**

MAGNETIC KEY. 2 pole 2 way 1.16th in. break, lamps 20 v. 2 coils each 120 ohms. Complete mounted in grey steel case. *Only* **5/-**

POWER UNIT TYPE 32. H.T. supply for T1154. *Brand new.* Input 12 v. Output 1,200 v. 50 mA., rating 240 watts, ideal for converting to a h.p. electric motor for use on A.C. or D.C. mains. Starter incorporated in each unit, which is fully smoothed. Enclosed in sound proof cabinet. *ONLY* **20/-**

R1132A RECEIVERS. As new in transit cases. **£3-4-6**

HALF PRICE OFFER.
D.C. AVOMINORS in original cases. *Brand new surplus.* List price £23/5/-. *Our price—* Just half **£2-12-6**

BELLING. 50 ohm co-axial cable 10 yds. for **6/-**

7/22 ENAMELLED COPPER AERIAL WIRE. 400 yd. REELS FOR ONLY per reel. **24/-**

THERMO-COUPLE METERS. 2 amp. 2in. Round. *Brand new.* Value **12/6**

B.P.L. 17 RANGE UNIVERSAL TEST SETS. *Brand new.* Unrepeatable at Formerly £10-10-0. **£6-19-6**

ELECTROLYTIC CONDENSERS. 16 mfd. 450 v. Tubular can. Or 6 for 15/-. *Each* **3/-**

TELESCOPIC AERIAL (ex. Dinghy). Extends from 12in. to 9ft. Ideal for use with field strength meters or portable receivers. **7/6**

FIXED RESISTANCE 14 ohms 7·5 amps. Comprising resistance unit in lightweight cabinet. **5/-**

TRANSFORMER TYPE 269. A heavy duty mains transformer with two 5-pin amphenol rectifying valveholders mounted and wired on heavy bakelite terminal panel. Primary 230 v. 50 c/s. Secondaries 4 v. 3·5 amps. C.T. 600 v. 150 m.A. **13/11**

2-Valve Battery-Operated MORSE OSCILLATOR FOR MORSE TRAINING. Incorporates note selective control, volume control, key and interference jacks. Size 8in. × 5in. × 8½in. Power supply required H.T. 60 v., GB 4½ v., L.T. 2 v. Provision for three inside cabinets. Complete with 2 valves, type PM1LF and LP2. Pair of phones (if supplied with unit), 8/6. Heavy duty morse key, 1/3. Valves carry 12 months guarantee. **15/-**

TUBULAR CONDENSER PARCEL. 100 assorted condensers from .0001—1 mfd. Per parcel. **7/11**

MINIATURE AUTO-TRANSFORMERS for matching low impedance phones to high impedance output, with jack and socket. **2/6**

EARTH RODS with brass terminal. 6 for **5/-**

Terms: Cash with Order

M·O·S MAIL ORDER SUPPLY CO. The Radio Centre, 33 Tottenham Court Road, London, W.1. MUS. 6887-8-9

RELAYS AND KEY SWITCHES

LARGEST EX-GOVT. STOCK IN GT. BRITAIN

Types 600-3000 Relays — Siemens High Speed
Also A.C. 250 volts 50 cycles

Uniselector Switches, Carbon insets, Telephone Components, Plugs, Jacks, Handsets, Co-Axial Cables — **Government Contractors**

JACK DAVIS (Dept. W.)
30 PERCY STREET, LONDON, W.1
Phones: MUSeum 7960, LANgham 4821

"ADCOLA" SOLDERING INSTRUMENTS

Reg. Trade Mark

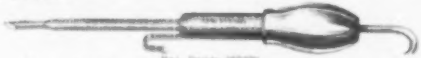

Reg. Design 840309

Designed for Wireless Assembly and Maintenance.
SUPPLIED FOR ALL VOLT RANGES FROM 6.7v. TO 230/50v.

The three Adcola Models cover the requirements of the **Television, Telecommunication and Radar Engineers** and assure thorough jointing.

⅛ in. dia. Bit. Standard Model —	22/6
¼in. dia. Bit. Standard Model —	25/-
⅛ in. dia. Detachable Bit — — —	30/-

Patented in England and Abroad.

Sole Manufacturers

ADCOLA PRODUCTS LIMITED
ALLIANCE HOUSE, CAXTON STREET, WESTMINSTER, LONDON, S.W.1. *Tele. MACaulay 4272.*

NEW S.T.C. SELENIUM RECTIFIERS. Largest L.T. range in Great Britain. Current products. NOT surplus. E.H.T. H4/200, W.W. Televisor, 29/6, H4/100 VR97, 19/6, post free.

HALF-WAVE RECTIFIERS.
16v., 1a., 7/-; 1a., 8/6; 2a., 9/10; 3a., 17/-; all post 6d. 4a., 18/-; 6a., 22/6, post 10d. 30v. 1a., 12/6; 2a., 14/8; 4a., 26/-; 6a., 38/6; 45v. 1a., 16/6; 2a., 21/-; 4a., 37/6; 6a., 54/-; 100v. 2a., 36/6; 4a., 69/-; 6a., 100/-, all p. 1/-.

HALF-WAVE HEAVY DUTY, 7½in. SQUARE COOLING FINS.
16v. 5a., 22/6; 10a., 24/6; 30v. 5a., 37/-; 8a., 43/6; 40v. 2.5a., 27/6; 5a., 50/6; 8a., 57/-, all post 1/-.

BRIDGE CONNECTED FULL WAVE. Special price. 230v. 1a., D.C., 90/-, 17v. 1.25a., 12/9; 2a., 16/4; 2.5a., 21/3; 3a., 23/-; 4a., 26/-; 5a., 27/6; all post free. 33v. 1a., 19/6; 1a., 22/6; 1.5a., 29/6; 2a., 32/6; 3a., 37/6; 4a., 45/6; 5a., 46/6; all post 10d. 54v. 1.5a., 41/-; 2a., 50/-; 3a., 57/-; 5a., 70/-; 72v. 1.5a., 53/-; 2a., 64/-; 100v. 1.5a., 76/-; all p. 1/-.

BRIDGE CONNECTED HEAVY DUTY 7½in. SQUARE COOLING FINS.
17v. 6a., 36/2; 10a., 44/-; 12a., 74/-; 20a., 84/-; 33v. 6a., 60/-; 10a., 75/-; 12a., 132/-; 20a., 140/-; 54v. 6a., 95/-; 10a., 106/-; 77v. 6a., 122/-; 10a., 138/-; 100v. 10a., 200/-, all p. 1/4.

BRIDGE INDUSTRIAL FUNNEL COOL. 17v. 12a., 80/-; 20a., 92/-; 30a., 130/-; 50a., 198/-; 33v. 6a., 73/-; 10a., 84/-; 12a., 132/-; 20a., 152/-; 54v. 6a., 97/-; 10a., 114/-; 72v. 6a., 120/-; 10a., 144/-; 100v. 6a., 168/-; 10a., 202/6, all post 1/6.

VALVE CHARGER REPLACEMENTS. No wiring alterations. Philips & Tungar. 2-12v. 4-5a. Charger Kit, 230 A.C. Vent. Case. Ammeter, £5/10/-, del.

Wholesale & Retail

T. W. PEARCE (Est. 18 yrs.)
66 GREAT PERCY STREET, LONDON, W.C.1
Off Pentonville Rd. Between King's Cross and Angel

AMC

TELEVISION

F. V. D.

FULL VISION DRIVE TUNING SCALE

New 3 colour scale Copenhagen plan now available for immediate delivery.

All Steel **CADMIUM PLATED POWER AND TIME BASE CHASSIS** valve-holders, 3 point and single socket and all necessary cut-outs.

SOUND PANEL CHASSIS ASSEMBLY, fitted with screens, valve-holders, formers and dust cores.

VISION PANEL CHASSIS ASSEMBLY, fitted with screens, valve-holders, formers and dust cores.

9in. C.R. TUBE SUPPORT for mounting on top of Gantry Assembly.

9in. CREAM MASKS.

5, SHAKESPEARE RD., FINCHLEY, N.3
'Phone: FINchley 2180

OPPORTUNITIES IN RADIO

Get this FREE Book!
"ENGINEERING OPPORTUNITIES"
reveals how you can become technically-qualified at home for a highly-paid key-appointment in the vast Radio and Television Industry. In 176 pages of intensely interesting matter, it includes full details of our up-to-the-minute home study courses in all branches of **TELEVISION and RADIO, A.M. Brit. I.R.E., City & Guilds, Special Television, Servicing, Sound Film Projection, Short Wave, High Frequency, and General Wireless Courses.**

We definitely Guarantee
"NO PASS—NO FEE"

If you're earning less than £10 a week, this enlightening book is for you. Write for your copy today. It will be sent **FREE** and without obligation.

BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY
BIET
388s SHAKESPEARE HOUSE
17/19 STRATFORD PLACE, LONDON, W.1

VENTEX CABINETS

have become the accepted standard for first quality 12 in. loudspeakers.

Type 1275 — **12 gns.** Type 1255 — **14 gns.**

• • •

Fit our FULLY COMPENSATED VOLUME CONTROL. Essential for high quality reproduction at low volume levels.

• • •

A range of High Quality Tuners and Amplifiers with an advanced specification will shortly be available. S.A.E. for details.

C. T. CHAPMAN (Reproducers) **Ltd.** FLAxman 3217
RILEY WORKS, RILEY STREET, CHELSEA, S.W.10
Daily demonstrations at Webb's Radio.

1 KW TRANSMITTERS. Two HY [illegible] output, CW. operation, 3.5 Mc. to 15 Mc.
HALLICRAFTERS BC-610 or HT 15, operating over 2 Mc. to 18 Mc. and modified for 27 and 28 Mc. Crystal and VFO on all bands, complete with speech amplifier antenna tuning unit, [illegible] cable and rotor for all bands, set 15 58 is also specially made for 80/10 and new values.
RCA TRANSMITTERS. Type ET-4336 B, 2 Mc. to 30 Mc., 350 W. C.W. 250 W. R.T. Two 813's output. Crystal controlled and modified for VFO. With separate speech amplifier.
50W TRANSCEIVERS. Very compact, weight 110lb. 50W output, 2 Mc. to 8 Mc. or 4 Mc. to 16 Mc. Phone and key. High class superhet receivers. Complete with power pack for 110/200 V.A.C. and two rotary converters for 12V. battery supply. Two sets of aerials-Dipole and complete whip aerial, microphone, spare key, headphones and set of spare valves.
AUTOMATIC HIGH SPEED TELEGRAPH EQUIPMENT "BOEHME" (U.S.A.) [illegible] or wireless.
AR.88 D.; LF.4X (8'x8.2') HRO'S with [illegible] coils.
METAL RECTIFIERS TYPE 7B. Max DC output at 20 V. 10 amps. Supply voltage 200/240 v. Brand new, in original cases.
All above items in excellent working condition. Working demonstration upon request. Ex Valves: 805, 810, 807, 813, 814, 826, 861, 866A, 872A, 816 [illegible] and many others. Large stock of transmitting condensers, crystals, and other components. Alignment and repair of communication receivers and all other amateur equipment undertaken.

P.C.A. RADIO

Transmitter Div.
The Arches Cambridge Grove,
London, W.6. Tel.: RIV 1978

Receiver Div.
270, Holthawk Road,
London, W.12. Tel.: SHE 4946

Rate 6/- for 2 lines or less and 3/- for every additional line or part thereof, average lines 6 words. Box Numbers 2 words plus 1/-. (Address replies: Box 0000 c/o "Wireless World," Dorset House, Stamford St., London, S.E.1.) Trade discount details available on application. Press Day: September 1950 issue, Friday August 4th. No responsibility accepted for errors.

WARNING

Readers are warned that Government surplus components which may be offered for sale through our columns carry no manufacturers' guarantee. Many of these components will have been designed for special purposes making them unsuitable for civilian use, or may have deteriorated as a result of the conditions under which they have been stored. We cannot undertake to deal with any complaints regarding any such components purchased.

NEW RECEIVERS AND AMPLIFIERS

UNIVERSAL ELECTRONIC PRODUCTS, 36, Marylebone High St., London, W.1. Welbeck 4058.
SPECIALISTS in the design and manufacture of high fidelity reproducing equipment from 5-100 watts for domestic or industrial purposes. Our new twin channel amplifier (type U.E.57), with independent bass and treble outputs, provides the most satisfying standard of reproduction we have yet experienced. It is now being demonstrated in our showrooms daily (we close Thursday 1 p.m., Saturday 4.30 p.m.) and we invite those who seek perfection from recorded music to hear this superb instrument. We also offer tuning units or complete chassis designed and constructed to individual requirements.

HALLICRAFTERS dual diversity receivers, complete with power units and loudspeakers; few only available.
McELROY ADAMS MFG. GROUP, Ltd. (Hallicrafters), 46, Greyhound Rd., London, W.6.

12-watt high quality amplifiers, bass and treble boost; £12/10; lists.—Broadcast & Acoustic Equipment Co., Ltd., Tombland, Norwich. [0067

BERNARDS, makers of television, radio, amplifier equipment, available for early delivery, television time-base chassis and E.H.T. supply combined, 5 valves, completely wired, tested, only new components used; £7/12/6.
BERNARDS, 12, Chelverton Rd., Putney, London, S.W.15. Put. 7558. [0097

CHARLES AMPLIFIERS, Ltd., are now able to produce amplifiers, radio units and electronic equipment to specification; enquiries invited for development work and for short production runs.—Charles Amplifiers, Ltd., 40, Kensal Rd., W.10. [0173

NEW amplifier by Midland Radio Coil Products. The Symphonic Seven High Fidelity portable, seven watts of high fidelity reproduction in highly portable form, full bass and treble tone controls, 2-stage N.F.B., high gain; price £10/15/6.—For full details of this and other amplifiers and radio feeders address a post card to 19, Newcomen Rd., Wellingborough. [5616

BUY direct from manufacturers, our radiogram chassis are truly remarkable value: 5-valve all-wave superhet, large fully illuminated glass dial, complete with valves and speaker, aerial tested ready for installation; price £12 inclusive, carriage paid; 2d stamp for illustrated leaflets; trade enquiries invited.—Bayly Bros., 46, Pavilion Drive, Leigh-on-Sea, Essex. [5575

SPENCER-WEST type AC/3 Birmingham or London pre-amplifiers ensure that the very best performance is obtained under difficult reception conditions; expressly designed and manufactured for long-distance reception and employed by the manufacturers themselves for consistent reception under typical difficult conditions; descriptive leaflet, circuit, etc., available on request.
SPENCER-WEST, Quay Works, Gt. Yarmouth.

CONNOISSEUR'S receiver, acclaimed by its users as the finest receiver for the enthusiast and the only one with the following facilities: 9-1,500-metre, world-wide results on highly sensitive 10-valve receiver, comparable with any good communication set, or by change of switch, maximum fidelity reception of local stations on non-superhet receiver with high quality 2-PX4 push-pull amplifier incorporating all refinements, bass and treble tone control (boost to cut), whistle filter and gram input, etc.; basis rebuilt R1155; write for details or call for demonstration. FEEDER units as above, or use with external high-quality amplifiers; R1155 specialists, receivers repaired and re-aligned, also modified as above, or to your requirements; R1155 circuit and values 2/- post free.—R.T.S., Ltd., 5, Gladstone Rd., Wimbledon, S.W.19. Tel. Lib. 3303.

TECHNICALLY far ahead of any other reproducer is the Williamson amplifier; a satisfied customer says: "After searching for 3 months and listening to many other so-called quality amplifiers, I have at last found what I want. The R.T.M.C. version of the Williamson is the finest product of the kind, and workmanship and parts used are unsurpassed. This goes for quality of reproduction, too." We have many other letters in similar strain. There is no doubt the Williamson amplifier will satisfy the most critical quality enthusiast. It is the ultimate choice if you want trouble-free reproduction with super quality. Price £23/10, 7-valve model, £28/10, 9-valve model (with built-in pre-amplifier). See previous adverts. Also "W.W." booklet on this famous amplifier. We are open all day Saturday for demonstrations. Send for details, photos (3d stamp) to R.T.M.C. (Ealing), Ltd., Laurel House, 141, Little Ealing Lane, W.5 (Ealing 6962). [5074

Partridge News

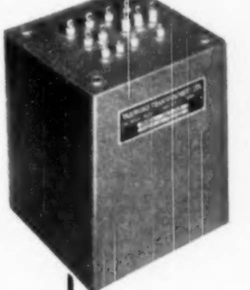

SCREENED

—and hermetically sealed in oil . . . !

REDUCTION of field 40 db at 50 c/s! These are the figures for the Type HS-MU sealed transformer shown above, and are typical of the advantages that these Partridge potted transformers bring. Apart from enhanced electrical efficiency, their performance is consistently maintained under *all climatic conditions* by reason of the permanent hermetic oil seal.

◆

All Partridge Precision Components (both standard and "To Specification") are now available as hermetically sealed units.

★

Fullest details gladly sent on request

PARTRIDGE

TRANSFORMERS LTD

ROEBUCK ROAD, KINGSTON BY-PASS
TOLWORTH SURREY
Telephone: ELMbridge 6737-8

NEW RECEIVERS AND AMPLIFIERS

C.J.R. ELECTRICAL & ELECTRONIC DEVELOPMENT, Ltd., Hubert St., Birmingham, 6 (Aston Cross 2440), the Midlands specialist manufacturers of high fidelity sound reproduction equipment, for the world-famous Williamson amplifier and associated accessories including tone control stages, loudspeaker crossover units, distortionless contrast expanders and radio feeders; send for details and prices. [5473

TELRAD ELECTRONICS, 70, Church Rd., Upper Norwood, London, S.E.19.—Designers and manufacturers of Telrad quality amplifiers; established as the most outstanding value in high-quality amplifiers, thanks to faithful reproduction at unrivalled price, these unique amplifiers are the first choice of the enthusiast; built to satisfy the discriminating ear, bass and treble independent controls, providing widest possible variation to suit all recordings and varying acoustic properties of one room with another; £18 complete; full details on request.—Write, call or 'phone Livingstone 4879. [0019

RECEIVERS, AMPLIFIERS SURPLUS AND SECONDHAND

HRO senior Rx's, complete from £12/10, plus carr.—R.T. & I. Service, 254, Grove Green Rd., London, E.11. Ley. 4986. [0055

20-watt amplifier with built-in radio unit, mic. and gram input, showroom demonstration model; price £29/10.
WODEN TRANSFORMER Co., Ltd., Moxley Rd., Bilston. [5512

HALLICRAFTER SX28A, with panoramic adapter, all in cabinet, hardly used, 230 or 110v a.c., with full instructions; offers near £60.—Box 5276. [5705

SALE, television receiver, aerial, feeder, etc., London or Midlands, stabilised power pack, full sensitivity, bands dih, 34 valves; s.a.e. for details; £35.—Box 5279. [5676

HAMMARLUND super-pro, ex. cond., power pack, two pairs Brown's phones and odd speaker.—Offers to E.ae, "Heurot," Laleham Reach, Chertsey, Surrey. [5648

U.S. Army BC348K communications receiver, converted to mains; short waves up to 18 m/c, 1.5-3.5 m/c range converted to medium waves; £12 or offers.—Box 5242. [5675

£40—Vortexion Super 50-watt amplifier, perfect condition, cost £58/10, under guarantee Feb., 1951; acoustical radio feeder unit, type H.R.1, cost £14, two months ago; cabinet to mount amplifier and feeder unit.—Box 5259. [5669

E. H. SCOTT Hi-Fidelity receiver, 23 valves, 2 chromed chassis, 3 speakers, 35 watts undistorted, 13-2,000 metres, continuously variable selectivity 2-16 kcs, sep. bass control, beat osc., appearance, performance, speaker cones, all as new.—Offers to Box 5070. [5659

SALE of private laboratory: communications receiver BC 348-O by R.C.A., New Jersey, 8-valve (2 R.F., 2 I.F., crystal control), 6 waveband 200-500kc and 1.5 to 18mc, powered by self-contained 24/28-volt D.C. input dynamotor, with instruction manual, used only a few times (less than 2 hours total) as a comparator, otherwise new and unused; £29/10; pair of up-to-date W.S. 38 Mk. III Walkie-Talkie transmitter receivers by M.R. Ltd., 7-9 m/c, range 5-20 miles, according to terrain, in cast aluminium cases, complete with external controllers, double sectional rod aerials, hand-set mic microphones and telephones, also dry batteries; again, used only a few times as comparators, otherwise new and unused; £36/10 the pair; items may be inspected by appointment.—Chesner, Redcroft, Bramhall, Cheshire. Tel. Bramhall 1086. [5706

NEW DYNAMOS, MOTORS, ETC.

BATTERY chargers, 4 models 2-6-12v, 1-2-4 amp D.C.; any mains voltage; also larger types special transformers, chokes, test gear, interior car heaters, etc.—The Banner Electric Co., Ltd., Hoddesdon, Herts. [2212

JANETTE d.c. to a.c. rotary converters, 200/250 volts d.c. input, 200/250 volts, 50 cycles, 1-phase, a.c. output at 300 watts, new, £20, 500 watts, £25; complete with smoothing for television and radio.—Johnson, 319, Kennington Rd., London, S.E.11. Reliance 1412-3.

ALL types of rotating electrical machinery up to 20kva available, including rotary converters, rotary transformers, motors, petrol and diesel-engined generating plants, alternators and d.c. generators. We are also in a position to quote for power transformers; as actual manufacturers we will be glad to quote for any quantity for home or export.
DIESEL Electric generating plants, 3kva, 230v with push-button remote control, starting equipment, ready for use; £195.
ROTARY transformers, input 20v d.c., outputs 6.5v d.c. and 500v d.c., permanent magnet field, 20/-; ditto, input 28v d.c. and 1,200v, 70ma d.c. output, energised field, 35/-; ditto, input 12v d.c., output 500v, 90ma d.c., energised fields, 35/-.
PETROL electric generator plants, comprising a J.A.P. No. 2a single cyl. engine coupled by vee rope drive to an alternator, giving an output of 230v, 50 cycles, 400 v.a., with screened ignition and filtering on generator, eminently suitable for operating television and radio on farms, etc., price £40; such plants can be supplied with various outputs, a.c. or d.c., for other applications.
CHAS. F. WARD, Lordscroft Works, Haverhill, Suffolk. Tel. 253. [0039

DYNAMOS, MOTORS, ETC.—SURPLUS AND SECONDHAND

AS new, electric dynamic wireless converter, 250 dc to 250 ac; offers.—Brookman, 81, College Rd., Epsom. Tel. 9520. [5656

COMPLETE L.P. RECORD SERVICE

Our 18 months' experience of solving the problems associated with L.P. records here and in the U.S.A. is now crystallised into a comprehensive service for you.

We are now stocking the complete range of L.P. records of serious music, and the associated playing desks. Over and above that is the quite unequalled range of Hartley-Turner high-fidelity equipment for reproducing these epoch-making discs with a degree of realism which is quite startling.

You are invited to come and hear what can be got from these discs when they are reproduced with real fidelity; and we shall be happy to supply your needs from a single record to a complete installation.

We are preparing "The reproduction of L.P. records" and this, together with a year's supply of critical reviews of records, will be sent to you for a subscription of 5/-. This is included as a free supplement to our "Selected Record Catalogue," price 25/-, and existing subscribers to the catalogue will get their copy in due course.

This complete service is extended to all our overseas friends. L.P. records can safely be sent by post, and we guarantee complete satisfaction in the farthest corner of the Empire.

Send today for free catalogues and literature, and don't forget "New Notes in Radio," price 2/6, a pocket guide to high-fidelity.

H. A. HARTLEY CO. LTD.
152 HAMMERSMITH ROAD
LONDON, W.6. *RIVerside 7387*

Southern Radio Supply Ltd.
46, Lisle Street, London, W.C.,

have now removed to NEW PREMISES at

11, Little Newport Street, London, W.C.2.

Five Doors from Charing Cross Road and Leicester Square Tube Station.

Telephone Number:—
UNCHANGED—GERRARD 6653.

ALL GOODS PREVIOUSLY ADVERTISED STILL AVAILABLE.

PLEASE NOTE NEW ADDRESS:—

SOUTHERN RADIO SUPPLY LTD.
11, Little Newport Street, London, W.C.2. GERrard 6653.

Five Doors from CHARING CROSS ROAD and LEICESTER SQUARE TUBE STATION.

DYNAMOS, MOTORS, ETC.—SURPLUS AND SECONDHAND

LIGHTING plants new and used, air and deep pipe, press button, or remote control starting; run on petrol, some on T.V.O. (very cheap fuel); also 1.2 and 3½hp new engines; see "Wireless World," July, page 88. Exide and Hart 6v 100-125amp H.Batts, heavy duty, £4, del. £15 for 4, also 72 and 85amp H. 110-250v double wound (not auto), trans. 1kva heavy duty, in steel case, £4 del.; heavy duty rectifier units 115/230/1/50 input 100-120 var. dc out, 2.5-5a; bridge conn. S.T.C. rects, steel case, £10 del.; 200-250v input, 90v dc dc var. tapped output mvc a meter; Westinghouse equipment, fuses, etc., £19 del.; large Devenset 2-circuit charger, two A. meters with resistances, overload switches, 200-250v input, £20 del.; special Westinghouse 200-250 input, 24v charging 26 amp condensers and choke control, full wave bridge rectifier, 3-pole on/off switch (2 ac+dc), 4 fuses, steel case; this is superior H.duty job; transformer same worth more than price asked, £12/10 del.; 1 battery charger by Lodge, 200-250v input, charging up to 50, 2v cells at 2a, S.T.C. rect, full wave, meter, resistance, fuses, steel case, £15 del.; see displayed advert page 56. S.T.C. rectifiers; terms, C.W.O. pro forma invoice or c.o.d. PEARCE, 66, Ot. Percy St., W.C.1. [0014

NEW LOUDSPEAKERS

HI-FI reproducer cabinets and playing desks to metal; stamp, leaflet.—Cabinetware, 1A, Hesse St., Blackburn. [0090

LOUDSPEAKERS—SURPLUS AND SECONDHAND

S.E. DX plus 7 Volt h.c. horn, super 8 cs. H.M.V. 12 p.s. acoustic QA12, cheap.—Box 5278. [5707

£18 Goodmans Axiom 22 high fidelity 20 watt loudspeaker, mounted less reflex cabinet, 1in thick, height 30in, width 22½in, depth 14in, lined 1in felt, light oak finish, cost £27/10 two months ago.—Box 5041. [5871

TRANSMITTING EQUIPMENT

TR9 transmitter-receivers, these were formerly sold at £6 each, the remaining few to be cleared at £5 - carriage paid. THE STAMFORD RADIO Co., 199, Stamford St., Ashton-under-Lyne, Lancs. [4796

HALLICRAFTER transmitters, Type HT4E (BC610) complete to makers' latest specification, covering all frequencies from 1mc to 30mcs, complete with speech amplifier, connecting cables, etc.; limited quantities only now available.

PANORAMIC adaptor, Type MC44, British-made, suitable fitment to any good-class communication receiver, in addition to all Hallicrafter models, immediate delivery.

HALLICRAFTER official sole agents in U.K. including service and spares.

McELROY ADAMS MFG. GROUP, Ltd., 46, Greybound Rd., London, W.6. Tel. Fulham 1802. Cables, Hallicraft, London. [5212

NEW TEST EQUIPMENT

AVAILABLE for early delivery, two-beam pack switch unit, 6 valves, self-contained power pack, variable switching frequency, professional price, £10/14/6, enables two separate traces to be displayed on standard oscilloscope. BERNARDS, 12, Chelverton Rd., Putney, London, S.W.15. Put. 7351. [0096

LABORATORY test equipment, signal generators, oscilloscopes, frequency meter, valve voltmeters, valve testers, megger, etc., by Marconi, Ferris, Clough-Brengle, Collins, Dossett, Ultra, etc.; list available.—Please state requirements to:— R.T. & I. Service, 254, Grove Green Rd., London, E.11. Ley. 4366. [0056

OSCILLOSCOPE and wobbulator complete £20. T.B. s/s 10 to 350,000 c/s X and Y plate amplifiers, easy to handle, has outstanding performance, fully guaranteed, immediate delivery with set leads and instruction. "Oscilloscope Technique"; further details from the manufacturers.—Erskine Laboratories, Ltd., Scalby, Scarborough. [3456

TEST EQUIPMENT SURPLUS AND SECONDHAND

TAYLOR 85A meter, 20,000 OPV, 90 ranges, as new, reasonable offer.—Box 5042. [5874

TAYLOR 240amp pattern gen., little used, as new, £12 each.—Bradley, Hospital Drive, Radcliffe, Notts. [5869

AUTOMATIC voltage regulators for a.c. mains. Ferranti 7.5kva, moving coil, frequency compensated, undistorted output waveform, tapped to suit any nominal supply between 200 and 250v, 1ph., 45 to 60cps, input voltage may vary from 80% to 100% of nominal, output 100%±½%, complete with voltmeter, spares, handbook, brand new in original sealed paper wrappers and export packing cases (for) surplus, offered at a fraction of normal cost; overseas enquiries invited.—P. B. Crawshaw, 166, Pixmore Way, Letchworth, Herts. [5156

SALE of private laboratory.—The following apparatus, all of recent manufacture, is available in condition virtually as new, best offers accepted: Marconi standard signal generator TF 1440, 85kc to 25mc, cost £143; Marconi circuit magnification meter TF 529G, 50kc to 50mc, cost £135; Cossor double beam oscilloscope with attachments, cost £45; Metro-Vick 8.B.2 vacuum leaking pump with filters, cost £54/3; Metro-Vick high vacuum oil condensation pump, type 02, cost £26/15; Edwardes & Co. rotary vacuum pump and compressor, type IV, cost £25/15; Philips high vacuum gauge by Edwards, power and meter units, to 10-2, cost £46/10; Walmall multi-range test meter, model 645, new and unused, cost £14/18/6, also Raven multi-range test meter, 810a, cost £14/14; items may be inspected by appointment.—Chesney, Redcroft, Bramhall, Cheshire. Tel. and Grams. Bramhall 1036. [5710

MICROGROOVE IS *HERE!*

Not "shortly" and not "in the near future"; no waiting lists but IMMEDIATE DESPATCH (if you order promptly) of excellent Microgroove Gramophone Units made by famous British manufacturer, and despatched ready to plug in. For 50-cycle A.C. mains of 100/130 and 200/250 volts; consumption approx. 12 watts. 10in. turntable revolving evenly at 33⅓ r.p.m. Auto stop and start. Lightweight High-Fidelity Magnetic Pickup giving delightfully clean quality. Output approx. 0.3 volt at 1,000 c.s., requiring no pre-amplifier or input transformer with normal amplifier or radio set. Frequency range 30-14,000 c.s. For use with Miniature steel or sapphire stylus. Complete with mounting accessories, tax paid, carriage paid, £7/5/- nett. Limited quantity available, so order now. Also the same model but 78 r.p.m. Mount the two side by side in one cabinet for the ideal playing desk; costs less than a single two-speed job, saves changing stylii, etc., and supplied tax paid, carriage paid, for £13 19/6 the two. Talk to us also if you would like a Microgroove Automatic Record Changer; and, of course, for ALL the high-quality equipment by Hartley-Turner, Wharfedale, Goodmans, A. C. Barker, Vortexion, Decca, Marconiphone, etc., etc. Meanwhile, get organised TODAY for Microgroove—WE'RE ready!

WIRELESS SUPPLIES UNLIMITED
264-266 Old Christchurch Road, Bournemouth, Hants

CABOT RADIO
A New Television Pre-amplifier

Model B. Has an effective gain of 10 times, and an extremely high signal noise ratio. Capable of operating at an input of 5 microV. without showing deterioation of picture quality due to its own generated noise. Uses Mazda 6F1 valve in an up-to-date circuit. Bandwidth 5 mcs. Entirely self-contained, and operates from 200-250 v. A.C. 50 c.p.s. only. Size: App. 4in. cubed. Available for London or Birmingham frequencies from your own dealer.

Price £5.15.0
Including 6F1 valve.

If in difficulty write direct to:

Cabot Radio Co. Ltd.,
28, Bedminster Parade,
Bristol 3
Tel: 64314

GOOD NEWS OF BARKER DELIVERIES

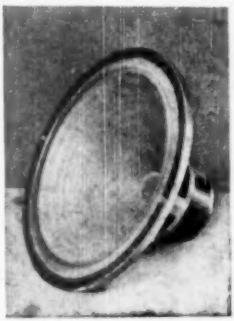

Increased output plus the normal fall in demand which always comes in summer has enabled us to overtake the intake and we are now pretty well level, with both the 148A and 150 almost ex stock. NOW is the time to get ready for the next season's good sound. Apart from the wealth of good music of which we can be sure, there is wide band television sound, which is a revelation of what radio reproduction can be when a really first-class speaker is used. Then we have the new Dec a Long Playing records which combine good recording with a silent surface almost on a par with that of acetate; it is a joy to be able to use the full extreme top response of the 148A and 150 without hearing the usual surface hiss.

NOW is the time to act. Don't wait for the autumn when everyone is calling for speakers and we may again be swamped by the demand.

Please write now for full details and the special summer plan. If you really do want and appreciate NATURAL, pleasing, satisfying sound reproduction you must sooner or later own a BARKER SPEAKER. Why not sooner?

BARKER NATURAL REPRODUCERS

BCM/AADU LONDON, W.C.1.

TEST EQUIPMENT SURPLUS AND SECONDHAND

DEALER clearing surplus stocks offers many bargains in test gear and components; send s.a.e. for list.—Bryan's Radio, west st., Crewe.

TAYLOR Wobbulator, new condition, £10.

O.E.C. Selector, £10; as new commercial television, pre-amp single-stage 6AM6 A.F., £1.—Kingsbury, Providence, Burnham-on-Crouch, Essex. [5677

MARCONI, std. sig. gen., TF144G, £50; Muirhead scope OM5B, £30; Hallicrafter valve voltometer, £6; BPO, £8; Weston circuit analyser, £10; all v. g. condition with handbooks; quality valves, formers, components, etc., worth £25, near offers considered, but prefer see, 50/ £80, or exchange good Leica camera.—Box 5677. [5706

NEW GRAMOPHONE AND SOUND EQUIPMENT

MAGNETIC tape, Emitape type 65 on 1,200ft spool, 25/-; paper tape, 25/-; blank recording disc, 14in d. med., 4/6; all from stock; full trade terms available.—SOUND DISCS (SUPPLIES), Ltd., 178, Bispham Rd., Southport, Lancs. Tel. 8155. [5335

INFINITE baffle corner deflectors, scientifically designed acoustic chambers for 8 to 15in speakers; lists.—Broadcast & Acoustic Equipment Co., Ltd., Tombland, Norwich. [5064

TRANSFORMERS, tone control and loudspeaker filter chokes for all "W.W." circuits; special designs promptly made.—R. Clarke, 30, Langland Crescent, S. Stanmore, Middx. Wor. 5521. [5976

E.M.I. equipment of special interest to amateurs and experimenters at attractive prices; including amplifiers, microphones, loudspeakers; only limited quantities available.—Full details and prices from E.M.I. Sales & Service, Ltd., Amateur Division, Head Office, Hayes, Middlesex. [5714

TAPE recording panels, a precision panel comprising two motors, high fidelity sound and erase head, high speed capstan of unique design giving tape speeds of 7½in and 15in per sec., suspended between ball races with heavy fly wheel to ensure freedom from wow, no unharting of tape is necessary for rewind; panel finished in black crackle, size 14in×12in; £20.

HIGH fidelity tape heads as fitted on our panels, record-playback, £4/4/0; erase heads, £4/10; standard record playback, £1/10; erase head, £1/10; osc. coil, 15/-; head to grid transformers, 7/6; circuits supplied with orders; trade inquiries invited.

MORECAMBE SOUND SERVICE, Sealand Works, Cross Cop, Morecambe. Tel. Heysham 570. [5078

GRAMOPHONE AND SOUND EQUIPMENT SURPLUS AND SECONDHAND

AMBASSADOR table radiogram, as new, a.c. bandspread, £39; new, gramophone, B.T.H. pick-up, £8.—Box 5246. [5692

MAGNETIC sound recording wire, stainless steel, temporary wooden spools, approx. 1½ hours' running time at 8ft per sec., 14/- per spool.—A. Smart, 40, Grange Rd., Halesowen.

H.M.V. angle record player, connoisseur pick-up, £5; 80 records 12in, 25 10in, popular classics, £6; 5 record carriers, 4 x 12in index cards, 22 copies "The Gramophone," £7; all in new condition.—Box 5240. [5670

FOR sale 1948 Fordson van equipped as mobile recording studio, twin Simon recorders, generators, cables, mics., all almost brand new; cost nearly £2,000; offers.—The Rapstone Radio & Recording Co., 44, Fountayne Rd., Stoke Newington, London, N.16. [5584

ONE B.S.R. direct disc recording outfit, as new, comprising one B.S.R. disc recorder and one B.S.R. recording amplifier (type R.1), each in leather covered teak instrument case, one Lustraphone microphone, one B.S.R. microphone transformer (type A.T.57), 50 and 600 ohm tappings, one B.S.R. de luxe telescopic microphone stand; £82.—Cohen & Wilks, Ltd., Derby St., Manchester, 8. [5625

H.M.V. 1604 table autoradiogramophone, list £65, accept £40; Panphonic 25 watt amplifier with playing desk and speaker, list £51, accept £35; two available, also cabinets for above, cost £17, accept £5; all new, guaranteed; television, Pye D167, Bush T91 consoles, secondhand, perfect order £55 each; several H.M.V. reconditioned radiogramophones; send for list.—B.ith, 5 High St., Pinner. Tel. 2666. [5661

NEW COMPONENTS

BRAND new guaranteed goods.

MAINS transformers, fully interleaved and impregnated; primaries, 200-230-250v, 50 cycs, screened; drop through types, half shrouded, 260-0-260v, 70ma, 6.3v 2a, 5v 2a, 12/11; 350-0-350v 70ma, 6.3v 2a, 5v 2a, 14/11; 250-0-250v 100ma, 6.3v 6a, 5v 3a, for 1355 converter, 22/9; 250-0-250v 70ma, 6.3v 2a, 5v 2a Midget, 14/-; 350-0-350v, 15/6; fully shrouded upright mounting types, 350-0-350v 100ma, 6.3v-4v 4a, C.T. 0-4-5v 3a, 21/9; Midget, 3-1-2½v/in, 250-0-250v 60ma, 6.3v 2a, 5v 2a, 15/6; 350-0-350v 150ma, 6.3v 4a, 5v 3a, 27/9; small filament trans., 200-230v input, 0-4-6.3v 2a output, 7/6; full range of mains trans. in stock; smoothing chokes, 60ma, 15h, 2000ohm, 4/5; 80ma 12h 350ohms, 5/5; 100ma 10h 500ohms, 5/9; 100ma 10h 100ohms, 7/6; 200ma 5h 100ohms, 7/6; Clix 1nt. octal valve holders, 2/11 doz. 25/- gross; T.V. focus coils, 9/6; T.V. 9in cream masks, 7/6; electrolytics, 8mfd 450v tubulars, 1/11; 8-8mfd 450v small cans, 2/9; 8-16mfd 450v cans, 3/3; 8-24mfd 350v cans, 2/3. Morganite vol. controls, 5 meg with D.P. switch, long spindle, 5/9 ea. or 2/11 ea. in doz. lots; c.w.o. or c.o.d. over £1; post free over £2; bargain list 3d, special lists for trade 3d.—Radio Supply Co., 13, Queen Square, Leeds, 4. [5088

L·R·S

FOR PROMPT & EFFICIENT SERVICE

CASH OR EASY TERMS

ARMSTRONG

ALL WAVE CHASSIS

(incl. speaker and output transformer)

Model EXP 83/3. Cash **£18/17/1**, or **£5** with order and 10 monthly instalments of **30/-**.

Model RF 103/3. Cash **£25/12/6**, or **£5/10/-** with order and 11 mon. inst. of **40/-**.

Model EXP 125/3. Cash **£47/16/-**, or **£11/10/-** with order and 10 mon. inst. of **£4**.

Model EXP 119 (less speaker). Cash **£43/19/7**, or **£10** with order and 12 mon. inst. of **62/-**.

We specialise in Armstrong Chassis. See maker's advert. on page 67.

LEAK & GOODSELL AMPLIFIERS AND TUNERS SUPPLIED ON EASY TERMS

LOUDSPEAKERS

Wharfedale W.2/CS 12in. less transf. Cash **£7/10/-**, or **£2** with order and 6 mon. inst. of **20/-**.

Goodmans, the new Axiom 150 (less trans.). Cash **£8/8/-**, or **£2** with order and 7 mon. inst. of **20/-**.

Other models supplied on similar terms, including Hartley Turner.

COLLARO

RECORD CHANGER

R.C. 500 with crystal pick-up. Cash **£10/15/-**, or **£3/12/-** with order and eight mon. inst. of **£1**. All other Collaro R.C. units and Record changers available on similar terms.

RADIOGRAM UNITS

A.C. 505 M.B. Cash price **£7/6/3** or **£2/2/-** with order and six monthly inst. of **£1**.

Full particulars with leaflet of any of the above on request. Kindly enclose stamp.

•

THE LONDON RADIO SUPPLY CO.

Est. 1925

BALCOMBE, SUSSEX

-towards perfection-

L. P. RECORDINGS

Demand a first-class PICK-UP!

LOWTHER DIAMOND MOVING-COIL answers this requirement £18 plus P. Tax

Or second best

LOWTHER WHITE SAPPHIRE MOVING COIL £7-7-0 plus P. Tax
(Lic. Pat. No. 439,028)

Pick-up Equaliser Units and De-emphasis Units (for L.S. lead) available for control or compensation

Further details:—

THE LOWTHER MANUFACTURING CO.

(The Laboratory Production Unit)

Lowther House, St. Mark's Road, Bromley, Kent RAV. 5225

EASY RADIO

Have you observed from our previous ads. how you can build radios the **easy** way and save money? Our range of **completely** prefabricated chassis are punched for **all** components. These—and our unique Construction Sheets and Tuning Units—enable **anyone** to build a variety of domestic receivers, feeder units and amplifiers with the sure knowledge that failure is impossible! Two examples from our range:

- 5 v. prefabricated chassis, size 12in. x 9in. x 2½in. ... 10/6
  "Easy-as-A.B.C." Construction Sheets, (A.C. or AC/DC) per set* 3/6
  No. 1 Tuning Unit (comprising model 30 3-waveband superhet. coil pack, pr. "MM" I.F.T.'s, 8in. x 6in. dial and 2-gang condenser—the whole aligned and sealed) ... 54/9 inc.

  leaving only valves and small components (which we can supply) to complete a factory designed receiver.
- 6 v. prefabricated chassis, size 12in. x 9in. x 2½in. ... 11/6
  Construction Sheets* ... 3/6
  No. 2 Tuning Unit (comprising model 40 3-waveband superhet. coil pack with R.F. stage, pair of "MM" I.F.T.'s, 8in. x 6in. dial and 3-gang condenser—the whole aligned and sealed) ... 86/3 inc.

  leaving only valves and small components (which we can supply) to complete a factory designed receiver, whose performance has been widely acclaimed second to none.

*FREE with all orders over £5.

Send 1/6 for your copy of the New "Home Constructor's Handbook" for all the "gen" on how to construct these, and many other receivers and amplifiers, etc. All standard radio lines in stock at current prices. Send us your enquiry or order marking it "W.W." for special attention. Mail Order Only.

RODING LABORATORIES
79 LORD AVENUE, ILFORD, ESSEX.

NEW COMPONENTS

CRYSTAL Microphone Inserts (Diamond) D/Mc-41, guaranteed brand new, 15/9 post free.
RADIO-AID, Ltd., 29, Market St., Watford, Tel. Watford 3869. [3169

HIGH quality mains and output transformers available in quantities large enough to be of interest to manufacturers.
12 Watt Mains Transformers. Primary, 110, 210 or 250 volts. 50 cycles. Sec. 1: 6v 4a. Sec. 2: 4.5v 2a. Sec. 3: 450v C.T. 150ma from rectifier. Frame, 2½in Stack Hole No. 6 stampings.
40 Watt Mains Transformers. Primary, 110, 210 or 250 volts 50 cycles. Sec. 1: 6.3v 2a. Sec. 2: 5v 3a. Sec. 3: 5v 2a. Sec. 4: 450v C.T. 60ma. Sec. 5: 950v C.T. 180ma. Frame, 3¼in stack. M.E.S. No. 19A stamp.nos.
15 Watt Output Transformers: Suitable for a five push-pull output stage. Sec. 1: for 600ohm line. Sec. 2: 15ohm and 4ohm. Frame, 1¼in Stack Hole No. 4 laminations.
40 Watt Output Transformers. Primary: Suitable for EL.37 valves in push-pull. Sec.: 15ohm and 4ohm. Frame: 1¾in Stack Hole No. 6 laminations.
ENQUIRIES to:—A. Kershaw & Sons, Harehills Lane, Leeds 8. Tel. Leeds 44601, ext. 15.

EHT Transformers, mains transformers, output transformers and chokes, open or boxed types; transformers designed to individual specification; samples of it impressive.
WILLESDEN TRANSFORMER COMPANY, Ltd., 701 Harrow Rd., N.W.10. Ladbroke 2686. [0075

YOU are bound to try an Osmor "Q" Output pack eventually and be delighted with the results; why not save time and money now? Send a stamp for free circuits and latest lists of coils, output packs, dials, etc., etc.
OSMOR RADIO PRODUCTS, Ltd. (Dept. W.C.A.), Borough Hill, Croydon, Surrey. (Tel. Croydon 1220.) [0046

TRANSFORMERS, 450watt, auto, 230/110, 20lb 50/-; ditto 1,200watt in metal cases £6/10/-; 15 trans. 250v imp., 24v 4.5a, out 35/-; rectifier for 10a at 4amp for same 37/6; 40ohm worm-drivesliders, 5 amp 18/6; Rola sin p.m. spkrs, less trans. 18/6; Lustraphone m.c. mikes 52/-; 2v trickle charger trans. and rect. 12/6, add postage; all goods new.
CHAMPION PRODUCTS, 43, Uplands Way, London, N.21. Tel. Lab. 4457. [0100

SPENCER-WEST type AC/4 Birmingham/London convertor unit, permits a London type receiver to be employed for the reception of Birmingham without alterations of any kind; the first and best convertor unit employing as it does 2 separate tuned oscillators, thereby ensuring correct reception of the single sideband Sutton Coldfield transmitter; illustrated leaflet available on request.
SPENCER-WEST, Quay Works, Gt. Yarmouth.

BEL television—"Wireless World" superhet teleptor, superior components for a superior receiver. To specification: Set of 20 coils £2/6; L. M. or Home Moss line transformers, non-centre formers 42/-, 6kv Westhet EHT rectifiers 48/-; 4 deflector coils mounted, 35/-; focus coil 37/6; P.M. focus rings, 25/-; blocking trans., 15/-; main trans., 77/6 and 90/-; copper RF and wound IF strips, with waveholders and screening boxes, assembled, 52/6; ECSE valves, 8/6; wire pots, condensers, etc. This set can be made for about £52 only; constructional book 2/6.
COILS: Midland VM, SE, and PW TRF coil sets, all with video chokes 18/6; pre-amp coils, formers, paxolin polytherene tube, test oscillator coil sets, iron core line transformers, and chokes, chassisware and made to measure coils; Williamson tuner coils, 7/6 pair; superhet L.M.S. coils, iron cored, 2/6 ea., ditto 10/6 share.
TEST equipment: 2-TF 517 SSG, £35 ea.; Salford 106 5-400mc/s, incomplete, £15 ea.; 10cm wavemeter Marconi, Pullick audio source, 2 Y-meters.
MANUFACTURERS, wholesale and trade enquiries invited.
BEL SOUND PRODUCTS Co., Marlborough Yard, London Arcade, N.19. Archway 5076.

54/9 only for the famous Model 30 tuning unit, consisting of 3-waveband Model 30 superhet coil pack, pair I.F. transformers, 2-gang condenser and attractive dial (8in. x 6in.); each component individually selected pre-aligned, sealed and the whole matched together as a unit; the superhet you build with this unit needs no further adjustment! Or supplied instead with the superb J.B. horizontal 3pin wheel tuner and dial assembly at 75/6. Full details of these and our other high quality products (coils, IFT's, mains transformers, etc.), together with many circuits and constructional tips, contained in the latest edition of the "Home Constructor's Handbook," price 1/6. Mail order office.
SUPACOILS, 98, Greenway Ave., London, E.17.

RADIO hardware in 1/- packets: 5-pt tag strips, mounting boards, fuse holders, spindle couplings, eye leads, 2, 4 or 6BA nuts, chassis-mount bits, 2, 4 or 6BA studding, Grommets, solder tags, pin tags, spade tags, tinned copper wire 16, 18, 20 or 22swg, sleeving 1, 1½ or 2mm., resin cored solder, 14/6, single 7w 18 colours; single or twin screened flex. Ae/E socket panels, voltage panels, indicator lamps ruby*, jack plugs*, jack sockets, 3amp plugs, DC adaptors, flex connectors, flexible couplers, grid caps, octal or Nuvistor, insulated tape, insulated staples, co-ax wiring clests 7/6, pointer knobs, plain knobs. All marked * in generous 1/- packets (* these items 1/- each). 12 packets 10/6 (inc. box). 20 packets £1 post free. Any type or assorted as you wish. See our lists, free on request for many other items.
FRITH RADIOCRAFT, Ltd., 69-71, Church Gate, Leicester. [0024

Improved 'High Fidelity' Results. Obtainable at

HOLLEY'S RADIO STORES

285, CAMBERWELL ROAD, S.E.5 Phone RODNEY 4988

By the new MICROGROOVE EQUIPMENT
DECCA L.P. UNITS & PICK-UPS
ACOUSTICAL new "QUAD" special AMPLIFIER
LEAK AMPLIFIER PICK-UP and TUNER
VORTEXION "STEREOPHONIC" & ACOS "GP20" PICK-UP
WILLIAMSON AMPLIFIERS & TUNERS by GOODSELL
SOUND SALES "TONEMASTER AMPLIFIER" & DX TUNERS
CORNER SPEAKERS by WHARFEDALE, TANNOY and DECCA
GOODMANS "AXIOM," W. B. "STENTORIAN" and BARKER SPEAKER UNITS
ARMSTRONG R.F. 103,3 and EXP 83 3 CHASSIS
TWO-SPEED ELECTRIC MOTORS, also
BRIGGS new Edition of "SOUND REPRODUCTION"

Demonstrations every evening until 6 p.m. except Thursday.

LABORATORY TEST EQUIPMENT

High Grade test equipment GUARANTEED equal in every way to the maker's specification. We offer only New or rebuilt instruments, recalibrated if and where necessary.

WAVEMETERS by R.C.A., Type TE.149. Frequency range 200 Kc/s. to 33 Mc/s., by harmonics. Directly calibrated dial from 2.5 to 5 Mc/s. Scale length 9 feet. Absolute accuracy 0.02 per cent. Crystal accuracy 0.005 per cent. Supplied with instruction book, spare valves and components in a well fitted transit case. Battery operated. NEW £14.

CONSTANT VOLTAGE TRANSFORMERS by Advance. Type MT143 input 190-260 v. Output 230 v. ± 1 per cent at 150 W. Also MT161 as above, except that output is 60 W. These transformers are in new condition.

TINSLEY GALVANOMETERS. Complete with light source. Various sensitivities from ± 2 — ± 7μA, in polished wood cases. Condition as new.

BEAT FREQUENCY OSCILLATOR. Type 195L by Marconi Instruments. Condition absolutely as new.

UNIVERSAL IMPEDANCE BRIDGE. Type TF373D by Marconi Instruments. Condition as new.

Also in stock we have valve voltmeters, wavemeters up to 1000 Mc/s. Precision attenuators, Signal generators type TF 144G, & TF 390F Oscilloscopes type Ultra Mk. II. Send for lists.

HATFIELD INSTRUMENTS

175, UXBRIDGE RD., HANWELL, LONDON, W.7.

Telephone: EAL 0779

A WINDOW WORTH LOOKING INTO

Television. Receivers Type 3585 complete with 45 mc/s. strip using 5 EF50's Diode and Cathode follower, together with a further 2 EA 50's, 1 EF 50, 4 SP 61's, 5VR 56, 3VR 55, 1 VR 3, 1 VR 54, also stacks of resistors condensers, 2 5,000 ohm relays and 2 1,000 ditto. These units are brand new in sealed cases and cost only **£5/10/-**.

Television. I.F. strips only. Ex the above Units, complete with 6 EF 50's, 1 EA 50, also brand new and unused, **62/6** each. Ditto less valves, **£2**. Limited number only.

Television. Units type 208a, 2 stage as above with 2 EF 50's, ideal as sound or vision units, **15/6** each.

Television. Brand New R 1355 Receivers, complete with valves as used in the "Inexpensive Televisor" suitable for London or Sutton Coldfield, **59/6** each.

Television. "Responser" Units 10 valve 1½ metre Superhet ideal for conversion for both Sutton and London, complete with all valves **45/-** each. Limited number only.

Television. Power Packs. Ex-Admiralty. 230 volt 50 cycle input, output 2,500 volt 5 m/a. 350 x 350 volt 200 m/a. 6.3 volt 15 amps. Fully smoothed and supplied complete with all valves **92/6** each.

Television. Coils wound on 1in. x ⅜in. polystrene with slugs single hole fixing, **6d.** each.

Television. Condensers, 1,000 pf. and 500 pf. midget moulded mica **4d.** each. High voltage types, 1,000 pf. moulded mica 5 kv., **1/3** each. 1,000 pf. ceramic, 9 kv, **1/3** each.

Television. Diode Holders, **3d.** each. High Voltage Valve tops fully insulated, **6d.** each. High voltage Sleeving **3d.** per length. High voltage Cable **1/9.** 12 yards.

Television. High Voltage .1 mfd. Condensers, oil filled Mansbridge type "Trouble Free", 1 mfd. 3kv. **2/-** each. .1 mfd. 4kv. **3/-** each. .1 mfd. 5kv. **3/3** each.

Television. Iron cored slugs for Aladdin formers, also for 1355 receivers, type 24, 25, 26, 27, U.H.F. units and 1155 receivers. **2d.** each.

Television, or 'Scope Transformers. Input 230 volt, 50 cycle. Output 700 volt, 20 m/a. 4 volt 1½ amp. twice with 5,000 volt insulation test ideal for voltage doubling. Ex-Admiralty brand new and boxed **17/6** each.

Chokes. L.F. 200 m/a, 5 henry, D.C. resistance 100 ohm., **3/6** each. 40 m/a, 25 henry resistance 1000 ohm, **4/6** each. 100 m/a, 1 henry 12 ohm resistance, **3/-** each.

BC 522. Transmitter modulation Transformers, limited number only **6d.** each.

AR.88. Complete Switch assembly with screening, for L.F. and D. models, brand new and boxed, **17/6** each.

All these special bargains of ours go very quickly. Don't be disappointed, send your order now without delay.

Open all day Saturday

G. W. SMITH & CO.
(RADIO) LTD.
3, LISLE STREET, LONDON, W.C.2
Phone: GERrard 8204.

NEW COMPONENTS

ELECTRONICS.—Write to the firm which specialises in electronic equipment for your requirements in relays, valves, thyratrons, photocells, electron multipliers, special c.r.t., image converters, selsyns, velodynes, etc., as well as all components.
J. McMILLAN, 5, Oakfield Rd., Bristol, 8.

COMPONENTS—SURPLUS AND SECONDHAND

WALTON'S OF WOLVERHAMPTON.

SPECIAL Summer Clearance Bargain List now available, prices cut by half! Send S.A.E. today to Walton's Wireless Stores, 203, Staveley Rd., Wolverhampton. [0061

SELENIUM metal rectifiers, various voltages at 4 amps or over available, state requirements.—WILFLO PRODUCTS, 222, Gorbals St., Glasgow, C.5. [5708

SOUTHERN RADIO SUPPLY, Ltd., 11, Little Newport Street, London, W.C.2. See our displayed advertisement page 58. [0016

ALLEN & GOULD, 5, Obelisk Parade, Lewisham, S.E.13, offer the following goods new and unused, unless otherwise stated:—
MAT resistors, 100ohm, 250w, 1/9; 350ohm, 250w, 1/6; SBC neons, 200-220v, resistor in cap, 2/-; SBC holders (cord-grip), 6d; Muirhead slow-motion dials (as on R1224), 6/-; mains transformers, PRI 0-200-220-240sec, 250-0-250v at 80ma, 6.3v at 3amp, 5v at 2amp, 11/6; .01 MFD 5kv wkg, 1/6; Jones P. and S. 6w 1/6, 8w 1/9, 10w 2/-, 12w 2/6; B & L P & S. 7-p 1/9, 10-p 2/-; Pye co-axial P & S, straight 1/3, angled 1/-; Pye co-axial connections 6d; Pye T pieces, 6d; rotary transformers, 24v in, 300v 150ma and 150v 20ma out, 12/6; rotary transformers, 14v in 600v at 140ma out, 17/6; switches (oak, Yaxley type, etc.), SP 3w 6d, SP 10w 1/9, 6w parallel 6d, 5-p 3w 1/-; toggle switches, laminated bakelite, stripped from unused equipment, SP on-off 1/-, DP on-off 1/3, DP DT 2/-; toggle switches, black bakelite, new, SP DP 1/-, DP on-off 1/9; 2in FCD 500ua cal 0-15, 0-600v, used, tested surplus, 4/-, 2in 0-300v d.c. 5/6, 2in 0-50ma d.c. 5/6, 2½in 0-25a d.c. MI 5/-; selenium rectifiers, heavy duty, 160v 600ma, 9/-; low-resistance phones with headband, lead and plug, 3/3 per pair; deaf aid type phones with two spare insets, 7/6 per pair; magnetic throat mikes, 1/9 per pair; dimmer switches for lamps or as extension speaker volume controls, 9d; crystal diodes, CV 102, IN 22, 3/3; volume controls w/w 5ohm, 50ohm, 500ohm, 1k, 5k, 8k, 10k, 15k, 20k, 25k, 35k, 50k; carbon 500ohm, 3k, 10k, 20k, 50k, 100k, 150k, 250k, 500k, 1m, 2m, 3m at 1/9; double carbon 500k+500k, 2/6; double w/w 2.5k+2.5k, 3/-; ceramic air spaced trimmers 3/30 pF, 4d each, 3/6 per doz, 24/- per 100. Special offer to hams: P.O. racks, 19in wide × 5ft 6in high, only 20/- each, carriage forward, limited number, so order now.
ALLEN & GOULD, 5, Obelisk Parade, Lewisham, S.E.13. Tel. Lee Green 4038. [5465

DEALER clearing surplus stocks offers many bargains in test gear and components; send s.a.e. for list.—Bryant's Radio, West St., Cromer.

RELAYS G.P.O. type 600, unused and boxed, 310 plus 310 ohms, 4 C/O, 400 plus 5.5 ohms, 4 C/O, 600 ohms, 2 C/O, all 5/- each.—Box 5237.

FOR disposal, several mains trans. by Bryce, Portminster, Radiospares, etc.; all unused; accept half list price, stamp detail.—Strange, 2a, Eastern Rd., London, E.17. [0073

SERVO-CONTROL equipment, Magslips, Selsyns, Velodynes, etc.—Hopton Radio, 1, Hopton Parade, Streatham High Rd., London, S.W.16. Tel. Streatham 6165. [0049

RELAYS (miniature) coil 14ma, 1,000 ohm, contacts 1.5amp S.P.C.O., 2/9 each; condensers (baby can) 8mf 450v, 1/- each.—K. Packer, 76, Spencer Rd., Harrow, Middx. [5694

"YOU'LL probably get it at Smith's, Edgware Rd.!" Everything for the constructor, from a 1/10watt resistor to a radiogram cabinet, lowest prices, biggest variety.—Near Metropolitan Music Hall. Pad. 5891. [8005

INDICATOR units type 184A, fitted 3in and 6in cathode ray tubes, type A.C.R.10 and V.C.R. 517B, and 17 valves, viz., 6 R.92, 5 V.R.91, 3 V.R.54, 3 V.R.65, metal rectifiers, chokes, transformers, potentiometers, resistances, condensers, etc., £3/10 each, carriage 10/-.
SIEMENS high speed relays, 75ohm double coil, 4/6 each, 45/- per doz; tuffnel jockey pulleys, 2in diam., fitted ball race for ¼in diam. spindle, 2/- each, 20/- per doz.
PERFORMANCE meters type No. 2, fitted standard mains 230 V.A.C. 50 cycle power pack, 2 V.R.91, 1 V.R.137, 1 5Z4G, 1 C.V.51, 1 V.R.92 and other useful components, £2/5 each, carriage 5/6.
EXTRACTOR motors, complete with fan 12v, 3½amps D.C./16 volts A.C., new in original packing, price 17/6, postage 1/6.
G.E.C. chokes, for use with mercury vapour electric lamps on 200/250 volts, 50 cycles supply, rating 400 watts, 30/- each, special quotation for quantities.
SOLENOIDS, fitted cantilever action, operating voltage 10/12 volts D.C., these are new dimensions, 3in long, 1in diam., price 5/6 each, post paid. Ditto, 5¼in diam., 3/- each, 30/- per doz.
B.T.H. compressors, fitted cut-out at 300lb. ¼hp motor would drive same, C.F.M. 368, ideal for garage and workshop, condition as new, price 30/- each, postage paid.
NEW Rolls-Royce "Coolant" pumps with tower, inlet 2½in diam., twin outlets, 1½in diam. approx., aluminium casing, brass impeller, pumps approx. 500 b.h.p., price 30/- each, carriage paid.
A large assortment of various ex-W.D. radar and radio equipment, relays power packs, oscillograph units, gears, photographic apparatus, available, s.a.e. for lists.
H. FRANKS, 58, New Oxford St., London, W.C.1. Tel. Museum 9594. [0057

Surplus Bargains!

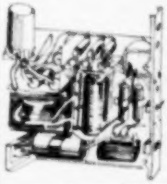

VIBRATOR UNIT 21. Store soiled, but containing electrolytics, resistors, condensers, chokes, metal rectifiers, transformer and vibrator, etc. **7/6**.

MIDGET ACCUMULATORS. Made by famous manufacturers, 2AH capacity. ONLY **2/6** each or **£1** dozen.

MERCURY BATTERIES, as reviewed in "Wireless World" May 1948. 94v. H.T., 1.3v. L.T., **5/6** each; 94v.-63v. H.T.s, 1.3v. L.T., **7/6** each.

MIDGET MOTORS, 3½in. long, 1¼in. dia., 1/133 H.P. on 27v., these will operate from 12v. D.C., from 110v. A.C., or from the mains with a suitable dropper. **9/6**.

TRANSFORMERS. Modulation transformers which may be used as mains auto-transformers (230-115v.) handling some 75 watts, **5/-**. Input transformers, with 2 very heavy windings (one tapped low resistance) which may be used as small mains transformers or heavy duty output transformers, **3/9**.

FIELD TELEPHONES. Of American manufacture, with bell, ringing generator, and standard type handset, in first-class condition. Webbing cases, **37/6**. Solid leather cases, **45/-**.

RECEIVER 18. Covering 6-9 m/cs., and complete with 4 battery valves, circuit, connecting data, and batteries, **25/-**.

RECEIVER 21. Covering 4.2-7.5 and 18-31 m/cs, and complete with 9 battery valves, circuit, connecting data and super capacity all-dry battery, **42/6**.

STATIC LIMITERS. These plug into the low impedance output circuit of any receiver. Fitted with jack-plug and socket, **3/9**.

PANELS, containing two .12, 450v., one .01 350v., one .1 600v., one 8 mfd. 150v. condensers, one L.F. choke, one valveholder, etc.; these are new and individually boxed. ONLY **1/9**.

CONDENSERS (new—not stripped). Tubular: 75 mfd. 12v., **12/6** doz.; .05 750v., **1/9** doz.; .25 350v., **1/9** doz.; Mica: .00002 2,000v., **2/-** doz.; .001 1,000v., **2/-** doz.; .0002 2,500v., **2/6** doz. Electrolytic: 25 mfd. 25v., **12/6** doz.

BRAND NEW 1355's. The ideal Television conversion unit, with 11 valves. These are in original maker's crates, but may have discoloured metalwork due to long storage. OUR PRICE, **55/-**, plus 7/6 carr.

CASED SPEAKERS. In attractive 9in dia. metal cases, with transformer for 2.5 or 15 ohm input. ONLY **19/6**.

RECEIVER TYPE 25. One of the best known sets for converting into a domestic receiver. With six valves (6.3v.), pair 460 k/cs. I.F.T.s and a host of resistors, condensers, etc. ONLY **22/6**.

RADIO EXCHANGE CO.,
9, Cauldwell Street,
BEDFORD. Phone 5568

All goods sold as used unless otherwise stated.

THE MODERN BOOK CO.

Television Servicing. By Hellar & Shulman. 47s. Postage 9d.

A Portable Televisor. By E. N. Bradley. 3s. Postage 2d.

The Radio Amateur's Handbook 1950 Edition. By A.R.R.L. 20s. Postage 9d.

Personal Portables. By E. N. Bradley. 2s. 6d. Postage 2d.

Cathode-Ray Oscillographs. By J. H. Reyner. 8s. 6d. Postage 4d.

Radio Receiver Servicing and Maintenance. By E. J. G. Lewis. 8s. 6d. Postage 6d.

The Cathode-Ray Tube Handbook. By S. K. Lewer. 4s. Postage 3d.

The Magnetic Amplifier. By J. H. Reyner. 15s. Postage 6d.

Wireless Amplifier Manual, number 2. 3s. Postage 2d.

Loudspeakers. By G. A. Briggs. 5s. Postage 3d.

Radio Valve Data, compiled by "Wireless World." 3s. 6d. Postage 3d.

References Data for Radio Engineers. By W. L. McPherson. 5s. Postage 4d.

Radio Handbook, 12th edition. By Editors and Engineers. 25s. Postage 1d.

Radio Receiver Design. By K. R. Sturley, volumes 1 and 2. 20s. each. Postage 9d.

The Technique of Radio Design. By E. E. Zepler. 25s. Postage 9d.

We have the finest selection of British and American radio books in the Country. Complete list on application.

19-23 PRAED STREET
(Dept. W.8)
LONDON W.2
PADdington, 4185

"You can rely on us"

FOR CLEAR COMPONENTS AT COMPETITIVE PRICES
IMMEDIATE DISPATCH

MIDGET COIL-PACKS

These are an ideal miniature Coil-Pack especially suited where space is limited. They consist of iron-cored miniature coils for both Aerial and Oscillator stages, built-in Wavechange switch and midget trimmers. They are intended for an I.F. of 465 Kc/s and I.F. Transformers type RS/GB 465 (12.6d. per pair) are the ideal companions for a trouble-free superhet.

TYPE "R"
MW/LW/GRAM Ranges 200-550 metres, 800-2,000 metres.
SIZE: Length 2½in. Width 1⅝in. Depth 1½in.

TYPE "S"
MW/SW/GRAM Ranges 200-550 metres, 17-50 metres.
SIZE: As Type "R."

TYPE "C"
LW/MW/SW Ranges 800-2,000 metres, 200-550 metres, 17-50 metres.
SIZE: Length 3½in. Width 1⅝in. Depth 1½in.

TYPE "R" and "S" each 25/-, TYPE "C" each 28/6. Post 6d.

All coils enclosed—All iron-dust cores adjustable. Completely wired, only five connections needed to external circuit.

Catalogue with Data, 3d.

RADIO SERVICING Co.
646, Wandsworth Road, London, S.W.8
Phone: MACaulay 4155.
TT, 17A, Bus: 28, Train, Wandsworth R.L.S.R. Station.
Open 9.0 6.30 p.m.

COMPONENTS SURPLUS AND SECONDHAND

RADIO CLEARANCE, Ltd., 27 Tottenham Court Rd., London, W.1.

COMMUNICATION receivers R21B, made by Marconi Wireless Telegraph Co., coverage 1.200m.-1500-15 miles, in 4 bands, turret switched coils, 50-division dial, calibrated all bands, a 6-valve super with 2-RFs (KTW63 R.F., mixer (X65), 3-IFs (KTW63's), DET and LF (DH63). B.F.O. (KTW63), output KT63, all stages metered, by switching fitted 230v 50~ L.T. transformer, but H.T. is required, precision job, size 22½x15x14in, supplied brand new, complete with circuit diagram and individual test reports, but less valves, at £9/19/6, plus 10/- carr.

50w MODULATORS, complete with power supplies, 0-110v-230 250v, 50c/s, 8 valves, 6C5 into 6C5's push-pull, into push-pull 807's, 5 rectifiers, paper smoothing condensers throughout, jacks for key, mike and line, the power unit gives 500v 200ma (d.c. smoothed) and 4.5v 3a. In addition to supplying the modulator, complete outfit, with circuit diagram, in metal case (21in rack mounting panel), contained in solid oak case, with carrying handles, no mod. transformer, £12/10/- carr. paid.

SUPER mains transformers, 420-550-575-0-575-550-420v, 250ma may be drawn from inner (575v) taps, and 200ma from either of the outer taps, simultaneously, 5v 3a 1w/ow is available for the rectifiers, enclosed, 3in. 6¼x5¼x5¼in, weight 24lb, by Parmeko, primary 230v 50c/s, 59/6, carr. paid; super chokes by Parmeko, 10 henries at 650ma, res. 50Ω, 7in.x5¼x5¼in, weight 34lb, fully enclosed, £4/5/- carr. paid.

PERSONAL receivers, 3-valve T.R.F. receivers, using I.T.4s, contained in handsome bakelite case, with lift-up lid, size 7x6½x5in, with lid closed, plastic carrying handle, frame aerial in lid; these receivers cover the medium waveband and operate from self-contained dry batts., standard types, W1455 and U2, output to a pair of lightweight high res. phones, complete, 2-M. tuning and reaction, opening lid switches on, supplied brand new, with valves, batteries, phones, an ideal set for many purposes, invalids, hosp. patients, etc., these receivers are not used surplus and are offered ready to play, £3/19/6, carr. paid. chassis (alone), 5x9½x5½in, drilled 4-button base holes, 1/9. 5x9x1½in, drilled 7-button base holes, 2/-. All 17x9½x2½in, drilled 7 int. oct. and square, open ends, 5/3. E.H.T. trans. 4kv, 10ma, 2v 2a, 4ma, 2½, 230v, 50~, gives approx. 3,500v with usual smoothing, 29/6, smoothing chokes, SH 200ma 100Ω 4/11, SH 200ma 100Ω 5/6; electrolytics, 8mf 450v 2/3, 8+32 450v Can 4/-, 16+8 350v Can 3/-, 15+15 450v+20mf 25v Can 4/6, 32mf 350v Can 4/-, 32 450v Can 5/-, 60+100mf 350v Can 5/-, 16+8 double-ended Can 450v 3/-, 25/25v 1/3, 25/50v 1/3, 50/25v 1/6, 100mf 12v 1/-, 50/12v 9d, 500mf 15v Can 2/-, 50+80mf 450v+20mf 25v Can 4/6.

P.M. SPEAKERS, 5in. less trans., 9-11; 6½in. less trans., 10/11, 10in. with trans. P.P. 4,500Ω, 21/-; outputs trans. 2,000/2Ω, 2,500-2Ω, 2,750-2Ω, 3,000-2Ω, 6,000-2Ω, 7,000-3Ω, all at 5/-; heavy duty, 7,000/2Ω 5/6, 3 ratios 7,000-3,500-1,750-4Ω 4/-; switches, standard size, 2P 4W 5B 2/6, 1P 10W2B 2/6, 2P 4W2B 2/6, 2P6W1B plus additional wafer with shorting plate, 2/3. All have 1in spindles, resistors, 100 assorted, 47 values, ranging 10Ω ¼w—100k, 3/-; all standard sizes; beat makes 10/6, post 6d; air-spaced variables, ceramic bases, 1in spindles, 1in long, straight, 25PF 5/-, 100PF 5/3; preset 50PF 6d; meters, metal cased, 2in circular, 0/500 micros 7/6, 0-15-60AV rec. ex. 7/6, 0-0.2Ma or 0-0.5Ma, with shunt, 5/-; bakelite cased, 2½in square, 0/1ma 7/6, 0/5ma 6/-, 0/50ma 7/-, 0/300v series res. supplied, 7/-, 0/20v 5/-; bakelite cased, 2½in circular, 0/5 micros 16/6, 0/5ma 7/-, 0/50ma 6/6, 0/100ma 6/-, desk type, 2½in, 0/1ma, 15/-; all meters flush mounting; visual indicators, type 1, crossover needle, 2-60 micros, with permanent magnet 5/-; B.M. diaps. as type R.F.26, 3in. cursor, 5/-; rotary power units, type 104, 12v D.C. input, output 250v 60ma, 6.5v 2.5a, P.M. rotary, mounted on chassis with supp. filt., type 61, 24v input, output as 104, 5/11; 2-gang condensers, 0005, per ganged, 1in spindle, 4/6; 3-gang, 0004 with epicyclic fitted, 5/6; superhet coils, 465kc/s in formers, M.W. H.F., A.R. or Osc., L.W. H.F., A.R. or Osc., 1/6 per pair; I.F. trans. 465kc/s, iron-cored, 1/6, set of 3 coils and cap, 9/6; 12-pin plugs and sockets, with keyway, 1/6 pr.; 6-way plugs and sockets, with cover, 1/6 pr.; telescopic aerials, all 15in closed, 20/6in extended, 5/6; bakelite cases, with lid, inside mess. 6x6½x3½in without lid, 2/6, 1in deep with former for frame aerial, lid ex gives 10x8x2½in; ideal for personal sets, meters, etc., 6/6, post paid; lightweight headph. res. high res. 2,000Ω 5/6 pr.; aircraft radio rec., type CRV 46151, 6-valve receivers, coverage 1.5Mc/s-15.5Mc/s, in 4 bands, 195-560, 560-1,500kc/s, 1.6-4.5mc/s, 4.5-15.5mc/s, switched, R.F. mixer, 3-1 F.S. det. output using 9-12SP7s, 1-12SA7, 1-12A6, B.M. dial, calibrated in kc/s, size 8½x7½x10in, provision for aerial or loop, powered from 28v self-contained dynamotor, supplied with valves and dynamotor, used, £5/19/6, carr. paid; mains trans., PRI 230v 50c/s, 4a, sec. 460v, 200ma 210v 150ma, 6.3v 3a 14/-.

RADIO compass MN26C 12-valve unit containing 7-valve rec. covering the broadcast band 150-1500kc/s, 1.700-203 metres, in 3 bands, with 6SK7 output, valves 3-6K7ts, 1-6SN7m's, 2-6J5m's, 1-6L7m, 1-6H6m, 1-6P6 powered by self-contained 28v dynamotor, good condition, £5/19/6, carr. paid.

EX-ADMIRALTY receiver B.21, covers 1-20mc/s in four bands, 9 valves, 2 RF, 2IF, B.F.O., output, standard octal types, power supply required.

(Continued on next page)

A COMPLETE RANGE OF TELEVISION COMPONENTS

- Line and Frame Scanning Assemblies.
- Focus Coils and P.M. Focus Units.
- Line and Frame Output Transformers.
- Line and Frame Oscillator Transformers.
- Combined Line Output transformers and E.H.T. Generators.
- Width controls.
- Video correction chokes.
- Filament transformers, E.H.T. transformers and Smoothing chokes.

Allen Components are specified for the Electronic Engineering Home Televisor and the range includes components suitable for use in all of the popular Home Constructor Sets.

ALLEN COMPONENTS LTD.
1, Shrewsbury Road, Stonebridge, N.W.10
Telephone: Willesden 3875 and 4901.

ENAMELLED COPPER WIRE ON REELS

for immediate delivery, quantities in all gauges from 10-50 SWG, very attractively priced, well below manufacturers' prices.

PRODUCTS & COMMERCE LTD.,
14, Dominion Street, London, E.C.2.
MET. 9542/3 & 0530.

POST RADIO SUPPLIES

OFFER EX STOCK

COPPER INSTRUMENT WIRE.
ENAMELLED, TINNED, LITZ.
COTTON AND SILK COVERED.
Most gauges available.
B.A. SCREWS, NUTS, WASHERS, soldering tags, eyelets and rivets.
EBONITE AND BAKELITE PANELS, TUFNOL ROD, PAXOLIN TYPE COIL FORMERS AND TUBES, ALL DIAMETERS.
Latest Radio Publications.

THE CRYSTAL VALVE
as used in radar receivers.

These Crystal Valves or Diodes are not Government Surplus but brand new goods manufactured by one of the largest and most famous Radar Equipment Manufacturers in the country.

3/6 each, postage 2½d.

Protective Tube and Fixing Brackets, 3d. extra. Send stamped addressed envelope for comprehensive lists. Trade supplied.

POST RADIO SUPPLIES
33, Bourne Gardens, London, E.4.
'Phone: CLissold 4688

HENRY'S

A few items from our current list, which will be despatched on receipt of a stamp.

VERY SPECIAL. HA200 EHT panel rectifiers, brand new, 2,400 v. 3 mA, only 15/- each. **ALSO.** The very latest slider pots, as used in all the latest T.V. receivers. Bank of 4, comprising 2 of 50K, 1 each of 100 ohm, 500 ohm. Only 6/- complete. Not repeatable.

R3515 I.F. STRIP. A complete I.F. unit comprising 5 EF50 I.F. stages tuned to 13.5 Mc/s, 1 EA50 diode detector and 1 EF50 or EF50 output or video stage. A few modifications only are required to adapt this unit which will give pictures of extremely good quality. Price complete with valves, and fool-proof modification instructions, 45/-, plus 2/- packing and carriage. Limited quantity only.

NO. 18 SET. RECEIVER PORTION. A four-wave superhet receiver operating from 6·9 Mc/s (22 m. 50m). Valve line-up: 2 ARP12 (VP23), and AK2 (HL23DD). Requires only 120 v. H.T., 2 v. G.B. and 2 v. L.T., in perfect condition, only 17/6, plus 2/6 packing and carriage. An absolute bargain, suitable brand new headphones can be supplied at 3/6 per pair.

N.B.—Each receiver is tested working, prior to despatch.

TYPE 6A INDICATOR UNITS. As recommended for ex-Govt. T.V. construction. Absolutely complete (including VCR97 with mu-metal shield, 4 EF50 and 3 EB34. Limited quantity only, at 67/6 each, plus 7/6 carriage and packing.

TYPE 6C INDICATOR UNITS. Comprising 3 in. VCR138 C.R.T. with mu-metal screen, 2 EF50, 2 EB34, plus high voltage condensers and resistors. In good condition, price 45/- only.

DUAL PURPOSE MAINS TRANSFORMERS. Special 200-0-200 v. 80 mA., 6·3 v. tapped 4 v. at 3 a., 5 v. tapped 4 v. at 2 a. Top chassis mounting, and fully guaranteed. 18/6 only, plus 9d. post.

A.M. RECEIVER UNIT. TYPE 161. Comprising 5 EF34, 1 EB22 and 4LS7. Differing set of many condensers and resistors. The whole in metal box, size 8½ × 6½in. × 3½in. New, a bargain at only 15/-, carriage paid.

RECEIVER TYPE 25. The receiver portion of the T.R. 1196. Covers 4.3-6.7 Mc/s, and makes an ideal basis for an all-wave receiver, as per "Practical Wireless," August issue. Complete with valves type EF36(2), EF36(3), EK32 and EB32. Supplied complete with necessary conversion data for home use. Only 22/6. Chassis only 8/6.

WAVE-FORM GENERATOR TYPE 54. EX A.M. Including 4 EF91, 2 EF50, 2 EB34 and one CV116. Also relays, transformers, pots, condensers and resistors. The whole contained in metal box size 11½ × 11 × 8in. In clean condition, an absolute bargain at 25/-, plus 5/- packing and carriage.

SKV ELECTROSTATIC VOLTMETER. 0-6 kV. panel mounting, 4½in. scale, brand new. 50/- each.

MIDGET I.F. UNIT IN ALUMINIUM CAN. 4½in. × 2½in. × 1½in. Comprising one valve type I.T. 4, Midget iron Cored I.F. Trans. 400 Kc/s and eight midget resistors and condensers. Bargain price of 2 for £1, post paid.

10 MFD. 2,000 v. W. OILFILLED AMERICAN CAPACITORS. size 4½ × 4½ × 4in. Porcelain terminals. Each individually wrapped and absolutely brand new—price only 17/6 each.

BIRMINGHAM EX-GOVT. T.V. We can supply brand new EF24 units, converted to cover EF50 frequency, at 25/- post paid.

PACKARD-BELL MICROPHONE PRE-AMPLIFIER TYPE K. Complete with valves 6SL7GT and 6SJ7, relay, etc., etc., for 28 volt D.C. input. In metal box, size 8in. × 4in. × 3½in. Complete with leads, plugs, switch, two 2-way terminal blocks, and printed instruction and circuit manual. In original sealed carton. Only 14/6.

E.H.T. TRANSFORMERS. Output 2,500 v. 5 mA., 4 v. 1.1 a., 2-0-2 v. 2 a. (for VCR97), 35/-only. Output 3,500 v., 5 mA, 6.3 v. 1 a., 2-0-2 v. 2 a. (for SCP1), 39/6. Output 4,000 v. 10 mA., 2-0-2 v. 2 a., 48/-. Output 5,000 v. 10 mA., 2-0-2 v. Only 60/-. All input 230 v. and fully guaranteed.

A SIGNAL TRACER at minimum cost. An easy-to-build unit that can be used for R.F., I.F. and Audio signal tracing, without any switching or tuning. Highly sensitive, easy-to-build, responds to signals picked up from an ordinary receiving aerial. The circuit is that of a high-gain, 3-stage resistance-coupled audio frequency amplifier, with a 3in. speaker in the Output of the Power Amplifier stage.

We shall be pleased to supply a complete kit for the construction of the above, right down to the last nut and bolt, for the low price of £3 18/6. Concise instruction and circuit are supplied. If preferred, circuit and instructions only can be supplied for 1/6 post free. All items may be purchased separately. This is a highly efficient instrument, and a MUST for every radio man.

WE ARE PLEASED TO ANNOUNCE THAT WE ARE ONCE AGAIN ABLE TO OFFER A RETURN OF POST SERVICE

5 HARROW ROAD, W.2

(Opposite Edgware Road Tube)

PADdington 1008/9 & 0401

COMPONENTS—SURPLUS AND SECONDHAND

(Continued from previous page)

supplied new ex valves. Air 18/6, plus 10/- carriage.

RADIO CLEARANCE, Ltd., 27, Tottenham Court Rd., London, W.1. Tel. Museum 9184. [5015

CAMBRIDGE vacuo-junctions, rated 5ma, 1/- each, 10ma output, 6.3mv 3/-, one hundred assorted pos. and resistors 20/30 ¼ to 2watt 1/6, multi-coloured flex, rubber covered, 5-core, 14 yds 6/-, 100 yds 17/6, sound 30/- cond. 4/6 dozen.

PASSELIGHAM, 95, North St., Keighley. [5002

SURPLUS, unused. 1,350v 2/6 doz. 20 1,000v 5/- doz. 20 500v 3/- doz. 1 500v 3/- doz. 40 mica 3/- doz. 40pf 2/- doz. 1mfd 500v 50 each. TRP cons 4/6 pair, etc. Helpfull, list from: J. O. Hovell & Co., 29, McWilliam Rd., Brighton, 7. [5019

12 lgs rects, 6v lgs rects, Morse keys, 0mfd, 2/6 doz. 1/- each, meter jacks, 4-pin 2-way sockets, 1/6 doz. 2/- doz. 40pf trimmers, 3d each. 10mfd 250v 4d. 120ma smooth chokes 5/-, many other bargains, post extra; money back guarantee, no c.o.d., s.a.e. lists.

ANNAKIN, 23, Ashfield Place, Otley, Yorks.

SEYMOUR PRODUCTS (CARBISHAW), Ltd. (In Liquidation)—The assets of the above, comprising electrical and radio equipment and stock, plant, tools, office furniture, unused corrugated cases and corrugated tools (H. W. and K. W.) are for sale. Offers may be obtained from the Official Liquidator with whom offers should be lodged.

JAMES MURRAY & Co., C.A., 31, Albert Square, Dundee. H. S. Graham, C.A., Official Liquidator.

UNUSED Surplus—Midget blower motors, 25-110 volt d.c. or 8/6, small panels, with two 17 450v, one .01 250v, one 1 600v, one 8mfd 150v tubular, one LF choke, 2,000 ohms resistance, valve holder, 1/6 each; 1/3 doz., 12/- doz., 0005 tuning condensers, 1/9, 15/- doz., 25A 25mfd tub. bias 1/- each, 9/- doz., 25mfd 15v working, 1/- each, 9/- doz. 60mfd 750v 1d per foot, wanted tape for wire recorder.—Hartman, 14, St. Mary's, Bedford. Tel. Bedford 5566.

G.C. SOUND TELEVISION, Aldershot.—All goods listed below are post free; list 1d. 2a resistors 6d, 9 ltny chokes 100 m/a, 6/6; neon bulb and holder 100v, 3/6; midget output or mike trans. 1/6; L.R. earphones 5/6; 21 5ks cond. 1/9; 001 subminiature postage stamp, 4/- doz.; 1 350v 4/- doz; 50k t/c with switch, 3/6; model 58 walkie talkies, guaranteed working on crystal for receive 59/- each, tested; sound powered phone inserts, 5/6 each.

SOUND TELEVISION, Co., 42, Elms Rd., Aldershot. Tel. 115. [5018

SUPREME RADIO, 746b, Romford Rd., Manor Park, London, E.12. Tel. Ill 1260. Est. 16 yrs.—2mfd 350v 1d; carbonized cond. 6d ea.; also 4mfd 450vw cond. 6d ea.; 4mfd screw base metal cond. 350vw 6d ea.; or, 4mfd 550vw metal screw base 1/- ea.; 8mfd cardboard tub. 450v 1/6 ea., 8+16mfd 450v metal can cond. 2/3 ea.; 16mfd 450v cardboard cond. 2/9 ea.; 16mfd dry-litic cond. 350vw, small can type, 1/9 ea.; cardboard 50mfd 50vw or 25mfd 25vw conds. 1/- ea.; also 16mfd 120 vw metal can cond. 1/- ea. 12/- doz.; or ass. doz.; 12mfd 50vw screw base metal cond. 6d ea.

5meg vol. controls, carbon 7/6d ea., 1meg carbon vol. controls 1/- ea.; 50kΩ t/c with switch 1/6 ea. 100kΩ vol. cont. with s/p switch carbon 2/6 ea.; 0.25mfd vol. cont., less switch, 2/- ea.; both long spindle; noise suppressor units consisting of 2-0.1mfd cond. 1mf choke 6d ea., 5/- doz.; fly-back type line trans. with provision for EY51 valve, 22/6 ea.; fully shrouded.

MAINS Trans. 350-0-350v 80 m/a, 4v 4amp and 4v 2amp tapped, primary 4/11 ea.; E.H. mains trans. 350-0-350v, 250m/a with all L.T. windings and screen, £3/10. 5 by 250 m/a choke 15/9 ea., 10 by 60 m/a choke 6/6 ea.; E.F.50 valve holders, ceramic 6d ea.; 5/6 doz.; retaining rings for same 6d ea.

Low resistors, 10Ω, 22Ω, 27Ω, 47Ω, 82Ω, 100Ω, 150Ω, 250Ω, 330Ω, 500Ω, 820Ω, 1kΩ, 5.6kΩ, 11kΩ, 470kΩ, and 10mΩ 1/6 doz. or ass. 10/6 gross or ass. 4w resistors, 2.2kΩ, 6.8kΩ, 16kΩ, 18kΩ, 2.5kΩ, 100kΩ, 150kΩ, 220kΩ, 2/- doz. or ass., 21/- gross only or ass. gross 1 watt resistors, 270Ω, 470Ω, 1kΩ, 2.2kΩ, 3.3kΩ, 10kΩ, 33kΩ, 56kΩ, 68kΩ, 1meg and 2meg, 4/- doz or ass. doz., mica cond., pyl type, 40pf, 50pf, 60pf, 65pf, 70pf, 80pf, 500pf, 550pf, 570pf, 580pf, 700pf, 1.0nf and 4.5nf, 4/- doz or ass. doz. 0.01mfd 2.2kv and 0.005mfd mica tag end cond. 0.0005mfd, 0.0005mfd and 0.001mfd 350v and 0.002mfd 500v 9d ea. 7/6 doz. or ass. tubular 0.02μ-vw cond. 0.01mfd 1kΩ/vw, 0.02mfd 350vw 0.05mfd 350v and 0.1mfd 350v or 500v, 6d ea., 5/6 doz.; component parts for constructor television and radio circuits our speciality.

TERMS: c.w.o. no c.o.d. send 5d extra for postage orders under £5. 2½d s.a.e. all enquiries and list. [6001

RADIO UNLIMITED, Elm Rd., Walthamstow, E.17, for guaranteed spotless surplus components. Speakers: 3in. 12/6, 5in. 13/6, 6½in. 10/-, 6in 11/-, 8in 12/6, 10in 14/6; output transf. 2/6, heavy dty. P.P. tapped, 2, 5, 8, 15ohm 12/6; condensers, all fresh stock, 1 350v 3d, 1 500v 3/-, 8mfd 500v 2/-, 16mfd 500v 3/3, 8+16 450v 3/9, 16+16 450v 5/9, 25mfd 25v 1/6, 50×50 1/9; all types in stock, order c.o.d.; m/coil 0-40 ammeter new/boxed, 3/9; T.X valve 807, 6/3; V control, 10K to 2 meg., long spindle, less switch, 2/6; with sw. 3/9; m/coil headphones, 4/6; lab/arm type with throat microphones, 4/6; throat mics., 1/6 pair; 1001 assrtd with 4001 pots, 4/6; Midget 465 I.F.T.s, 11/- pair; hundreds other lines; s.a.e. list, or tel. Key. 4813. [5002

GALPINS

ELECTRICAL STORES

400 HIGH ST., LEWISHAM, LONDON, S.E.13

Tel. Lee Green 0067 Near Lewisham Hospital

TERMS: CASH WITH ORDER. NO C.O.D.

THURSDAY EARLY CLOSING

EXTENSION P.M. SPEAKERS, 3½in. by Johnson & Phillips, will handle 1½ watts. New boxed, 7/6 each. Post 9d.

EX R.A.F. MICROPHONE TESTERS. These contain a 2½in. scale 0 to 450 Microamp meter shunted to 1 m/amp, calibrated 0 to 10 volts moving coil, complete with 1 mA. rectifier, "Mike transformer," etc., all contained in polished wood box, as new, 17/6 each.

MAINS TRANSFORMERS, 200/250 volts input in steps of 10 volts, output 350/0/350 volts 180 m/amps., 4 volts 4 amp., 5 volts 3 amps., 6.3 volts 4 amp. 37/6 each, ditto 500/0/500 volts 150 m/amps. 4 volts 4 amp., 5 volts 3 amp., 6.3 volts 4 amp., 42/6 each; ditto 425/0/425 volts 180 m/amps. 6.3 volts 3 amps. twice, 5 volts 3 amps. (Williamson Amplifier), 39/6 each; ditto, 350/0/350 volts 180 m/amps. 6.3 volts 8 amps. 5 volts tapped 4 volts 3 amps., 39/6 each.

EX R.A.F. D.C. TO D.C. MOTOR GENERATORS, 24/28 volts input 1,200 volts 72 m/amps. output, as new, 7/6 each, post 1/6.

MAINS TRANSFORMERS, 230 volts A.C. 50 cycs. input 17½ volts 50 amps. output, 52/6 each, carriage 5/-; another auto wound, output 14 and 17 volts output at 30 amps., 35/- each, carriage 7/6; another with 2 × 4 volt 20 amp. windings, 25/- each, P.P.

PRE-PAYMENT 1/- SLOT ELECTRIC LIGHT CHECK METERS, all electrically guaranteed, 200/550 volts 50 cycs. 1 ph., A.C. input, 2½ amp. load, 27/6 each; 5 amp. load, 38/- each; 10 amp. load, 42/6 each; 20 amp. load, 50/- each, carriage 2/- extra; in quantities of one dozen or more a special discount of 10%.

POWER TRANSFORMER AUTO WOUND voltage changer tapped 0, 110, 150, 190 and 230 volts at 1,600 watts, £5/5/- each, carriage 3/6; ditto, 2,000 watts, £6/5/- each, carriage 3/6; another tapped 0, 110, 200, 230 volts at 350 watts, at 47/6 each, carriage 2/-.

ELECTRIC LIGHT CHECK METERS, quarterly type, for sub-letting garages, apartments, etc., all fully guaranteed electrically for 200/250 volts A.C. mains 50 cycs. 1 phase, 5 amp. load, 17/6 each; 10 amp. load, 20/-; 20 amp. load, 25/- each; 50 amp. load, 37/6 each; 100 amp. load, 45/- each; carriage 2/- extra on each; special discount of 10% on quantities of one dozen or more.

MAINS TRANSFORMERS input 200/250 volts, 50/1 in steps of 10 volts, output tappeo 0, 6, 12 at 24 volts at 10/12 amps., 47/- each; ditto as above but at 25/30 amps. output, 68/6 each.

MAINS TRANSFORMERS, 200/250 volts 50/1 ph. in steps of 10 volts. Output 500/0/500 volts 300 m/amps. o.3 v. 8 a., 6.3 v. 8 a., 6.3 v. 4 a., 5 v. 4 a., 4 v. 4 a., at 67/6 each; another same input, outputs, 450/0/450 volts 300 m amps., o.3 v. 8 a., 6.3 v. 8 a., 4 v. 5 a., 5 v. 4 a., at 62/6 each.

CELL TESTING VOLT-METERS, moving coil, reading 3/0/3 volts by well-known makers, complete with test leads, 7/6 each.

MAINS TRANSFORMERS, 200/250 volts, input in steps of 10 volts, output 350/0/350 volts 300 m amps., 4 volts 4 amp., 5 volts 4 amp., 6.3 volts 8 amp., 6.3 volts 8 amp., 62/6 each. Smoothing chokes 10 Henry 100 m/amps. 200 ohms D.C. resistance, 9/- each.

MAINS VARIABLE SLIDER RESISTANCES, protected type, by well-known makers, 450 ohms, 9 amps., 22/6 each; ditto, 1,500 ohms to carry 45 amps., 22/6 each, not protected, 0.4 ohms, to carry 25 amps., 10/- each; 14 ohms to carry 1.4 amps. 12/6 each.

EX GOVERNMENT AUTO WOUND TRANSFORMERS (as new), 1,000 watts output 115/230 volts or vice versa, £4/10/- each, carriage 5/-; another 1,000 watts from 0 to 230 volts with various tappings inclusive of 110, 150, 60, 90, etc., etc., all tapping at 1,000 watts, £5/10/- each, carriage paid.

MAINS TRANSFORMERS, input 200/250 volts in steps of 10 volts output 350/0/350 volts, 300 m.amps. 4 volt 8 amp., 4 volt 4 amp., 6.3 volts 6 amp. 3.6 volts 2 amp., tapped at 2 volts (electronic) at 57/6 each; another same input as above, output 500/350/0/350/500 volts 250 m/amps. 5 volts tapped at 4 volts 4 amps. twice, 6.3 volts tapped at 2 volts 2 amps., 67/6 each.

EX NAVAL CATHODE RAY INDICATOR UNITS, as new, containing loads of very useful components, condensers, resistances, transformers, chokes, etc., etc., weight 90lb. last few to clear, 25/- each, carriage paid.

ALL GOODS SENT ON 7 DAYS' APPROVAL AGAINST CASH, all letters answered. We regret we have no lists available at present. We would be pleased to quote.

POTENTIOMETERS

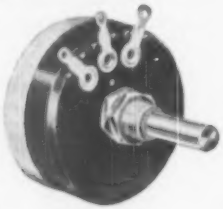

by RELIANCE

Wire wound and Composition types, Single, Ganged, Tandem Units.

Characteristics: linear, log, semi-log, non-inductive, etc.

Full details from

RELIANCE

Manufacturing Co. (Southwark) Ltd.

Sutherland Rd., Higham Hill, Walthamstow E.17

Telephone: LARkswood 1245

Autofeed SOLDERING IRON

Simple self-feed speeds up soldering. Better work. Saves solder.

Write for leaflet 20/J

RUNBAKEN · MANCHESTER 1

SPECIAL OFFER

BRAND NEW WALKIE TALKIES

5 valve Trans-Receivers, Type No. 38. Freq. range 7.4-9 mc/s. Complete with Phones, Throat Mike, set of Aerial Rods, and instructions. Guaranteed in working order. **£4.19.6.** Carriage 2/6. Less accessories, **£4.2.6.** Carriage 1/6.

36 FT. AERIAL MASTS

R.A.F. Type 50. Complete kit consists of 9 Tubular Sections. Length 4ft. Dia. 2in. Set of Pickets, Top Plate Guys and all fittings. Brand New in canvas carrying case. **£3.15.-.** Carriage 7/6.

HEAVY DUTY TRANSFORMERS

Prim. 200-240 v. 50 cy. Sec. 6.3 v. 15 amp. **19/-.** Carriage 1/6. Prim. 200-240 v. 50 cy. Sec. Tapped 20 v. 14 v. 20 amps. **37/6.** Carriage 2/-. Prim. 200-240 v. 50 cy. Sec. 4.2 - 4.2 v. 10 amp. **17/6.** Carriage 2/-.

BRAND NEW BATTERY RECEIVERS

Type 18. Freq. Range 6-9 mc/s. Complete with 4 valves and data card. **17/6.** Carriage 1/-.

SAMSONS SURPLUS STORES

169/171, Edgware Road, London, W.2.
Tel.: Padd. 7851

125, Tottenham Court Road, London, W.1. Tel.: Euston 4982

All Mail Orders to our Edgware Road Branch please.

HUNDREDS OF BARGAINS FOR CALLERS.

COMPONENTS, SURPLUS AND SECONDHAND

LITTLEWOODS, North London's best selection of radio and television components, pay us a visit or post or phone your enquiries; no lists. LITTLEWOOD & GRUNER, Ltd., 27, Ballards Lane, Finchley, N.3. Fin. 5060. [0055

H.R.O. receivers, complete with 7 coils and power pack, £32. Drab wire recorder, £65. Hallicrafters, S27, SX24, AR77, ARSOLF and Hammerlund Super Pro receivers from stock at reduced prices; ex Army R107 receivers, complete and in good order, £15; rotary converters, all voltages and wattage; 20-watt rack mounting amplifiers, complete with heavy duty a.c. power pack, 200-250v. PX25 p.p. output, less valves, new, 45/- each. £3 Transformers, 6v-50v. all current ratings, special types to order at competitive prices. We invite your enquiries. S meters for AR88, H.R.O., Hammerlund, etc., available; mag. clips in pairs, boxed, 5in. bore, £1.7.6 pair. Bendix 522 transmitter chassis, including 2 852 ball coils, etc., etc., 5/6 each; special offer of new meters: 5 m.a. 4/6, 100 m.a. 7/6. 5 thermo amp meters, 5/6, all 2in. scale, ex Government R.T.C. ball microphones, perfect, £4.17.6. 12in and 15in energised and p.m. speakers. Bulla G12. Magnavox 8". etc., pm resistance phones, 5/6 pr.; high resistance 7/6 pr. U.S.A. m-coil, 7/6 pr. special offer of first grade m-coil meters, 500 m.a., 2½in. scale, flush mounting, 7/6 each. 500 micro-amps, with 2in scale, 4/6 each. 200 micro amps, 5-inch scale, flush mounting, 65/- each. 50 micro amps, 5in. projecting type, 50/- each. 1 m.a. meter rectifiers, 5/- each. Ex-service aerial masts (spring), 10ft., 25/- each. new hand bearing compass, with battery compartment in handle, new, 45/- each. Transmitting valves: 807, 5/6, 813, 45/-, T21 A.R., 30/-, 832, 27/-, 832 A, 30/-, 25/-, 6SH7, 5/-, T21A, 951A, T24A, also available. h.t. rectifiers, type H.176, 8/- each. Bendix receiver, type 26, ARC5, 3-6 mc/s, complete with 8 valves and 28v dynamotor, new, in sealed cartons, 45/- each. 20-way rotary stud switch, 5½in.×5½in., 5/6 each. a.c./d.c. 1/20hp. motors, 200-250v, suitable for sewing machines, 45/-. auto transformers from 100w. up to 7kw in stock. Large and comprehensive stock of relays, types 600-8000, and Siemens high speed uniselectors. Telephone handsets, pipes, jacks, switches, etc. Co-axial cable, special offer of mains transformers, 200-250v a.c., tapped 250-0-250, 100 m.a. 6v 4amp, 5v 3amp, £1 each, special offer of new 1-phase induction reversible motors (ideal suitable for remote mechanisms, etc.), 200-250v A.C., 1/80hp, 1,500 r.p.m., 55/- each. New powerful Garrard double-spring clockwork motors, complete with 100ft. cord, 8½ each. New 8½in diam. A.C. 200-250v induction motors, 1/100hp, suitable for models, etc., 30/- each; postage extra on all goods.
SERVICE RADIO, 44 Lisle St., London, W.C.2. Tel. Ger. 1754. [9452

NOTICES

BRITISH SOUND RECORDING ASSOCIATION.—Membership essential to all interested in or actively engaged in sound recording, and in high quality reproduction. Advice freely available to non-members. The current issue of the Journal, 2/9 p.f. Manual of Equipment and Accessories, 1/2 p.f. Full information, with prospectus and membership application form, may be obtained from the Membership Secretary, Harrie J. King, 48, Mount View Rd., North Chingford, London, E.4. [2133

WANTED, EXCHANGE, ETC.

WANTED, any type magnetophone machine or parts.—Box 4181. [5491

WANTED, Magnetophon Tone B, with spares (amplifier not required).—Box 2065. [5074

VALVES, type 813, must be genuine R.C.A. manufacture and new, any number.—Box 4154. [5495

WANTED, dynamometer a.c. test set, also oscilloscope (type 339A, also L050A oscillator).
LESLIE DIXON & Co., 214, Queenstown Rd., Battersea, S.W.8. Macaulay 2159. [0176

SERVICE Sheets wanted, also old copies Wireless World, best prices.—J. Bull, 246, High St., Hampden, N.W.10. [0042

WANTED AR.88s, RX 24s, BC348 (not modified), any quantity.—P.C.A. Radio, Cambridge Grove, London, W.6. Tri. Riv. 5279.

WANTED, all kinds of laboratory test equipment, standard signal generators, bridges, oscilloscopes, "Q" meters, etc.; send price and details.—
HATFIELD INSTRUMENTS, 175, Uxbridge Rd., Hanwell, W.7. Tel. Ealing 0779. [0057

WANTED, all types of radio equipment, test instruments, radio receivers, personal sets, television components, etc., etc.; cash waiting, send or phone.
MILLER'S RADIO, 93a, Newport Court, Charing Cross Rd., London. [5523

WANTED, surplus relays, impulse switches, sparking plugs, 5-way, push-button units, any condition; large or small quantities; highest prices paid.—Box 4060. [5579

WANTED speech amplifiers for BC-610 Hallicrafters transmitters (type BC-614-A or B, C, D, E, or HT-5B) and microphones, type T-30.—P.C.A. Radio, Cambridge Grove, London, W.6. Tri. Riv. 5279. [0201

REPAIRS AND SERVICE

MAINS transformers rewound; new transformers to any specification.
MOTOR rewinds and complete overhauls; first-class workmanship, fully guaranteed.
F.M. ELECTRIC Co., Ltd., Bunters Bldgs., Warser Gate, Nottingham. Est. 1917. Tel. 36556.

SPECIAL BARGAINS

Govt. Surplus, Manufacturers' Surplus & Bankrupt Stocks.

We can offer for immediate delivery

Resistors 1/8, 1/4, 1/2, 1 2 & 3 Watt. ALL VALUES

16 Foot Sectional Aerial in Canvas Carrying Bag

Magnifying Lens.
Rubber Mask.
Burgoyne Solder Guns.
Bakelite Accumulators. Ex Govt. S.W.
Condensers. All Types.
Meters.
Switches, Toggle and Yaxley.
Headphones, L.R. and H.R.
Vibrators, 6 and 12V.
Speakers, All Types.
Volume Controls.
Output Transformers.
Chokes.

Receivers, R1155, 1355 and 184 brand new in original cases. Dinghy Radio Transmitter SCR 578

Your enquiries are invited.

Wholesale and Export only

Please enquire for our 12-Page Bulletin.

RADIO MERCHANDISE Co. Ltd.

65, Farringdon Road, London, E.C.1.

Telephone: Holborn 6377

RADIO G200 OFFERS

BATTERY CHARGERS Input 200/250 v. 50 c/s single phase, or 400 v. three phase, both types rated on a. 10 amperes out, and using metal rectifiers. Price only **£25** each.

METAL RECTIFIERS H.W. 250 v. 50 mA. Price **5/6** each.

Trade and Overseas Enquiries Invited.

ARTHUR HOILE. 58, Union Street, Maidstone, Kent. Phone 2155.

U.H.F. TRANSMITTER - RECEIVERS

of special interest to all enthusiasts on 420 Mc/s.

We have been fortunate to obtain a very limited number of complete Transmitter-Receivers Type RT-3A/ARN-1. These consist of an F.M. Transmitter and Receiver (a total of 13 valves are included), each containing a built-in Power Pack for direct operation from a 24-volt supply. Black Crackle cases, slightly store soiled. SPECIAL PRICE **79/6.**

Carr. and packing paid.

Send S.A.E. today for our Special Summer clearance list.

WALTON'S WIRELESS STORES,
203, STAVELEY ROAD,
WOLVERHAMPTON.

"INEXPENSIVE TELEVISION"

DATA BOOK NO. 4 just out, **1/6** post paid.

R1355 RECEIVER. New but slightly store soiled, **49/6** carriage paid.

45 Mc/s "Pye" Strips. NEW. Less valves, **39/6**, complete with all valves, **62/6**. Carriage paid.

RF UNIT TYPE 25. For London frequency. Slightly soiled. **15/-** plus 1/6 post and packing.

RF UNIT TYPE 26. Not at present available. We can offer brand new RF24 correctly converted to either sound or vision (Sutton Coldfield). Specify which is required when ordering. Priced at **27/6** plus 1/6 post and packing. Note. No carriage charge for the RF Unit if ordered with an R1355 Receiver.

INDICATOR UNITS TYPE 62A. Contains 12 EF50, 4 of SP61 (CV118), 2 of EB34, 3 of EA50, 13 pots, 1 VCR 97 tube. This is the finest Indicator Unit of them all. Unused but chassis slightly soiled. Offered to CALLERS ONLY. Price **£4/19/6.**

INDICATOR UNIT TYPE 96. Very similar unit to the 6A series. Contains a VCR97, 3 of EB34, 6 of VR65 (SP61), 1 VR92 diode, 14 pots and hosts of condensers and resistors. Dimensions, 7½ x 8½ x 19 in. CALLERS ONLY. **45/-.**

INDICATOR UNIT 116H. A more up to date version of the famous 6A and the ideal Indicator Unit for TV use. The unit is brand new and contained in manufacturers original wooden crate. Contents include a VCR97 tube, 4 of EF50, 3 of EB34 and numerous useful components. Only **£4/10/-**, plus 7/6 carriage.

AUXILIARY EQUIPMENT FOR THE INEXPENSIVE TELEVISOR

MAINS TRANSFORMERS. For the R1355. 200-250 v. input. Outputs 250-0-250 at 130 mA, 6.3 v. at 6A, 5 v. at 3A. Fully shrouded top chassis mounting. Guaranteed **27/6** post paid.

TIME BASE TRANSFORMER. 350-0-350 v. 80 mA, 6.3 v. tapped 4 v. at 3A, 5 v. tapped 4 v. at 2 A. Top chassis mounting. Guaranteed. **18/6** plus 9d. postage.

EHT TRANSFORMER. For VCR97 or VCR518 tubes. 2,000 v., 4 v., for tube heater, and 4 v. tapped at 2 v. for E.H.T. rectifier. **30/-.**

ALL VALVES, CATHODE RAY TUBES, ETC. IN STOCK AT ATTRACTIVE PRICES.

ENLARGERS. Of latest design and manufacture. Oil filled plastic type. Increases picture size to approx. 9in. with minimum distortion. **25/-** plus 1/6 postage.

CO-AXIAL CABLE. 75 ohms, new and standard. **9d.** per yard.

AERIALS. Prices from **21/-**. Weatherproofed. High efficiency assured.

Our TV service is second to none. A competent technical staff always available to advise and suggest.

RECEIVER UNIT 25/73. Receiver portion of the TR1196. Valve line-up: 2 of EF39, 1 of EK32, 1 of EBC33 and 2 of EF36; and one pair of 460 Kc/s I.F. Transformers, resistors, condensers, etc. Easily and rapidly converted into a superfine superhet receiver. Circuit and conversion data supplied. In very good condition. **22/6** each, post paid.

RECEIVER R1155A. Aerial tested and perfect. **£9/10/-** or packed in original transit case, **£9/19/6**, carriage paid.

POWER PACK AND OUTPUT STAGE FOR THE R1155. Enables this receiver to be operated direct from A.C. mains. Just plug in! **£3/10/-**, carriage paid.

During this month we are clearing out various interesting oddments at real "knock-out" prices. Make sure you pay us a visit.

Best buy at Britain's

CHARLES BRITAIN (RADIO) LTD.

11, UPPER SAINT MARTIN'S LANE, LONDON, W.C.2

(3 minutes from Leicester Square Station) Telephone: TEM 0545.

Shop hours: 9 to 6 p.m. 9 to 1 p.m. Thursday
OPEN ALL DAY SATURDAY.

REPAIRS AND SERVICE

LOUDSPEAKERS rewound and cones fitted, any make, prompt service.—Model Loudspeaker Service, 54a, Bullingdon Rd., Oxford.

MAIN and output transformers rewound to pattern or specification, return post service. —H. Pughe, Radio Rewind Service, Brithdir, Nr. Dolgelly, N. Wales. [3243

MAINS transformers rewound or constructed to any specification; prompt delivery.—Bede Transformer Co., Ltd., Bedeway, Bede Trading Estate, Jarrow. [3198

TELEVISION, radio and amplifier repairs or modifications; home built receivers aligned and tested; quotations by return; any type transformer or coil supplied. BERNARDS, 12, Cheverton Rd., Putney, London, S.W.15. Put. 7538. [0099

REPAIRS to moving coil speakers, cones, coils fitted, field rewound or altered, speaker transformers, clock coils rewound; guaranteed satisfaction, prompt service. L.S. REPAIR SERVICE, 49, Trinity Rd., Upper Tooting, London, S.W.17. Balham 2359.

ALL types of ammeters, voltmeters, Avos, etc., repaired; quick, efficient service, estimates free.—Donvin Instrument Co., 91, Princedale Rd., London, W.11. Tel. Park 4463. [0059

ELECTRICAL measuring instruments of every make repaired and standardised.—The Electrical Instrument Repair Service, 329, Kilburn Lane, London, W.9. Tel. Lad. 4168. [5715

A REWIND service which duplicates or modifies as required; transformers, loudspeakers, etc., prompt returns.—Rabiel Services, 49, Lr. Addiscombe Rd., Croydon. Cro. 6537.

REPAIRS.—E.H.T., mains and O.P. transformers, field coils and chokes; also armatures and motors; new transformers designed to any specification, all work fully guaranteed. WILLESDEN TRANSFORMER Co., Ltd., 781, Harrow Rd., N.W.10. Tel. No. Ladbroke 2846.

"SERVICE with a smile."—Repairers of all types of British and American receivers; coil rewinds; American valves, spares, line cord. —F.R.I., Ltd., 22, Howland St., W.1. Museum 5675. [1575

RADIO MAINTENANCE SERVICE for guaranteed rewinds and repairs; armatures, F.H.P. motors, vac. units, portable tools, etc., good deliveries.—139, Goldhurst Terrace, N.W.6. Mai. 6133. [9925

"STURDY" rewinds, mains transformers, chokes and fields, first-class work, prompt deliveries and satisfaction guaranteed. —Sturdy Electric Co., Ltd., Sturdy Works, Burnopfield, Newcastle-on-Tyne. [2450

A SECOND-to-none rewind service, reliable, neat, return of post service; your television requirements promptly executed, EHT, LHT and heater transformers, stamp for quotations.—R. E. F., 137a, Ashton Rd., Oldham. [3519

ALIGNMENT and repairs of communication receivers and all other short wave equipment; receivers and amplifiers built to specification; experimental and design work executed. P.C.A. RADIO, Cambridge Grove, London, W.6. Tel. Riv. 3279. [0095

24-HOUR service, 6 months' guarantee, any transformer rewind, mains outputs and i.f.s., etc.; all types of new transf., etc., supplied to specification; business heading or service card for trade prices.—Majestic Winding Co., 180, Windham Rd., Bournemouth.

METROPOLITAN RADIO SERVICE for rewinds, mains and E.H.T. transformers, chokes and field coils; delivery 3-5 days; new transformers designed and manufactured singly or in quantities.—Metropolitan Radio Service Company, 1021, Finchley Rd., London, N.W.11. Tel. Speedwell 3000.

WORK WANTED

SPECIAL receivers, test gear, electronic apparatus, experimental and design work.—If you have a problem which needs expert handling, write in first instance to J. Mort, B.Sc., A.M.I.E.E., BCM/HIFIDEL, London, W.C.1.

DRAUGHTING, tracing and photoprinting services, estimates free; contractors to the Ministry of Supply and the Admiralty for drawing and tracing work to their requirements and specifications, sub-contracting work of this nature undertaken. DRAWING & TRACING, Ltd., 456a, Ewell Rd., Tolworth, Surbiton. Tel. Elmbridge 7406. [4183

MISCELLANEOUS

SUPERB quality walnut radiogram cabinets; stamp, leaflets.—Cabinetware, 1A, Heyes St., Blackburn. [0091

PROCEEDINGS of the Institute of Radio Engineers for disposal; Vols. 8 to 36 incl.—Full particulars from and offers to Catt, 35, Hempstead Rd., King's Langley, Herts. [5692

COPPER wire for sale, 32 gauge E.D.W.S., 36/-; .0076 P.D.S.C., 31 gauge and 35 gauge E.D.W.S. as new.—Apply Monitor Radio & Communications Co., Stechford, Birmingham, 9.

ENGRAVING, amateurs and trade could take the opportunity of engraving problems in the future by getting in touch with A.G. Engraving, 19a, Windmill Rd., London, S.W.18. Brass, bronze erinoid, perspex dials; one knob or repetition equally entertained. [0034

ALLSCREWS, Ltd., for B.A. screws, nuts, washers, studding, grub-screws, bolts, soldering tags, woodscrews, etc., plain or nickel or cadmium plated, one-gross packets or large quantities; stamp for lists.—270a, King St., Hammersmith, W.6. Riv. 7762. [5426

FLUORESCENT lighting, 40 watt ballast with bi-pins and starter, 28/9; 80w ballast kit, 35/9; buy tubes locally; bench grinder 3,000rpm ½in shaft with 4in. grindstone, 37/6; all three for 210-240v ac; illustrated list.—Malden Transformer Supplies, oppos. G.P.O., George St., Richmond, Surrey. [0038

You're SURE to get it at

STERN'S

ESTABLISHED 25 YEARS

"MAINS or BATTERY PERSONAL KIT"

A complete KIT OF PARTS to build our new MIDGET 4-VALVE SUPERHET PERSONAL SET, covering MEDIUM and LONG WAVES and designed for MAINS or BATTERY operation is now available. This 2-Waveband Superhet Receiver is designed to operate on A.C. mains 200/240 volts, or by an "All-Dry" Battery, either method being selected by means of a Rotary Switch. It is so designed that the Mains Section (size 4½in. x 1⅛in. x 1⅛in.) is supplied as a separate Kit, which may be added at any time. The kit therefore can be supplied either as an "All Dry" Battery Personal Set, or as a Midget Receiver for Combined Battery/Mains operation.

The circuit incorporates Delayed A.V.C. and Pre-selective Audio Feedback. A Rola 4in. P.M. Speaker with generous size Output Transformer ensures excellent quality reproduction. Ready Wound Frame Aerial, Fully aligned I.F. Transformers, and a Drilled Midget Chassis are included.

Valve line up:—1R5 (F.C.), 1T4 (I.F. Amp.), 1S5 (Diode Det. and Audio Amp.) and 3S4 (Output Tet.).

The Set is quite easily built from the very detailed assembly instructions supplied, which includes a practical component layout, with point to point wiring, and a circuit diagram for both the Set and the Mains Unit.

Price of COMPLETE KIT (less Mains Unit), **£6/13/9.**
Price of COMPLETE MAINS UNIT KIT, **£1/17/6.**
EVER READY Type B114 BATTERY, **9/7.**

An attractive Walnut Finished Cabinet, size 9in. x 5½in. x 3½in., of the hinged lid type, suitable to house the Combined Set is available for **19/9.**

THE COMPLETE ASSEMBLY INSTRUCTIONS mentioned above can be supplied separately for **1/9.**

A Midget T.R.F. Battery Portable "Personal" Kit. A Complete Kit of Parts to build a midget 4-valve All-dry Battery Personal Set. Consists of Regenerative T.R.F. Circuit employing Flat Tuned Frame Aerial, with Denco Iron Dust Cored Coil, thereby ensuring maximum gain for Single-Tuned Stage covering medium Waveband.

Valve Line up: 1T4 (R.F. Amp.), 1T4 (Detector), 1S5 (1st A.F.), and 3S4 (output). Includes latest Rola 3in. Moving Coil Speaker, and a Chassis already drilled and shaped. A consumption of only 7 m/a. ensures long battery life. The Kit is designed for a cabinet, minimum size 6¼in. x 4½in. x 3in. Detailed Building Instructions, with Practical Layout and Circuit included with Kit make assembly easy.

Price for Complete Kit, £3/18/9 (plus **16/7** P.T.). Suitable unpolished Cabinet 6¼in. x 4¼in. x 3in., **12/9.** Ever Ready B114 Battery, **9/7.** Building Instructions, Circuit, etc., supplied separately, **1/-.**

A Complete Kit of Parts to build a **Midget "All Dry" Battery Eliminator,** giving approx. 69 volts H.T. and 1.4 volts L.T. This Eliminator is suitable for any **Personal** Set requiring H.T. and L.T. voltages indicated above (or even for sets requiring up to 90 volts). The Kit is quite easily and quickly assembled and is housed in a Light Aluminium Case, size 4in. x 1⅝in. x 3⅝in.; it can therefore be accommodated inside most makes of Personal Sets. **Price of Complete Kit, £1/17/6.**

"Wireless World" Midget A.C. Mains 2-Valve Receiver. We can supply all the components, including valves and M/Coil Speaker to build this set as specified in the March issue at a total cost of **£2.** Reprint of detailed assembly instructions and circuit supplied separately for **9d.**

"Wireless World" Midget A.C. Mains 2-Valve Receiver, covering Long and Medium Wavebands. We can supply all the Components, including Drilled Chassis, Valves, Moving Coil Speaker, etc., to build this Set, as specified in the Feb. issue, at a total cost of **£4/5/0** including a reprint of the complete Assembly Instructions and Circuit (this is available separately for **9d.**).

An attractive **Walnut Finished Cabinet** is now available for this W. World 2-Valve Set at **21/-**, or it can be supplied with a complete Dial and Drive Assembly which includes the latest Station Name Dial and Dial Escutcheon, and a Combined Switch/Volume Control to effect very slight modification. Inclusive price, **35/-** (Dial and Drive Assembly with Switch/V. Control supplied separately for **14/-**.)

Send 2d. stamp for our Comprehensive Stock List. Hundreds of components are shown, together with various Kits of Parts. When ordering please cover packing and postage.

STERN RADIO LTD.,

109 & 115, FLEET STREET, E.C.4.

Telephone: Central 5814 and 2280

GOVT. SURPLUS, UNUSED

CONDENSERS

of all types . . .

We can offer, FOR IMMEDIATE DELIVERY from very generous stocks, a wide range of ultra-high quality fixed paper Condensers, from .001 μF to 8 μF. Also STOCKS of small, genuine MICA Condensers from .00001 (10 pf) to .01 μF (10,000 pf). *Prices are exceedingly moderate.*

Enquiries are invited for manufacturers' requirements, wholesale and export only for bulk quantities, and for scheduled deliveries over a period as required.

Most condensers are now available for immediate delivery.

Please request our 4 page bulletin CONSEVEN 0111

CLAUDE LYONS LTD.

180 Tottenham Court Rd., London, W.1
and 76, Oldhall St., Liverpool 3, Lancs.

MISCELLANEOUS

COPPER wires enamelled, tinned, Litz, cotton, silk covered, all gauges; BA screws, nuts, washers, soldering tags, eyelets, ebonite and laminated bakelite panels, tubes, coil formers; Tufnol rod, headphones, flexes, etc.; latest radio publications, full range available; list, s.a.e.; trade supplied.—Post Radio Supplies, 33 Bourne Gardens, London, E.4. [1454

SITUATIONS VACANT

LONDON COUNTY COUNCIL.

SOUTH-EAST London Technical College.—Applications are invited for the post of lecturer in radio communication to commence duties in September, 1950. Applicants should have a university degree or the equivalent and have had industrial experience.
SALARY in accordance with the London Burnham technical scale, which would be in the range of from £336—£15—£603 a year, plus graduate and training allowance where applicable. To a suitably qualified candidate an addition to the scale of £50 may be paid. Initial increments will be paid for suitable previous teaching and/or industrial experience.
APPLICATION forms may be obtained by forwarding a stamped, addressed foolscap envelope to the Secretary, South-East London Technical College, Lewisham Way, London, S.E.4, and should be returned not later than fourteen days after the appearance of this notice. (876) [5681

LONDON COUNTY COUNCIL.

POPLAR TECHNICAL COLLEGE.—Required in September, 1950, an evening class instructor in radio service work. Candidates should possess suitable qualifications in radio service and preferably hold the City and Guilds Certificate in this subject. Classes will be held on Friday evenings from 6.45 to 9.15. Fee per evening, 27/-.—Application forms, returnable by July 29th, 1950, from the Secretary at the College, Poplar High St., E.14. (915) [5721

LONDON COUNTY COUNCIL.

SOUTH EAST LONDON TECHNICAL COLLEGE.—Applications are invited for the post of Senior Assistant for the Radio Communication section of the department of Electrical Engineering and Applied Physics.
APPLICANTS should have a university degree or its equivalent, together with industrial and teaching experience.
SALARY £700×£25-£800, plus London allowance of £36 or £46, also degree and training allowances where applicable.
APPLICATION forms obtainable from the Secretary (stamped addressed foolscap envelope necessary), South East London Technical College, Lewisham Way, S.E.4, should be returned not later than 14 days after the appearance of this notice. (915) [5720

RADIO (Meteorological) Mechanics.

VACANCIES exist in the Meteorological Office, Air Ministry for Radio (Meteorological) Mechanics to maintain radio and radar equipment.
APPLICANTS must possess a knowledge of the fundamental principles of radio and radar and have had practical experience in the maintenance and use of radar equipment, including cathode ray oscilloscopes. The duties mainly involve the maintenance and operation of radar equipment used in the Meteorological Office for the determination of upper winds.
COMMENCING weekly wages £6/13 25 years or over, rising annually by 5/- to a maximum of £8/3 subject to provincial differentiation. The commencing wage of £6/13 is subject to a deduction of 5/- each year below age 25.
APPLICATIONS for appointment should be addressed to the local Employment Exchange or to the Air Ministry, S.2.(b), Cornwall House, Stamford St., London, S.E.1. [5687

TELEVISION engineers for East London district, write, stating experience, salary required, driving ability, etc.—Box 4702. [5591

SOBELL INDUSTRIES Ltd. require experienced television engineers with own cars in N. and N.W. London.—Tel. Supervisor, Valentine 8766. [5696

FERRANTI, Ltd., Moston Works, Manchester, have staff vacancies in connection with long-term development work on an important radio tele-control project.
(1) ENGINEERS and scientists; ref. R.Sc.; qualifications include a good degree in physics or engineering, and preferably experience in electromechanical and servo control work, or microwave valve and/or circuit work; salary according to age and experience, in the range £500-£1,000 p.a.
(2) TECHNICAL assistants; ref. R.Tech.; for experimental work on radar, electronic circuits, microwaves, servo control and electromechanical devices; qualifications required, H.N.C. or its equivalent in electrical or mechanical engineering; salary in the range £275-£550 p.a., according to age and experience.
(3) DESIGNER draughtsmen, draughtsmen and junior draughtsmen; ref. R.D.; with experience in design of precision medium and light mechanical and electromechanical devices or electronic equipment; salary according to age and experience based on A.E.S.D. rates as minimum.
THE company has a staff pension scheme.
APPLICATION forms from The Staff Manager, Ferranti, Ltd., Hollinwood, Lancs. Please quote appropriate reference. [5541

DRAUGHTSMEN, senior, required in S.W. London district, experienced in electronic engineering, light mechanical design and knowledge of workshop practice an advantage.—Write, giving full details, past experience, age and salary required to Box 5247. [5696

GEE BROS. RADIO LTD

JONES PLUGS AND SOCKETS. We hold a large range in stock of these items. 1-way 2/-; 4-way 2/6; 6-way 3/-; 8-way 3/6; 10-way 4/-; 12-way 4/6.
BELLING LEE PLUGS AND SOCKETS. 5 pin 1/6; 7-pin 1/9; 10-pin 2/-.
METAL RECTIFIERS L.T. 24v. at 12 amps, 42/-; 12 v. at 4 amps 18/6; 12 v. at 1 amp 7/6; 6v. at 1 amp. 7/6.
PHOTO ELECTRIC CELLS, Type CMG22, Osram, Brand new 18/6 each.
3½in. **CATHODE RAY TUBE.** Type VCR138, complete with Mu-Metal screen and holder these tubes are Ex-Govt. but guaranteed perfect known as the Mullard E.C.R.35. Price only 25/-.
TRANSMITTING VALVES. Type 829B, 80/-; 723 A/B, 40/-; 931A, 25/-; 725A, 60/-; 2J39 60/-; 8011 25/-; 805 12/6; 803 12/6. Also many other types prices on application.
4 MFD. 2,000V. PAPER CONDENSERS. Type 131 upright mounting, size: 4⅞in. 2½in. x 4⅞in., 10/- each.
PRECISION VARIABLE RESISTORS. Brand New, 152 ohms, at 2 amps. 22/6 each.
5K WIRE WOUND POTENTIOMETERS, 40 watts, 5/- each.
FULLY SHROUDED 100K WIRE WOUND V CONTROLS. 25 watts, C.V. 25 Type, 12/6 each.
RECEIVERS TYPE R1155 in good condition, £9, plus 5/- carriage.
EX U.S. GOVT. MIDGET HEADPHONES. Low resistance. New and boxed. 9/6 pair.
R.C.A. 100 K.C. CRYSTALS. 20/- each.
We have a very large selection of all types of relays and spare coils from 100 ohms to 5,000 ohms, prices on application.

GEE BROS. RADIO LTD.,
15, Little Newport St., London, W.C.2.
Tel.: GER. 6794.

"Globe-King" (REGD) MARVEL IN MINIATURE SHORT-WAVE RADIO KIT

Probably the smallest one valve Short-Wave Radio receiver in the world using standard parts with Bandspread tuning device. "Magnificent performance" . . . vide testimonials British Isles and Abroad. Built and designed to precision standards, complete kit costs only 49/6d—write today for descriptive catalogue.

JOHNSONS (RADIO SPECIALISTS) MACCLESFIELD CHESHIRE (ENG)

BRASS, COPPER, DURAL, ALUMINIUM, BRONZE

ROD, BAR, SHEET, TUBE, STRIP, WIRE.
3,000 STANDARD STOCK SIZES
No Quantity too Small *List on application*

London: **H. ROLLET & Co., Ltd.** Liverp'l:
6, Chesham Place, S.W.1. Kirkby Estate.
SLOane 3463 SIMONSWOOD 3271/3

B. & H. RADIO
EAST STREET, DARLINGTON

BASS & TREBLE SEPARATOR
Enables the use of separate speakers for bass and treble. Permits adjustment of amount of treble relative to bass and also allows speakers of different impedance to be used. Kit of parts £1 9 6

SCRATCH FILTERS
Give marked reduction of scratch level without serious effect on treble response 15 0

VARIABLE SELECTIVITY I.F. TRANSFORMERS. 465 k/cs. Give 3 degrees of selectivity. Per pair £1 0 0

WHISTLE FILTER
Completely eliminates that annoying 9 k/cs inter-station whistle. Easily inserted in speaker leads and suitable for any impedance 2 to 30 ohms. Gives a very sharp, narrow cut, guaranteed better than 40 db, with negligible insertion loss £1 13 6

LYONS RADIO

POWER UNITS TYPE 234A. One of the finest power units made. Input 200-250 v. 50 cps. Outputs: 250 v. at 80 mA. (with internal switch for reduced H.T.) and 6.3 v. at 4.5 A. Exceptionally well smoothed. Includes 5Z4 rectifier valve. Suitable for most types of communication receivers. Incorporates 2½in. meter indicating A.C. input voltage which by means of a panel switch shows H.T. output voltage. New and unused supplied in maker's transit case. PRICE 90/-. Carriage 5/-.
RESPONSER UNITS. 10 valve 1½ metre superhet units, ideal for conversion into a Midlands or London Television receiver. Contain 6-12 Mc/s I.F. transformers, 4 Mc/s bandwidth, 6 valves type VR65 (SP61), 2—VR92's (EA50), and 1 each of VR136 and 137, 3 tuneable slugged coils and dozens of other useful components. PRICE 22/6, carriage 4/6.
TRANSMITTERS, TYPE BC778. Powered by a built-in hand generator. Sends automatic S.O.S. on 500 Kc/s or can be manually operated. Complete with morse tapper, valves (1 each 12SC7 and 12A6), neon indicator lamps, aerial wire, etc. Housed in waterproof cases which are slightly dented externally but in good condition internally. PRICE 30/-, carriage 4/-.
AERIAL RODS. Copperised steel rods 12in. long can be plugged into each other to form an aerial any desired length. PRICE 3/- per dozen, post paid.
"Introduction to HAM RADIO." A splendid book for those who have just, or wish to, obtain a Transmitting Licence. PRICE 3/8, post paid.

3, GOLDHAWK ROAD (Dept. M.W.)
SHEPHERDS BUSH, LONDON, W.12
Telephone: Shepherds Bush 1729

DEMOBBED VALVES 2/8 Post Free

Service Valves and their Commercial Equivalents—

Complete Lists FREE

EX-WAR DEPT. CHASSIS

WITH BRAND NEW condition Valves: IR5, IT4, 1S5, 1S4, complete with Circuit Diagrams, showing how this can be converted to a very excellent set for Beach, Lawn, Picnics, etc. Bargain price only **27/6**. Post 1/-. A Personal Radio for your Holidays and after.

SERVICE SHEETS—The one you require FREE in a dozen at **10/6**.

EASY TERMS up to 10 months—and very near cash price on all Taylor Meters.

FREE Catalogue, Payment Plan and Order form.

NEW—Taylor Television Test Gear: Model 240A, 170A, 65C also on H.P.

AMPLION ALL-PURPOSE TEST-METER

1,800 ohm per volt on all D.C. and A.C. ranges.

10 v., 100 v. and 500 volts D.C. and A.C.

50 mA. and 500 mA. D.C.

Resistance up to 200,000 ohm (3,000 ohm centre scale) with self-contained battery.

5,000 volts range with a separate H.T. test prod (9/6 extra).

Supplied with test prods.

Multicolour scale easily readable.

£3 - 17 - 6

BULGIN

the NEW NEON Test Prod, **10/-**.

BELLING & LEE

Television Aerials, to suit every pocket and every location, from **25/-**.

'VIEWMASTER'

Pre-Amplifier Kit, for London or Midlands, **23/6**.

Wiring Diagram, **1/-**.

HIVAC

Midget and Sub-Miniature Valves

Midget	Each	Sub-Miniature	Each
XSG, 1.5 v. & 2 v.	15/6	XWO.75B	17/6
XW, 1.5 v.	15/6	XY1.4B	17/6
XH, 1.5 v.	10/6	XY1.4C	17/6
XD, 1.5 v.	10/6	XFW10	17/6
XL, 1.5 v.	10/6	XFY 10	17/6
XLO, 1.5 v.	10/6	XFY 11	17/6
XP, 1.5 v.	12/6	XFY 12	17/6
XY, 1.5 v.	15/6	XFG 1	17/6
XVS only 2 v.	15/6		

Order C.O.D. or remit with order.

When writing please mark envelope (WW).

RADIO **BULLS** VALVES
246 HIGH ST. HAMPTON, S.W.12
Telephone: RIVerside 4444

SITUATIONS VACANT

RADIO and television service engineer required, preferably able to drive; permanent position; good wages and commission.—Henderson, 351, Fulham Rd., S.W.10. [5755]

EXPERIENCED radio/TV engineer, good, comfortable, permanent situation available to good man.—Perkins (Leyton), Ltd., 459, High Rd., E.10. Ley. 5300. [5564]

ESTIMATOR required, accustomed to working on own initiative on production radio equipment; only experienced men need apply. S.W. London area.—Box 5258. [5666]

TELEVISION engineer required, experienced on well-known domestic receivers; permanent position with good prospects.—Full details to Norwest Services, Ltd., Edgware 6092.

DETAIL draughtsmen required, preferably accustomed to light electro-mechanical or electronic equipment, or with light engineering or instrument experience.
APPLY, quoting Ref. CHC(102), to Personnel Officer, The General Electric Co., Ltd., Radio and Television Works, Upon St., Coventry. [5691]

APPLICATIONS are invited from senior radio development engineers who are interested in the electrical or mechanical design of airborne radio equipment to service specifications.
WRITE quoting Ref. C.H.C.(2) to Personnel Officer, General Electric Co., Ltd., Radio and Television Works, Coventry. [5711]

EXPERIENCED television and radio engineer required by Provincial firm of high standing, within 40 miles of London; possibility of advancement to responsible position for right man.—Apply Box 5248.

THE BRITISH THOMSON-HOUSTON Co. Ltd., has a few vacancies on the design staff for electronic engineers experienced in development work on audio-frequency, radio-frequency, or radar display equipment, age 25-30.
QUALIFICATIONS: Hons. degree or equivalent in engineering, with subsequent experience in circuit development work; salary according to qualifications, age and experience.
APPLY, giving full particulars, to: Manager, Electronic Engineering Dept., The British Thomson-Houston Co., Ltd., Rugby. [5675]

SENIOR designer-draughtsmen with light engineering, instrument or electro-mechanical experience are required for development work on light mechanisms and/or the mechanical design of electronic equipment to service requirements.
APPLICANTS, preferably with practical training and qualifications to H.N.C. standard, must be capable of working on their own initiative.
WRITE, quoting Ref. CHC(101), to Personnel Officer, The General Electric Co., Ltd., Radio and Television Works, Coventry. [5690]

CHIEF engineer required to take charge of small laboratory at radio manufacturers in N.E. London; must have good technical ability in design of R.F. test equipment and radio components; write, giving full particulars of qualifications and experience, stating age and salary required.—Box 5066. [5646]

RADIO Engineer required by rapidly expanding organisation with headquarters in Brandon; experience in the repair, aligning and calibrating of commercial receivers and amplifiers essential; experience of television receivers an advantage; apply stating age, experience and salary required to—Box 5243. [5656]

A NUMBER of senior and junior vacancies for radio, radar, electronic, television, set-development, service engineers, draughtsmen, wiremen, testers, inspectors, etc., urgently required 50 television service engineers.—Write in confidence, Technical Employment Agency, 176, Clapham Rd., S.W.9. (Brixton 5667). [5105

DRAUGHTSMAN.—Vacancy West London for young draughtsman with experience light mechanisms or instruments; some electronic knowledge an advantage; applicants with interest in design of electro-mechanical products preferred; state age, full details, experience, technical training and salary required.—Box 5481.

MARCONI'S WIRELESS TELEGRAPH Co. Ltd., Chelmsford, require experienced draughtsmen for (a) design of radio communication and radar equipment, (b) design and detail of light structural steel work, (c) installation drawing office; previous D.O. experience essential, preferably on radio or electronic equipment; for (c) previous electrical layout experience would be suitable.—Write, giving details of age, qualifications and experience, quoting reference 142, to Central Personnel Services, English Electric Co., Ltd., 24-30, Gillingham St., London, S.W.1. [5597

A NUMBER of vacancies will arise this summer for draughtsmen at the Bradford works of the English Electric Company; this is due to further expansion, and stable employment under excellent conditions is offered to suitably experienced men; the new drawing office will be concerned with control gear for rolling mills and mining equipment to be manufactured at Bradford. Applications are invited from switchgear and control gear draughtsmen, electrical and mechanical draughtsmen who have not had previous experience in this field but who have had sound electrical or mechanical D.O. experience will also be selected; junior or intermediate grade draughtsmen who wish to gain experience of this interesting electro mechanical work are also invited to apply.—Write, giving full details, quoting reference 138, to Central Personnel Services, English Electric Co., Ltd., 24-30, Gillingham St., London, S.W.1.

No other receiver in its price-class can approach the Armstrong RF103/Type 3 with its 10-valve circuit, highly efficient R.F. stage and its two stages of I.F. amplification with a selectivity better than 7 Kc/s. Among its many refinements are the three stages of A.V.C. negative feed-back, slide rule dial and flywheel tuning. Wave band coverage is from 16-50, 195-550 and 800-2,000 metres, and mains voltage is 200-250 A.C. When the chassis is used as a gramophone amplifier the large amount of amplification available enables a high quality pick-up of the miniature type to be used without additional amplification.

19 Gns. plus P. Tax

OTHER ARMSTRONG CHASSIS

Model EXP83/3. An eight-stage all-wave radiogram chassis is designed to provide quality radio and record reproduction for the "not-so-rich." **£15 . 8 . 8** Plus P. Tax

Model 125/2. The "Armstrong" triumph—a 14-valve all-wave radiogram chassis with a S.W. band down to 10.9 metres. The chassis for the man who wants the best. **£33 . 12 . 0** Plus P. Tax

ARMSTRONG TELEVISION — MODEL T.V.20. A wide-range 21-valve instrument incorporating a 12in. C.R. Tube. **£52 . 10 . 0** Plus P. Tax

Write now for full information

ARMSTRONG

THE CHASSIS PEOPLE

Armstrong Wireless & Television Co. Ltd., Warlters Road, Holloway, London, N.7. *Tel. NORth 3213*

3589

SUCCESSFUL SALES! SATISFIED CUSTOMERS!

Pennine RADIO

THE ALL SEASON SENSATION. ACCLAIMED THE COUNTRY OVER. THE INTIMATE RECEIVER WHICH COMBINES APPEARANCE AND PERFORMANCE. HOUSED IN A BEAUTIFUL WALNUT CABINET. EACH SET FULLY GUARANTEED.

HEIGHT 10", WIDTH 12½", DEPTH 5½"
4 Valve SUPERHET

THE SET THAT SELLS ITSELF!

UNBEATABLE VALUE £11 9 7 INC. TAX

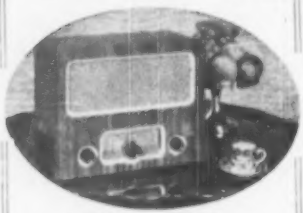

"THE ROVER"

SUPPLIED ONLY THROUGH SELECTED WHOLESALERS. ILLUSTRATED LEAFLETS AND ATTRACTIVE DISPLAY CARDS.

PENNINE AMPLIFIERS
ELLAND YORKS ENGLAND
TEL. ELLAND 2107

BULLANCO 66 QUEEN'S R^D S.E.15 TEL NEW CROSS 1092

ALUMINIUM

SHEET EXPANDED TUBES, ANGLES, BARS, RODS, MOULDINGS, RIVETS

ANY SIZES CUT OR FOLDED

LOCKWOOD
makers of
Fine Cabinets
and woodwork of every description for the Radio and allied trades
LOCKWOOD & COMPANY
Lowlands Road, Harrow, Middlesex. Byron 3704

AMPLIFIERS Quality KIT for HOME CONSTRUCTORS

A complete set of components to construct a 10 watt amplifier including Woden potted mains transformer, 5 valves, 10in. speaker with transformer. Components of the highest quality. No Govt. surplus. Three switched inputs, negative feed back, push-pull output, tone control, steel chassis. Suitable home or small hall. CASH WITH ORDER

Price Complete to the last screw £8 0 0 (Subject)

BEETHOVEN LTD
ELECTRIC EQUIPMENT
Chape Lane, Sands, High Wycombe Tel 1152/3

SITUATIONS VACANT

DRAUGHTSMEN.—It is necessary to expand considerably Marconi's Wireless Telegraph Co., Ltd., drawing office at Acton, all grades of draughtsmen (electrical or mechanical D.O. experience) are required for design and detail work on radio and electronic equipment.—Write, giving full details, quoting reference 123A, to Central Personnel Services, English Electric Co., Ltd., 24-30, Gillingham St., London, S.W.1.

DESIGNER draughtsman required for the design and development laboratory of an engineering company of international repute in London; applicants must possess Higher National Certificate or equivalent qualifications, and have a practical experience of plastic moulds, small special purpose machinery, press tool work and general machine tool knowledge; apply stating age, qualifications and experience.—Box 5071.

DEVELOPMENT engineers required, electrical engineers fully acquainted with up-to-date electronic work and with sound mechanical knowledge are eligible for vacancies in our development laboratory; B.Sc., A.M.I.E.E. or Higher National Cert. essential.—Write, stating personal details, qualifications, experience and salary required, to Personnel Manager, Edison Swan Electric Co., Ltd., Ponders End, Enfield.

ENGLISH ELECTRIC Co., Ltd., Chelmsford, require a junior engineer for design and development work on high power transmitting valves; the successful applicant will be required to serve at least 12 months testing transmitting valves in order to gain necessary experience. Write, giving full details, quoting reference 119A, to Central Personnel Services, English Electric Co., 24-30, Gillingham St., London, S.W.1. [5624

SENIOR television engineer required by the English Electric Co., Ltd., to supervise development and design work, technical control of television receiver engineering at this Liverpool works; applicants, who should be qualified engineers with extensive experience in this class of work, should write giving full details, quoting reference 447, to Central Personnel Services, English Electric Co., Ltd., 24-30, Gillingham St., London, S.W.1. [5654

ELECTRONIC engineers are required by a large aircraft company for experimental work on a new and interesting project; applicants, who should preferably be under 35 years of age, must have received technical education up to a degree standard and should be experienced either in U.H.F. design and measuring techniques or in instrumentation work.—Apply stating age, experience, and salary required, to Box 5061. [5627

JUNIOR electrical engineers are required for the development and design of television camera and associated equipment at Marconi's Wireless Telegraph Co., Ltd., Chelmsford; salary £350-£550 p.a.; senior engineers with research or development experience in this field also required; salary £600-£700 p.a.—Send full details, quoting reference 525A, to Central Personnel Services, English Electric Co., Ltd., 24-30, Gillingham St., London, S.W.1. [5652

TELEVISION.—An opportunity occurs for a competent man to manage a distributive depot in the Midlands for a new company; investment required £1,000 for one-third share, covering existing premises, stock, and vehicle; salary £400 p.a., plus profits; applicant should have had some previous experience in control and organisation of a depot; first-class references required and given.—Write Box 2455, Willings, 362, Grays Inn Rd., London, W.C.1.

AN experienced design draughtsman is required for the Nelson Research Laboratories of the English Electric Co., Stafford; the successful applicant will be required for duties connected with special electronic valves and other vacuum devices and it is essential that applicants should be experienced in this class of work.—Write, giving full details quoting reference 145, to Central Personnel Services, English Electric Co., Ltd., 24-30, Gillingham St., London S.W.1. [5586

SANGAMO WESTON, Ltd., have a vacancy in their instrument sales correspondence section; applicants should have a good general technical training, with some specialisation in electrical measuring apparatus; they should be capable of expressing themselves clearly and concisely both in conversation and correspondence.—Applications should be sent, in strict confidence, to the Employment Manager, Sangamo Weston, Ltd., Cambridge Rd., Enfield, Middlesex. [5400

ELECTRONICS.—Interesting vacancies now exist in the Nelson research laboratories of the English Electric Co., Ltd. University trained engineers or physicists are required for design of special circuits for electronic computing machines at Stafford and in the London area. Vacancies also exist in these laboratories for electronic engineers with H.N.C. (Elec.).—Please write, giving full information, quoting reference 505, to Central Personnel Services, English Electric Co., Ltd., 24-30, Gillingham St., London, S.W.1. [5651

ENGLISH ELECTRIC VALVE Co., Ltd., Chelmsford, require two junior engineers for micro wave work. Previous experience not necessary, but applicants must hold physics or engineering degree or exemption qualifications from Graduate I.E.E. Also senior engineer for work on Klystron and travelling wave tubes. Qualifications: Engineering or physics degree or exemption qualifications from A.M.I.E.E. and several years experience.—Write, giving full details, quoting reference 446A, to Central Personnel Services, English Electric Co., Ltd., 24-30, Gillingham St., London, S.W.1. [5600

WE DON'T

supply anything Ex-Government

ALL BRAND NEW GOODS
—fully guaranteed—

AUTOCHANGERS IN STOCK

GARRARD. RC65A. A.C. D.C. Mixed Records. Standard lightweight magnetic head. £20 15 -.

GARRARD RC65A. A.C. Mixed Records. Standard lightweight head. £15 13 6.

GARRARD RC70A. A.C. Non-mixed. £10 9 1.

INTERCHANGEABLE GARRARD plug in heads for the above. Lightweight. £2 6 8. High fidelity. £3 5 -. Adaptor for RC65 and 70. 6 6.

E.M.I. MARCONI. A.C. Auto-changer. Non-mixed. Hi-Fi head. Complete with transformer. £10 10 0.

COLLARO RC500. A.C. Auto-changer. Non-mixed. Crystal or Hi-Fi head. £10 15 -.

CABINETS. Unpolished for all the above changer. Motor boards ready cut to fit. £3 10 - 33⅓ and 78 r.p.m. GRAM. MOTORS are now becoming available, and we are booking orders in STRICT ROTATION.

TAYLOR TEST GEAR

The entire range by this famous maker is now available on hire purchase. S.A.E. for catalogue and terms.

ALL AVO TEST GEAR NOW IN STOCK. Leather cases for AVO 7, £2 2 6, post free. We are the largest actual stockists of AVO METERS in England. S.A.E. for catalogue and price list.

All items can be supplied C.O.D. up to 15lb. in weight. Otherwise cash with order, please. Special attention to overseas orders, which are free of purchase tax.

MODERN ELECTRICS LTD.
164, Charing Cross Road, London, W.C.2.
Telephone: TEMple Bar 7587.

TRANSFORMERS & COILWINDERS
NEW AND REWINDS

All transformers interleaved & impregnated. Tested for (1) Shorted turns. (2) Insulation at 2 K.V. minimum. E.H.T. A SPECIALITY.
WILLIAMSON O.P. TRANSFORMER.
£3 12 6
J. E. THORNBER & SONS
3 DEAN AVE. MANCHESTER 16
CHO 3849 EST. 1925

TRANSFORMERS & COILS TO SPECIFICATION.
MANUFACTURED OR REWOUND
Filter Coils ± 1% a Specialty.
JOHN FACTOR LTD.
9-11 EAST STREET, TORQUAY, DEVON
'Phone: Torquay 2162

1925 – 1950

For 25 years we really have endeavoured to give an unrivalled service in quality, value and delivery; from the many letters of appreciation we have received, we think, with some success. May we reserve for you our comprehensive

25th BIRTHDAY
RADIO & TELEVISION COMPONENT
CATALOGUE
(Ready Mid August. 6d. Post paid)
Express Service. Complete Satisfaction.
FROM COVENTRY RADIO
Dept. "W"
189, DUNSTABLE ROAD, LUTON

NUSOUND PRODUCTS

136 WARDOUR ST., LONDON, W.1

Tel. GERrard 8845

HOME BUILT TELEVISION AND AMPLIFIER SPECIALISTS

Full Mail Order Facilities (Add Postage)

Mon.-Fri. 9-5.30 p.m. Sat., 9-1 p.m.

A QUALITY TRF RADIO FEEDER UNIT. The feeder unit is a 3-stage wide band TRF, preset to the three main stations with single switch control and including a gram. position. Using two B7G miniature valves and a diode output stage this makes a compact unit, size 7in.-6in.-3in. COST: **£6 10 8** inc. Constructional booklet available. Price **1/8** post free. Cost to build, approximately **£3 10/-**.

A PUSH-PULL 8-WATT QUALITY AMPLIFIER. 7 valves inc. 6V6 output. 3 stages treble and bass boost—2 stages treble cut—neg. feedback. A real quality amplifier for PP fans at the reasonable price of **14 gns.** complete. An AC/DC model will shortly be available.

A 4½-WATT QUALITY AMPLIFIER. This is a quality amplifier at a low cost and incorporates many features usually only obtainable in the more expensive types. Includes 3-stage neg. feedback—separate bass and treble boost controls—top cut, and pre-amp. stage. Uses 6V6 output and a special Hi Fi output transformer. Constructional booklet for AC and AC/DC models **1/8** post free. Can be built for as little as **£7** (surplus valves) AC/DC model **£8** (new valves). Built and tested both models cost **10 gns.**, complete with new valves. (Please send stamp for descriptive leaflet of all our products.)

GRAMOPHONE EQUIPMENT. Connoisseur pickups: Standard, **£3 19/-**; Trans. **13/-**; L/weight, one head, **£5 14 8**; Trans., **15/-**; fibre pickup, **£4 3/-**; special trans., **25/-**; Acos GP20, **71/3**; Goldring lightweight, **61/4**; Miniature or standard sapphire, **6/8**; ruby, **8/8**; Connoisseur Steel 20 for **2/10**; Trailer Sapphire, **6/6**. We stock a full range of Wharfedale speakers. W.B. Duplex speaker, **£6 6/-**; Goodmans Axiom 150 Twin Cone, **£8 8/-**; Goodmans Audiom 60, **£6 15/-**; Goodmans Audiom 22 20 watt twin cone, **£12 13/-**.

METAL RECTIFIERS. Voltages equal D.C. output volts.
S.T.C. H4/250 2.4 kv. 3.5 m/a. **29/6**. S.T.C. RM2/36 420 v. 150 m/a. **21/9**. S.T.C. RM18/20 250 v. 60 m/a. **15/-**. S.T.C. H1 H wave 1 m/a. **2/6**. Westinghouse 36EHT/100, 2.5 kv., pulse input 6.5 kv., **26/8**. 16HT36 1.76 kv. 8 m/a., **21/-**. 36 EHT25 875 v., pulse input 1.8 kv., **13/6**. 14A86 240 v. R.M.S. 180 m/a. MAX.1, **21/2**.

NUSOUND TRANSFORMERS. (Tapped pri. unless otherwise stated.)
A few selections from our wide range, and we can wind to your own spec., delivery 4 days. Estimates free.
250-0-250 v. 150 m/a., 6.3 v. 4 a., 5 v. 3 a., **£2**.
250-0-250 v. 100 m/a., 6.3 v. 3 a., 5 v. 2 a., or 4 v. version, **£1 6 3**.
250-0-250 v. 75 m/a. 6.3 v. 3 a., 5 v. 2 a., or 4 v. version, **£1 1 9**.
200-0-200 v. 60 m/a., 6.3 v. 3 a., 5 v. 2 a., or 4 v. version, **£1 0 3**.
250-0-250 v. 60 m/a., 6.3 v. 3 a., 5 v. 2 a., or 4 v. version, **18/9**.
700 v. 10 m/a., 6.3 v. 1.5 a., 4 v. 1 a., **18/6**.
250-0-500 10 m/a., 6.3 v. 2 a., 4 v. 1 a., **18/6**.
6.3 v. 1½ a. Heatertrans. 230 pri. only, **6/9**.
4 v. 2 a. Heatertrans. 230 pri. only, **6/9**.
6 v. 6 a. C.T. Heatertrans. 230 pri. only, **15/6**.
6.3 v. 3 a. C.T. Heater trans. 230 pri. only, **12/6**.
12 v. 1 a. C.T. Heatertrans. 230 pri. only, **8/6**.

NUSOUND CHOKES.
CH4, 10 H., 150 ohms, 75 m/a., **4/6**.
CH5, 10 H., 300 ohms, 60 m/a., **4/6**.
CH12, 15 H., 250 ohms, 80 m/a., shrouded, **10/9**.
CH8, 10 H., 300 ohms, 100 m/a., shrouded, **9/6**.
CH9, 10 H., 200 ohms, 150 m/a., shrouded, **12/9**.
CH2, 5 H., 80 ohms, 250 m/a., shrouded, **19/6**.

Television aerials can be sent to any part of the country (send for list). Let us quote you by return of post for components of all types.

Our comprehensive list on TV—Radio and Gramophone equipment, etc., is now available. Price **4d.** post free.

MORSE CODE TRAINING

There are Candler Morse Code Courses for

BEGINNERS AND OPERATORS

Send for this Free

"BOOK OF FACTS"

It gives full details concerning all Courses.

THE CANDLER SYSTEM CO.

(Room 55W), 121 Kingsway, London, W.C.2

Candler System Co. Denver, Colorado, U.S.A.

SITUATIONS VACANT

RADIO Engineers required. — The General Electric Co., Ltd., are expanding their Radio Development Laboratory at Coventry and a number of vacancies for Senior and Junior Engineers exist at present and a further considerable number of vacancies will occur during the next few months in the new Laboratory.
APPLICATIONS are invited from Development Engineers with experience of microwave radio or radar techniques who are capable of developing equipment and components to Service Specifications.
WRITE quoting Ref. CHC (3) to Personnel Officer, General Electric Co., Ltd., Radio and Television Works, Coventry. [5725

APPLICATIONS are invited by Kolster-Brandes, Ltd., Footscray, Sidcup, Kent, for a development engineer aged 25-35 years; must possess experience and first-class honours degree in physics, electrical engineering or telecommunications; capable of carrying out work in connection with television development on own iniative.—Apply in writing stating age and qualifications to the Personnel Officer at the above address.

APPLICATIONS are invited for the position of technical representative in the Manchester and Northern area in connection with the Company's manufactures of industrial electronic equipment; appropriate technical and commercial experience with this class of equipment is essential; the position is permanent and the successful candidate will be required to live in the Manchester area; car will be provided.—Apply, quoting reference 556B, to Central Personnel Services, English Electric Co. Ltd., 24-30, Gillingham St., London, S.W.1. [5642

SKILLED tradesmen wanted as Staff Sergeants Armament Artificers in R.E.M.E. If you have completed your apprenticeship as Electrical Fitter, Radio technician, Instrument maker, Toolmaker, Machinist, Motor fitter, Fitter, and are between 20 and 35 years of age you can become a Sergeant in the Royal Electrical and Mechanical Engineers after a brief military (not necessary if you have previous service) and full technical training, with promotion to Staff Sergeant Armament Artificer after an 18-month technical course.
R.E.M.E. offers a variety of work including all the latest modern equipments. Life in R.E.M.E. offers you travel to many foreign countries and plenty of sport and adventure.
PAY after six weeks initial military training 15/6 a day, after 18 months technical training 16/- a day. Staff Sergeants R.E.M.E. are eligible for promotion to warrant officer Class 1, and Commissioned rank as Assistant Electrical and Mechanical Engineers. Marriage Allowance of 40/- to 45/- a week. Rations and clothing free.
MEN engage initially for 12 years, which may be extended. After 22 years an Armament Artificer is eligible for pension.
FULL particulars from any Recruiting Office or write to A.G.21, The War Office, London. [5722

APPLICATIONS are invited for the position of technical design engineer in the F.H.P. motor laboratory at a large electrical engineering company in the West London area; experience of F.H.P. motor design and performance and ability to accept full responsibility of a project from the initial design stage to factory production is essential; applicants should possess engineering degree or equivalent qualifications; salary will be in the region of £600 to £900 per annum according to qualifications.—Apply, giving details of age, education and job history, to the Employment Officer, Hoover, Ltd., Perivale, Greenford Middx. [5691

B.B.C. invites applications for the following posts in Planning and Installation Department, London. Applicants should have a University Degree in Electrical Engineering or equivalent qualification. Studio Section: Applicants should also have a good basic knowledge of television theory and practice. (1) Engineer for work on development of television recording processes, preparation of specifications for manufacture of equipment, supervision of installation and acceptance trials and conduct of necessary correspondence. Practical experience of cinematographic equipment for sound and picture recording and knowledge of optics, photography, control of film processing, and mechanical design of cameras are desirable. (2) Engineer for planning and development of television studios and preparation of specifications, etc., as in (1). Practical experience of television cameras and associated equipment and apparatus for film scanning, etc., and/or working knowledge of film studio practice are desirable. (3) Engineer for assistance in television work. Practical experience of television studio or O.B. equipment is desirable but applicants with considerable experience of studio sound equipment considered. Radio Section: (4) Engineer for preparation of specifications for radio and video frequency transmitters, supervision of installation and acceptance trials and conduct of necessary correspondence. Thorough basic knowledge of power and radio engineering is essential. Experience in planning and installation of short wave and v.h.f. transmitters and associated equipment desirable. Knowledge of television theory and practice and/or transmission line and aerial technique advantageous. Salaries for posts (1) (2) and (4) in grade with annual increments of £40 and maximum £890 per annum; salary for post (3) in grade with annual increments of £30 and maximum £690 per annum.—Applications stating age, qualifications and experience and for which post application is being made to reach Engineering Establishment Officer, Broadcasting House, London, W.1, within 7 days.

SALE! SALE!

To make space in our Warehouses in preparation for re-organisation we are "slaughtering" prices of goods offered below. Help us and help yourselves while supplies last. First come, first served, so avoid disappointment and order early.

R.1155 COMMUNICATIONS RECEIVERS. This world renowned 5 waveband R.A.F. receiver is too well known for the specification to be repeated. Every set is guaranteed in working order, and is aerial tested before despatch. Full conversion details for mains use supplied. ONY **£7/19/6** (carriage 12/6).

RECEIVERS TYPE 25/73. Part of the TR.1196. Covers 4.3-6.7 Mc/s, and makes an ideal basis for an all wave superhet, modification details supplied. Complete with six valves: 2 ea. of EF36 and EF39, and 1 ea. EK32 and EBC33. New condition. ONLY **19/6** (postage etc. 2/6).

RECEIVERS 18. Covers 6-9 mc/s and only requires normal battery supply to operate. Complete with 4 valves: 3 of VP23 and 1 of HL23DD. New condition. ONLY **15/-** (postage etc. 2/6).

BATTERY AMPLIFIERS. Ex-R.A.F. Originally used for inter-com. on aircraft but ideal for use as a pre-amp. or with a gramo. pick-up. Complete with valves QP21 and HL210 in original transit cases. ONLY **19/6** (postage etc. 2/6).

RECEIVERS R1132A. Covers 100-124 mc/s, but lends itself to conversion for other frequencies. Has superb slow motion drive and tuning scale, and 0-.5 ma. tuning meter. Complete with 11 valves and only requires normal power pack for 6.3v. valves to operate. ONLY **59/6** (carriage etc. 12/6).

T1154 TRANSMITTING ASSEMBLY. A vital part of the famous T1154 Transmitter this assembly contains some beautiful transmitting condensers, pre-set tuning devices, variable inductances, large bar and circular knobs, etc., etc. Designed as a complete replacement unit these are BRAND NEW IN MAKERS' CARTONS. ONLY **7/6** (carriage 3/6).

POWER UNITS TYPE 10. Ex-R.A.F. Input 24 v. Output 6 v. 5 a., 150 v. 10 a., 300 v. at 70-240 ma. ONLY **12/6** (carriage 5/-).

AMERICAN INDICATOR UNIT APN4. Less valves but complete with CR Tube 5CP1. Ideal for conversion into a 'scope, or worth pounds in breakdown value. In perfect condition. ONLY **37/6** (carriage etc. 12/6).

AMERICAN RADAR RECEIVER APN4. Less valves. In addition to the receiver components this aircraft receiver contains the power supply for the indicator. Contains shoals of components, including 15 valve holders, high voltage condensers, switches, I.F. transformers, etc. etc. Perfect condition. ONLY **17/6** (carriage etc. 5/-).

INDICATOR TYPE 62. Less valves and CR Tube. This fine two deck unit is another first class proposition for component value. Contains 20 valve holders, condensers, resistors, potentiometers, etc., etc. ONLY **17/6** (carriage etc. 7/6).

Cash with order and please write name clearly.

U.E.I. CORPORATION

RADIO CORNER

138, Grays Inn Rd., London, W.C.1.

(Phone: Terminus 7937.)

Open until 1 p.m. Saturdays. We are two minutes from High Holborn (Chancery Lane Station) and 5 minutes from King's Cross.

PLEASE NOTE THAT WE SHALL BE CLOSED FROM AUGUST 8th-14th.

THE
BRITISH NATIONAL
RADIO SCHOOL
ESTD. 1940

NOW IN OUR ELEVENTH YEAR AND STILL

NO B.N.R.S. STUDENT HAS EVER FAILED

To pass his examination(s) after completing our appropriate study course!

NOTHING SUCCEEDS LIKE SUCCESS

and what we have done a thousand times already, for others, we can do again, for YOU!

A.M.I.E.E.,† A.M.Brit.I.R.E. and CITY and GUILDS Radio and Telecommunications Exams., etc., etc.

† *In specially approved cases*

Six months' trial period without obligation to continue.

Please mention this advt. and send for free booklet and sample lesson to:—

STUDIES DIRECTOR
BRITISH NATIONAL RADIO SCHOOL
66, ADDISCOMBE ROAD, CROYDON
Phone: Addiscombe 3341

METAL STAMPINGS
FOR
or
Wireless & Electrical Industries
Let us have your enquiries
M. & J. TOOLS CO.
1 Silvermere Ave., Romford. *Phone: 1337*

TO DEALERS
We can offer a limited number of Dealers a reliable and quick
RADIO & TELEVISION REPAIR SERVICE
REGO-FRASER
TELE-RADIO ENGINEERS
82, Nare Street, Woolwich, S.E.18
Tel. WOO. 1804

THE NORTHERN POLYTECHNIC
HOLLOWAY ROAD, N.7.
Principal: T. J. DRAKELEY, D.Sc., Ph.D., F.R.I.C., F.I.R.I.

Department of Radio and Musical Instrument Technology.

Head of Department:
S. A. Harris, O.B.E., M.C., M.Brit. I.R.E.

Full-time Day Courses in
TELECOMMUNICATIONS ENGINEERING
in preparation for all recognised qualifications in this subject. Practical laboratory and workshop experience provided.
Prospectus free on application to Secretary. New term begins September 25th

SITUATIONS VACANT

QUALIFIED engineer required for television aerial and transmission line development and research for laboratory in the London area: wide experience of S.W. aerial measurements essential: permanent position offered with liberal salary to suitable candidate.—Write Antiference, Ltd., 67, Bryanston St., London, W.1. [5685

ESTIMATING engineer required by the component division of the Plessey Co. Ltd. Applicants should have experience which will enable them to handle detailed estimating for mass production machine and light assembly work.—State full details of experience, with age and salary required, to Personnel Manager, The Plessey Co., Ltd., Ilford, Essex. [5684

THE DE HAVILLAND AIRCRAFT Co., Ltd., have vacancies for electrical draughtsmen, aircraft experience preferred but consideration will be given to those experienced in switchgear and associated component design who could readily adapt themselves to aircraft installation technique.—Apply in writing to Chief Draughtsman, The De Havilland Aircraft Co., Ltd., Hatfield Aerodrome, Herts.

SENIOR physicist or electronic engineer is required by the English Electric Valve Co. Ltd., Chelmsford, for research and development work on travelling wave tubes.—Applicants with considerable experience in this field should write, giving full details of qualifications and experience, quoting reference 440, to Central Personnel Services, English Electric Co., Ltd., 24-30, Gillingham St., London, S.W.1. [5625

SITUATIONS WANTED

RADIO engineer, aged 41, having just disposed of own business, requires position of responsibility with retailer or manufacturer; twenty-five years' experience, including eight with E.M.I. Service, Ltd.—Tel. Hatch End 978 for appointment. [5678

AGENCIES

ENGINEER / SALESMAN seeks first - class agencies or representation.—Taylor, 2, Argyle Rd., Ilford. [5656

TECHNICAL TRAINING

CITY & Guilds (Electrical, etc.), on "No Pass—No Fee" terms. Over 95% successes. For full details of modern courses in all branches of Electrical Technology send for our 176-page handbook, free and post free.—B.I.E.T. (Dept. 368A), 17, Stratford Place, London, W.1.

TUITION

TELEVISION.

THE Gothic Television School specialises solely in training in television. All tutors possess university degrees and/or corporate membership of professional institutions and are appointed individually to postal course students to ensure complete and thorough training. Principals M.B.E., B.Sc., M.Brit.I.R.E., education committee members, etc. Courses assume no previous television knowledge and provide guaranteed training for Brit.I.R.E. and R.T.E.B. examinations. Numerous well-known companies have adopted the School's Basic Television Course as standard television training for their staffs. Moderate fees.—Details from Gothic Television School, 15, North Avenue, London, W.13. [0051

RADIO training.—P.M.G. exams. and I.E.E. Diploma; prospectus free.—Technical College, Hull. [0611

CAREERS in radio, television and electronics; write for free brochure giving details of 1-year, 2-year and 5-year day courses. E.M.I. INSTITUTES, Dept. WW, 10, Pembridge Sq., London, W.2. Bayswater 5132-3. (Associated with "His Master's Voice.") [0001

WIRELESS officer's attendance and "Radiocerts" postal course.—Apply Manager, The Wireless School, Manor Odns., London, N.7.

NOTHING succeeds like success! What we have done a thousand times we can do again, for you.—See the B.N.R.S. Advt. on page 70. [6811

A.M.I.Mech.E., A.M.Brit.I.R.E., City and Guilds, etc., on "no pass—no fee" terms, over 95% successes. For details of exams. and courses in all branches of engineering, building, etc., write for 176-page handbook.—B.I.E.T. (Dept. 367B), 17, Stratford Place, London W.1. [1577

TELEVISION postal course for radio trades Examination Board's diploma, also postal courses for P.M.G. 2nd and 1st class Certificates and Amateur Radio Transmitting licence.—Apply British School of Telegraphy, Ltd., 179, Clapham Rd., London, S.W.9. (40 years' experience in training students in wireless telegraphy and allied subjects.) [2586

THE Institute of Practical Radio Engineers have available home study courses in every phase of radio and television engineering, specialising in the practical training of apprentices in the retail trade; enrolments limited; fees moderate.—The Syllabus of Instructional Text may be obtained post free from the Secretary, I.P.R.E., Fairfield House, 20, Fairfield Rd., Crouch End, London, N.8. [0088

BUSINESSES FOR SALE AND WANTED

TRANSFORMER Manufacturing company desire to dispose of their Rewind department; hundreds of satisfied customers retained during past 12 years; stock and goodwill at low price to those who proved ability to continue this service; details to principals only.—Box 5245. [5688

BUILD YOUR OWN BASS-REFLEX CABINET!

Finished cabinet stands 2ft. 6in. high × 1ft. 3in. wide × 1ft. deep with hole for 8in. speaker at top and slotted vent near bottom, internal reflector. It is ready for staining and polishing or painting, lacquering, etc. Scientifically designed by acoustics expert to give superb bass response and full treble. For use with high-quality amplifiers or to revolutionise the tone of the domestic radio set. Complete kit of all 8in. patent timber, materials and full instructions, 70/-, or ready built, 85/-. High-grade 8in. p.m. speaker unit to handle 6 watts, 25/-, or Wharfedale Super 8in. with cloth surround, 80/-.

SYMPHONY No. 1 (Amplifier) by R.S.S.! The most versatile domestic audio amplifier on the market today. Independent control of bass, middle and top, separate scratch-out, negative feedback. For A.C. 200–250 v. Input for magnetic, hi-fi and crystal pickups; 3 w. output 3 ohms or 15 ohms. Full provision for Tuner. Price £8/19/6. Money refunded if not delighted!

SYMPHONY No. 2. Same theme as No. 1, but having 10 watts push-pull output, superb quality. 3, 7.5 and 15 ohms. Inputs for magnetic, crystal and hi-fi pick-ups, full provision for Tuner. Built on handsome black-crackle chassis. Wodon mains and output transformers. Price 13 gns.

No. 1. HIGH-QUALITY TUNER, specially recommended for above amplifiers and kind. Wilkinson, Charles, Rogers and other quality amplifiers. L. & M. wave T.R.F., with infinite impedance detector, illuminated "Airplane" dial with escutcheon and glass virtually indestructible. Price of Complete kit and Constructional Manual £4/10/- or ready built £5/10/-.

No. 2 QUALITY SUPERHET TUNER, L.M. & S. wave, large full-vision dial assembly, spin-wheel tuning. As kit, £7/10/-; built, £8/10/-.

AUTOCHANGERS: Collaro BC48, 8 records mixed, £14/6/5; Marconi, 10 records mixed, with hi-fi lightweight pick-up taking miniature needles, 10 Gns. incl. transformer and filter network, or £4/10/- in polished table cabinet.

COLLARO STANDARD MICROGRAMS, new in original cartons, £13/10/-. Case with motor-board only 47/6.

RADIOGRAM CABINETS, de luxe job in veneered walnut, 3ft. 3in. high × 2ft. 6in. wide × 1ft. 4in. deep, £11/10/-.

FULL BARGAIN CATALOGUE, 9d. DEMONSTRATIONS—daily. Terms: C.W.O. or C.O.D.

NORTHERN RADIO SERVICES
18, Kings College Road, Swiss Cottage, London, N.W.3. *Phone: PRImrose 8314*

The Voigt Loudspeaker is still ahead of all others. P.M. Unit with 22,000 line gap flux £40 ex works. Corner Horns (in the white) £19 10 0 or £47 10 0 ex works.

Home demonstrations arranged in London area.

Order from
VOIGT PATENTS LTD.,
Sydenham, S.E.26 *Tel: Syd 6666*

ELECTRONICS
DUPLEY
LTD.
CRANMER AV. EALING.W 13.
Transformer and Coil Manufacturers to the Trade
Telephone: EALing 5689

TWIN TEST METER PANEL
comprising
Microfl 0-5 m/a and Microfl 0-40 v. meters. Variable resistance shunt (soldered). 6-way Yaxley switch. SP-ST Toggle switch. 3 Potentiometers etc.
Outstanding value at 12/6 *post free*

MAKE YOURSELF HEARD
MOBILE (6 volt) P.A. EQUIPMENT *comprising*
4 valves, 7 watt amplifier, housed in metal carrying case 12" x 6½" x 6½" fitted with control panel. Supplied complete with Vibrator power supply.
Offered at 9 Gns. *Carr. Paid*
RADIO UNLIMITED,
ELM ROAD, LONDON, E.17
Tel.: KEY 4813

SELENIUM RECTIFIERS, CHARGER KITS, CHARGERS

New Goods with Full Guarantee

S.T.C. SELENIUM L.T. RECTIFIERS, up to 300 watts, bridge, h.w. or c. tap, 200 m/a to 10 amp., with or without transformer. Popular types from stock. A few of our large stock—6 v. 0.5 amp., **4/10**; 2 v. 0.3 amp., **3/10**; 6 v. 1 amp., **7/2**; 6 v. 2 amp., **9/-**; 6 v. 4 amp., **16/6**; 6 v. 10 amp., **22/6**; 12 v. 1 amp., **9/6**; 12 v. 2 amp., **12/6**; 12 v. 2.5 amp., **17/-**; 12 v. 4 amp., **19/6**; 12 v. 10 amp., **42/6**. Higher voltages in stock. Add postage **9d.** up to **12/6**, **1/-** above.

FOOLPROOF CHARGER KITS. New Minor Kit as illustrated, 12 v. 1 amp. rectifier, 20 watt transf., ballast bulb, case screws, etc., **42/-**, post 1/4. Iron case, **32/6**, for 2 v. to 12 v. charging. New 2 amp. kit for 2 v., 6 v., 12 v. transformer, ballast bulb, 4in. diam. rectifier, **38/6**, or with case as illus., **52/-**. Automat 2 amp. 6 v., 12 v. charger ready for use, **65/-**, with 18 months' guarantee. "Automat" 2 v., 6 v., 12 v. 4 amp. slider charger, weight 22 lb., **£6 5 0**, plus 12/6 crate and carr.

HEAVY DUTY KITS. S.T.C. 12/15 v. 4 amp. rectifier, 70 watt transformer, barrette for 2 v., 6 v., 12 v. charger, foolproof operation, full instructions, **52/6**. Ditto but for 2 v., 6 v. 4 amps., **48/6**, post 1/4. Slider Kit, 100 watt transf., 4 amp. rectifier, slider resistator, high grade ammeter for 6 v., 12 v. charger, **£3 15 0**. Ditto but 150 watt trans. and giant finned 6 amp. rectifier, slider res., ammeter, **£5**, weight 18 lb. For small radio store 1 to 20 cell 1.2 amp. kit transformer 100 watts, 2 amp. rectifier, barrette bulb, for continuous running, **£4 15 0**, post 1/6.

ELIMINATOR KIT for 120 v. 50/60 m/s eliminator, 20 watt trans., 120 v. 30 m/a h.t. rect., 2 v. 0.3 amp. trickle mod., 2 x 8 mfds. condensers, case, etc., **42/-** or without case **35/-**, post 1/3.

SELENIUM SMALL SPACE H.T. RECTIFIERS. 250 v. 60 m/a w. fors. c. d.c. sets, **7/-**; 110 v. 60 m/a, **6/-**; 200 v. 100 m/a bridge, **13/6**; 300 v. 0-250 v. 80 m/a c.t., **13/6**, post 6d. extra.

BURAT. Accumulator cell demulphater and conditioner, **1/6**, post 4d.

CHAMPION PRODUCTS

43 Uplands Way, London, N.21. Phone LAB 4787

THE "FLUXITE QUINS" AT WORK

"Our T.V. is working O.K.
This Fight is the high spot today.
Gosh! Brutiser looks sick
It's a knockout! Look! Quick!
"You're right! Fetch the FLUXITE!"
hauled EH.

See that **FLUXITE** is always by you—in the house—garage—workshop—wherever speedy soldering is needed. Used for over 40 years in Government works and by leading engineers and manufacturers. Of all ironmongers—in tins, **10d.**, **1/6** and **3/-**.

TO CYCLISTS! For stronger wheels that will remain round and true, here's a time-tested tip. Tie the spokes where they cross with fine wire AND SOLDER. It's simple—with FLUXITE—but IMPORTANT.

The **FLUXITE GUN** puts **FLUXITE** where you want it by a simple pressure. Price **2/6**, or filled, **3/6**.

FLUXITE

SIMPLIFIES *ALL* SOLDERING

Write for Book on the Art of "SOFT" Soldering and for Leaflet on CASE-HARDENING STEEL and TEMPERING TOOLS with FLUXITE. Price 1d. each.

FLUXITE LTD. Dept. WW., **BERMONDSEY STREET, LONDON, S.E.1.**

BOOKS, INSTRUCTIONS, ETC.

"A PORTABLE TELEVISOR."

BRADBROOKS proudly announce their second First-ever publication by Edwin N. Bradley, "A Portable Televisor" gives 56pp of complete information for building a 5in or 6in TV set for either area, the 5in prototype measuring only 15in.×11in.×7in with powerpack, tube, speaker, etc., all self-contained; not a hashed-up conversion but a new design with some novel features. order your copy, price 5/- (5/2 post paid) from Bradbooks, Sennen, Penzance, Cornwall. Do not forget "Personal Portables," too, a mine of information at 2/6 pp. [5667

BERNARDS Radio Publication. Send 1d stamp for list now. MASON & SON, Ltd., Wivenhoe, nr. Colchester, Essex. [0094

WEBB'S 1948 radio map of world, new multi-colour printing, with up-to-date call signs and fresh information on heavy art paper, 4/6, post 6d; on linen, on rollers, 11/6, post 9d.—Webb's Radio, 1-4, Soho St., W.1. Gerrard 2089.

I.P.R.E. Technical Publications: 5,000 alignment peaks for superheterodynes, 4/9 post free; The Practical Radio Engineer, quarterly publication of the Institute, sample copy 2/- post free; membership and examination data, 1/- post free.—Secretary, I.P.R.E., 20, Fairfield Rd., London, N.8. [0089

CRYSTALS

of OUTSTANDING QUALITY

TYPE "S"

Frequency range: 100 Kc/s to 15 Mc/s. Black bakelite case, $1\frac{1}{2}$" high, $1\frac{5}{16}$" wide, $\frac{7}{8}$" thick, with two $\frac{1}{4}$" diameter pins spaced $\frac{7}{8}$" apart.

BROOKES CRYSTALS

10, Stockwell St., Greenwich, London, S.E.10

Phone: GREenwich 1828. Cables: Xtals London. Grams: Xtals Green London.

THE SERVICE ENGINEER'S FIRST CHOICE

TAMSA

HIGH QUALITY MAGNETIC TAPE HEADS

are now available from stock, also TAPE OSCILLATORS and other COMPONENTS BOOKS (5/4 post free G.B.) & CONSTRUCTOR'S ENVELOPE (4/3 post free G.B.).

AMPLIFIER DELIVERIES ARE RAPIDLY IMPROVING

TAPE DECKS & RECORDERS SOON!

Write for latest Price List

AUDIGRAPH LTD.

Dept. MR3, 74, Great Hampton Street, HOCKLEY, BIRMINGHAM, 18

More British Bargains

METERS. A.C./D.C. Switchboard, 1.C. 4½in. G.E.C. new, 0-40 amps and 0-60 volts, **35/-** ea. 5in. Switchboard 300 volts and 50 amps, **35/-**. 4½in. I.C. Switchboard 14 amps., **35/-**. 14 amps. D.C. only M.C., **25/-**. Panel Meters A.C./D.C. Thermal Ammeters 2½in. flush 0-6 amps. Ferranti, new, **10/-**. D.C.M.C. Milli-ammeters 2½in. flush 0-1 m.a., **15/-**, 0-50 m.a., 200 m.a., 500 m.a., **7/6** ea. Voltmeters D.C.M.C. 100-0-100, **7/6**. Ammeters 2in. D.C.M.C. 50-0-50 amps., **5/-**, 0-20 amps., **5/-**.

VITAVOX H.F. HORNS. 2ft. 8in. x 1ft. 4in. x 3ft. long, as new, **30/-**. Vitavox Units, **40/-**. 21in. square mouth Horns, **25/-**. Bellmouth speaker horns, **25/-**. Carriage extra.

RECEIVERS 1132A and 1326. V.H.F. 11 valve superhets, 2 models identical 100-126 Mc/s or 65-85 Mc/s, grey cabinet 19in. x 11in. x 10in. Price with valves, **45/-**. Carriage 7/6.

COSSOR 339 DOUBLE BEAM OSCILLOSCOPE, rebuilt, recalibrated, tested and as new.

HAND MAGNETO GENERATORS, 4-magnet type, wound armature driven by gearing in handle, output 75 volts 25 m.a. A.C. approx., **18/6**. Carriage 2/- extra.

D.C. ELECTRO MAGNETS, weight 10 oz. twin coil, lift 4 lb. on 6 volts, 3 lb. on 4 volts, and 1½ lb. on 2 volts, **5/-**. Postage 6d.

S.L.S. 36, circular horseshoe Magnets 1⅞in. dia., ⅝in. thick, ¼in. polar gap drilled poles, weight 2 oz., lift 3 lb., **2/6** each.

DYNAMOS. New surplus machines, high current for plating work etc., 12 volts 55 amps, 3,000 r.p.m., **£6 10/-**. Carriage 5/-.

WINDMILL DYNAMOS. 12 volt 10/15 amp. C.A.V. totally enclosed, 1,425 r.p.m., **40/-**. Carriage 5/-.

MOTORS. Croydon 1/12 H.P. A.C. 230 volts, 3,000 r.p.m., **25/-**. 1/3 H.P. S.P. 230 volt new capacitor, 1,425 r.p.m., **£6**. ½ H.P. 3-ph. 400 volts, **£6 10/-**. Reconditioned ½ H.P. 230 volt A.C. motors, 1,425 r.p.m., **£4 10/-**. Carriage on any motor 5/- extra.

ELECTRADIX RADIOS

214 QUEENSTOWN RD., LONDON, S.W.8

Telephone: MACaulay 2159

5 SOLON MODELS

SOLON electric soldering irons have proved their capacity for continuous service under the most exacting conditions. 5 models; 240 watt oval tapered bit; 125 watt oval tapered and round pencil bits and 65 watt oval tapered and round pencil bits. Each model complete with 6 feet of Henley 3-core flexible. Now available from stock. Write for folder Y.10.

HENLEY SOLON ELECTRIC SOLDERING IRONS

W. T. HENLEY'S TELEGRAPH WORKS CO. LTD.
51-53 Hatton Garden, London, E.C.1

HILL & CHURCHILL LTD.

BOOKSELLERS

SWANAGE · DORSET

Available from stock :

Ghirardi—" Radio Physics Course "	37.6
Ragan—" Microwave Transmission Circuits "	72.6
Ridenour—" Radar System Engineering "	64.-
Lawson & Uhlenbeck—" Threshold Signals "	42.6
Bronwell & Beam—" Theory and Application of Microwaves "	51.-
Zworykin & Morton—" Television "	56/-
Smith—" Antenna Manual "	17.6
Wellman—" Elementary Radio Servicing "	21.-

(Postage extra)

CATALOGUE ON APPLICATION

THIS Does these

ACCURATELY and QUICKLY Chassis, Brackets, Shrouds Condensers and Transformer Clips, in Steel or Aluminium. (Five sizes—12" to 36") Trepanner available

"SNAP" Cutter, Notcher and Shearer.

Details with pleasure.

Please Quote File No. or Serial No. of your tool if possible.

Our 6 page illustrated 1950 FOLDER will be ready shortly and copies reserved for our many " W.W. " Friends. Please ask for yours, quoting Ref. No. or date of your original enquiry.

A. A. TOOLS (W), 197a Whiteacre Road ASHTON-U-LYNE

QUARTZ CRYSTAL UNITS

QCC

For—

***AIRCRAFT, MARINE AND COMMERCIAL USE* are available in the complete range from 35 kilocycles to 15 megacycles.**

Alternative mountings in standard two-pin A.M. pattern 10X, International octal, and miniature type FT243, can be supplied for most frequencies.

Prices are fully competitive, and we specialise in prompt deliveries for urgent requirements.

WE WELCOME YOUR ENQUIRIES.

THE QUARTZ CRYSTAL Co., Ltd.
63-71 Kingston Road.
NEW MALDEN, SURREY
Telephone : MALden 0334

BASS REFLEX CABINETS

Our RU12 is the best for the Axiom 12 and 22, the Barker, and Wharfedale Golden Units. *From* **£10**

Stamp for leaflets from

CABINETWARE
SUMMIT WKS., HEYES ST. BLACKBURN

YOUR METER DAMAGED ?

Leading Electrical Instrument Repairers to the Industry.

Repairs to rolled enclosures of all makes and types of Voltmeters, Ammeters, Microammeters, Milliammeters, Test meters, Electrical Thermometers, Ammeters, Instruments, Synchronous Clocks, etc. Quick deliveries—for speedy estimate send defective instrument by registered post to:

L. GLASER
Electrical Instrument Repairers
341 CITY ROAD, E.C.1
Tel. Terminus 2489

ENGINEERS !

Whatever your age or experience, you must read "ENGINEERING OPPORTUNITIES". Full detail of the easiest way to pass A.M.I.Mech.E., A.M.I.C.E., CITY & GUILDS (Electrical, etc.), MATRIC., etc., on "NO PASS—NO FEE" terms, and details of Courses in all branches of Engineering—Mechanical, Electrical, Civil, Auto., Aero., Radio, etc., Building, etc. If you're nothing beneath £10 a week, let us show what intelligent use and settled study may do. Send for "ENGINEERING OPPORTUNITIES" today—FREE!

176 PAGES Free!

B.I.E.T.
387 Shakespeare Hse.
17-19 Stratford Place
London, W.1.

BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY

MINIATURE RELAY

D.C. *up to 24 volts* TYPE *MIN/SI*

DOUBLE POLE CHANGE-OVER CONTACTS

SIZE 1½" × 1¾" × 1"

Ask for Cat. 124/W/W

LONDEX LTD

Manufacturers of Relays

207, ANERLEY RD., LONDON S.E.20.
SYDenham 6258-9

WILCO ELECTRONICS

RECEIVERS R.1132A. Brand new, in perfect condition, range 100 to 124 mc/s., standard 19in. rack mounting, fitted tone control, manual and A.V.C., large calibrated slow motion dial tuning meter etc., a really first class receiver. Our price **£4/19/6.**

POWER PACK, type 3, for above receiver. Brand new, in perfect condition, input switched 200 to 250 volts, A.C. 50 cycle, with two smoothing chokes, fitted D.C. voltmeter 0-300, milliampere meter 0-150, fuses, etc. A superb job. **£4/19/6.**

SPECIAL OFFER. For above receiver and pack, **£8/17/6** the pair.

PYE STRIPS, Five R.F. stages, det., and video. Ideal for vision strip. Our price **37/6,** less valves. Post 2/6.

OSCILLOSCOPE units to build your own miniature 'scope. Case 11 x 9 x 6½in., with 3 valves, tube holder and base for VCR139A, brill. and focus controls, shift controls. Only **18/-.** Carr. 1/6.

C.R. TUBES. VCR139A, 2½in., **15/-** each post and pkg. 2/6. Holders for same, **2/-** each.

CRYSTAL PICK UP. Rothermel Senior, **35/-** each.

TRIMMING TOOLS. In Holder, **15/-** set.

WIRELESS FILM RECORDERS, for 35 mm. Film. With cutting head etc. Incorporating a 230 v. Mains motor **£20.**

CUTTERS STYLII, 6/- per doz.

201 LOWER ADDISCOMBE ROAD, CROYDON ADD. 2027

RECONDITIONED TIMESWITCHES

Ideal for 1,000 automatic switching jobs — Shop windows, poultry lights, heaters, radios, neons etc. Every one guaranteed for a year. Wholesale & Export enquiries invited. From **30/-** each (key, instructions post free)

Write: J. DONOHOE
2, UPPER NORFOLK STREET,
NTH. SHIELDS, NORTHUMBERLAND

URGENTLY WANTED

15 RECEIVERS BC-312

In good condition, preferably not converted.

Box 5294
c o " Wireless World "

TYPE AC/3 TELEVISION PRE-AMPLIFIER

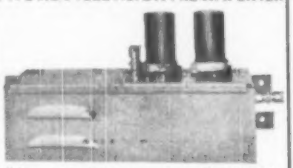

" Unquestionably the best TELEVISION Pre-Amplifier, as a consideration of the specification and a trial will prove."

Circuit Specification.

● Two triode stages ensuring low " noise."
● 1st stage neutralized, 2nd stage operating as a low impedance load for the neutralized stage, thereby still further reducing the " noise," without sacrifice of gain. ● Self-contained power supply to suit 200-250 v. A.C. mains. ● Balanced and unbalanced socket connections to suit all receivers. ● Gain 16.5 dbs at full band width. Noise factor, 6-8 dbs compared with normal pentode valves. ● An improved performance is guaranteed. Types AC/3L (London) and AC/3B (Birmingham).

Further particulars on request. See under " Classified " for further announcements.

Spencer-West, Quay Wks., Gt. Yarmouth, N'f'k

Printed in Great Britain for the Publishers, Iliffe & Sons, Ltd., Dorset House, Stamford St., London, S.E.1, by The Cornwall Press Ltd., Paris Garden, London, S.E.1. Wireless World can be obtained abroad from the following: Australia and New Zealand: Gordon & Gotch, Ltd. India: A. H. Wheeler & Co. Canada: The Wm. Dawson Subscription Service Ltd.; Gordon & Gotch, Ltd. South Africa: Central News Agency, Ltd. William Dawson & Sons (S.A.), Ltd. United States: The International News Co.

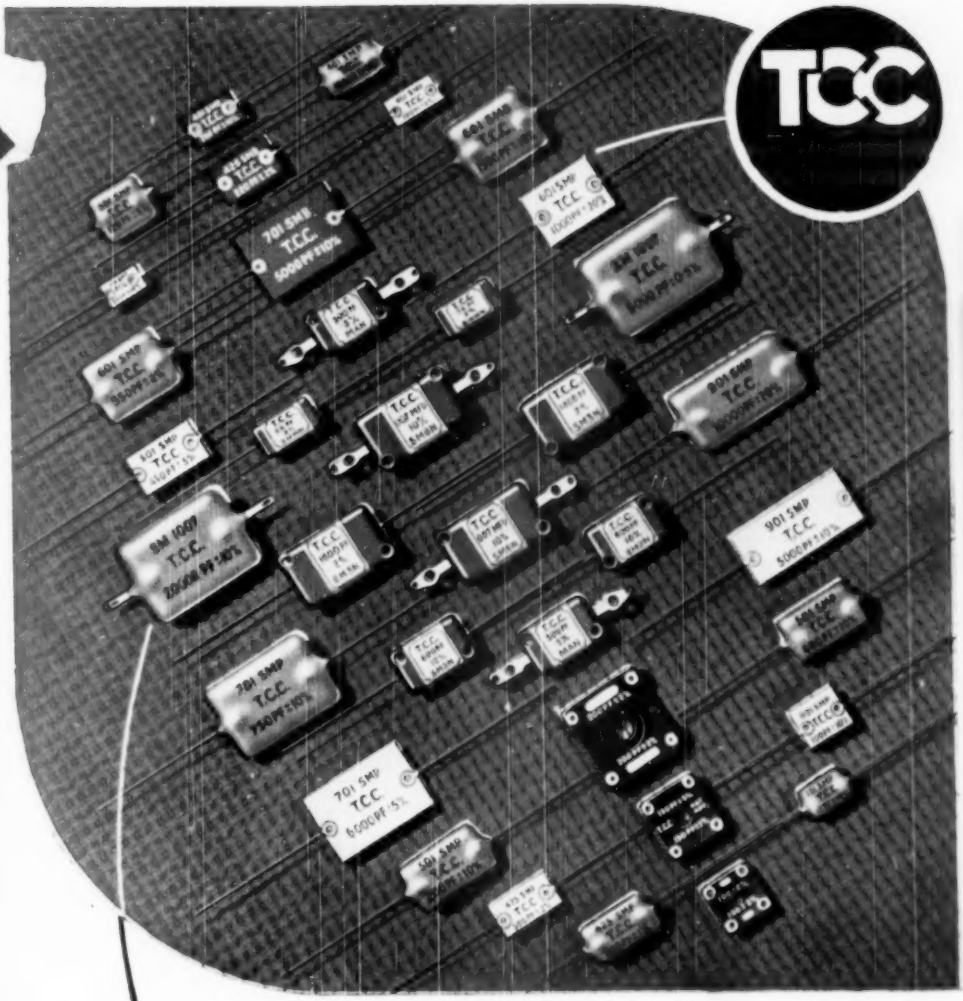

SILVERED MICA CONDENSERS

Some of these condensers are wax protected, some are in moulded bakelite cases, and others are coated with synthetic enamel. This ensures that there are types to meet not only normal requirements, but also the demands of tropical and other severe conditions. All combine capacitance stability, low losses and accurate tolerances, with minimum dimensions.

The intimate contact between the silver electrode and mica dielectric ensures a high degree of stability.

Write us about your requirements.

THE TELEGRAPH CONDENSER CO. LTD

RADIO DIVISION: NORTH ACTON, LONDON, W.3. Tel: ACORN 0661

SOME MAKERS CALL THEM *Condensers*

OTHER MAKERS CALL THEM *Capacitors*

—BUT THEY *ALL* AGREE THAT THEIR MANUFACTURE CALLS FOR

Ersin Multicore Solder

The Finest Cored Solder in the World

Manufacturers all over the world rely on *Ersin Multicore Solder* in the manufacture of radio and television components. They know that only *Ersin Multicore*—with its three-core construction—gives guaranteed flux continuity, instantaneous melting and freedom from 'dry' or H.R. joints. In addition, because *Ersin Multicore* contains extra-active, non-corrosive Ersin flux, joints can be made easily on heavily oxidised surfaces.

At the Plessey Company Limited's Works, Ilford, where Ersin Multicore Solder is used for bridging the gap between the stator plates and terminals of variable condensers.

Soldering tags and wires of radio type tubular paper capacitors with Ersin Multicore Solder at the Dubilier Works, London.

Illustrated are the Nominal 7lb. reel (for factories) and the Size 1 carton (for Service Engineers and Workshops). Manufacturers are invited to write for technical information, samples and bulk prices.

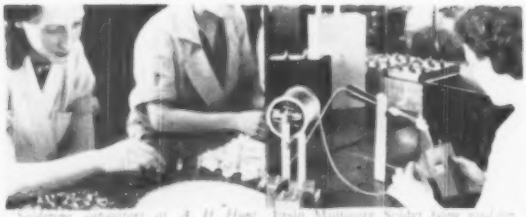

Soldering capacitors at A. H. Hunt Limited. The capacitors are heated together with other physical lengths of Ersin Multicore.

Ersin Multicore Solder being used for soldering condenser connections in the factory of T.C.C., London.

SIZE 1 CARTONS—5/- RETAIL

Catalogue Ref. No.	Alloy Tin lead	S.W.G.	Approx. Length per Carton
C16014	60/40	14	26 feet
C16018	60/40	18	60 feet
C14013	40/60	13	22 feet
C14016	40/60	16	42 feet

MULTICORE SOLDERS LTD.

MELLIER HOUSE, ALBEMARLE STREET, LONDON, W.1. Telephone: REGent 1411